

Algorithmic Design Methodologies and Design Porting of Wireline Transceiver IC Building Blocks Between Technology Nodes

**S.P. Voinigescu¹, T.O. Dickson¹, T. Chalvatzis¹, A.
Hazneci¹, E. Laskin¹, R. Beerkens², and I. Khalid²**

1) University of Toronto



2) STMicroelectronics, Ottawa, Canada

CICC, San Diego, Sept.19, 2005

Outline

- **Introduction**
- **Low-noise broadband input comparators**
- **Mm-wave VCOs**
- **High-speed logic gates**
- **Circuits beyond 40 Gb/s**
- **Summary**

  
Si(Ge Bi)CMOS speed is free ... if you can afford the mask costs!



MOS-HBT
(BiCMOS)
Cascode

- MAG > 8 dB @ 65 GHz in HBTs and MOSFETs
- HBT-based cascodes have highest gain
- Benefits of the MOS cascode questionable at 65 GHz

Fundamental limitations of dynamic range

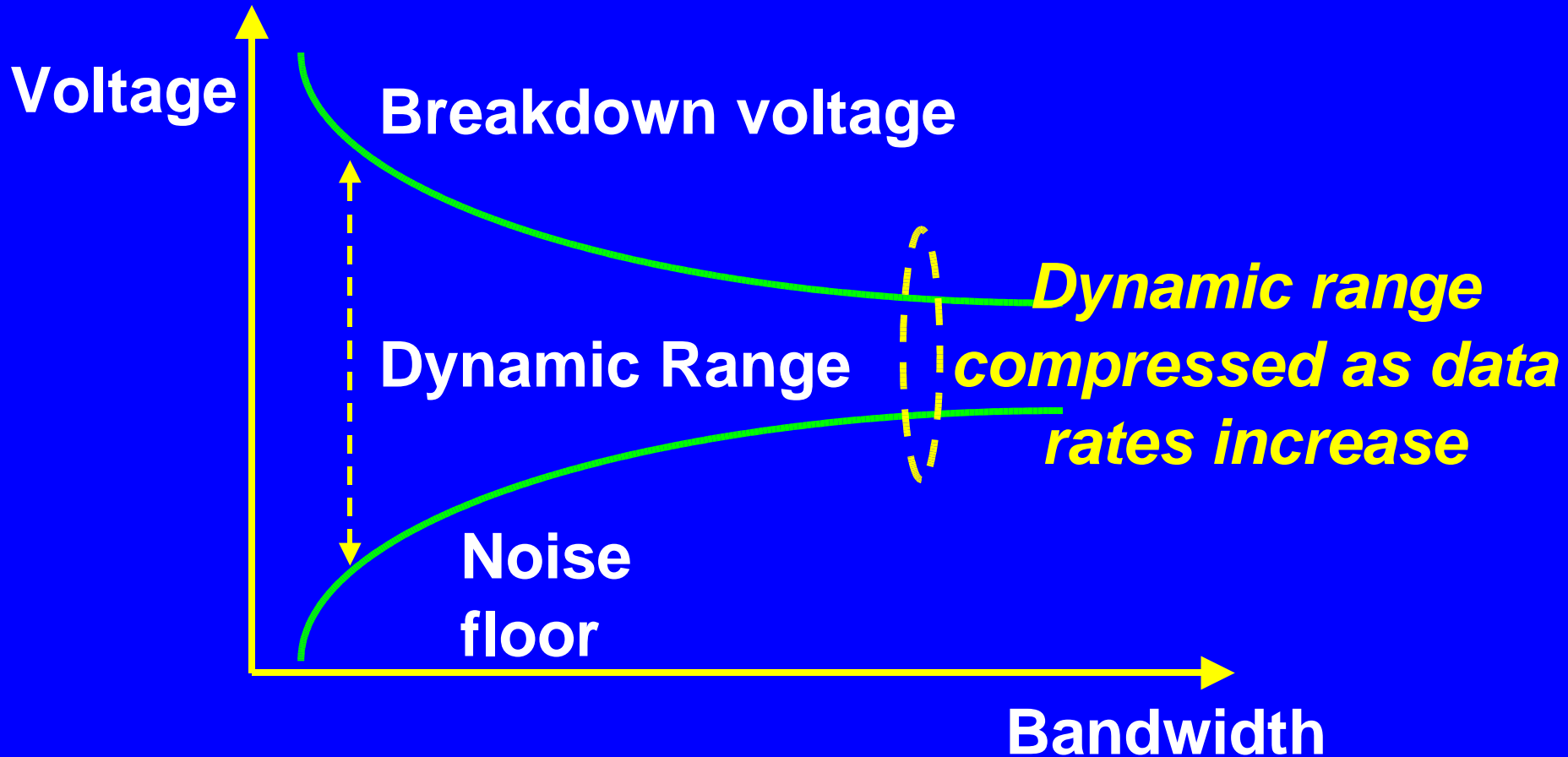

Emphasizes need for low-noise design methodologies

Power dissipation a major limitation in circuits beyond 40 Gb/s

- Bipolar only implementations suffer from
 - $V_{cc} \geq 3.3V$
 - 40 GHz latch consumes more than 50 mW
- CMOS has lower supply voltage and lower power dissipation but
 - 40 GHz latch has yet to be demonstrated
 - must design in 90/65 nm with first pass success

Emphasizes need for new low-voltage, high-speed logic topologies and robust design methodologies


Goal of this presentation

- Prove that algorithmic design methodologies exist for optimal solutions for all wireline building blocks
 - Broadband input amplifiers
 - VCOs
 - (Bi)MOS-CML logic gates
- Prove that CMOS implementations are portable between technology nodes and foundries


Key enablers

- Invariance of characteristic current densities in MOSFETs
- Low-noise broadband matching, biasing, and sizing
- Low-voltage (Bi)CMOS topologies
- Small footprint (less than 20 μm per side) inductors with $\text{SRF} > 100 \text{ GHz}$

 
MOSFET characteristic current densities invariant across nodes & foundries



Peak f_T @ 0.3 mA/ μ m

 


Peak f_{MAX} @ 0.2 mA/ μ m

 


NF_{MIN} @ 0.15 mA/ μ m

Characteristic MOSFET current densities invariant over CS and cascode topologies

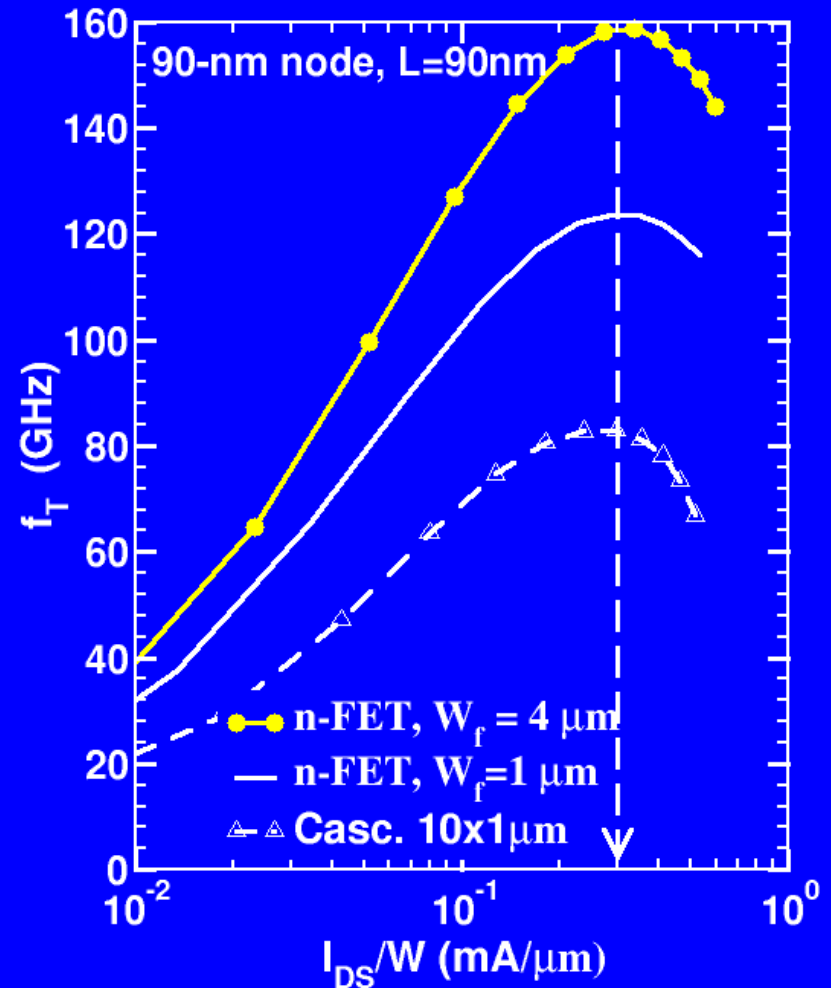- The peak f_T current density of a MOSFET cascode stage remains 0.3 mA/ μm
- Cascode stage can be treated as a composite transistor in circuit design (f_T , f_{MAX} , NF_{MIN})
- f_T of MOSFET cascode is $< 60\%$ of MOSFET f_T





 Vertically stacked, multi-metal inductors for CML logic





- Q is not important
- Size is important
- Maximize $L * SRF$ to trade-off tail current for bandwidth
- Use 3-7 metals

Low-noise broadband amplifiers

  

Transistor low-noise design

(S. Voinigescu et al., BCTM 1996)

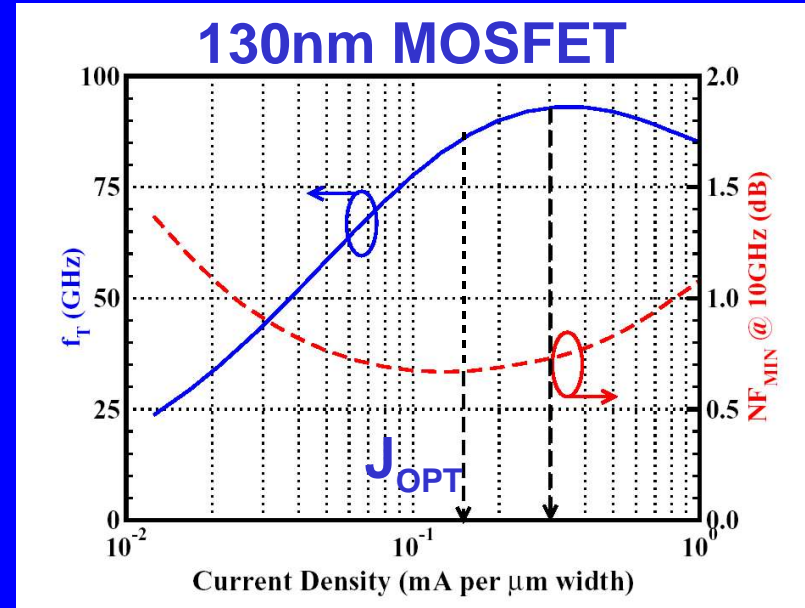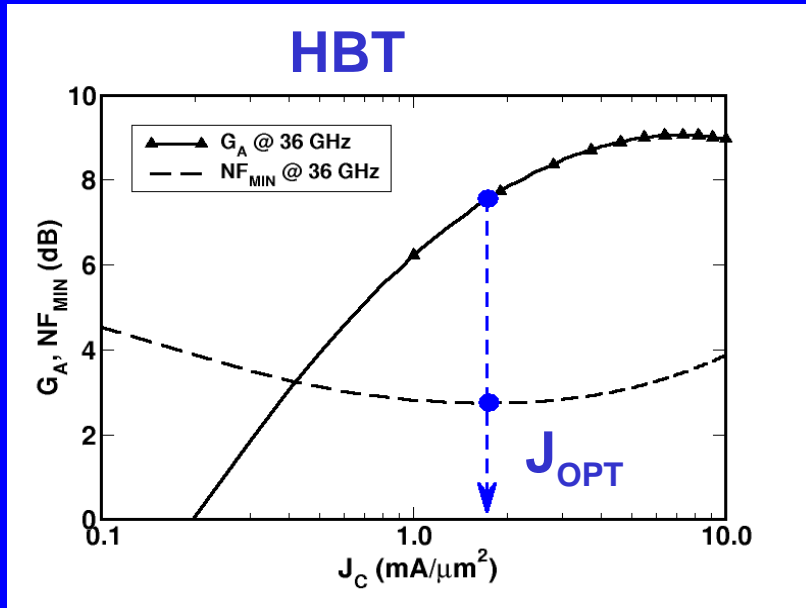

Lowest noise achieved when transistor biased at J_{OPT} ($0.15 \text{ mA}/\mu\text{m}$).


Transistor noise parameters scale with emitter length/ gate width.

$$R_N = R/L_E \quad G_N = G\omega^2 L_E \quad G_{COR} = G_C \omega^2 L_E \quad B_{COR} = B\omega L_E$$

$$R_N = R/W \quad G_N = G\omega^2 W \quad G_{COR} = G_C \omega^2 W \quad B_{COR} = B\omega W$$

Optimal biasing and sizing of transistor @ BW_{3dB} is key to low noise design.

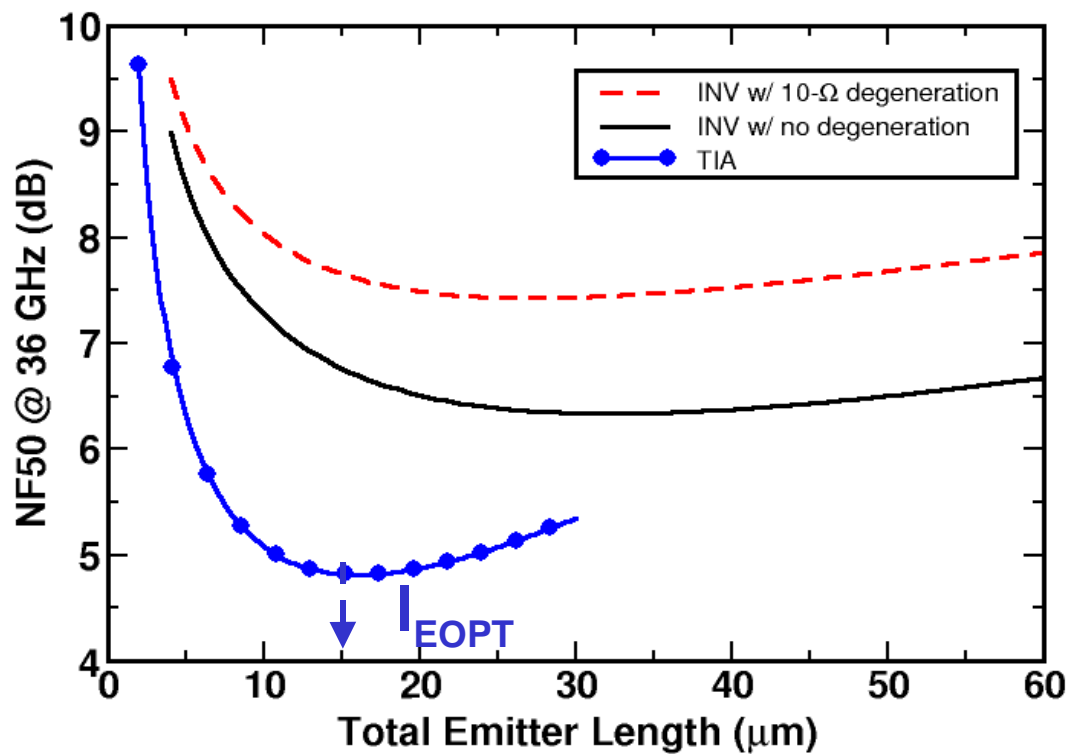Sizing SiGe HBT TIA & INV designs for noise matching






TIA requires much smaller transistor size:

Higher bandwidth

Broadband input match

Lower power consumption

Broadband CMOS LNA topology scaling

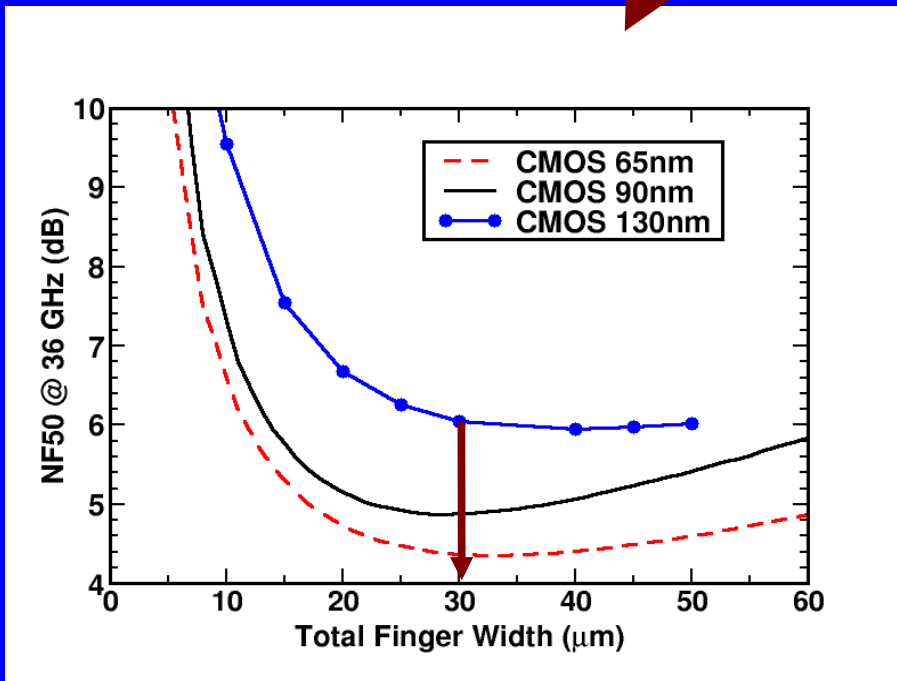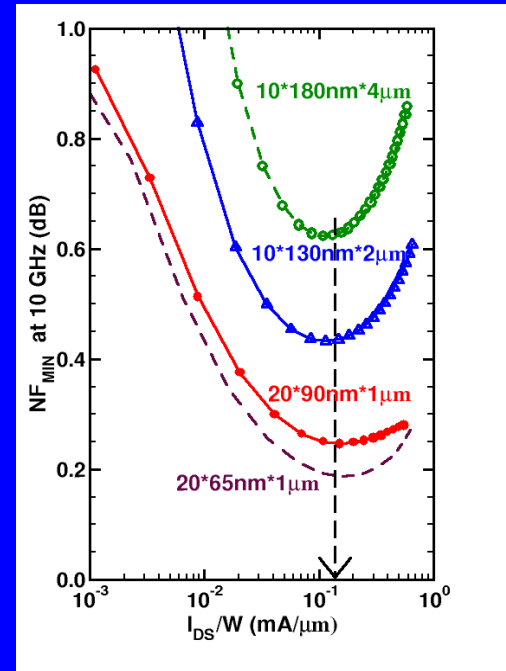 


- Biased at $0.15 \text{ mA}/\mu\text{m}$
- W, I_{DS} do not change with nodes
- NF_{50} and BW_{3dB} improve as technology scales


Algorithmic design methodology for broadband low-noise TIAs

 1. Bias HBT(MOSFET) at optimal noise current density J_{OPT} (0.15 mA/ μm) at 3dB frequency
2. Choose the **DC voltage drop** across R_C for linearity requirements. This fixes the loop gain $T = g_m R_C (=g_m * r_o)$
3. Set the feedback resistance R_F for 50 Ω input match.
4. Size the emitter length (gate width) of Q1 for low-noise, such that the TIA noise impedance is 50 Ω .
5. Add inductors to extend bandwidth and filter high-frequency noise.

Measured single-ended 50-Ohm noise figure



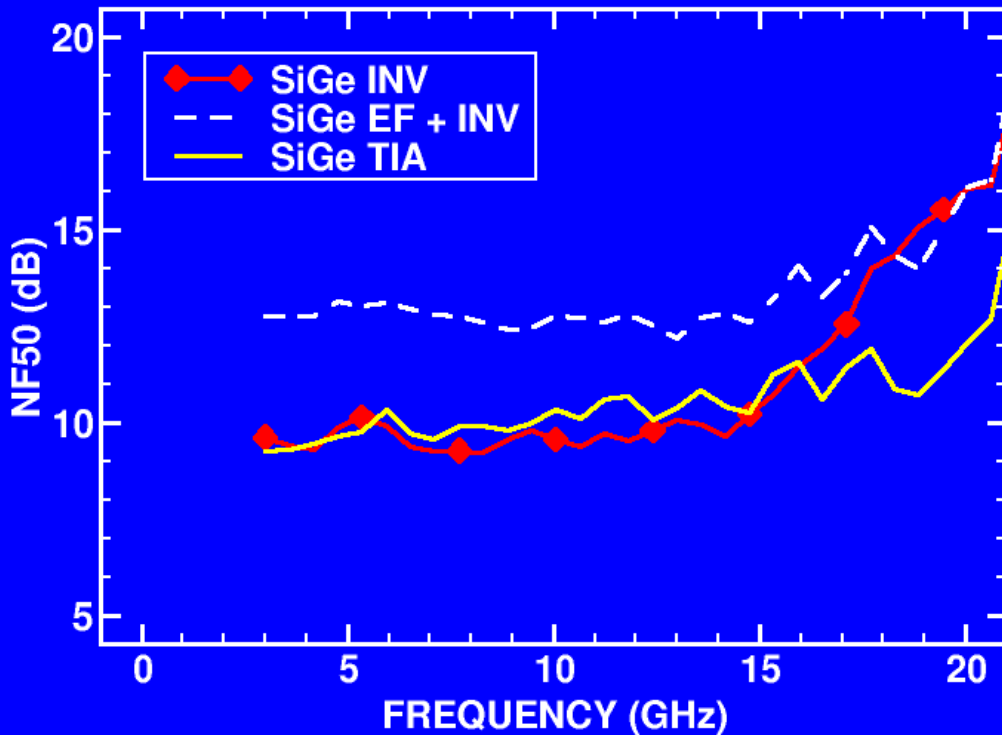
- Differential versions of three circuits implemented
- Measured single-ended noise figure in 50 Ohm



TIA has low noise over entire measured bandwidth

40-Gb/s eye diagrams

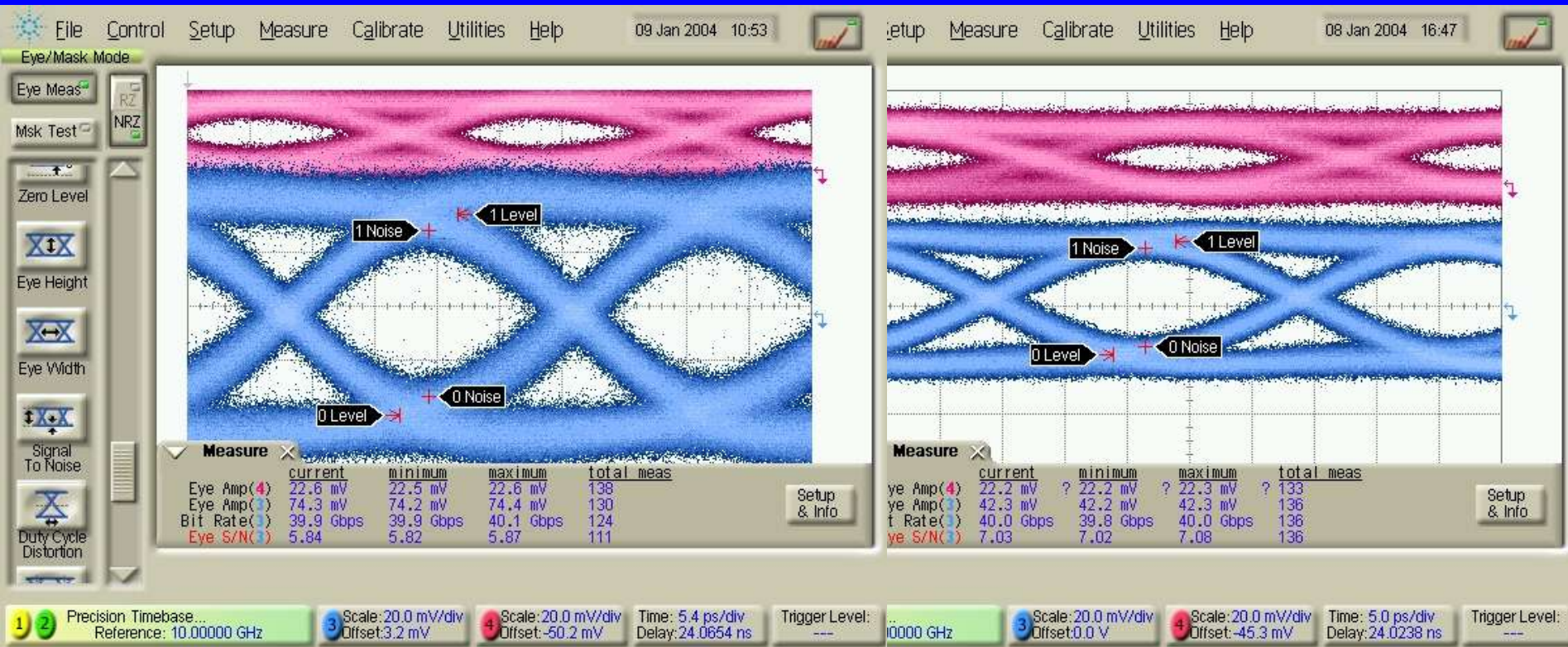20-mV single-ended input (10-mV per side)






EF-INV

TIA

Eye quality better for TIA (7.0) than EF-INV (5.8)

90-nm SOI TIA

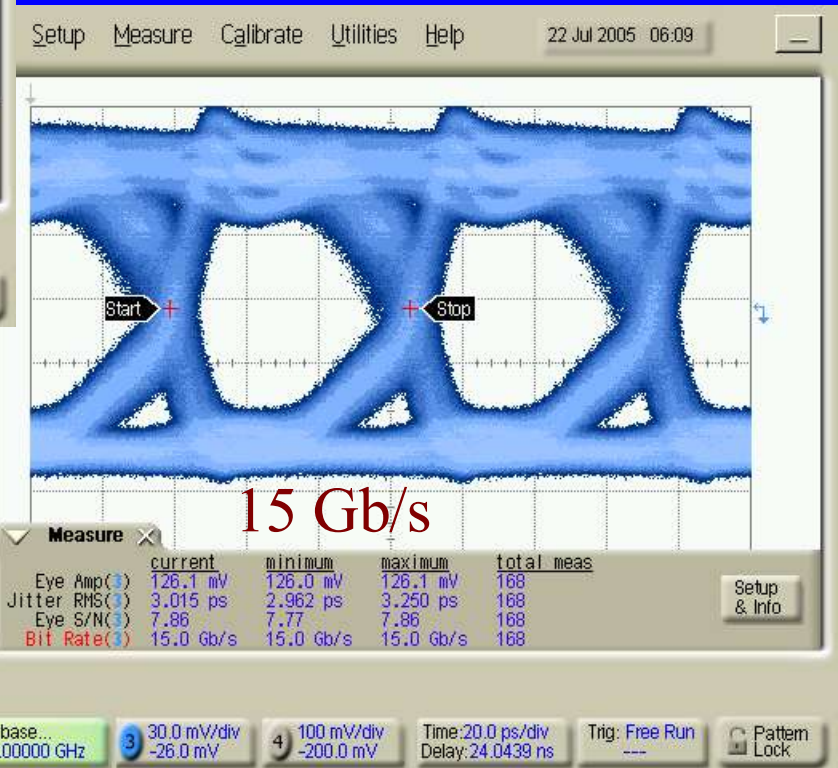 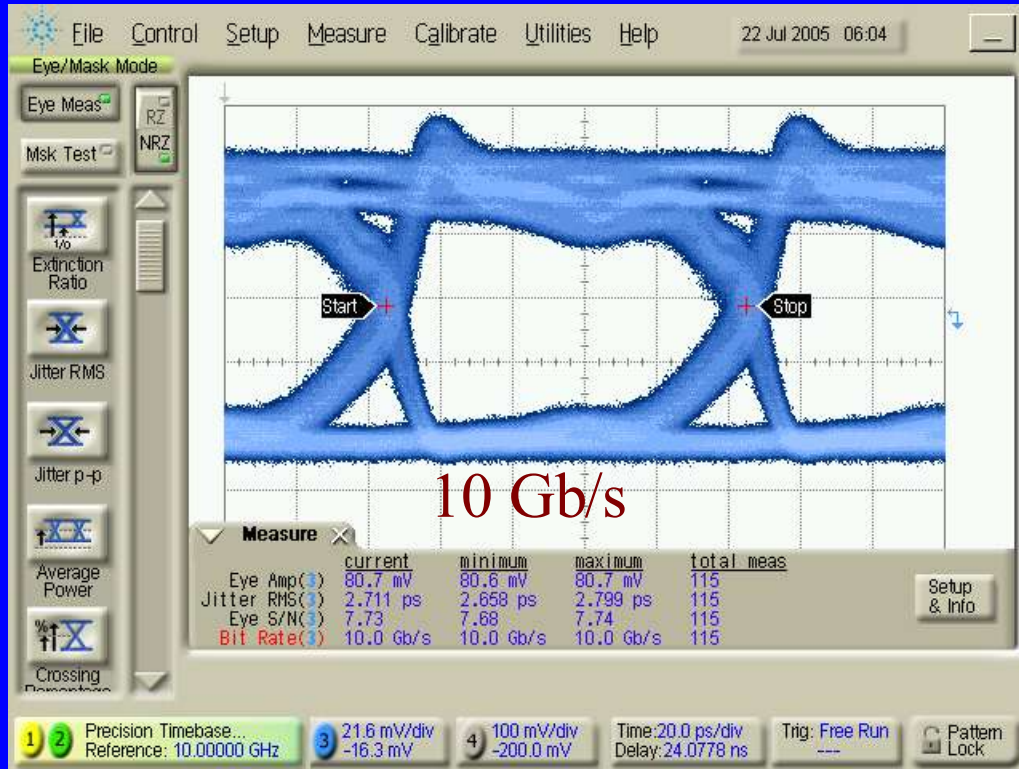

- 8-dB noise figure
- 1V supply
- 6 mW
- p-MOS load



VCOs

HBT VCOs

- Differential Colpitts topology


$$\text{Neg. Res.} = R_b - \frac{g_m}{\omega^2 C_1 C_2}$$
 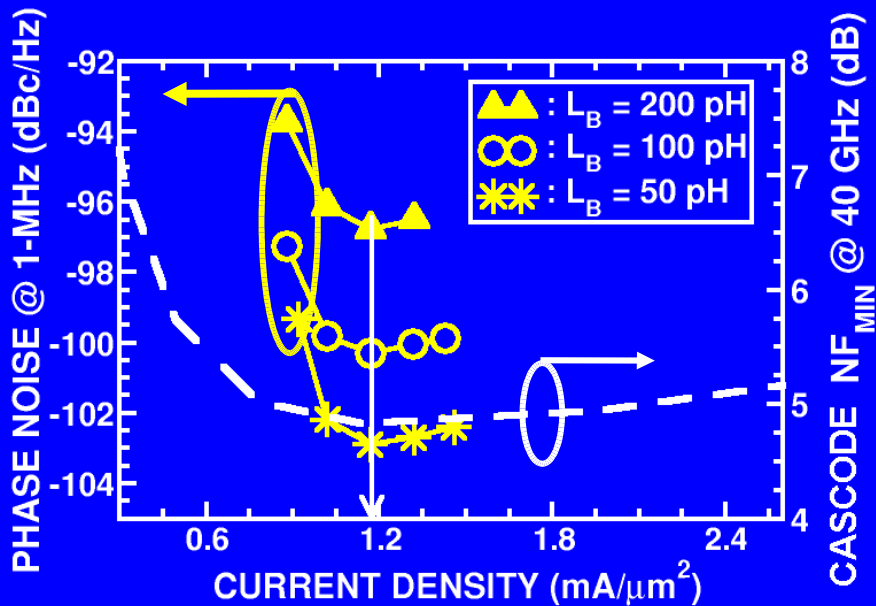
$$f_{osc} = \frac{1}{2\pi\sqrt{L_B C_{EQ}}}, \quad C_{EQ} = \frac{C_1 C_2}{C_1 + C_2}$$




SiGe HBT oscillator measurements

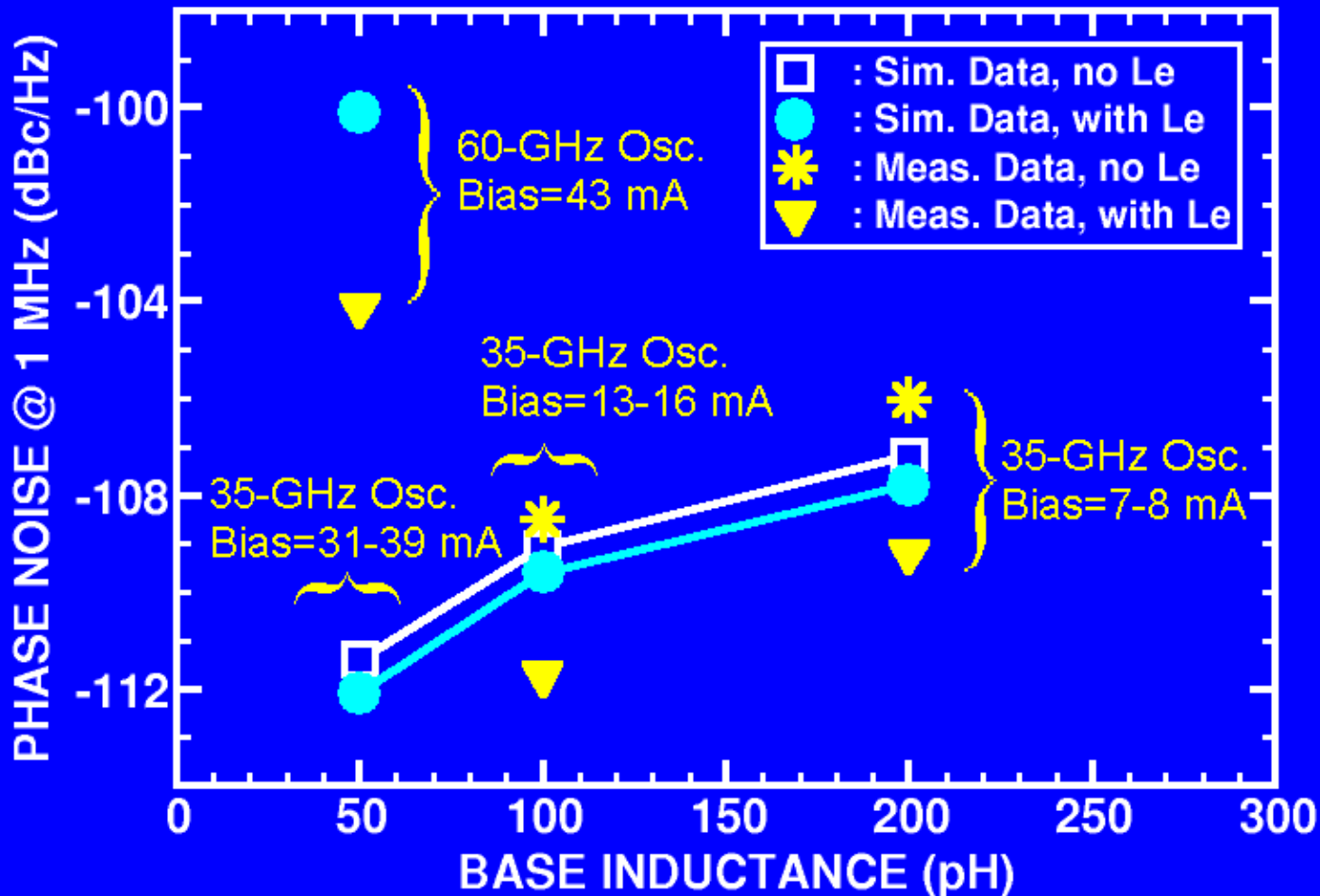
- Impact of:**
1. base (tank) inductor
 2. inductive emitter degeneration (L_E)



CMOS VCOs

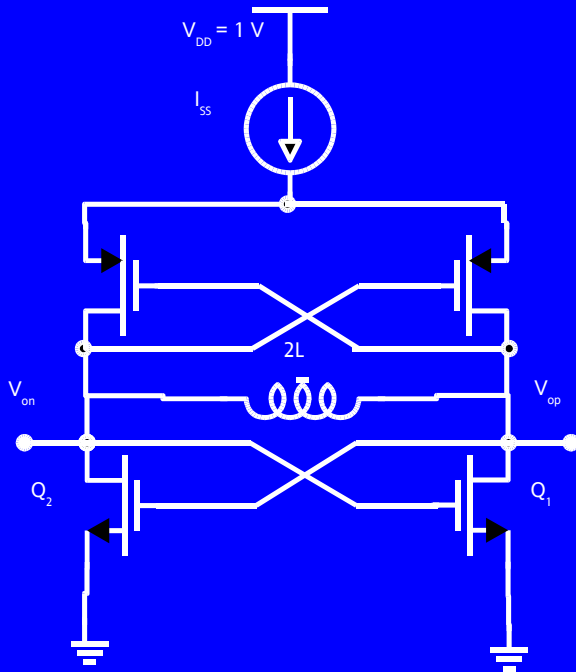


 
$$\omega_{osc, CMOS} \leq \frac{2}{3} \frac{g'_m Q_{eff}}{C'_{gs} + 4C'_{gd} + C'_{db} + \frac{C_L}{W}}$$



$$\omega_{osc, n-MOS} \leq \frac{g'_m Q_{eff}}{C'_{gs} + 4C'_{gd} + C'_{db} + \frac{C_L}{W}}$$

$$W_{n-MOS, cross} \leq \frac{1}{\omega_{osc}^2 L [C'_{gs} + 4C'_{gd} + C'_{db}]}$$

Colpitts CMOS/BiCMOS VCOs

  


$$W_{n-MOS, Colpitts} \leq \frac{1}{\omega_{osc}^2 L \left[\frac{C'_{gs} C'_{sb}}{C'_{gs} + C'_{sb}} + k C'_{gd} \right]}$$

$$A_{E, HBT, Colpitts} \leq \frac{1}{\omega_{osc}^2 L \left[\frac{C_{jbA} \frac{C_{var}}{A_E}}{C'_{jbA} + \frac{C_{var}}{A_E}} + k C_{jcA} \right]}$$

Colpitts has higher f_{osc} and
built-in buffering over X-coupled

BiCMOS cascode oscillator measurements

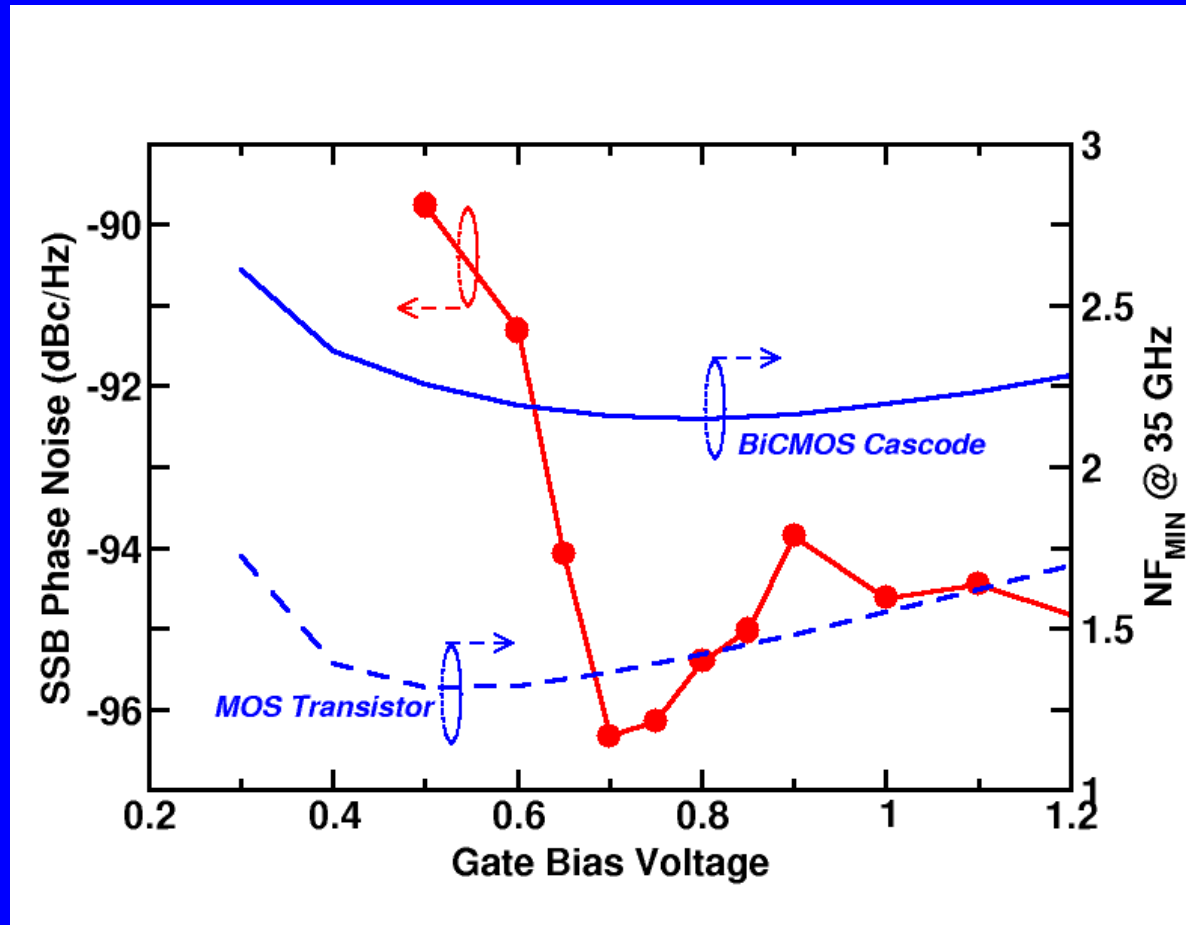


- Measured phase noise at 35 GHz and simulated NF_{MIN} of SiGe MOS-HBT cascode stage as a function of gate voltage

VCO design methodology

VCOs treated as LNAs matched to the “source” impedance R_p . This is generally not possible in cross-coupled VCOs!

 - VCO topology (CS/CE or cascode) biased at optimum NF_{MIN} current density (0.15 mA/ μm in FETs)
- V_{osc} must be set close to V_{MAX} to minimize phase noise
- Lower inductance, higher bias current, better $L(f_m)$
 - HBT-VCOs have 6..10 dB better phase noise due to larger V_{MAX}



$$L(f_m) = \frac{|I_n|^2}{V_{osc}^2} \times \frac{1}{f_m^2} \times \frac{1}{C_1^2 \left(\frac{C_1}{C_2} + 1 \right)^2}$$

High-Speed Logic

Logic families


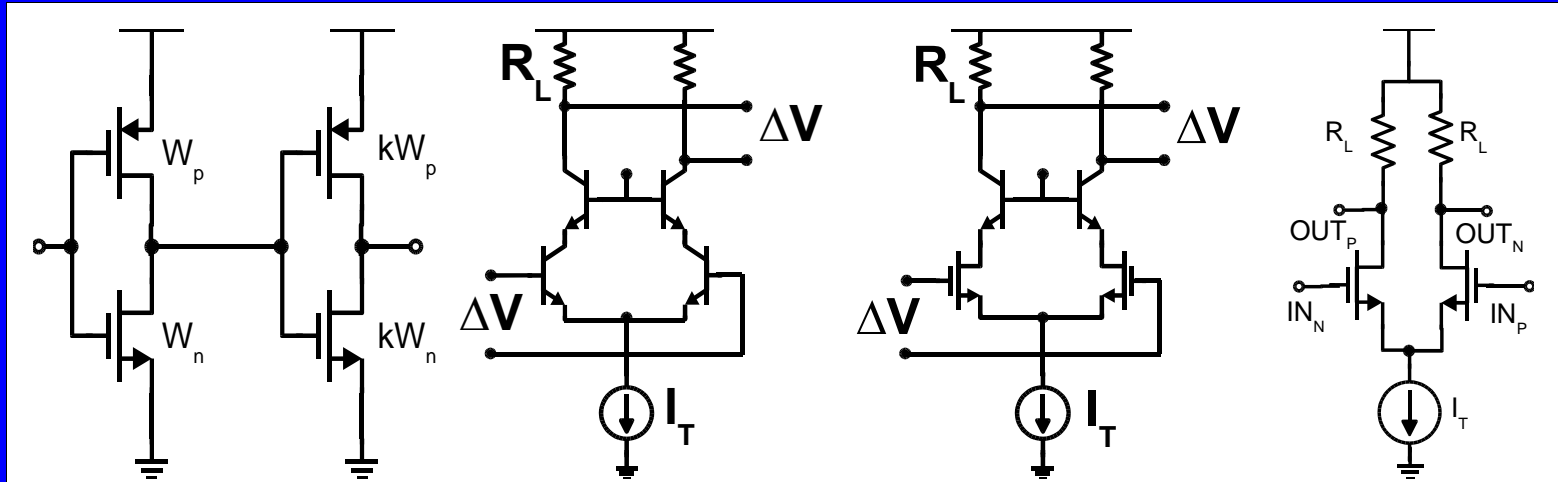
 


Fig. 9. Inverters in various CMOS and SiGe BiCMOS logic families.

- Unlike conventional CMOS, gate & subthreshold leakage is not a problem in MOS-CML
- In MOS-CML $low-V_T$ is desirable
- MOS-CML with peaking is $> 3x$ faster than CMOS

MOS/BiCMOS CML device sizing & biasing

 

$\sqrt{2}V_{eff} \leq \Delta V \leq 2V_{eff}$ scales with L

$$W = \frac{I_T}{1.5 J_{peakfMAX}} = \frac{I_T}{0.3 \text{ mA}/\mu\text{m}}; \quad A_E = \frac{I_T}{1.5 J_{peakfMAX}}$$


$$L_p = \frac{C_L R_L^2}{3.1} \quad L_p = \frac{C_L}{3.1} \frac{\Delta V^2}{I_T^2}$$

$$BW_{3dB} = \frac{1.6 \times I_T}{2\pi \Delta V C_L}$$


$$I_{Tmin} = \Delta V \sqrt{\frac{C_L}{3.1 L_{pmax}}}$$

- For a given speed and technology there is a maximum realizable L_{pmax}
- Speed improvement as CMOS scales is due solely to V_{eff} (ΔV) scaling.

BiCMOS ECL latches (> 49 GHz)

 






2.5 V supply, $I_T=2 \dots 4\text{mA}$

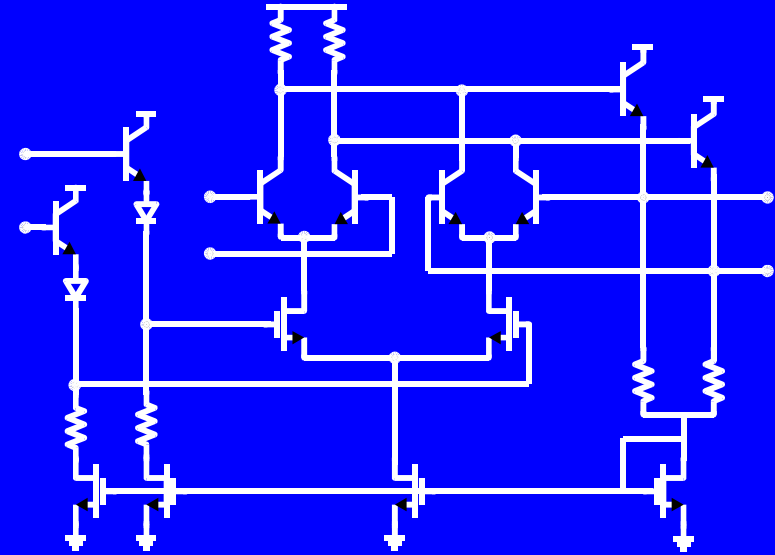

3.3 V supply, $I_T=2 \dots 4\text{mA}$





- BiCMOS cascode with EF (SF)
- EF vs. SF:
 - higher gain, lower E-S capacitance
 - $V_{BE} > V_{GS}$

Evolution to 1-V, 40-GHz latch

     


Wireline circuits beyond 40 Gb/s



2.5-V, Broadband 49-GHz MS DFF

 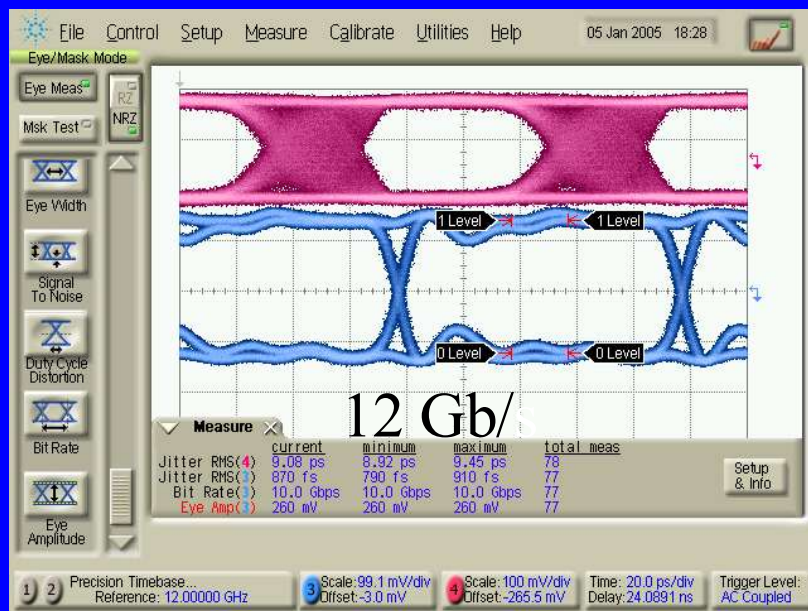 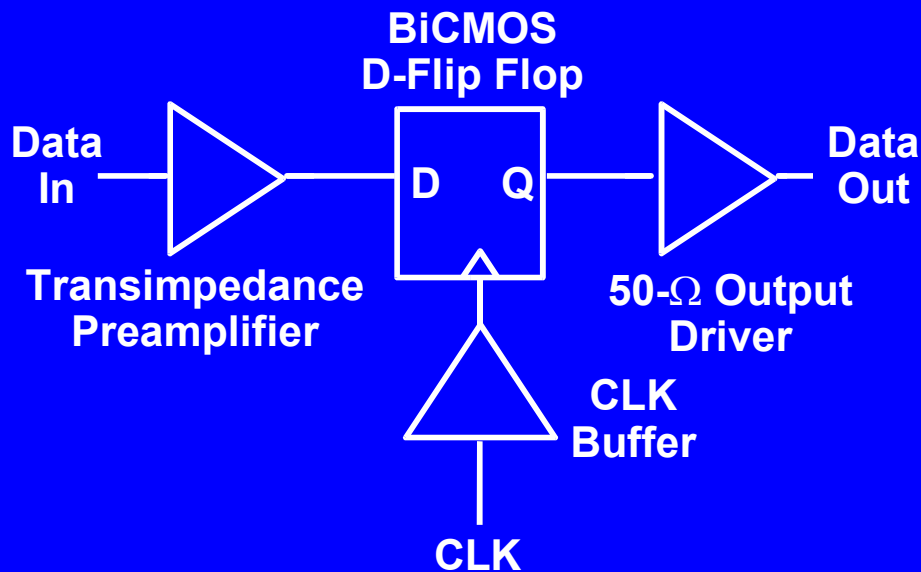


 
2.5-V, 80-GHz driver with pre-emphasis and gain control



  
- Adjustable gain with peaking
- Gain > 0 dB @ 94 GHz
- $S_{22} < -12$ dB up to 94 GHz
- 130-nm MOS-HBT cascode



  
80-Gbs SiGe BiCMOS $2^{31}-1$ PRBS Generator






Selector: BiCMOS 80-Gb/s

 

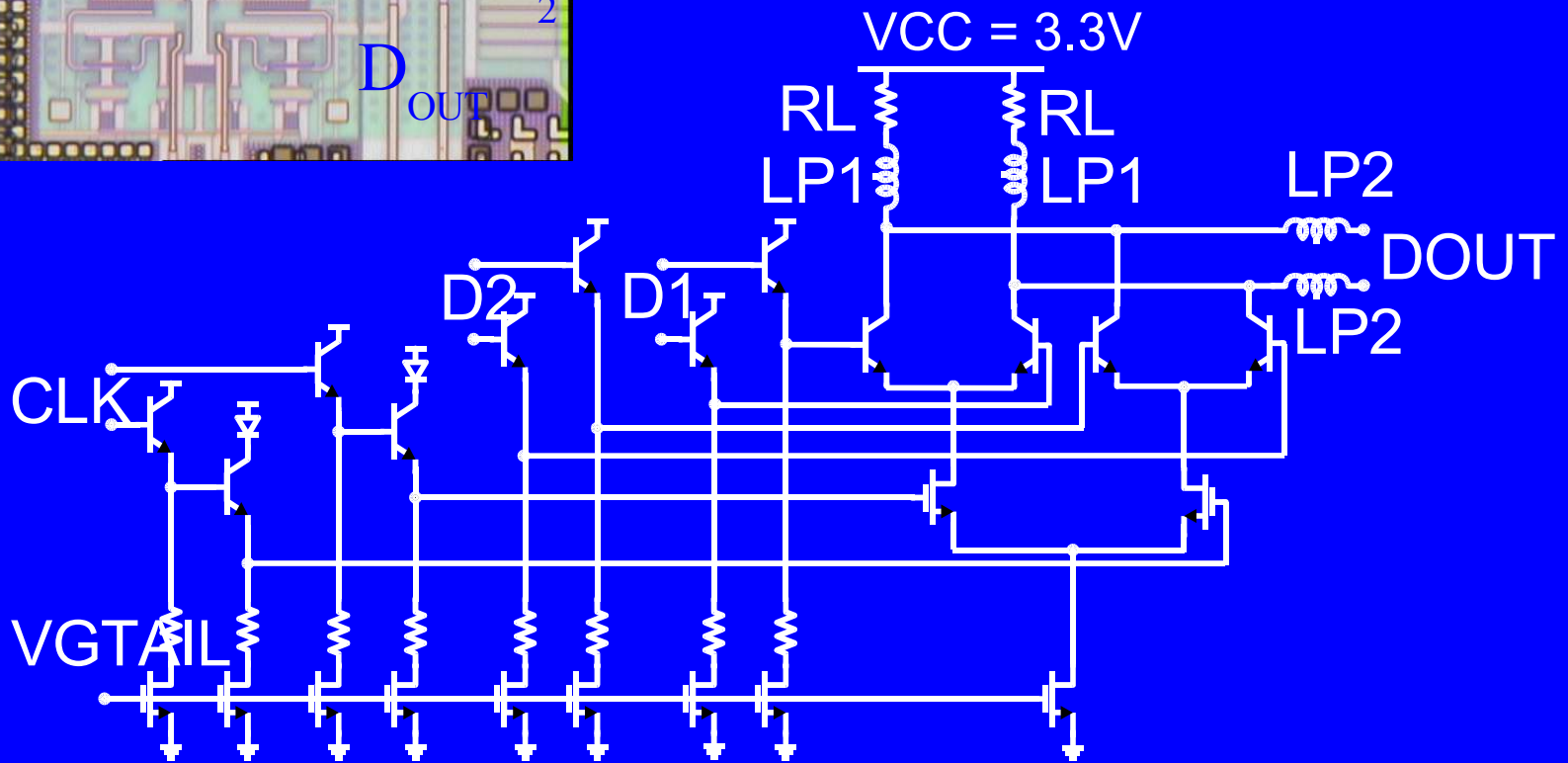- EF^2 & series-shunt peaking for highest speed
- 3-D stacked inductor for reduced area and high SRF





40-Gb/s Feed Forward Equalizer

 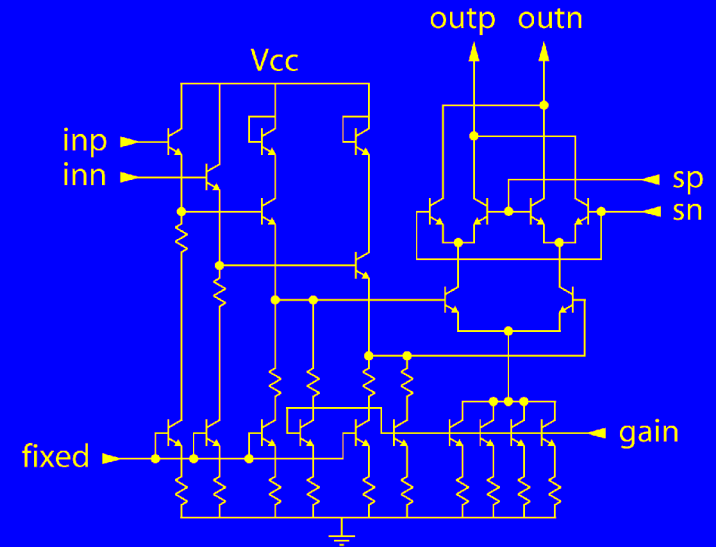
 


- core of each gain stage is a Gilbert cell
- tail current of the differential pair controls the tap weight (GAIN pad)
- SP/N pads control the tap sign





40 Gb/s over 9-ft SMA cable + 3dB attn.

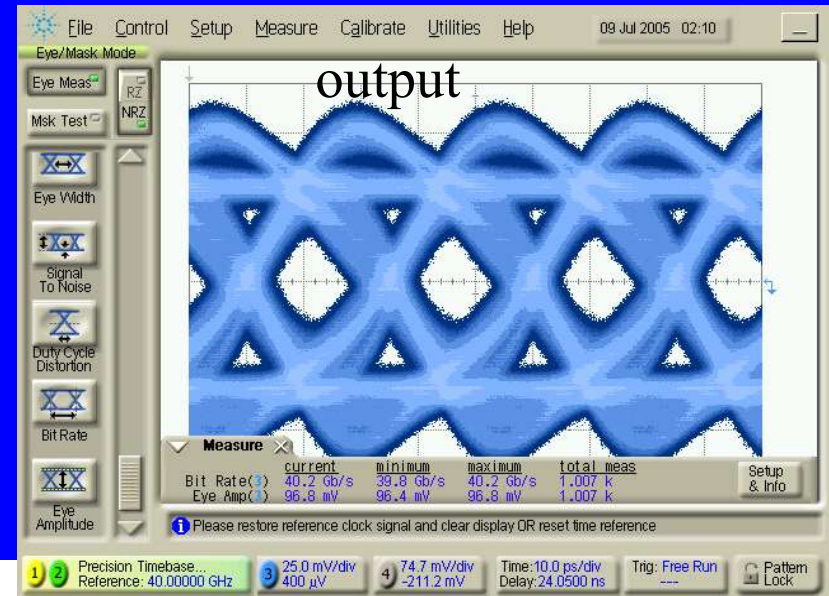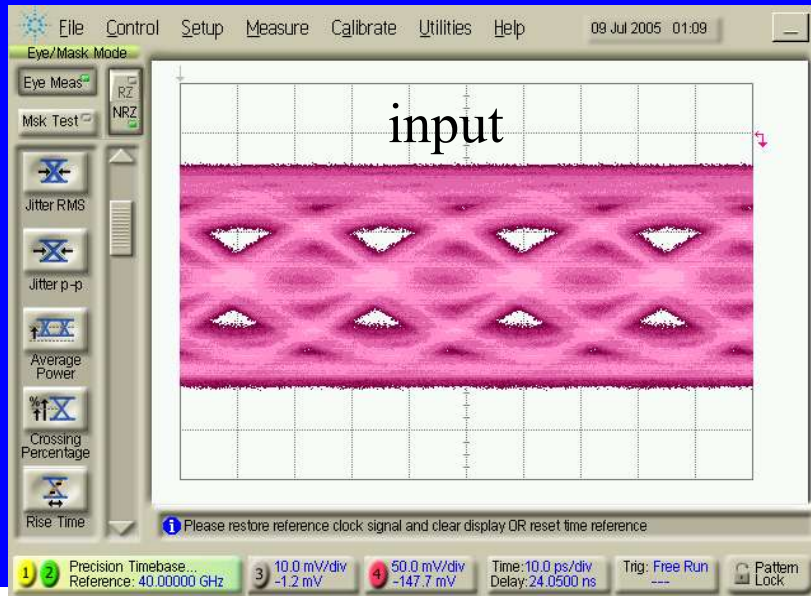


40Gbps 2^7 PRBS out vs FFE in vs FFE out

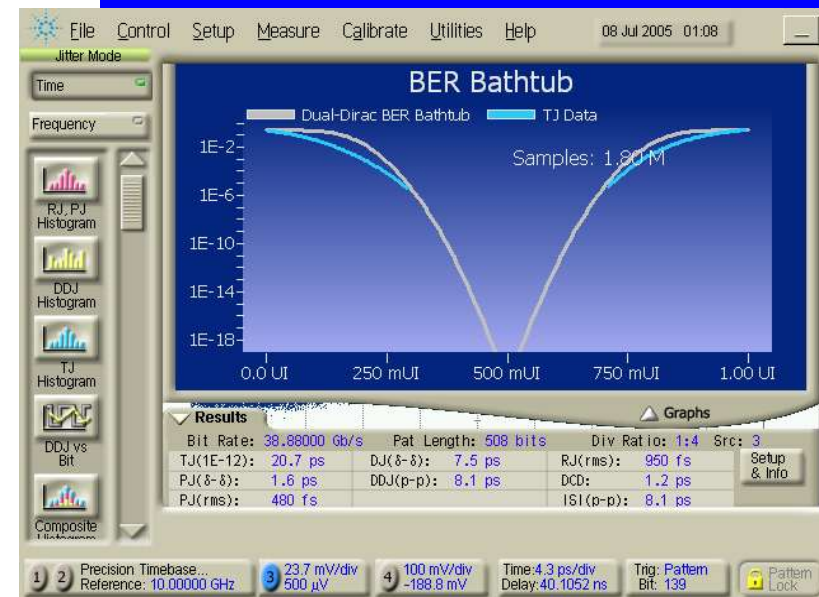 

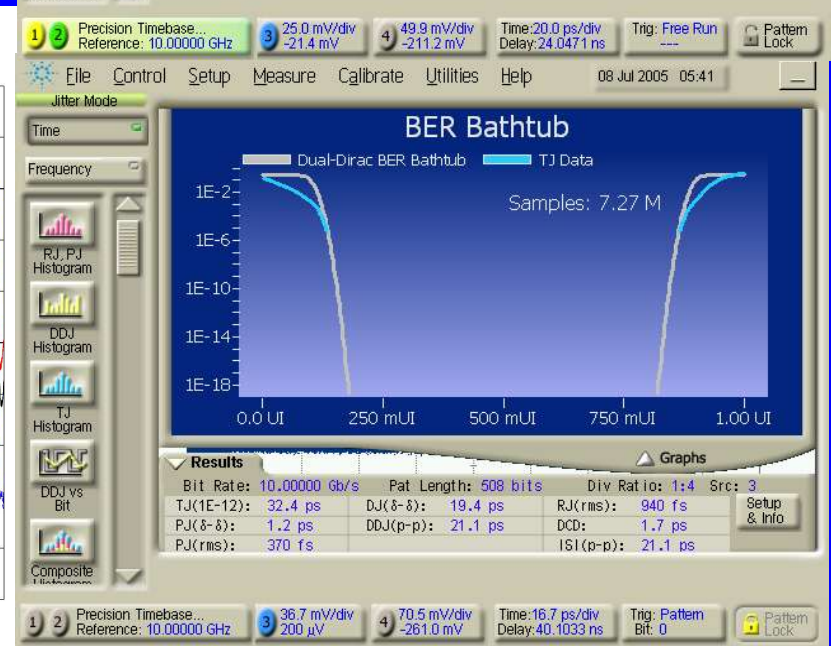
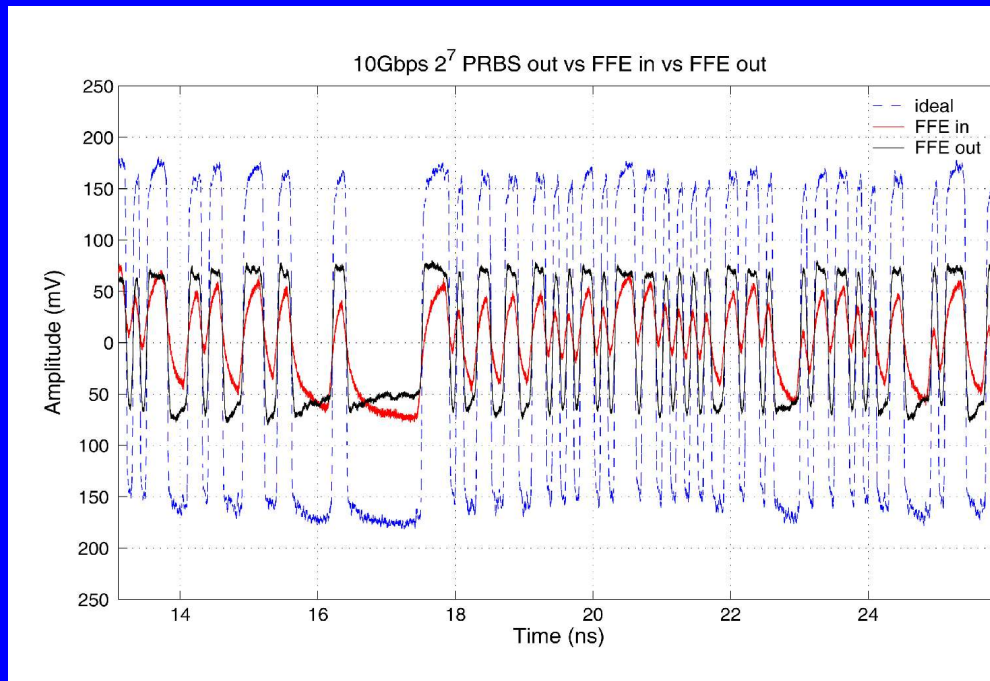
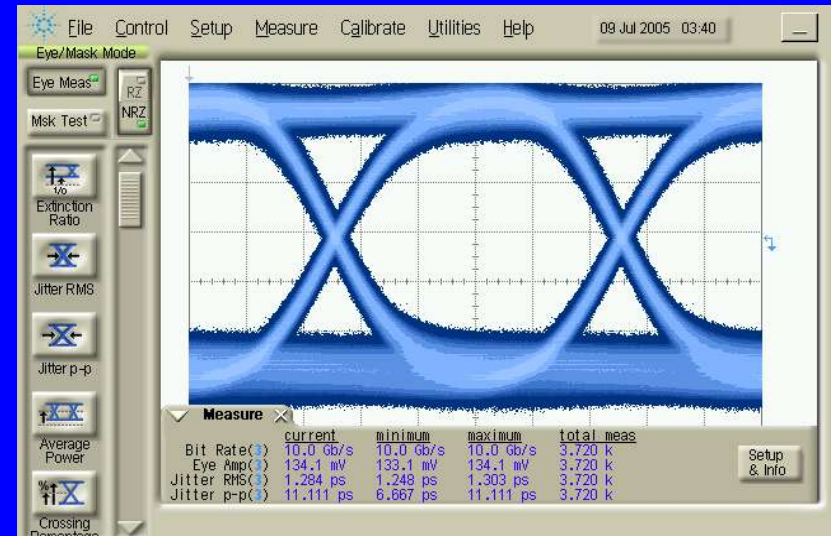
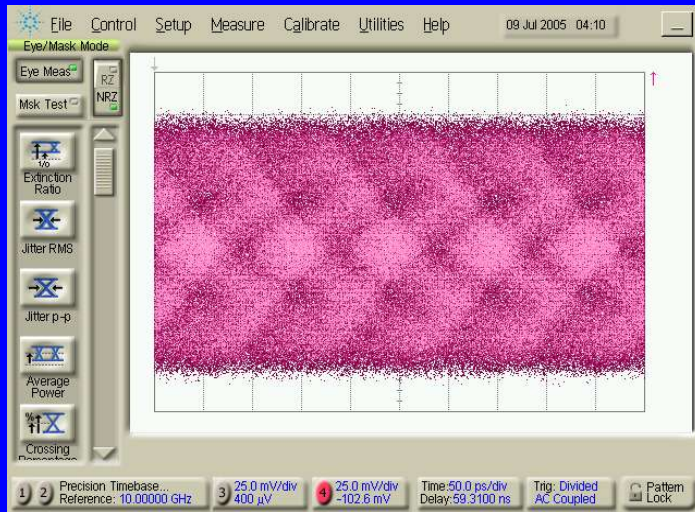
10 Gb/s equalization over 24-ft SMA cable +6dB attn.



 100-Gb/s transmission over 5cm of on-chip interconnect possible in 90nm SiGe BiCMOS



    - Model extracted from meas. on 3.6-mm long line
- 7-tap FFE equalizer



Summary

- Key design ideas:
 - Optimal solutions exist for LNA, TIA, VCO, (Bi)CMOS-CML gate topologies
 - Biasing at minimum noise figure current density
 - Matching noise impedance to signal source (tank) impedance
- Key MOSFET circuit scaling ideas
 - FETs should be biased at constant current density
 - Circuit size and bias current invariant over nodes while performance improves with scaling
- Circuits in the 50-80 GHz range
- Sub-3W, 100 Gb/s Ethernet transceiver possible in 250-GHz, 90-nm SiGe BiCMOS technology

Acknowledgments

- Bernard Sautreuil for his support over many years
- STMicroelectronics for fabrication
- Micronet, NSERC, Gennum Corporation and STMicroelectronics for financial support
- OIT and CFI for equipment grant
- CMC for CAD licenses

Backup

Impact of scaling in deep-submicron MOSFETs (500nm to 50nm)

- As a result of the constant-field scaling rules being applied to every new CMOS technology node:
 - Voltages scale by factor S
 - Vertical & lateral electric fields remain constant
 - Charge per unit gate width and current per unit gate width remain constant
 - The classical MOSFET I - V square law remains valid only at very low V_{eff} beyond which it becomes linear

Mobility degradation


- Mobility degradation due to the vertical gate field dominates behaviour (based on Intel data, S. Thompson, IEDM'99 Short Course).

$$\mu_{eff} = \frac{\mu_{ac} \mu_{sr}}{\mu_{ac} + \mu_{sr}}$$


$$\mu_{ac} \left[\frac{cm^2}{Vs} \right] \approx 330 E_{eff}^{-1/3} \left[\frac{MV}{cm} \right]$$

$$\mu_{sr} \left[\frac{cm^2}{Vs} \right] \approx 1450 E_{eff}^{-2.9} \left[\frac{MV}{cm} \right]$$

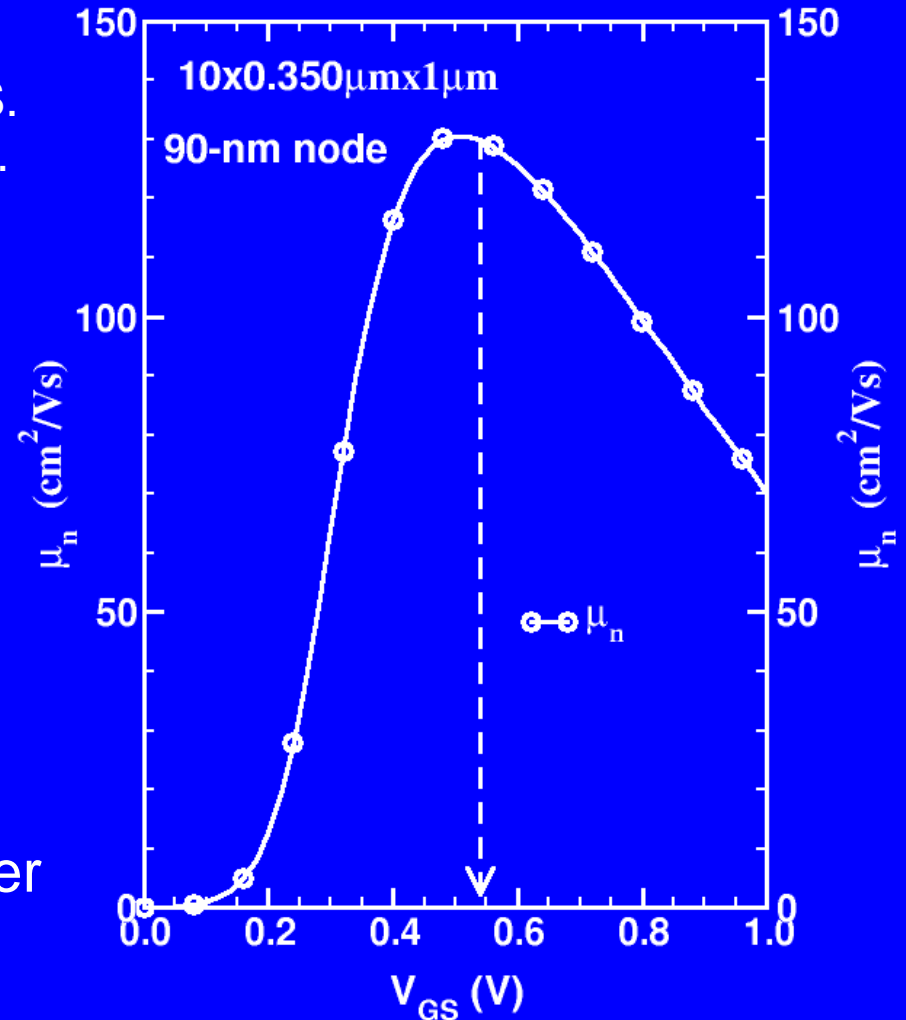
- The lateral field (due to V_{DS} bias) is about 50 times smaller than the vertical field



 
Measured transfer & subthreshold characteristics in 90-nm n-MOSFETS



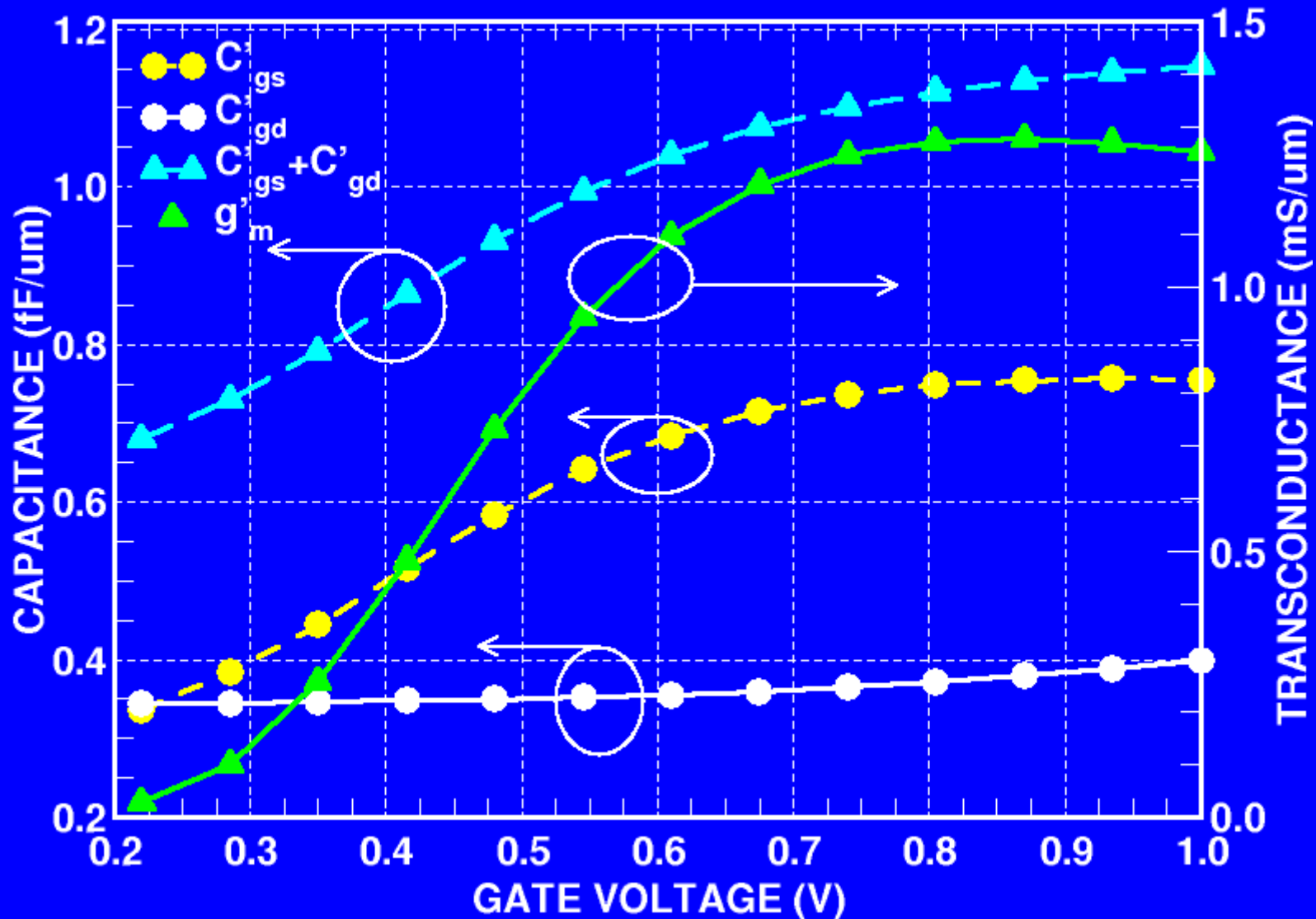Measured small signal g_m , C_{gs} , C_{gd} characteristics in 90-nm n-MOSFETs



Si vs. III-V FETs: f_T , f_{MAX}

 

S. Voinigescu et al. JHSES,
March 2003

peak f_T : 0.3 $\text{mA}/\mu\text{m}$

peak f_{MAX} : 0.2 $\text{mA}/\mu\text{m}$

Consequences of constant-field scaling in 500 nm to 50 nm MOSFET channels:

- $C'_{gs'}$, $C'_{gd'}$, C'_{db} constant over nodes down to 130 nm then decreasing as scaling of t_{ox} stopped at 1.2 nm
- $g'_{m'}$, $g'_{ds'}$, $f_{T'}$, f_{MAX} increase
- $F_{MIN'}$, R_n decrease
- RF & high-speed performance (except output swing) improves with scaling
- Constant current density biasing ensures design robustness over bias current, $V_{T'}$, process variation, nodes & foundries

Scaling is good for high-speed digital/wireline


60-GHz, single metal inductor for VCOs

Planar spiral inductor:

Diameter = 27 μm

Turns = 1 $\frac{3}{4}$

S = 2 μm , W = 2.5 μm

 

Applying negative feedback for noise matching

- Negative feedback has similar impact on noise and input impedance
- Use Y -matrix to analyze noise params of:
 - Multifinger MOSFETs
 - CMOS inverter topology
 - Parallel (transimpedance) feedback circuits
- Use Z -matrix to analyze noise params of:
 - Differential stage
 - Series feedback circuits:
 - Tuned LNA with L (xfmr) degeneration
 - EF input
 - Inverter with resistive degeneration

Series feedback for noise matching

$$Z_{SOP} = \sqrt{r_{SOPA}^2 + \frac{r_{NF}}{g_{NA}} + 2r_{CORA} \Re(Z_{11F}) + \Re^2(Z_{11F}) + \frac{|z_{CORF} - Z_{11F}|^2 g_{NF}}{g_{NA}}} + j[X_{SOP} - \Im(Z_{11F})]$$

$$F_{MIN} = 1 + 2g_{NA} [r_{CORA} + r_{SOP} + \Re(Z_{11F})]$$

Parallel feedback for noise matching

$$Y_{SOP} = \sqrt{G_{SOPA}^2 + \frac{G_{NF}}{R_{NA}} + 2G_{CORA} \Re(Y_{11F}) + \Re^2(Y_{11F}) + \frac{|Y_{CORF} - Y_{11F}|^2 R_{NF}}{R_{NA}}} + j[B_{SOP} - \Im(Y_{11F})]$$

$$F_{MIN} = 1 + 2R_{NA} [G_{CORA} + G_{SOP} + \Re(Y_{11F})]$$

Inverter noise matching

$$F_{Z_0} = 1 + \frac{1}{1 + \left(\frac{\omega L_0}{Z_0}\right)^2} + Z_0 \left(R_N \left| Y_{COR} + \frac{2}{Z_0} \right|^2 + G_N \right) \quad I_E(W_{OPT}) = \frac{1}{\omega} \frac{2}{Z_0} \sqrt{\frac{1}{\frac{G}{R} + G_C^2 + B^2}}$$

TIA noise matching

$$F_{Z_0} = 1 + R_{NA} Z_0 \left| Y_{CORA} + \frac{1}{Z_0} + \frac{1}{R_F} \frac{1 - j\omega_0}{1 + \omega_0^2} \right|^2 + Z_0 G_{NA} + \frac{Z_0}{R_F} \frac{1}{1 + \omega_0^2}$$





$$I_E(W_{OPT}) = \frac{1}{\omega} \sqrt{\left(\frac{1}{Z_0} + \frac{1}{R_F} \frac{1}{1 + \omega_0^2} \right)^2 + \left(\frac{1}{R_F} \frac{\omega_0}{1 + \omega_0^2} \right)^2} \sqrt{\frac{1}{\frac{G}{R} + G_C^2 + B^2}} \quad Z_{IN} = \frac{R_F}{1 + R_C I_T}$$

$R_F > Z_0$ for 50Ω match, resulting in lower noise & smaller transistor size than low-noise INV design

CMOS topology



- In 90-nm CMOS, the p-MOSFET is low-noise and fast enough for most applications up to 40 Gb/s
 - Use CMOS inverter to improve g_m/I , R_n to save current over NMOS-only implementations

 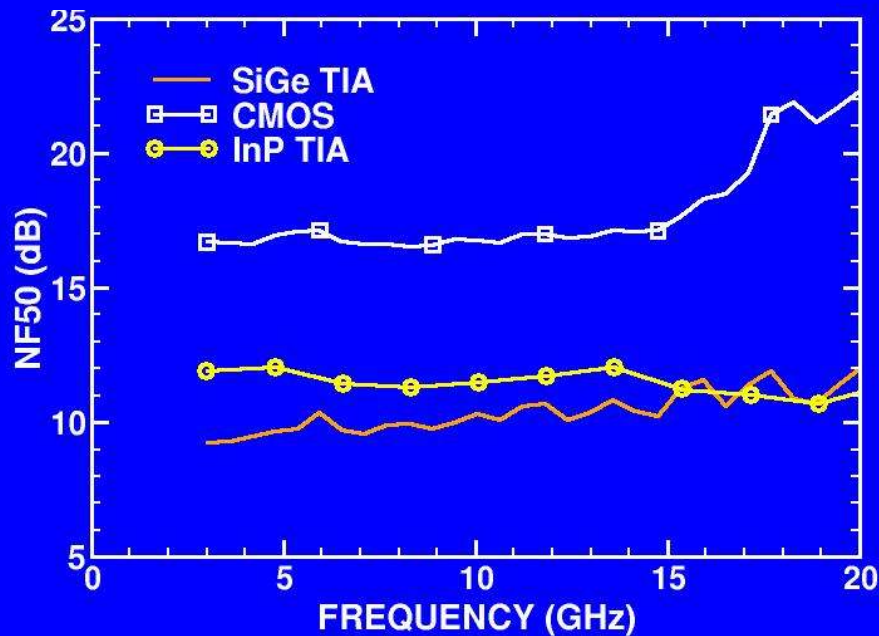  Si CMOS, SiGe BiCMOS, InP low-noise broadband preamps



Low-noise broadband preamps: InP vs. SiGe BiCMOS

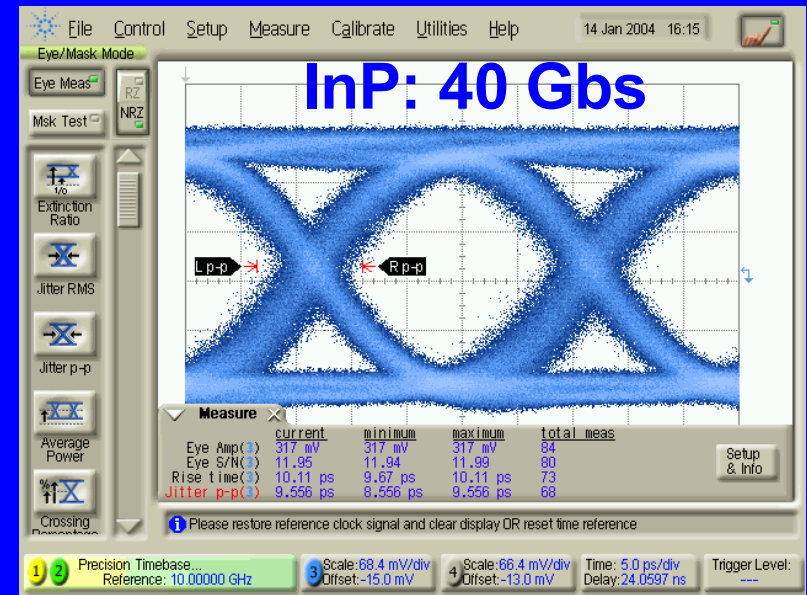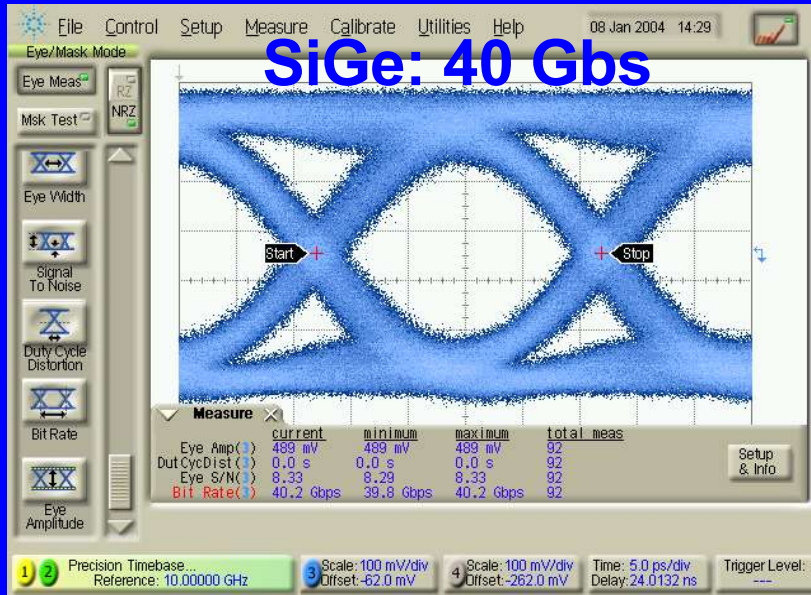
(H. Tran et al. GaAs IC Symp. 2003 for InP TIA)



	NF at 10 Ghz	Data Rate	Sensitivity
CMOS	16.5 dB	20 Gb/s	20 mVpp
SiGe-HBT	10 dB	40 Gb/s	20 mVpp
InP-HBT	11.5 dB	40 Gb/s	8 mVpp

Push-Push VCO measurements (con't)

Tuning characteristics:

 

CMOS VCO design scaling and porting

- As technology scales to next node, g'_m increases but V_{MAX} decreases,
 - Ideally W and I_{DS} are fixed to maintain V_{OSC}
 - In reality W and I_{DS} must be reduced in sync with V_{MAX}
 - *maximum* f_{OSC} increases hence larger C_{var} can be used
- Scaling allows for smaller I_{DS} & W but not necessarily better $L(f_m)$

High-Speed Logic FoM: CML Gate Delay


$$SL_{HBT} = \frac{I_{Cpeak} \tau_T}{C_{bc} + C_{cs}}$$

$$SL_{FET} = \frac{I_{Dpeak} \tau_T}{C_{gd} + C_{db}}$$

$$\tau_{HBT} \approx \Delta V \frac{C_{bc} + C_{cs}}{I_T} + \left(k + \frac{R_b}{R_L} \right) \Delta V \frac{C_{\pi} + (1 - A_V) C_{bc}}{I_T}$$

$$\tau_{FET} \approx \Delta V \frac{C_{gd} + C_{db}}{I_T} + \left(k + \frac{R_g}{R_L} \right) \Delta V \frac{C_{gs} + (1 - A_V) C_{gd}}{I_T}$$
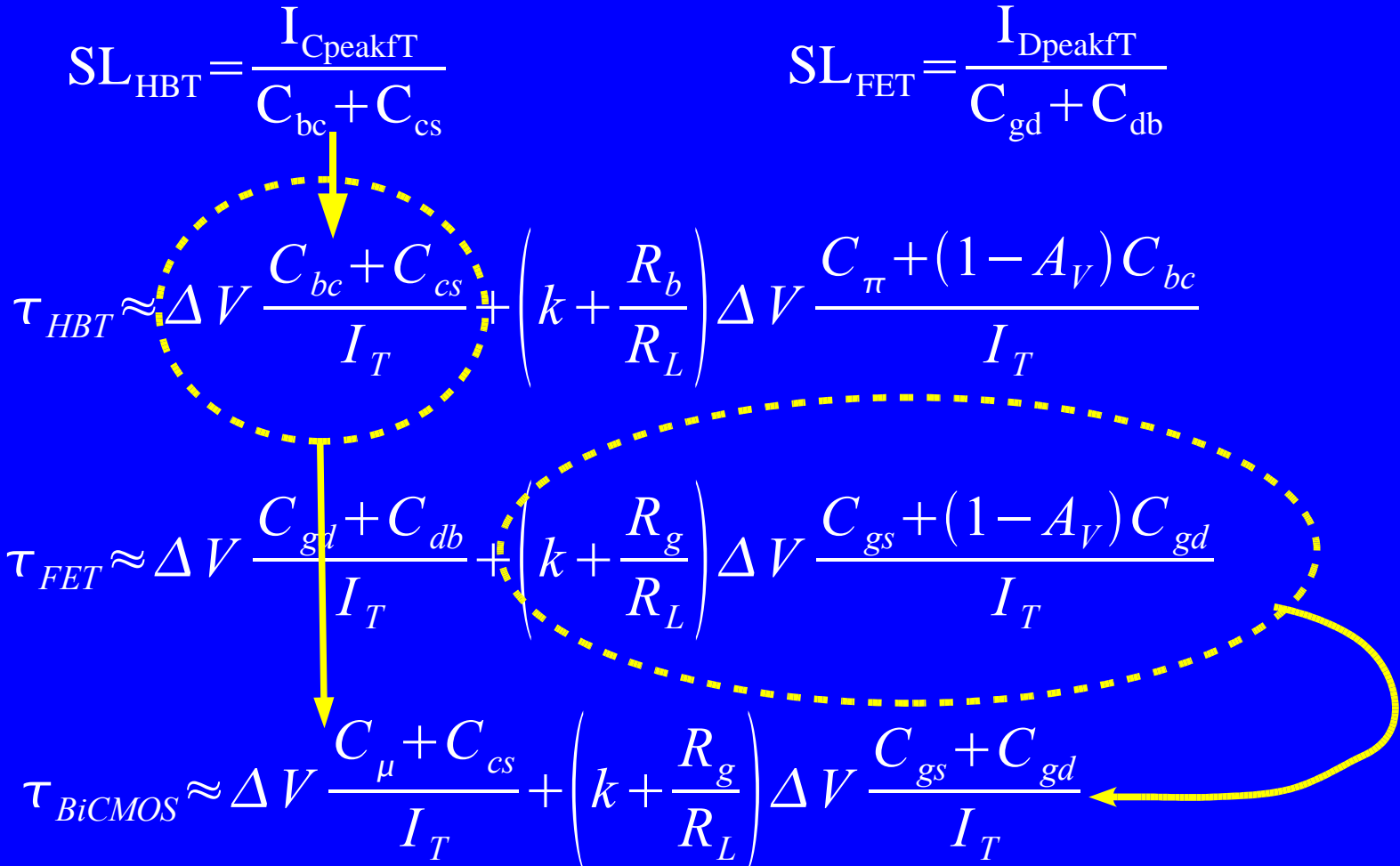
$$\tau_{BiCMOS} \approx \Delta V \frac{C_{\mu} + C_{cs}}{I_T} + \left(k + \frac{R_g}{R_L} \right) \Delta V \frac{C_{gs} + C_{gd}}{I_T}$$



Scaling of MOS/BiCMOS CML logic

Table 1: fanout-of-1 latches ideal i.e. no parasitics, *) measured

<i>Latch Family</i>	<i>Rate:Gbs</i>	V_{DD} (V)	ΔV (V)	I_T (mA)	P_D (mW)	Ind (nH)
130nm MOSCML	40	1.8	0.5	1.5(2.4)	2.7	2
130nm BiCMOS CML	40	1.8	0.2	0.83 (1.6)	1.5 (2.9)	1
130nm BiCMOS CML *)	12	2.5	0.2	1	2.5	0
130nm BiCMOS ECL *)	50	2.5	0.25	7.5(12.5)	18(30)	0.25
90nm MOSCML	40	1.2	0.38	1.8	2.2	0.5
90nm BiCMOS CML	40	1.5	0.2	1	1.5	0.5
90nm BiCMOS CML extracted	30	1.5	0.2	1	1.5	0.5
65-nm MOSCML	60	1	0.35	2.5	2.5	0.5

- Assumes maximum inductor SRF of 80 GHz*nH and SRF=2*Bitrate
- Numbers in brackets include emitter(source) followers

49 Gb/s over 6-ft cable

