



Ali Sheikholeslami

# Source Degeneration

Welcome to "Circuit Intuitions"! This is the second article of a series that will appear regularly in this magazine. As the title suggests, each article provides insights and intuitions into circuit design and analysis. These articles are aimed at undergraduate students but may serve the interests of other readers as well. If you read this article, I would appreciate your comments and feedback as well as your requests and suggestions for future articles in this series. Please send your e-mails to ali@ece.utoronto.ca.

We said in the previous article that looking into a node, one can see the Thevenin or Norton equivalent circuit for that node. We now look deeper into one particular circuit that consists of an NMOS transistor with a resistor in series with its source terminal in a configuration known as *NMOS transistor with source degeneration*. We offer a simple method for the small-signal analysis and design of this configuration. The case for the PMOS transistor is similar but not discussed in this article for brevity.

Figure 1 shows a source-degenerated NMOS transistor along with equations for its Thevenin and Norton equivalents. These include the open-circuit voltage ( $v_{oc}$ ), the short-circuit current ( $i_{sc}$ ), and the equivalent resistor ( $R_{eq}$ ). We make three observations regarding the role

of the series resistance  $R_s$  in this configuration:

- 1)  $R_s$  has no effect on the open-circuit voltage ( $v_{oc}$ ).
- 2) Including  $R_s$  increases the resistance looking into the drain.
- 3) Including  $R_s$  reduces the overall transconductance of the circuit (i.e.,  $i_{sc}/v_{in}$ ).

We now elaborate on these effects and capture them in a new equivalent transistor to be used in the analysis and design of other circuits containing this configuration.

To determine the open-circuit voltage (the Thevenin equivalent voltage) at the drain, we assume there is zero small-signal current flowing into the drain of the transistor, as shown in Figure 1. This zero current forces the voltage across  $R_s$  to be zero and, hence, renders  $R_s$  irrelevant to  $v_{gs}$  and  $v_{oc}$ .

The equivalent resistance looking into the drain is increased by  $(1 + g_{me}R_s)$ , where  $g_{me}$  is the effective  $g_m$  of the transistor (taking into account the transistor's body effect). This multiplying effect is the same effect that we explore in cascading transistors.

The short-circuit current is reduced by the same factor that increases the output resistance. This is simply because  $i_{sc} = v_{oc}/R_{eq}$  and  $v_{oc}$  is independent of  $R_s$ .

Now let us combine these properties to construct an equivalent transistor for a source-degenerated NMOS transistor. Since the overall effect of including  $R_s$  is to have a higher output impedance (call it  $R_o$ ) and a lower equivalent transconductance (call it  $G_m$ ), we can capture these two properties in a new equivalent

transistor with a new  $G_m$  and  $R_o$ , as shown in Figure 2. We can do this because a transistor in small signal is effectively a transconductance in parallel with a resistor. Note that by defining  $G_m$  and  $R_o$  according to the

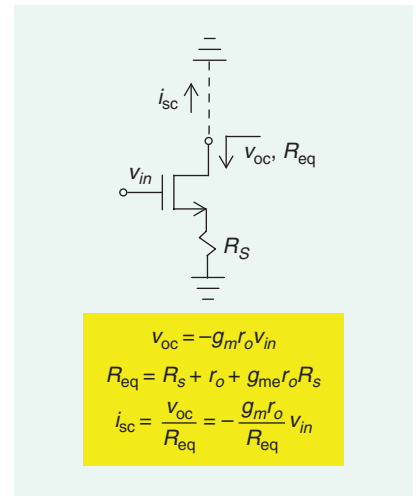


FIGURE 1: A Norton/Thvenin equivalent circuit looking into the drain of an NMOS transistor with source degeneration.

 
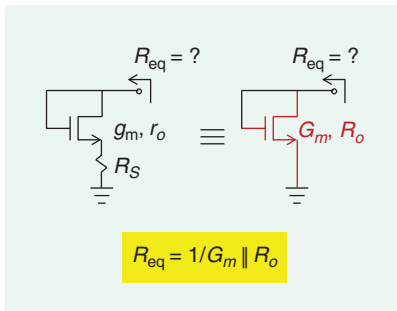


FIGURE 2: An NMOS transistor with source degeneration is equivalent to a single transistor with a smaller transconductance ( $G_m$ ) and larger output impedance ( $R_o$ ).

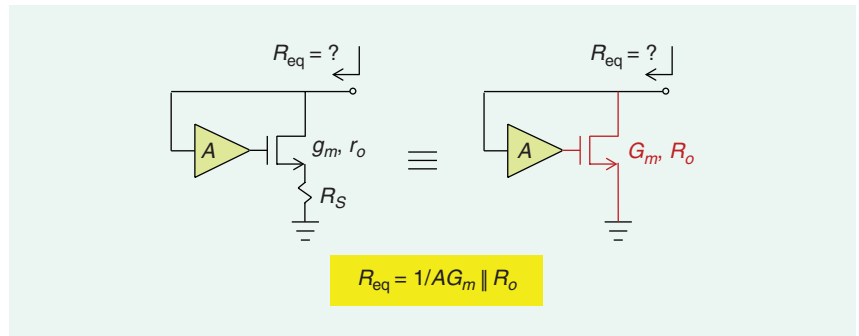


**FIGURE 3:** The equivalent resistance of a diode-connected NMOS with source degeneration.

equations presented in Figure 2, we have also guaranteed that  $v_{oc}$  of the equivalent transistor is independent of  $R_s$ . In other words, the new transistor has the same Thevenin and Norton equivalent circuits as those of the original source-degenerated NMOS transistor.

Before utilizing this equivalent transistor in the analysis and design of other circuits, let us entertain a few simplifying assumptions for further intuition. If we assume  $g_m r_o \gg 1$  and  $g_m R_s \gg 1$ , then the equivalent  $G_m$  becomes  $1/R_s$ , independent of the transistor parameters. This outcome is significant because it shows how a constant transconductance can be produced despite variations and the unpredictability of transistor parameters. Note that even if the assumptions on  $g_m r_o$  and  $g_m R_s$  are not valid, the fact remains that the equivalent transconductance is less dependent on transistor parameters when  $R_s$  is included. Another consequence of including  $R_s$  is an increase in linearity of the circuit due to negative feedback. We will discuss this in detail in a future article.

Now let us use the equivalent transistor we just introduced to analyze a couple of sample circuits. In Figure 3, we attempt to find the equivalent resistance looking into the drain of a diode-connected NMOS transistor with source degeneration.



**FIGURE 4:** The equivalent resistance looking into the drain when a voltage gain amplifier,  $A$ , is inserted between the drain and the gate of a source-degenerated NMOS transistor.

This can be done by simply replacing the source-degenerated NMOS with the equivalent transistor. Now using Element #4, which was discussed in the previous article, one can quickly observe that the equivalent resistance is  $1/G_m \parallel R_o$ . Since both  $1/G_m$  and  $R_o$  are higher (approximately by a factor of  $g_m R_s$ ) compared to those of the original transistor, the equivalent resistance of this circuit is also higher by the same factor compared to a diode-connected NMOS transistor.

Figure 4 shows another common circuit in which a voltage gain  $A$  is inserted between the drain and the gate of a source-degenerated NMOS transistor. Again, we can find the equivalent resistance of this circuit by simply replacing the source-degenerated NMOS transistor with its equivalent transistor. The equivalent circuit is slightly different in this case than Element #4 of the previous article; nevertheless the equivalent resistance can be calculated easily. To this end, we apply a small-signal voltage source ( $v_x$ ) to the output node and find the current it provides to the circuit. The voltage source can be replaced by two independent voltage sources: one that is applied only to the

drain of the transistor and one that is applied only to the input of the amplifier, producing  $Av_x$  at the gate of the transistor. Now, we use superposition to find the current. We first zero the voltage source feeding the drain and then zero the voltage source feeding the gate of the transistor (one at a time), finding the drain current each time. By superposition, the total current drawn from  $v_x$  is the sum of  $G_m Av_x$  and  $v_x/R_o$ . Therefore, the equivalent resistance is  $1/AG_m \parallel R_o$ .

In summary, including  $R_s$  in the source of an NMOS transistor effectively creates a new NMOS transistor with a transconductance ( $G_m$ ) that is more robust to variation and an output resistance ( $R_o$ ), which is much higher than  $r_o$  of the transistor.

*In other words, the new transistor has the same Thevenin and Norton equivalent circuits as those of the original source-degenerated NMOS transistor.*

## References

For Thevenin and Norton equivalent circuits, refer to R. E. Thomas, et al., *The Analysis & Design of Linear Circuits*, 7th ed. New York: Wiley, 2012, pp. 109–122.

For small-signal analysis of transistor circuits, refer to A. S. Sedra and K. C. Smith, *Microelectronic Circuits*, 6th ed. London, U.K.: Oxford Univ. Press, 2010.

B. Razavi, *Fundamentals of Microelectronics*. New York: Wiley, 2008.

