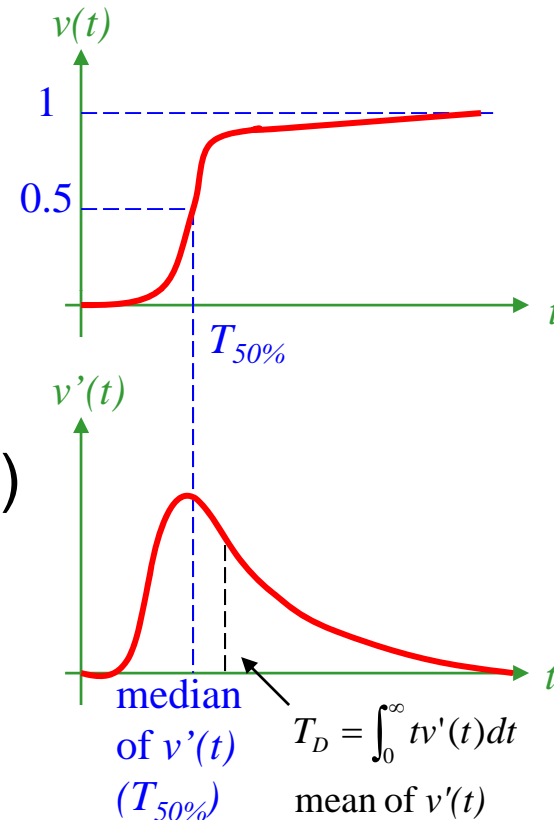


Elmore Delay for Monotonic Responses

- Assumptions:
 - Unit step input
 - Monotone output response
- Basic idea: use of mean of $v'(t)$ to approximate median of $v'(t)$

$v(t)$: output response (monotone)

$v'(t)$: rate of change of $v(t)$



Elmore Delay for Monotonic Responses

- $T_{50\%}$: median of $v'(t)$, since

$$\int_0^{T_{50\%}} v'(t) dt = \int_{T_{50\%}}^{+\infty} v'(t) dt$$

= half of final value of $v(t)$ (by def.)

- Elmore delay $T_D = \text{mean of } v'(t)$

$$T_D = \int_0^{\infty} v'(t) t dt$$

Why Elmore Delay?

- Elmore delay is easier to compute analytically in most cases
 - Elmore's insight [Elmore, J. App. Phy 1948]
 - Verified later on by many other researchers, e.g.
 - Elmore delay for RC trees [Penfield-Rubinstein, DAC'81]
 - Elmore delay for RC networks with ramp input [Chan, T-CAS'86]
 -
- For RC trees: [Krauter-Tatuianu-Willis-Pileggi, DAC'95]
$$T_{50\%} \leq T_D$$
- Note: Elmore delay is not 50% value delay in general!

Elmore Delay for RC Trees

- Definition


- $h(t)$ = impulse response
- T_D = mean of $h(t)$

$$= \int_0^{\infty} h(t) \cdot t \, dt$$

- Interpretation

- $H(t)$ = output response (step process)
- $h(t)$ = rate of change of $H(t)$
- $T_{50\%}$ = median of $h(t)$
- Elmore delay approximates the median of $h(t)$ by the mean of $h(t)$

$h(t)$ = impulse response

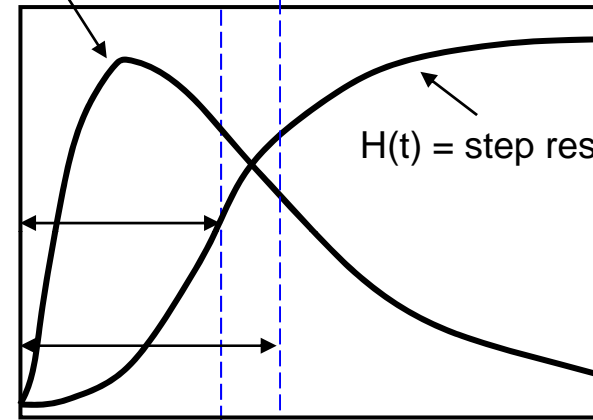

$H(t)$ = step response

median
of $v'(t)$
($T_{50\%}$)

$$T_D = \int_0^{\infty} tv'(t)dt$$

mean of $v'(t)$

Elmore Delay of a RC Tree

[Rubinstein-Penfield-Horowitz, T-CAD'83]

Lemma: when a step input is applied to a RC tree

$v_i(t)$ is monotonic in t for every node i in tree

Proof: $\Leftrightarrow v'_i(t) \geq 0$ at every node i ($v'_i(t) = h'_i(t)$)

\Leftrightarrow impulse response $h_i(t) \geq 0$ at every node i

Let $h_{\min}(t)$ be the min. voltage of any node at t

$h_{\min}(0+) \geq 0$

Assume that $h_{\min}(t_0) < 0$

Then, $\exists t_1 < t_0$ s.t. $h'_{\min}(t_1) < 0$

Let node i_{\min} achieve $h_{\min}(t_1)$ at t_1


Then, the current from any node i to i_{\min} is ≥ 0 at t_1

Since $h_i(t_1) \geq h_{\min}(t_1)$ & i connects i_{\min} via resistors

Since all currents $i \rightarrow i_{\min}$ charge the capacitor at i_{\min}

$h'_{\min}(t_1) \geq 0 \Rightarrow$ contradiction!

Apply impulse func. at $t=0$:

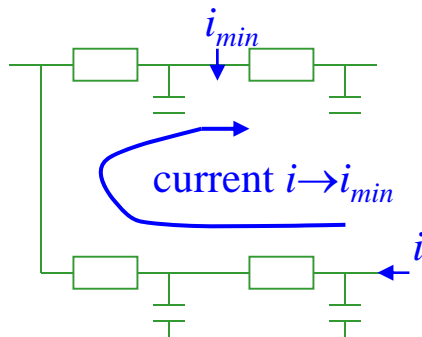

Elmore Delay in a RC Tree (cont'd)


P_i : path from input to node i ; S_i subtree rooted at i

R_{jk} : resistance of common path

$P_j \cap P_k$ from input to j & k

Theorem : Elmore delay to node i

$$T_{D_i} = \sum_k R_{ki} C_k$$

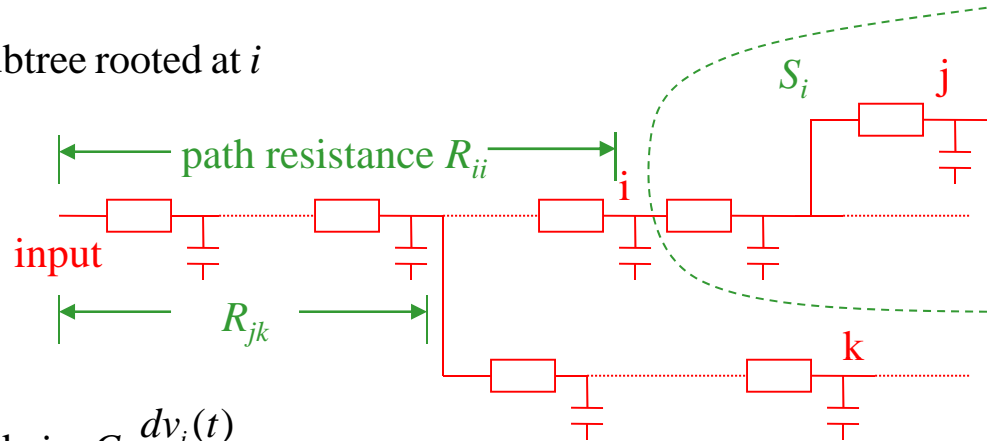

Proof : The current to cap. of node $i = C_i \frac{dv_i(t)}{dt}$

$$1 - v_i(t) = \text{The voltage drop on } P_i = \sum_{k \in P_i} R_k \cdot (\text{current to all cap's in } S_i)$$

$$= \sum_k (\text{current to cap } k) \cdot (\text{common path res. between } P_i \text{ and } P_k)$$

$$= \sum_k C_k \frac{dv_k(t)}{dt} \cdot R_{ki} = \sum_k R_{ki} C_k \frac{dv_k(t)}{dt}$$

$$T_{D_i} = \int_0^\infty v_i'(t) t \cdot dt = v_i(t) \cdot t \Big|_0^\infty - \int_0^\infty v_i(t) dt$$

$$= \lim_{T \rightarrow \infty} [v_i(T) \cdot T - \int_0^T v_i(t) dt] = \lim_{T \rightarrow \infty} (v_i(T) - 1) \cdot T + \int_0^\infty (1 - v_i(t)) dt$$

Elmore Delay in a RC Tree (cont'd)

- We shall show later on that $\lim_{T \rightarrow \infty} (1 - v_i(T)) \cdot T = 0$
i.e. $1 - v_i(T)$ goes to 0 at a much faster rate than $1/T$ when $T \rightarrow \infty$

- Let $f_i(t) = \int_0^t [1 - v_i(x)] dx$

$$\begin{aligned} f_i(t) &= \int_0^t \sum_k R_{ki} C_k \frac{dv_k(x)}{dx} dx \\ &= \sum_k R_{ki} C_k v_k(t) \\ &= \sum_k R_{ki} C_k - \sum_k R_{ki} C_k [1 - v_k(t)] \end{aligned}$$

$$f_i(\infty) = \sum_k R_{ki} C_k$$

$$\begin{aligned} \therefore T_{D_i} &= \lim_{T \rightarrow \infty} (1 - v_i(T))T + \int_0^\infty [1 - v_i(t)] dt \\ &= f_i(\infty) = \sum_k R_{ki} C_k \end{aligned}$$

