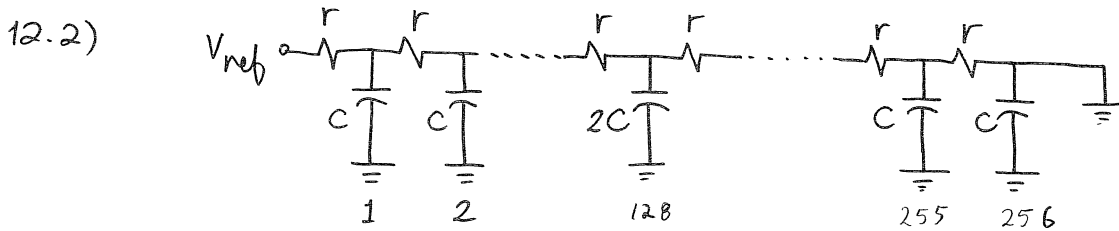


## Chapter 12 - Problems

12.1) The total number of switches is  $\sum_{i=1}^N 2^i = \underline{\underline{2(2^N - 1)}}$



In the equivalent circuit shown,  $r = \frac{400}{256} \Omega$ ,  $C = 0.1 \text{ pF}$ .

$2C$  represents the capacitance of the only switch that is ON.

This switch is considered to be in the middle of the string for the worst case time constant.

$$\begin{aligned}
 \tau &= \sum_{i=1}^{255} [(ir) \parallel (256-i)r]C + C(128r \parallel 128r) \\
 &= rc \sum_{i=1}^{255} \frac{i(256-i)}{256} + 64rc \\
 &= rc \sum_{i=1}^{255} i - \frac{rc}{256} \sum_{i=1}^{255} i^2 + 64rc \\
 &= rc \frac{(255)(256)}{2} - \frac{rc}{256} \frac{(255)(256)(510+1)}{6} + 64rc = 10987rc \\
 &= 10987 \times \frac{400}{256} \times 0.1 \text{ p} = \underline{\underline{1.7 \text{ ns}}}
 \end{aligned}$$

The settling time to 0.1% is  $\underline{\underline{7\tau = 12 \text{ ns}}}$

12.3) The total number of switches is  $2^{N/2} \cdot 2^{N/2} + 2 = 2^N + 2$

12.4) For the output opamp, the offset that can be tolerated is:

$$\frac{1}{2} \frac{0.1}{100} \times V_{ref} = \frac{1}{2} \frac{1}{1000} \times 5V = \underline{2.5 \text{ mV}}$$

For the two opamp in the middle, the offset must be less than

$$\frac{1}{2} \times 2.5 \text{ mV} \times 64 = \underline{80 \text{ mV}}$$

Note that the offset introduced from the middle opamps will be divided by 64 ( $=2^6$ ). The " $\frac{1}{2}$ " factor accounts for two opamps in the middle.

12.5) The ratio between the largest and the smallest resistor is

$$\frac{2^{10} R}{2R} = 2^9 = \underline{512}$$

the current ratio is the same as above.

12.6) The matching accuracy required for the  $b_2$  resistor,  $b_3$  resistor, and  $b_4$  resistor is 2 times, 4 times, and 8 times the matching accuracy of  $b_1$  resistor, respectively.


12.7) The worst case DNL happens at the transition from nominal 7LSB to 8LSB, assuming  $-0.5\%$  error for  $C$ ,  $2C$ , and  $4C$ , and  $+0.5\%$  error for  $8C$ .

$$DNL = 8LSB(1.05) - 7LSB(0.95) - LSB = \underline{\underline{0.75LSB}}$$


12.8) The largest resistance, in this case, is  $2^{N/2}R$  while the smallest resistance is  $2R$ ! Therefore, the resistance ratio is  $2^{(N/2-1)}$ . Noting the resistance ratio for a binary-scaled A/D is  $2^{N-1}$ , we have:

$$\text{Resistance ratio improvement} = \underline{\underline{2^{N/2} \text{ times}}}$$

12.9)

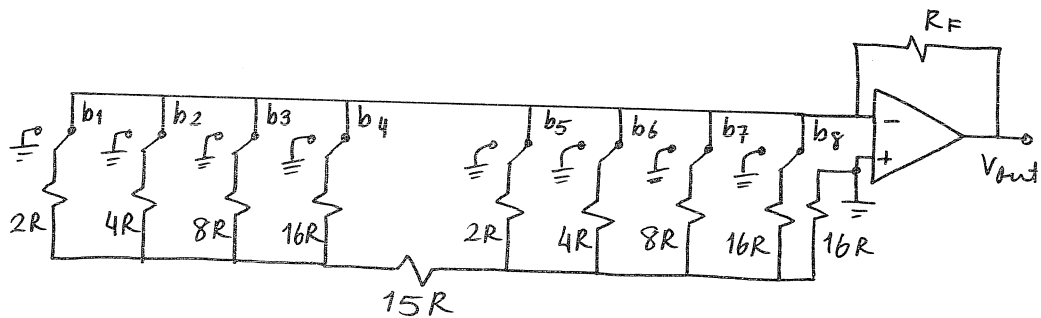

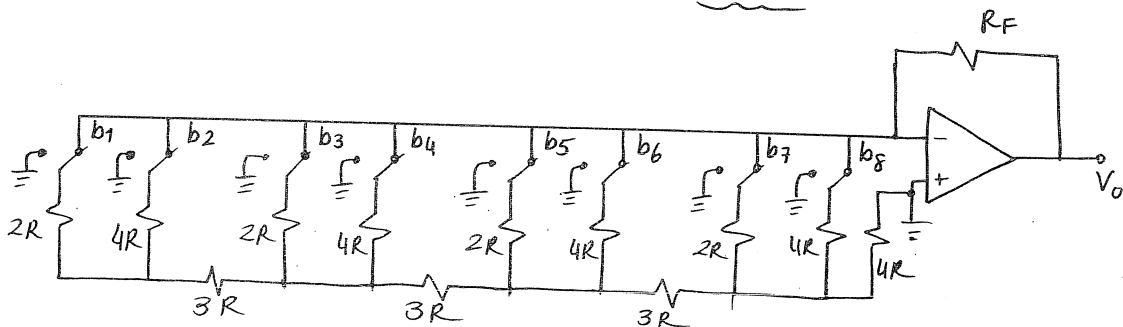
$$\text{Resistance Ratio} = 16R/(2R) = \underline{\underline{8}}$$




$$\text{Resistance Ratio} = 4R/(2R) = \underline{\underline{2}}$$

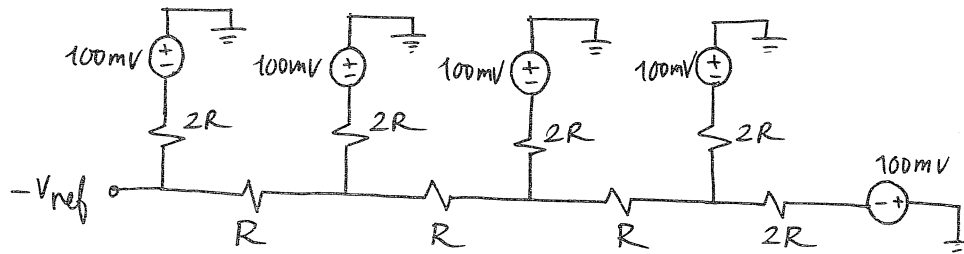12.10) The equivalent circuit for current calculation in  $2R$  - branches is shown below:



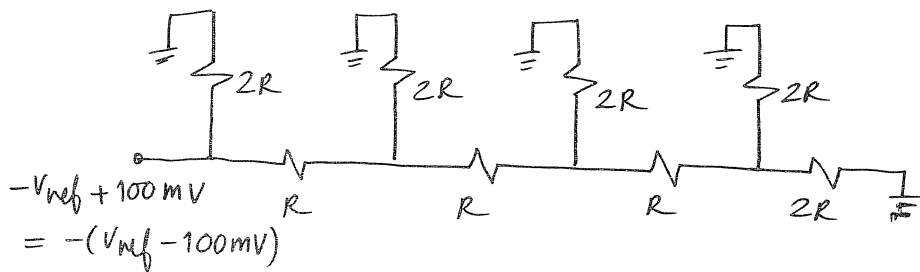The 100-mV voltage sources model the voltage drop of the switches. One end of  $2R$ -resistor is connected to  $-100\text{mV}$ . Therefore, they can all be connected together and the 100 mV voltage-source can be moved and added to the  $V_{ref}$  source. This will not change the current calculations of  $2R$ -resistors.



∴ In effect,  $V_{ref}$  has decreased by 100 mV and the circuit still operates as if there is no voltage drop across the switches.

12.11) If  $R_A = 2.01 R_B$ , the output error is:


$$\left(\frac{2}{2.01} - 1\right) \times 16 \text{ LSB} \approx \underline{0.08 \text{ LSB}}$$

If  $R_C = 2.01 R$ , the output error is:

$$\left(\frac{2}{2.01} - 1\right) \times 1 \text{ LSB} = \underline{0.005 \text{ LSB}}$$

It's obvious that precision for  $R_A$  is more important than the precision for  $R_C$ .

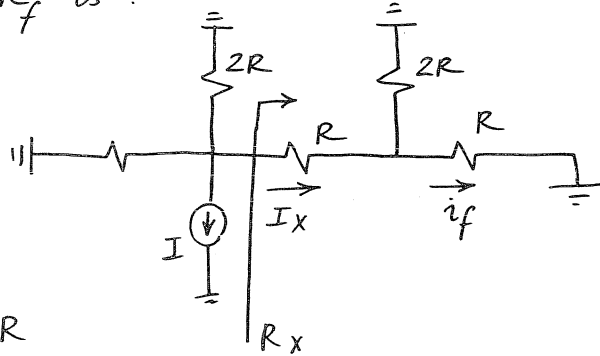12.12) Assuming only  $b_1=1$ , the current drawn through  $R_f$  is  $I$ .  
 " "  $b_2=1$ , " " " " " "  $I/2$ .  
 " "  $b_3=1$ , the equivalent circuit to find the current through  $R_f$  is:



$$R_x = R + \frac{2R}{3} = \frac{5}{3}R$$

$$I_x = I \frac{R}{R + \frac{5}{3}R} = \frac{3}{8}I$$

$$i_f = \frac{2R}{2R + R} I_x = \underline{\frac{1}{4}I}$$

With similar analysis, it can be shown that the current through  $b_4$  &  $R_f$  is  $\frac{I}{8}$ . Therefore,


$$\underline{V_o = 2R_f I (2^{-1} b_1 + 2^{-2} b_2 + 2^{-3} b_3 + 2^{-4} b_4)}$$

(Cont.)

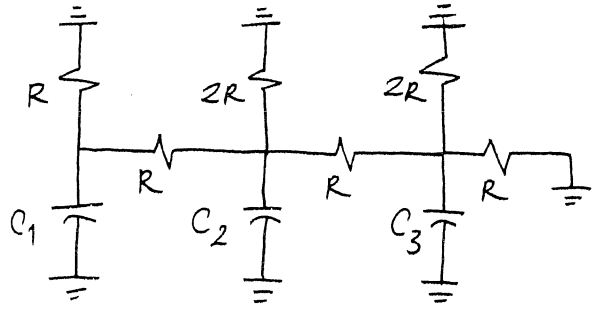12.12) (cont.) The equivalent circuit for the open circuit time-constant analysis is shown:

where

$$R = 10 \text{ K}\Omega, C = 0.5 \text{ pF}$$



$$\tau = C_3 \frac{R}{2} + C_2 \frac{5R}{8} + C_1 \frac{21R}{32} = 1.78125 RC = 8.9 \text{ nsec}$$

$$\Rightarrow \underline{\omega_{3dB} = \frac{1}{\tau} = 2\pi \times 17.9 \text{ MHz}}$$

12.13) Assuming  $R_f = 2 \text{ K}\Omega \Rightarrow 8 \text{ LSB} = 2 \text{ V} \Rightarrow 1 \text{ LSB} = 0.25 \text{ V}$

For "0000" input,  $V_o = (0 + 0.15) \text{ LSB} = \underline{0.0375 \text{ V}}$

For "1000" input,  $V_o = (8 + 0.15 + \frac{0.2}{2}) \text{ LSB} = \underline{2.0625 \text{ V}}$


For "1111" input,  $V_o = (15 + 0.15 + 0.2) \text{ LSB} = \underline{3.8375 \text{ V}}$

12.14)  $\frac{0.5}{2^{(4-1)}} = \frac{0.5}{8} = 62.5 \text{ mV}$


12.15) Let's denote the voltage of the node connecting  $Q_1$ ,  $Q_2$ , &  $Q_3$  by  $V_x$ . The following table shows  $V_x$  as a function of  $d_i$  &  $\bar{d}_i$ .

| $d_i$     | $\bar{d}_i$ | $V_x$      |
|-----------|-------------|------------|
| 0         | 0           | -1         |
| 0         | $-V_{SS}$   | $-V_{GS2}$ |
| $-V_{SS}$ | 0           | -1         |
| $-V_{SS}$ | $-V_{SS}$   | $-V_{SS}$  |

The  $V_x$  wave forms:

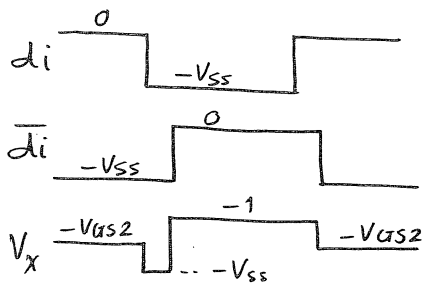


overlapping  $d_i$  &  $\bar{d}_i$

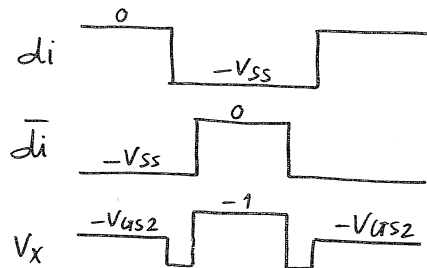

non-overlapping  $d_i$  &  $\bar{d}_i$

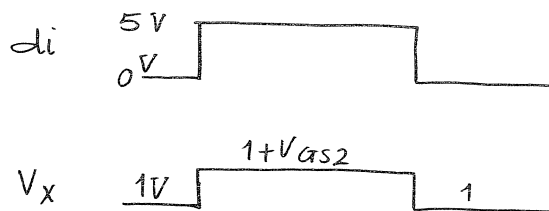12.16) Let's denote the voltage of the node connecting  $Q_1$ ,  $Q_2$ , and  $Q_3$  by  $V_x$ .



12.17) Using (1.67) with  $I_D = 0.1 I_{ref} = 5 \mu A$ , we have

$$5 \mu = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2 = (46 \mu) \frac{W}{L} (3-1)^2$$

$$\Rightarrow \frac{W}{L} = 0.027$$

$$\Delta I_D = g_m \Delta V_{GS}$$

$$\text{where } g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t) = 96 \mu \times 0.027 \times 2 = 5 \frac{\mu A}{V}$$

$$\& \Delta V_{GS} = 1 mV$$

$$\Rightarrow \Delta I_D = 5 \frac{\mu A}{V} \times 1 mV = \underline{5 nA}$$

12.18)  $50 \mu = (46 \mu) \frac{W}{L} (3-1)^2 \Rightarrow \frac{W}{L} = 0.27$

$$g_m = \frac{2 I_D}{V_{GS} - V_t} = \frac{100 \mu}{2 V} = 50 \frac{\mu A}{V}$$

$$\Rightarrow \Delta I_D = g_m \Delta V_{GS} = 50 \frac{\mu A}{V} \times 1 mV = \underline{50 nA}$$