

System-on-Chip Design Beyond 50 GHz

*Sorin Voinigescu, Michael Gordon, Chihou Lee,
Terry Yao, Alain Mangan, and Ken Yau*

University of Toronto

July 20, 2005



Outline

- Motivation
- Optimal sizing of active and passive devices at mm waves
- 60-GHz building block design methodologies
- 60-GHz SOC example
- Conclusions



Why mm-waves ?

- Speed is free ... if you can afford CMOS mask costs!
- With TI's 2-GHz digital transceiver ... the days of RF are (almost) over
- Larger bandwidth => higher data rates, simpler radio architectures
- MOSFET scaling improves f_T , f_{MAX} , NF_{MIN} , g_m/I , R_n while V_{DD} saturates
- Smaller passives with higher Q (except varactors), on-chip antenna feasible for some applications

Simpler, smaller area, and lower cost circuits






Applications

- **77-GHz automotive radar** (60 million cars produced in 2002) and others ...
 - ◆ Mm-wave imaging (dental, airport security, 3D inspection of objects)
 - ◆ Mm-wave sampling ADCs
 - ◆ 60/80 GHz WLAN and Gigabit Ethernet
 - ◆ Mm-wave sensors and motes
 - ◆ Instrumentation
 - ◆ High-speed data communications



   What can you count on in production today?




MOS-HBT
Cascode

- $f_T, f_{MAX} > 140$ GHz for both HBTs and FETs
- f_T of MOSFET cascode is $< 60\%$ of MOSFET f_T
- Use CS/CE or HBT-based cascodes




 Device scaling: Can SiGe HBTs reach 500 GHz?



- 45-nm n-MOSFETs with strain > 400 GHz?
- SiGe HBT > 500 GHz with $NF_{MIN} = 1.6$ dB @ 60 GHz

Impact of scaling on OP_{1dB}

 




- Linearity depends on $f_{MAX}(V_{GS})$ flatness at peak
- Linear voltage swing at input/output decreases with every new node
- current swing is constant over nodes
- Current and transistor size must be increased to generate the same power as in older nodes

$$OP_{1dB} \propto \frac{\Delta I_{DS} \times V_{MAX}}{8} = 50 \frac{\mu W}{\mu m} \text{ in 90-nm MOSFETs}$$

$$OP_{1dB} \propto \frac{\Delta I_C \times V_{MAX}}{8} = 376 \frac{\mu W}{\mu m} \text{ in SiGe HBTs}$$

Inductors & transformers ... are getting smaller

   - Minimize footprint and stripe width to reduce substrate loss
- Use series-staked multi-layer design



T. Dickson et al. IMS-2004

Sorin Voinigescu, IWSOC, Banff, July 20, 2005

Mm-wave vs. RF/microwave design

- The Good

- ◆Inductor size becomes comparable to transistor size
- ◆Optimal transistor size, bias current and power dissipation decrease with frequency
- ◆CG/CB noise matching becomes coincidental with 50- Ω matching around 70 GHz

- The Bad

- ◆Higher noise, reduced gain, and reduced output power
- ◆Linearity (IIP1, IIP3) and dynamic range suffer due to lower bias currents, exacerbated by lower breakdown voltages
- ◆ R_n increases making noise matching more sensitive to process variations.

- The Ugly

- ◆Test setups are cumbersome and test equipment cost is prohibitive



Mm-wave VCO design


- Colpitts has higher f_{osc} and built-in buffering over cross-coupled topology

$$\frac{1}{f_{osc}} = 2\pi \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} + k C_{GD} \right)}$$


$$\omega_{osc}(n-MOS) \leq \frac{g'_m Q_{eff}}{C'_{gs} + 4C'_{gd} + C'_{db} + \frac{C_L}{W}}$$

$$\omega_{osc}(Colpitts) \leq \frac{g'_m Q_{eff}}{C'_{as} + C'_{sb}}$$


 
- Bias at optimal NF_{MIN} current density (J_{opt}) of transistor/cascode
- HBT version has 6-10 dB better phase noise due to higher V_{osc}



$$L(f_m) = \frac{|I_n|^2}{V_{osc}^2} \times \frac{1}{f_m^2} \times \frac{1}{C_1^2 \left(\frac{C_1}{C_2} + 1 \right)^2}$$

 

Record low phase noise SiGe BiCMOS VCOs

  

- Cascode stage for improved buffering
- Inductive degeneration for linearity and low noise
- AMOS varactors for high Q and C ratio

C. Lee et al. CSICS-2004



Optimal of mm-wave LNA topology: largely unchanged

Common emitter/source



- ◆ low-voltage, low-noise, good linearity,
- ◆ poor isolation => difficult to separately design input/output network

Common base/gate

- ◆ low-to-moderate noise, good isolation
- ◆ poor linearity, difficult to simultaneously match noise and source impedance

Cascode (CE+CB, CS+CG, CS+CB)

  - ◆ best isolation, low-to-moderate noise, easy to match, good linearity
- ◆ higher supply voltage



RF LNA design methodology works beyond 50 GHz!

$$L_S = \frac{Z_0}{\omega_T(\text{cascode})}$$


$$G \approx \left(\frac{f_T}{f}\right)^2 \frac{R_P}{Z_0}$$

$$Z_{in} \approx Z_O + j\omega(L_G + L_S) + \frac{1}{j\omega C_{in}}$$

$$L_G \approx \frac{1}{\omega^2 C_{in}} - L_S$$

$$Z_{SOPT} = Z_O$$

$$Z_{IN} = Z_O$$




 


$$h_{21} = \frac{y_{21}}{y_{11}} = \frac{f_T}{jf}$$



$$y_{11} = \frac{f}{f_T} y_{21} \approx j \frac{f}{f_T} g_m$$

- Matching of real part of input impedance is
 - ♦ broadband,
 - ♦ independent of transistor size, and
 - ♦ independent of bias current => can increase current for better linearity
- Increasing Z_0 (to save power) degrades gain.

    180-nm SiGe HBT vs. 90-nm CMOS LNAs @ 52 GHz




  - identical inductors
- identical centre frequency
- g_m & inductors dictate performance






M. Gordon et al. ESSCIRC-2004


 
Portfolio of 65-GHz SiGe BiCMOS building blocks



  
 
65 GHz 2-stage cascode SiGe LNA
 $V_{CC} = 2.5V$ ($I_{CC} = 13mA$)



  65-GHz Doppler radar transceiver with patch antenna



  RX single-ended conversion gain at IF=730MHz



File Operation Status, A:\T14.GIF file saved



Conclusions

- Mm-wave SOCs can be realized in today's production 180-nm SiGe BiCMOS and 90-nm RFCMOS technologies.
- Circuit topologies and design methodologies are largely unchanged from those used at 2-10 GHz.
- Mm-wave die size and cost (significantly) smaller than at 2-10 GHz.
- Low-to-moderate volume products make economic sense in coarser lithography SiGe BiCMOS technology.
- Testing is the bottleneck ... but why bother testing at mm-waves?






Acknowledgements

- Jazz Semiconductor and TSMC for chip fabrication
- NSERC, Micronet, CITO, Gennum, Jazz Semiconductor and Quake Technologies for funding
- CFI and OIT for equipment grants
- CMC and Jaro Pristupa for CAD support



   n-MOSFET characteristic current densities invariant across technology nodes and foundries (65-nm sims only)




Peak f_T @ $0.3 \text{ mA}/\mu\text{m}$

Peak f_{MAX} @ $0.2 \text{ mA}/\mu\text{m}$

NF_{MIN} @ $0.15 \text{ mA}/\mu\text{m}$



 Biasing at I_{peakFT} in power amplifier, linear amplifier, or upconvert mixer



- Linearity depends on $f_{MAX}(I_{DS})$ flatness

$$OIP3 \sim \frac{f_{MAX}}{\frac{\partial^2 f_{MAX}}{\partial I_{C(DS)}^2}} \text{ vs. } \frac{g_m}{\frac{\partial^2 g_m}{\partial I_{C(DS)}^2}}$$

- f_{MAX} captures both input (through f_T) and output linearity (through g_{ds})
- But optimal linearity bias corresponds to peak



$$f_T : 0.3 \text{ mA}/\mu\text{m}$$

- Allows for 400 $\mu\text{A}/\mu\text{m}_{(p-p)}$ or 460 mV_{p-p} of

linear swing



The mirage of the linearity “sweet-spot”

  

$$OIP3 \sim \frac{f_{MAX}}{\frac{\partial^2 f_{MAX}}{\partial V_{GS}^2}} \text{ vs. } \frac{g_m}{\frac{\partial^2 g_m}{\partial V_{GS}^2}}$$

$$OIP3 \sim \frac{f_{MAX}}{\frac{\partial^2 f_{MAX}}{\partial I_{C(DS)}^2}} \text{ vs. } \frac{g_m}{\frac{\partial^2 g_m}{\partial I_{C(DS)}^2}}$$

Small signal linearity (oxymoron?) vs. large signal linearity!





Why AMOS vs. pn-junction varactors @ mm-waves?

- Higher Q
- Larger cap. ratio
- Linear tuning curve
- Lower supply voltage

Use **minimum** finger length and width for highest Q

C. Lee et al. CSICS-2004

  



Mm-wave circuit design guidelines

- Use RF-like lumped rather than distributed passives:
 - ◆ Inductor vs. t-line tanks and matching networks
 - ◆ Transformers vs. hybrid couplers
 - ◆ Inductor/MIM poly-phase filter vs. 90deg hybrid coupler
- Isolation remains biggest issue:
 - ◆ Possible to have ground plane below inductors to improve isolation
 - ◆ Patch antenna with M1 ground plane



SiGe HBT LNA: Linearity Measurements

  Measured 1dB compression at
50 GHz ($V_{CC}=3.3V$)



- Input 1 dB compression point of **-14 dBm**
- Output 1 dB compression point of **3 dBm**

M. Gordon et al. ESSCIRC-2004

