
Project 1
ECE1371S

1) Feedback

Consider the feedback circuits shown below in fig 1(a) and 1(b) and using the simple opamp model shown in 1(c).

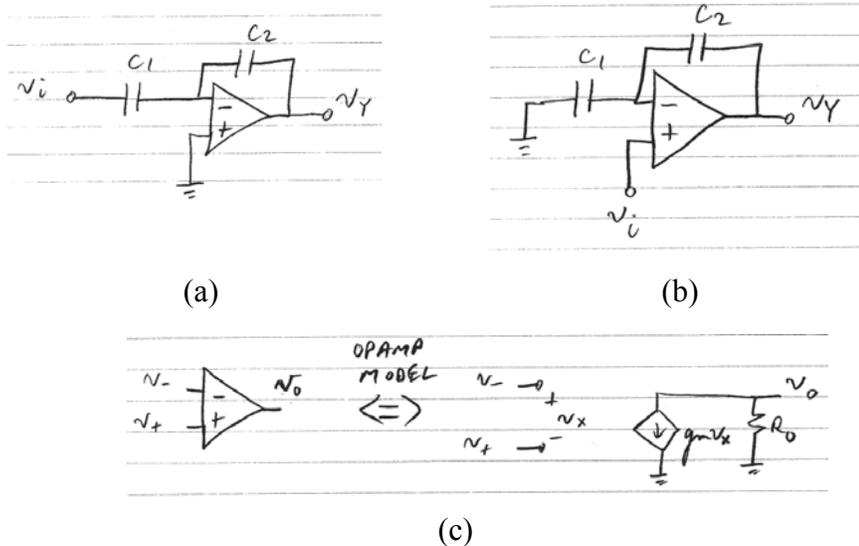


Figure 1

Use feedback analysis from Sedra/Smith and replace the opamp by its model in fig. 1(c). (note that there is a feedforward term in fig. 1(a) so be careful to deal with it)

- Find $A(s)$ and $\beta(s)$ for both the circuits in 1(a) and 1(b) using the 2-port approach of Sedra/Smith.
- Defining the 2-port loop gain as $L_2(s) \equiv A(s)\beta(s)$, find $L_2(s)$ for both circuits in 1(a) and 1(b).
- Find the pole of the system for both cases when $g_m R_0 \gg 1$.
- Using the different $L_2(s)$ for the 2 cases, find example values where the phase margin is significantly different in the 2 cases (use matlab here).