

(CT1)

CONTINUOUS-TIME Δ - Σ MODULATORS

SOME OF THE LOWEST POWER AND HIGHEST SPEED Δ Σ MODULATORS BUILT USING CONT-TIME LOOP FILTERS

EX IN 2010 ISSCC PAPER 27.1

SIGNAL BANDWIDTH 125 MHz (LOWPASS)

SAMPLE RATE 4 GHz (OSR = 16)

45 nm CMOS, $V_{DD} = 1.1, 1.8$

3rd ORDER CT ADC, 4b QUANTIZER

POWER = 256 mW

DR = 70 dB THD = -74 dB FS

SNR = 65 dB SNOR = 65 dB

ADVANTAGES


- INHERENT ANT-ALIASING BEFORE SAMPLING
- SAMPLING TAKES PLACE AT AN INSENSITIVE POINT IN LOOP
- CAN BE CLOCKED FASTER THAN SC COUNTERPART (PERHAPS 2-4 TIMES FASTER)
CT \Rightarrow LIMITED BY QUANTIZER + DAC
SC \Rightarrow LIMITED BY OPAMP SETTLING

DISADVANTAGES

- USUALLY POORER LINEARITY
- SENSITIVE TO CLOCK JITTER OF DAC

LOOP FILTER DESIGN

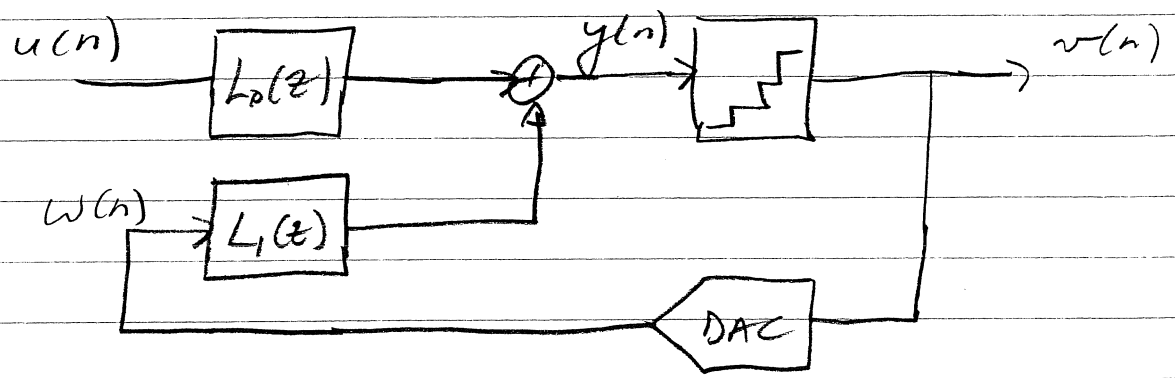BASED ON MATCHING DISCRETE-TIME MODULATOR



DISCRETE-TIME SAMPLE-RATE, T

$$T = \frac{1}{f_s}$$

WANT

$$z^{-1} [L_1(z)] = \mathcal{L}^{-1} [R_c(s) L_{c1}(s)] \Big|_{t=nT}$$


INVERSE Z

INVERSE LAPLACE


TRANSFORM

TRANSFORM

=> IMPULSE INVARIANT METHOD

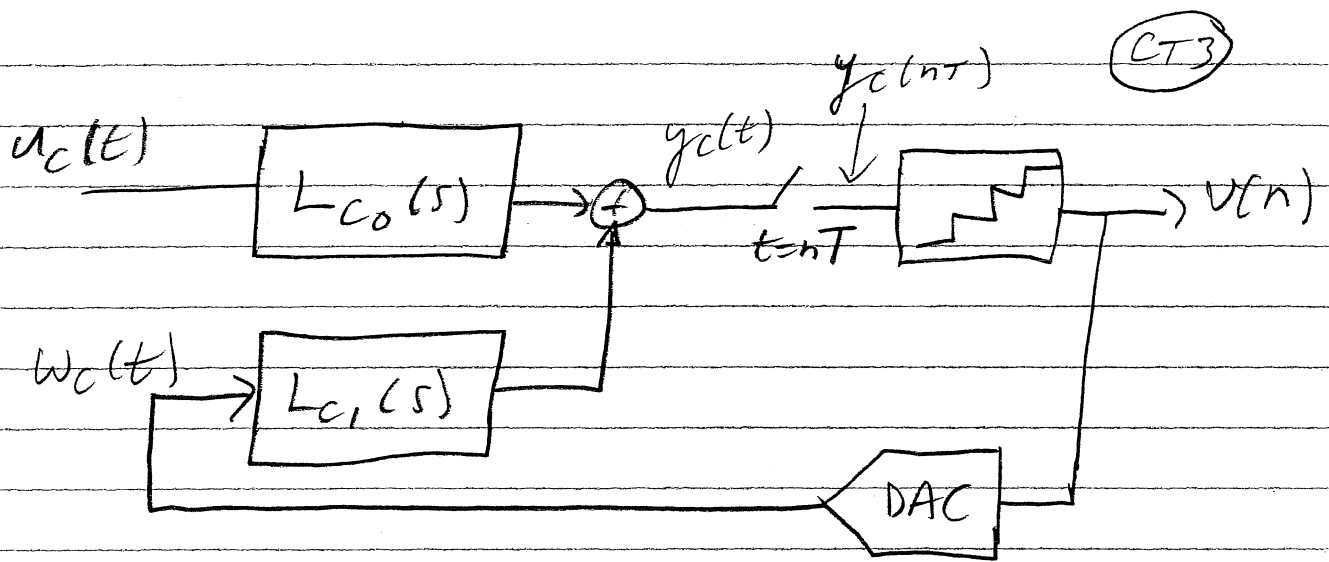

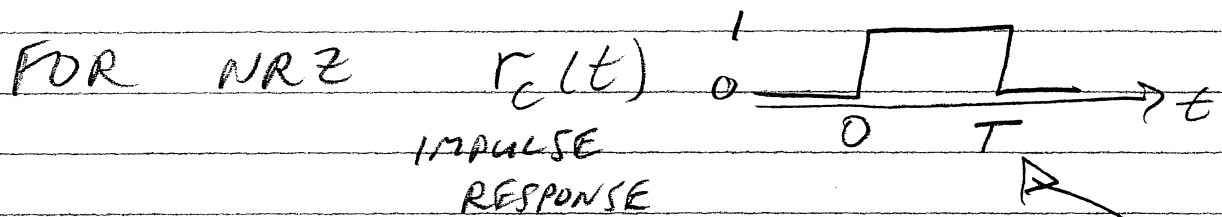$R_c(s)$ REPRESENTS DAC PULSE TRANSFER FUNCTION



IN CASE OF NRZ $R_c(s)$ ABOVE

Z-DOMAIN	S-DOMAIN
$\frac{1}{z-1}$	$\frac{1}{Ts}$
$\frac{1}{(z-1)^2}$	$\frac{-Ts+2}{2T^2s^2}$
$\frac{1}{(z-1)^3}$	$\frac{2T^2s^2 - 3Ts + 6}{6T^3s^3}$

IMPULSE INVARIANCE EQUIVALENCIES
TABLE (1)

EXAMPLE

$$\text{GIVEN } NTF(z) = (1 - z^{-1})^2$$

$$\& STF(z) = z^{-1}$$

$$\text{FIND } L_{C_0}(s), L_{C_1}(s)$$

$$1) \text{ FIND } L_0(z), L_1(z)$$

$$L_0(z) = \frac{STF(z)}{NTF(z)} = \frac{z^{-1}}{1 - 2z^{-1} + z^{-2}}$$

$$L_0(z) = \frac{z}{z^2 - 2z + 1} \quad (1)$$

$$L_1(z) = 1 - \frac{1}{NTF(z)} = \frac{NTF(z) - 1}{NTF(z)}$$

$$= \frac{-2z^{-2} + z^{-2}}{1 - 2z^{-1} + z^{-2}}$$

$$L_1(z) = \frac{-2z + 1}{z^2 - 2z + 1} \quad (2)$$

2) BREAK $L_0(z)$ & $L_1(z)$ INTO PARTIAL FRACTION EXPANSIONS

$$L_0(z) = \frac{1}{z^2 - 2z + 1} + \frac{-1}{z - 1}$$

$$L_0(z) = \frac{1}{(z-1)^2} + \frac{1}{z-1} \quad (3)$$

(CTS)

$$L_1(z) = \frac{-1}{(z-1)^2} + \frac{-2}{z-1} \quad (4)$$

3) USE TABLE (1) TO FIND $L_{C_0}(s), L_{C_1}(s)$


$$L_{C_0}(s) = \frac{-Ts+2}{2T^2s^2} + \frac{1}{Ts}$$

$$L_{C_0}(s) = \frac{Ts+2}{2T^2s^2} \quad (5)$$


$$L_{C_1}(s) = \frac{Ts-2}{2T^2s^2} + \frac{-2}{Ts}$$

$$L_{C_1}(s) = \frac{-3Ts-2}{2T^2s^2} \quad (6)$$

4) IMPLEMENTATION

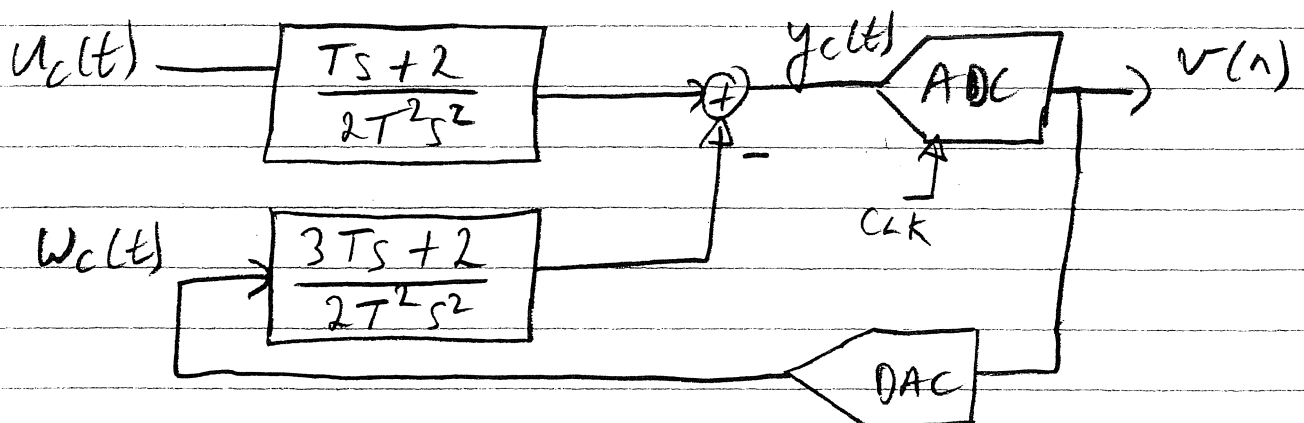


CT6

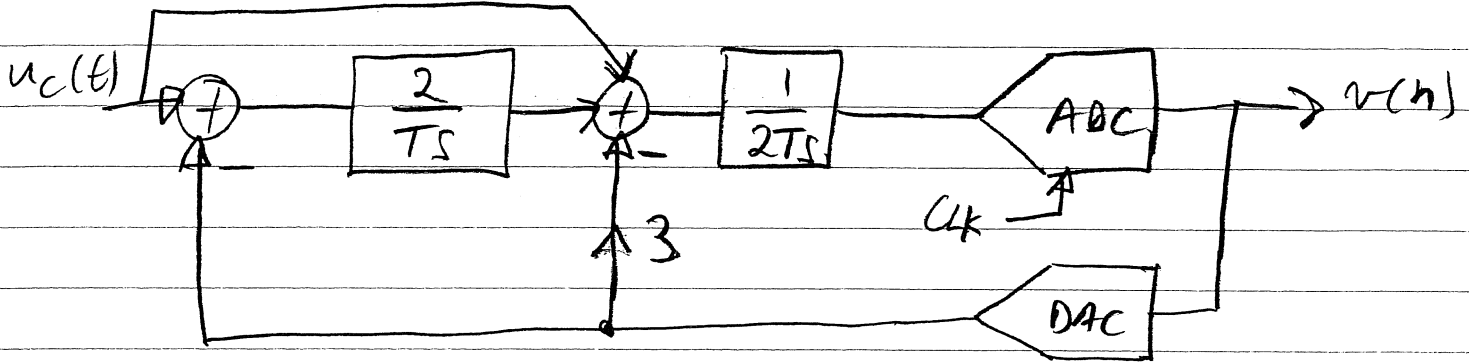

POSSIBLE IMPLEMENTATION

EXCESS LOOP DELAY

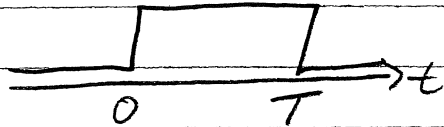
ABOVE WAS FOR CASE OF ADC/DAC
IMPULSE RESPONSE





BUT THIS LEAVES NO TIME FOR ADC TO
RESOLVE ITS DIGITAL OUTPUT & DAC
TO TURN ON.

MORE PRACTICAL IS TO HAVE


ADC/DAC IMPULSE RESPONSE OF

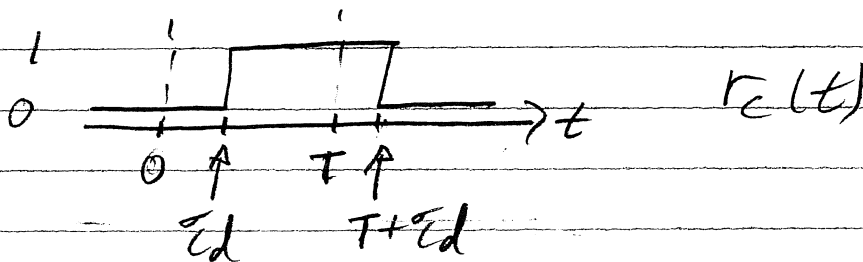

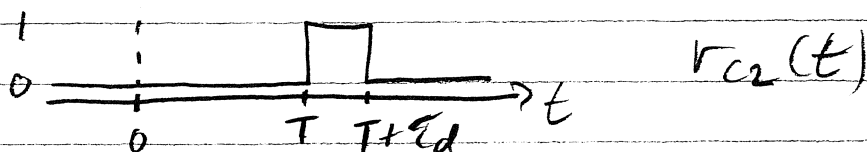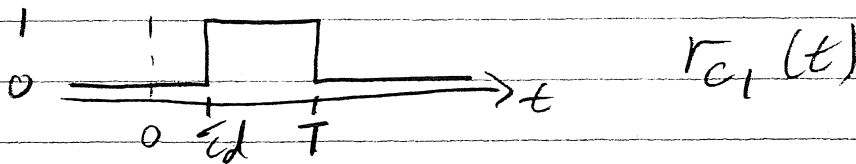CAN BE THOUGHT OF AS SUM
OF 2 PULSE RESPONSES $v_c(t) = v_{c1}(t) + v_{c2}(t)$



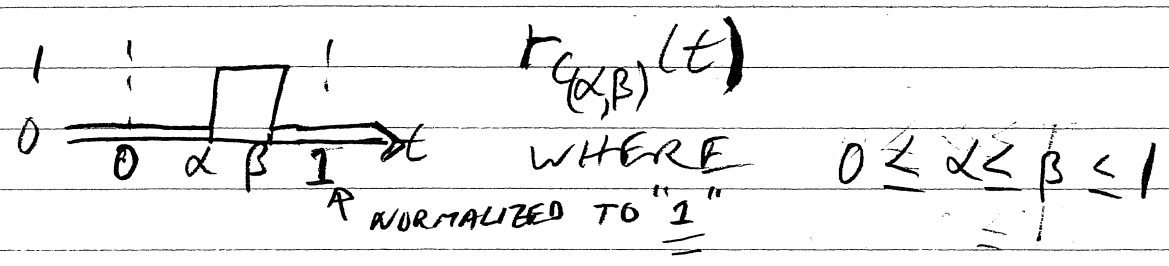NEED TO FIND NEW IMPULSE INVARIANCE TABLE. CAN SHOW FOR



S-DOMAIN	Z-DOMAIN
$\frac{1}{Ts}$	$\frac{\beta - \alpha}{z - 1}$
$\frac{1}{Ts^2}$	$\frac{\left[\beta - \frac{\beta^2}{2} - \alpha + \frac{\alpha^2}{2}\right]z + \left[\frac{\beta^2}{2} - \frac{\alpha^2}{2}\right]}{(z - 1)^2}$

SO $\Gamma_{C_1}(t)$ HAS $\alpha = \sigma_d/T$
 $\beta = 1$


$\Gamma_{C_2}(t)$ HAS $\alpha = 0$
 $\beta = \sigma_d/T$
AND OCCURS IN NEXT SAMPLE

SO

$$\Gamma_C(t) = \Gamma_C\left(\frac{\sigma_d}{T}, 1\right)(t) + \Gamma_C\left(0, \frac{\sigma_d}{T}\right)(t - T)$$

FOR ABOVE, WE CAN FIND.

FOR $r_c(t)$

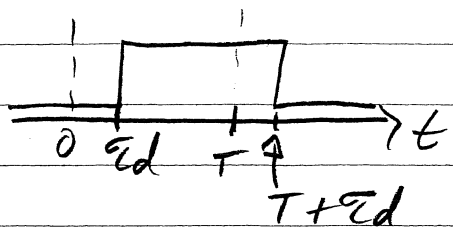

$$\tau_d' = \frac{\tau_d}{T}$$

TABLE (2)

$\frac{1}{TS}$	$\frac{1 - \tau_d'}{z-1} + z^{-1} \frac{\tau_d'}{z-1}$
$\frac{1}{T^2 S^2}$	$\frac{(0.5 - \tau_d' + 0.5 \tau_d'^2)z + 0.5 - 0.5 \tau_d'^2}{(z-1)^2}$ $+ z^{-1} \frac{(\tau_d' - 0.5 \tau_d'^2)z + 0.5 \tau_d'^2}{(z-1)^2}$

DUE TO PULSE EXTENDING INTO NEXT TIME INTERVAL => MAKES z-DOMAIN ORDER 1 HIGHER AND MORE UNSTABLE


EXAMPLE

CONSIDER $NTF(z) = (1 - z^{-1})$

$$L_1(z) = \frac{1 - NTF(z)}{NTF(z)} = \frac{1 - (1 - z^{-1})}{1 - z^{-1}} = \frac{z^{-1}}{1 - z^{-1}}$$

$$L_1(z) = \frac{1}{z - 1}$$

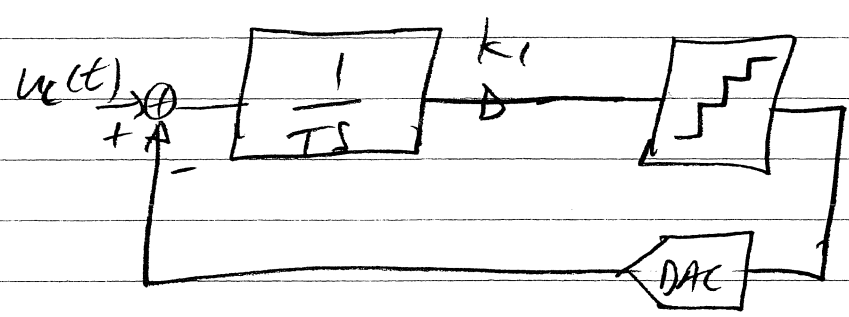$\Rightarrow L_{c1}(s) = \frac{1}{TS}$ IF NO EXCESS DELAY LOOP



BUT IF ADC HAS DELAY OF $\epsilon'_d = \frac{\epsilon_d}{T}$


$$L_{c1}(s) = \frac{k_1}{TS} \Rightarrow L_1(z) = k_1 \frac{(1 - \epsilon'_d)}{z - 1} + \frac{k_1 z^{-1} \epsilon'_d}{z - 1}$$

$$L_1(z) = \frac{k_1 (1 - \epsilon'_d)}{(z - 1)} + \frac{k_1 \epsilon'_d}{z(z - 1)}$$

$$L_1(z) = \frac{k_1(1 - \epsilon'd)z + k_1\epsilon'd}{z(z-1)}$$

NO LONGER 1ST ORDER!!

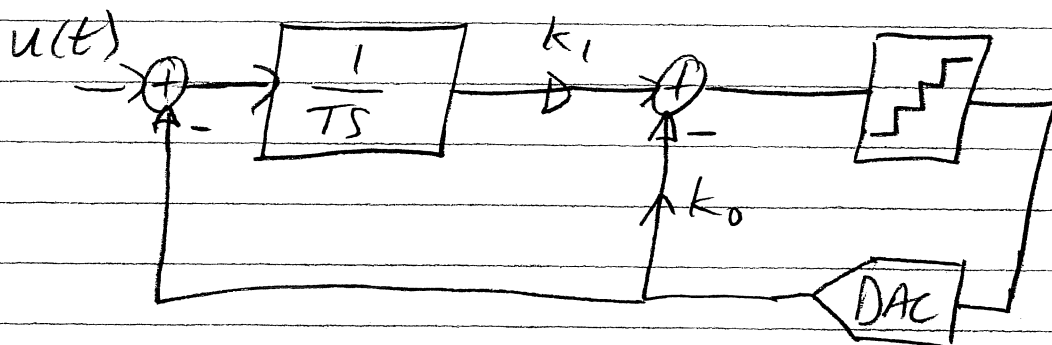TO CORRECT ADD EXTRA FEEDBACK
COEFF AROUND A/D/DAC LOOP



$$L_0(s) = k_0 + \frac{k_1}{TS}$$


$$L_1(z) = k_0 z^{-1} + \frac{k_1(1 - \epsilon'd)z + k_1\epsilon'd}{z(z-1)}$$

$$= \frac{(k_1 - k_1\epsilon'd + k_0)z + (k_1\epsilon'd - k_0)}{z(z-1)}$$

WANT $L_1(z) = \frac{1}{z-1}$

REASON $L_1(z) = k_0 z^{-1} + \dots$

DAC IMPULSE RESPONSE

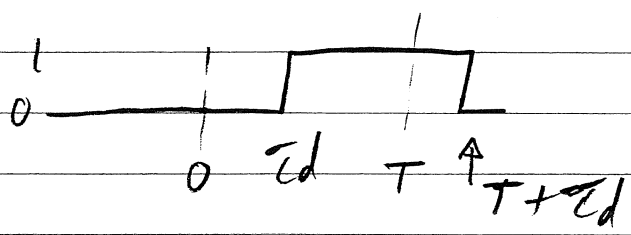

SO DISCRETE-TIME IMPULSE RESPONSE IS

0 1 0 0 0 ...

(A SINGLE "1" AT $n=1$)

AND THAT MULTIPLIED BY k_0 AND ADDED TO INPUT OF ADC (NO FILTER)

$$\text{So } k_1 \bar{e}_d - k_0 = 0 \Rightarrow k_0 = k_1 \bar{e}_d$$

$$\text{and } k_1 - k_1 \bar{e}_d + k_0 = 1$$


$$k_1 - k_1 \bar{e}_d + k_1 \bar{e}_d = 1 \Rightarrow$$

$$\boxed{\begin{array}{l} k_1 = 1 \\ k_0 = \bar{e}_d \end{array}}$$

$$L_1(z) = \frac{1}{z-1}$$

MORE COMPLICATED FOR HIGHER-ORDER SYSTEMS, USE SYMBOLIC EQN SOLVER.


IN GENERAL,

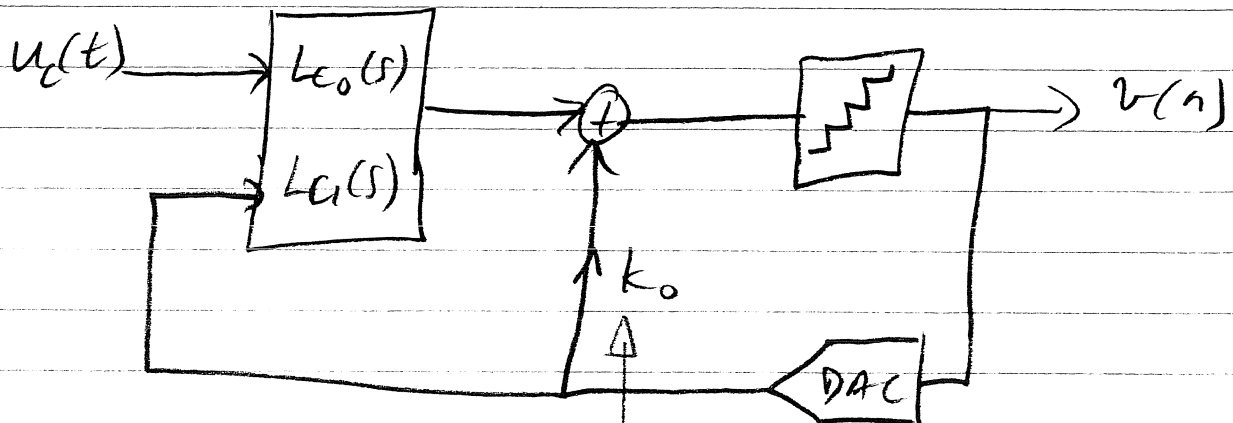

ADDED FOR
EXCESS LOOP DELAY

A COMMON CASE IS $\tau_d = \frac{T}{2}$

so $\tau_d = \frac{1}{2}$

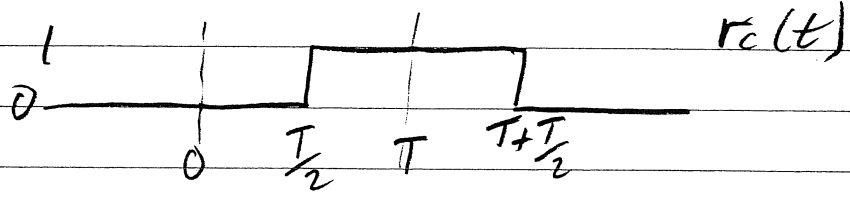

Clock ADC AT TIME 0 AND THEN PUT DAC PULSE OUT AT TIME $\frac{T}{2}$

HERE

<u>CONT-TIME</u>	<u>DISCRETE-TIME</u>
$\frac{1}{Ts}$	$\frac{0.5 + 0.5z^{-1}}{(z-1)}$
$\frac{1}{Ts^2}$	$\frac{\frac{1}{8}z + \frac{3}{4} + \frac{1}{8}z^{-1}}{(z-1)^2}$