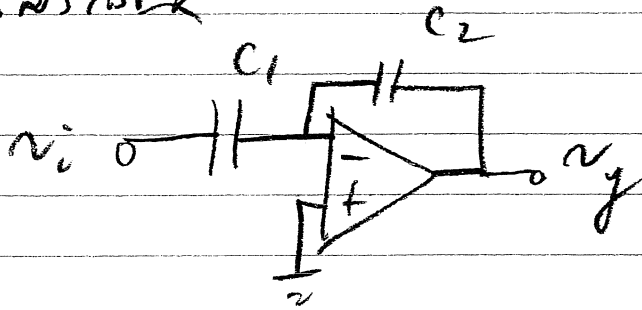



# FEEDBACK RE-VISITED

(1)

CONSIDER




a)


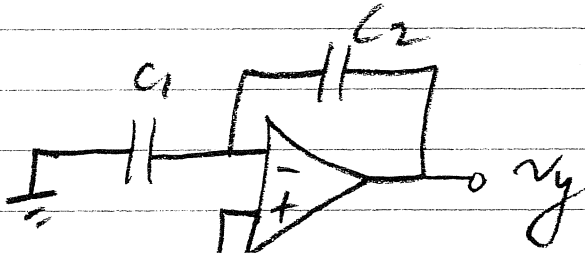


b)

WHERE OPAMP MODEL IS

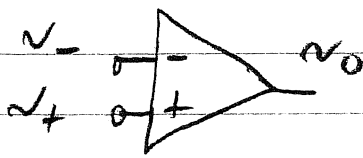

$\Leftrightarrow$

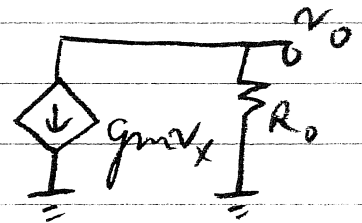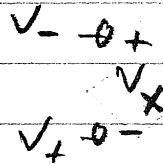

(1A)

WANT TO USE FEEDBACK

ANALYSIS TO FIND  $A(s)$ ,  $\beta(s)$



FOR a) & b)

AND FIND POLE FOR BOTH


CASES WHEN  $g_m R_o \gg 1$

$C_2 \gg C_1$

a)

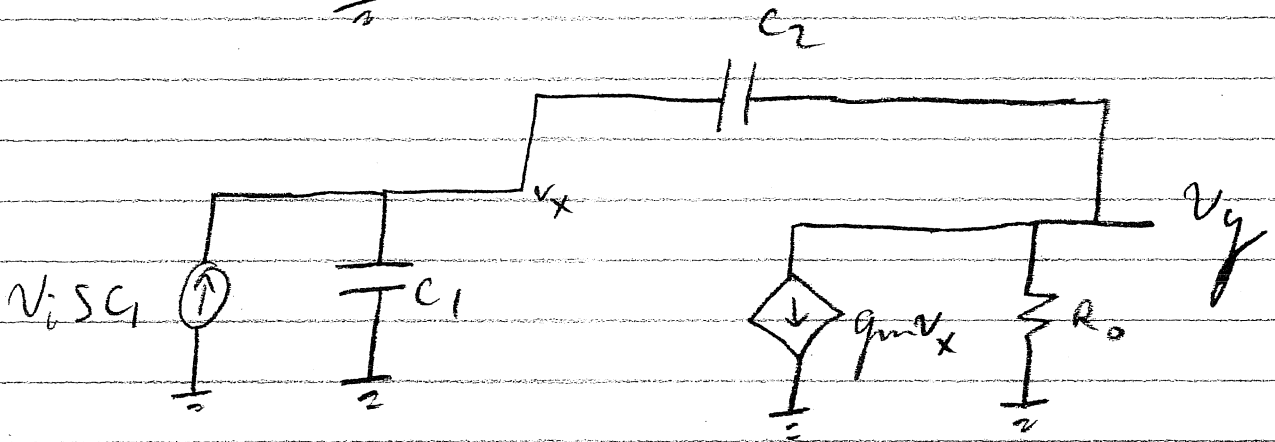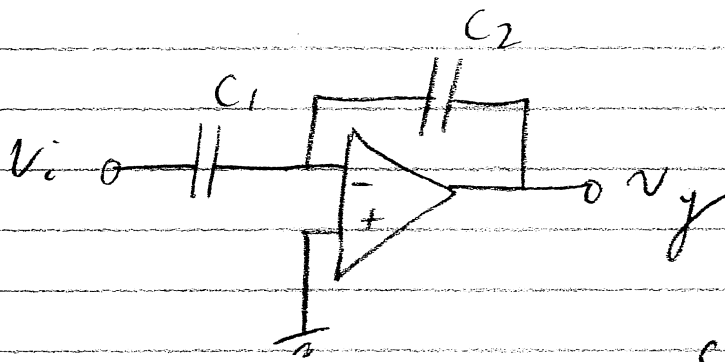

RECALL

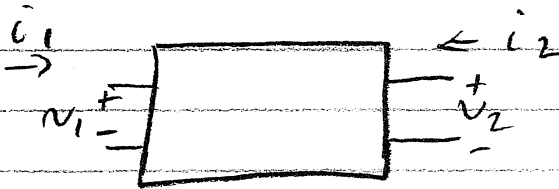

$y \Rightarrow$  ADMITTANCES

$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}$$


$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0}$$

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$





10

EQUIVALENT CIRCUIT

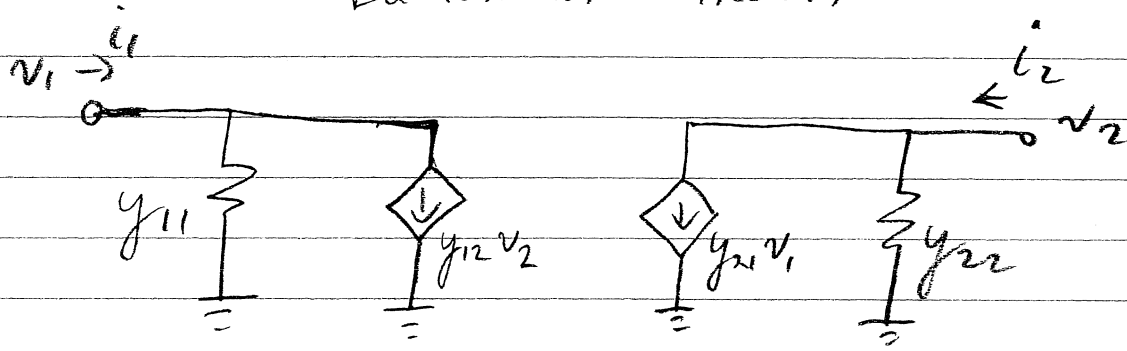


2

SD FOR

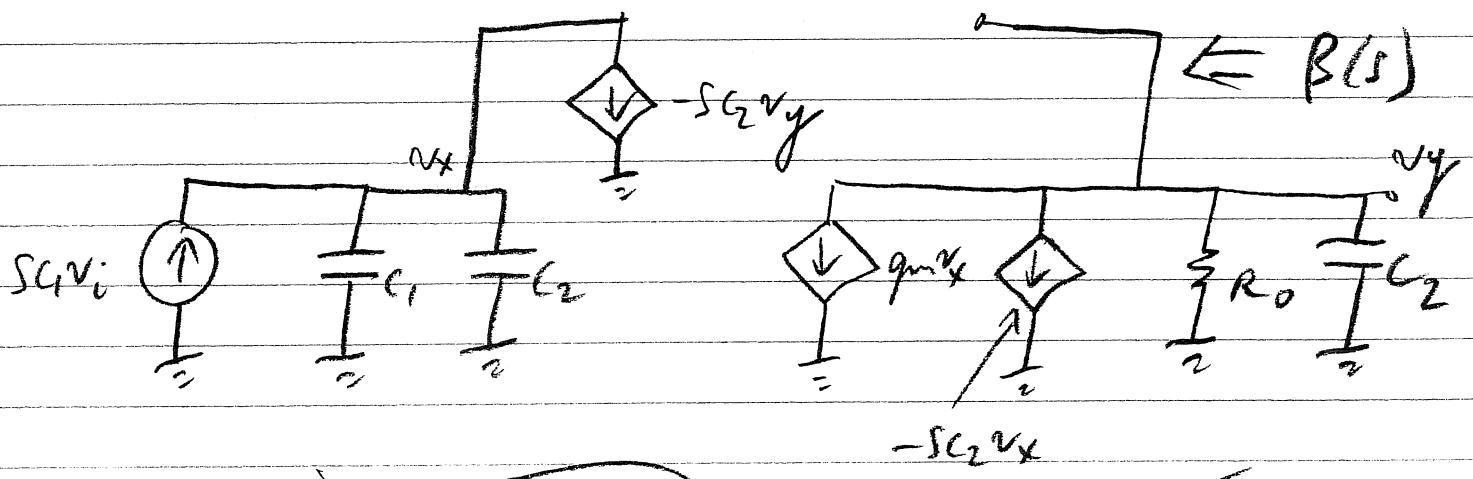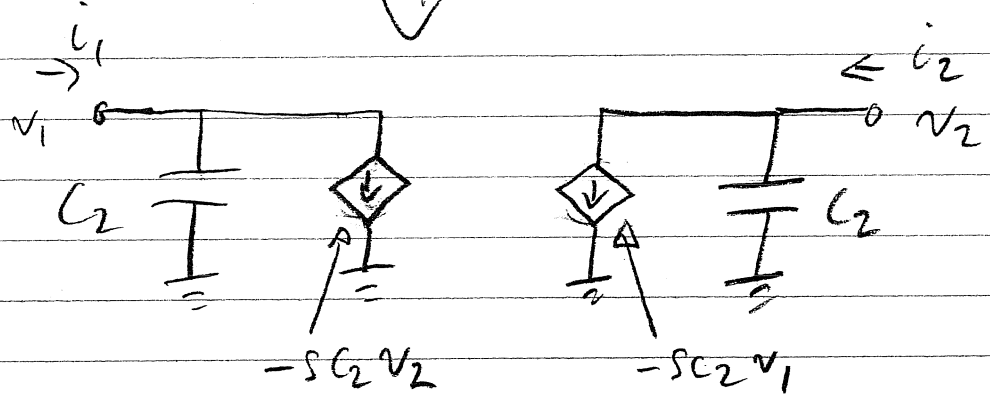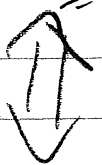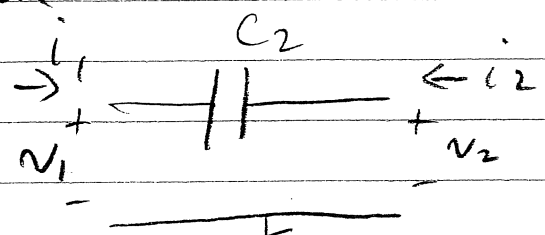


A(s)

A(s)

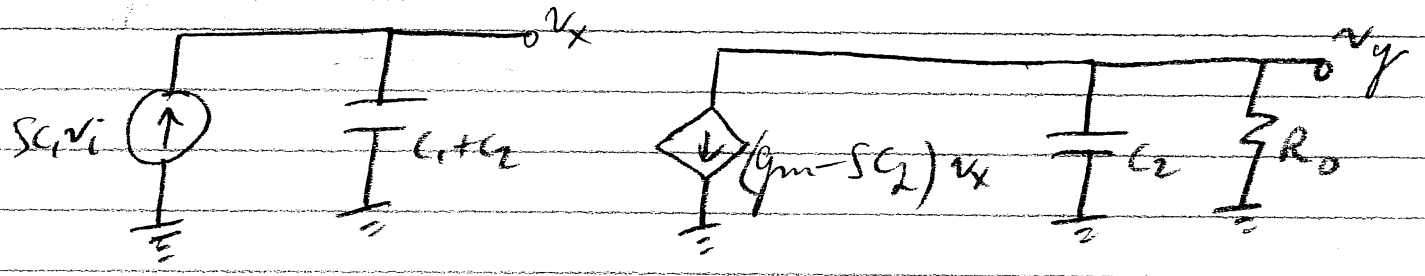

$$A(s) = \frac{v_y}{sC_1 v_i} = \frac{-1}{s(C_1 + C_2)} (g_m - sC_2) \left( R_o \parallel \frac{1}{sC_2} \right)$$

B(s)

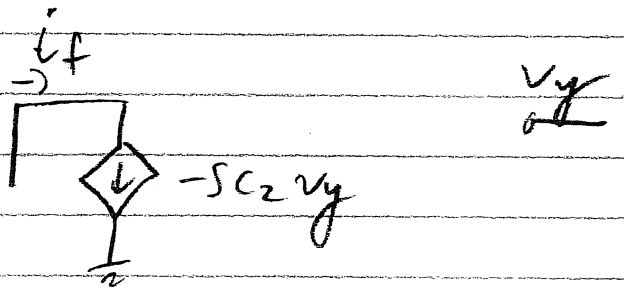

$$\beta(s) = \frac{i_f}{v_y} = -sC_2$$

CLOSED LOOP GAIN

$$A_{CL} = \frac{A(s)}{1 + A(s)\beta(s)} = \frac{v_y}{sC_1 v_i}$$

$$\frac{v_y}{v_i} = \frac{sC_1 A(s)}{1 + A(s)\beta(s)}$$

4

$$\frac{v_y}{v_i} = \frac{s C_1 (s C_2 - g_m) (R_o \parallel \frac{1}{s C_2})}{s(C_1 + C_2) + s C_2 (g_m - s C_2) (R_o \parallel \frac{1}{s C_2})}$$
$$= \frac{C_1 (s C_2 - g_m) R_o}{C_1 + C_2 + s C_1 C_2 R_o + g_m C_2 R_o} = \frac{N(s)}{D(s)}$$

POLE AT  $D(s) = 0$

$$\Rightarrow s = - \frac{(g_m R_o C_2 + C_1 + C_2)}{C_1 C_2 R_o}$$



FOR  $g_m R_o \gg 1$  &  $C_2 \gg C_1$

POLE  $s \approx - \frac{g_m}{C_1}$

---

---

b)

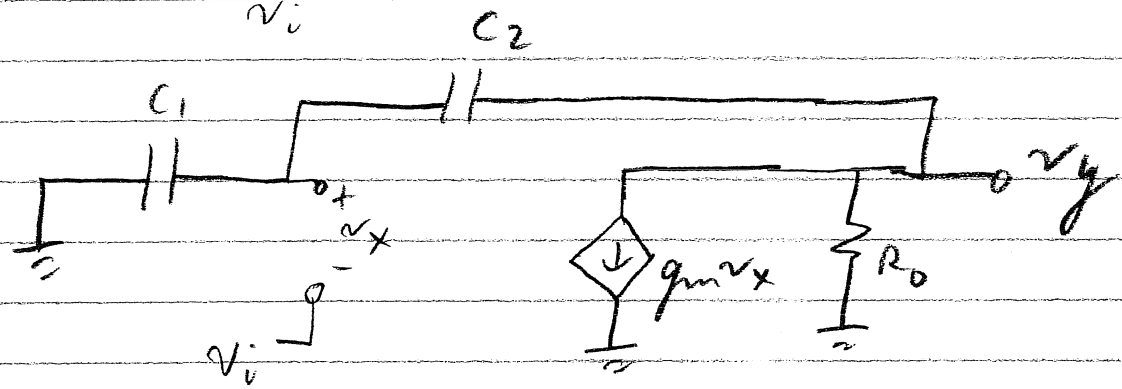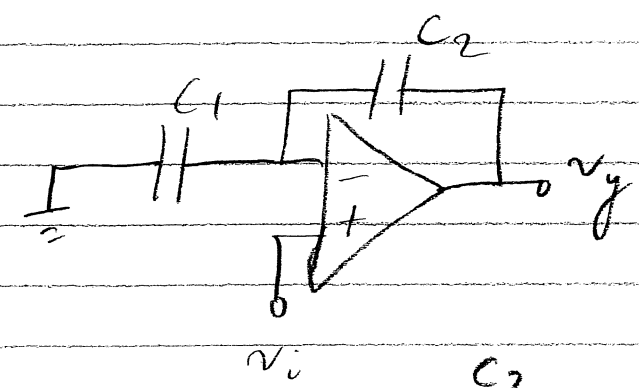

$$A(s) = +g_m \left( R_o \parallel \left( \frac{1}{sC_1} + \frac{1}{sC_2} \right) \right)$$

$$\beta(s) = \frac{C_2}{C_1 + C_2}$$

$$A_{CL} = \frac{A(s)}{1 + A(s)\beta(s)}$$

$$A(s) = +g_m \left( \frac{R_o (C_1 + C_2)}{C_1 + C_2 + sC_1 C_2 R_o} \right)$$



6

$$A_{CL} = \frac{g_m R_o (C_1 + C_2)}{C_1 + C_2 + s C_1 C_2 R_o + g_m R_o C_2} = \frac{N(s)}{D(s)}$$

POLES AT  $D(s) = 0$

$$s = \frac{-(g_m R_o C_2 + C_1 + C_2)}{C_1 C_2 R_o}$$

SAME AS a)

SO FOR  $g_m R_o \gg 1$  &  $C_2 \gg C_1$

$$s \approx -\frac{g_m}{C_1}$$

NOTE HOWEVER THAT  $A(s) \neq \beta(s)$

DIFFERENT FOR CASES a) & b)

7

IN GENERAL, LOOP GAIN  $L(s)$

$$L(s) \equiv A(s) \beta(s)$$

POLES OCCUR AT  $1 + L(s) = 0$

HOWEVER WRITE

$$L(s) = \frac{N_L(s)}{D_L(s)}$$

$$\therefore 1 + L(s) = 0$$

$$D_L(s) + N_L(s) = 0$$

$$\underline{\underline{\text{IF}}}$$
 
$$L_2(s) = \frac{N_L(s) - D_2(s)}{D_L(s) + D_2(s)} \quad \begin{array}{l} \text{ARBITRARY} \\ D_2(s) \end{array}$$

POLES ASSOCIATED WITH LOOP GAIN  $L_2(s)$

$$1 + L_2(s) = 0 \Rightarrow 1 + \frac{N_L(s) - D_2(s)}{D_L(s) + D_2(s)} = 0$$

$$D_L(s) + D_2(s) + N_L(s) - D_2(s) = 0$$

$$D_L(s) + N_L(s) = 0$$

SAME POLES AS  $L(s)$  !

8

FOR A GIVEN SET OF CLOSED  
LOOP POLES THERE ARE  
MULTIPLE LOOP GAINS GIVING SAME  
POLES. EACH LOOP GAIN MAY  
HAVE DIFFERENT PHASE + GAIN  
MARGINS !!