

# Body Effect for MOS Transistors


David Johns

University of Toronto


*david.johns@utoronto.ca*
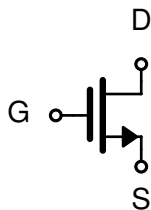
# Body, or Bulk (or Substrate)

- So far, we have assumed a 3 terminal MOSFET
- Actually, a MOSFET is a 4 terminal device




3 terminal

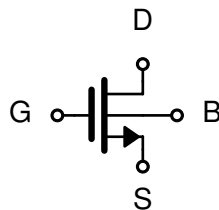

4 terminal


- B  $\Rightarrow$  Body or Bulk (or Substrate)

# Body, or Bulk (or Substrate)

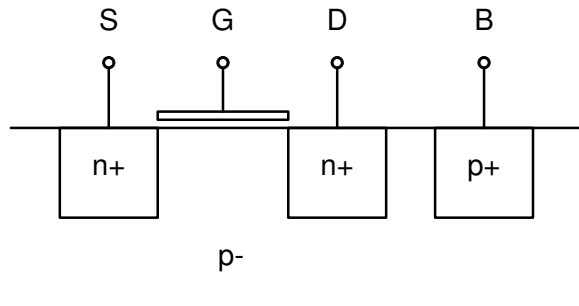

- p+ is used to connect metal to p- body
- If p+ is not used, metal direct to p- would result in a Schottky diode


# Schottky Diode

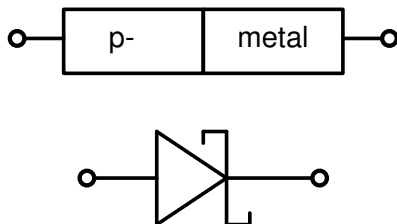

- on voltage  $\approx 0.3\text{ V}$
- We DO NOT want a Schottky diode (current only one direction and a voltage drop)
- By using metal to p+ to p-, we have an ohmic connection

# Body Effect - Large Signal

- $V_{SB}$  effect

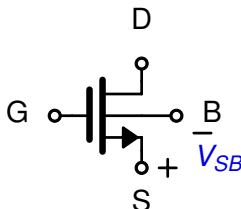

- Effect of  $V_{SB}$  can be modelled as changing the threshold voltage,  $V_t$ .

$$V_t = V_{t0} + \gamma[\sqrt{2\Phi_f + V_{SB}} - \sqrt{2\Phi_f}] \quad (1)$$

where

- $V_{t0}$  is the threshold voltage with  $V_{SB} = 0$
- $2\Phi_f \approx 0.6V$  (surface potential)
- $\gamma = \sqrt{2qN_A\epsilon_s}/C_{OX}$   
( $N_A$  - doping concentration of p-;  $\epsilon_s$  - permittivity of silicon;  $C_{OX}$  is gate oxide capacitance per unit area)

# Body Effect - Large Signal

- $V_{SB}$  effect
  - As  $V_{SB} \uparrow$  then  $V_t \uparrow$
  - In other words, if the source voltage is greater than the bulk voltage, the threshold is increased.
- $V_t$  increase due to body effect
  - Will reduce available signal swing especially for source-follower amps
- Bulk connection acts like another "gate" if the source is held constant
  - If  $V_{BS} \uparrow$  then  $V_t \downarrow$  and  $I_D \uparrow$
- For DC analysis,  $V_t$  depends on  $V_{SB}$  and  $V_{SB}$  may depend on  $V_t$ 
  - Hand analysis requires an iterative approach
  - Best left for simulation

# Body Effect - Small Signal

- Recall the definition for  $g_m$  which relates the change in drain current to the change in  $V_{GS}$

$$g_m \equiv \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial(0.5\mu_n C_{ox}(W/L)(V_{GS} - V_t)^2)}{\partial V_{GS}} \quad (2)$$

$$g_m = \mu_n C_{ox}(W/L)(V_{GS} - V_t)$$

- Since the body also "controls" the drain current, we can also find  $g_{mb}$

# Body Effect - Small Signal

- We define

$$g_{mb} \equiv \frac{\partial I_D}{\partial V_{BS}} \quad (3)$$

$$\begin{aligned} g_{mb} &= \frac{\partial(0.5\mu_n C_{ox}(W/L)(V_{GS} - V_t)^2)}{\partial V_{BS}} \\ &= \mu_n C_{ox}(W/L)(V_{GS} - V_t)(-1) \left( \frac{\partial V_t}{\partial V_{SB}} \right) \left( \frac{\partial V_{SB}}{\partial V_{BS}} \right) \\ &= \mu_n C_{ox}(W/L)(V_{GS} - V_t) \left( \frac{\partial V_t}{\partial V_{SB}} \right) \\ &= \left( \frac{\partial V_t}{\partial V_{SB}} \right) g_m \end{aligned} \quad (4)$$



# Body Effect - Small Signal

- Using (1) and defining  $\chi$  as



$$\begin{aligned}\chi &\equiv \frac{\partial V_t}{\partial V_{SB}} \\ &= \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}}\end{aligned}\tag{5}$$

- We have that  $g_{mb}$  is related to  $g_m$  as

$$g_{mb} = \chi g_m\tag{6}$$


- Typical values for  $\chi$  are 0.1 to 0.3

# Body Effect - Small-Signal Model

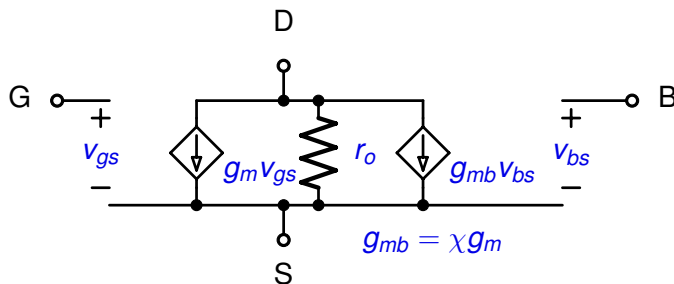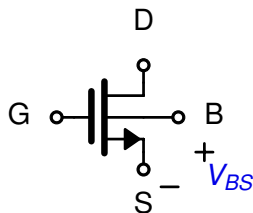

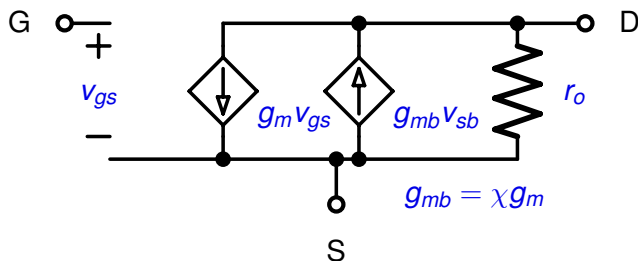
# Body Effect Small-Signal Model

- In the case where the bulk is a small-signal ground



- This is common in integrated circuits
- Let's look at 3 amps with body at small-signal ground
  - Common-gate
  - Common-drain
  - Common-source


# Common-Gate

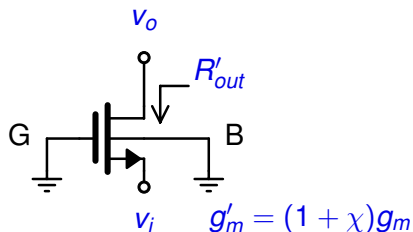

$$R'_{out} = r_o \qquad i'_{sc} = \frac{(1+g'_m r_o)}{r_o} v_i \qquad v'_{oc} = (1 + g'_m r_o) v_i$$

- All results same as 3 terminal device except that  $g_m$  increased by  $(1 + \chi)$
- Due to  $v_{sg} = v_{sb} = v_s$  since  $v_g = v_b = 0$

# Common-Drain

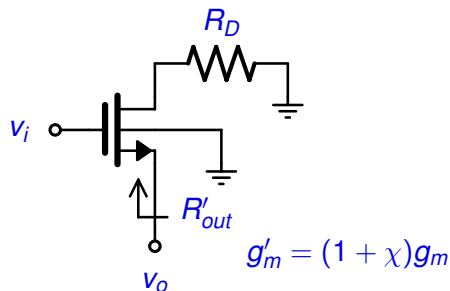

$$R'_{out} = \frac{r_o + R_D}{1 + g'_m r_o} \quad i'_{sc} = \frac{g_m r_o}{r_o + R_D} v_i \quad v'_{oc} = \frac{g_m r_o}{1 + g'_m r_o} v_i$$


- $R_{out}$  same as 3 terminal device except larger  $g_m$
- $i_{sc}$  same as 3 terminal device since output shorted so  $v_{sb} = 0$

- For  $g_m r_o \gg 1$

$$v'_{oc} \approx \frac{g_m}{g'_m} v_i = \frac{1}{1 + \chi} v_i \quad (7)$$

- $V_{oc}$  is reduced
- $R_{out}$  also reduced but usually overall gain is reduced by body effect.

# Common-Source

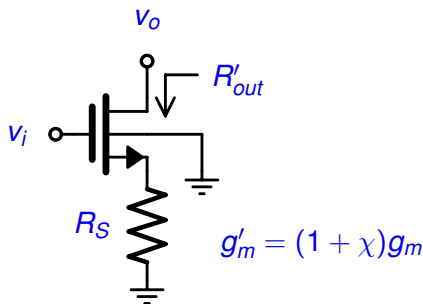

$$R'_{out} = r_o + (1 + g'_m r_o) R_S \quad i'_{sc} = \frac{-g_m r_o}{r_o + (1 + g'_m r_o) R_S} v_i \quad v'_{oc} = -g_m r_o v_i$$

- $R_{out}$  same as 3 terminal device but larger  $g_m$
- $v_{oc}$  same as 3 terminal device since when drain open, no current through  $R_S$  so  $v_s = 0$  so  $v_{sb} = 0$

- For  $g_m r_o \gg 1$


$$\begin{aligned} i'_{sc} &\approx \frac{-g_m r_o v_i}{r_o + g'_m r_o R_S} = \frac{-g_m v_i}{1 + g'_m R_S} \\ &\approx \frac{-v_i}{(1/g_m) + (1 + \chi) R_S} \end{aligned} \tag{8}$$

- Body effect:
  - $i_{sc}$  reduced
  - $R_{out}$  increased



# Example 1

- Common-drain

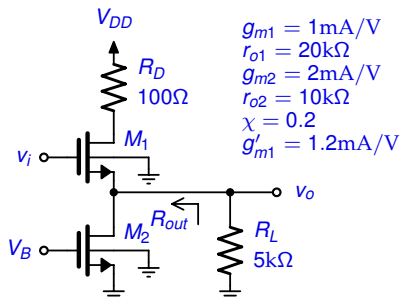

- $M_1$  has body effect since  $V_B \neq V_S$
- $R_{out} = R_{S1} || R_{D2}$
- $R_o = R_{out} || R_L$
- $R_{D2} = r_{o2} = 10\text{k}\Omega$ ;  $R_{S1} = \frac{r_{o1} + R_D}{(1 + g'_{m1} r_{o1})} = 804\Omega$

## Example 3

- $R_{out} = R_{S1} || R_{D2} = 744\Omega$
- $R_o = R_{out} || R_L = 647\Omega$
- For  $i_{sc}$  we have  $i_{sc} = G_m v_i$  where
- $G_m = (g_{m1} r_{o1}) / (r_{o1} + R_D) = 995\mu A/V$
- $v_o / v_i = G_m \times R_o = 0.644V/V$
- Without body effect
  - $v_o / v_i = G_m \times R_o = 0.74V/V$
  - A gain reduction of 13% when body effect included

## Example 3 - Approx Solution

- $R_{S1} = (1/g'_{m1}) + R_D/(g'_{m1}r_{o1}) = 838\Omega$
- $R_{D2} = r_{o2} = 10k\Omega$
- $v_{oc} = \frac{1}{1+\chi} v_i = 0.833v_i$
- $v_o$  node is a resistor divider node
- $v_o = \frac{(R_{D2}||R_L)}{(R_{D2}||R_L)+R_{S1}} v_{oc} = \frac{3.33k}{3.33k+838} (0.833)v_i$
- $v_o/v_i = 0.665V/V$