

ECE 331 — Nov 19, 2024 — 50 min

**Term Test 2**

---

ANSWER QUESTIONS ON THESE SHEETS **USING BACKS IF NECESSARY**

- Equation sheet is on the last page of this test.
- Notation: 15e3 is equivalent to  $15 \times 10^3$
- Non-programmable calculator is allowed; No other aids are allowed
- Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.



[5] **Q1.** Consider a first-order lowpass filter with a dc gain of 10 and a 3dB frequency of 100Mrad/s.

a) Estimate  $\omega_t$  assuming the dc gain is much greater than 1.

b) Find the exact value of  $\omega_t$  as well as the exact phase (in degrees) at  $\omega_t$  (both values to at least 3 significant digits).

---

## Solution

Defining the dc gain to be  $K_{dc} = 10$  and the 3dB frequency to be  $\omega_{p1} = 100\text{Mrad/s}$ , we have the following transfer function

$$H(s) = \frac{K_{dc}}{1 + s/\omega_{p1}}$$

a) Assuming the dc gain is much greater than 1, we have (see equation page)

$$\omega_t = K_{dc} * \omega_{p1} = (10) * (100\text{e}6) = 1\text{Grad/s}$$

b) For exact  $\omega_t$ , we have

$$1 = \left| \frac{K_{dc}}{1 + j\omega_t/\omega_{p1}} \right|$$

$$1^2 = \frac{K_{dc}^2}{1^2 + \omega_t^2/\omega_{p1}^2}$$

$$\omega_t = \omega_{p1} \sqrt{K_{dc}^2 - 1}$$

$$\omega_t = \omega_{p1} * \text{sqrt}(K_{dc}^2 - 1) = (100\text{e}6) * \text{sqrt}((10)^2 - 1) = 995\text{Mrad/s}$$

and the phase at  $\omega_t$ ,  $\phi_t$ , is given by

$$\phi_t = 0 - \text{atand}(\omega_t/\omega_{p1}) = 0 - \text{atand}((995\text{e}6)/(100\text{e}6)) = -84.26^\circ$$



[5] **Q2.** Assume the following technology parameters for NMOS transistors

$$V_{tn} = 0.4\text{V}; \mu_n C_{ox} = 240\mu\text{A}/\text{V}^2; \lambda'_n = 50\text{nmV}^{-1}; C_{ox} = 8.5\text{fF}/\mu\text{m}^2;$$

$$t_{ox} = 4\text{nm}; L_{ov} = 40\text{nm}; C_{db0}/W = 0.3\text{fF}/\mu\text{m};$$

a) Given a transistor of size  $W = 3\mu\text{m}$  and  $L = 200\text{nm}$ , find the values of  $C_{gs}$ ,  $C_{gd}$  and  $C_{db}$  for the transistor (all in  $\text{fF}$ ). Assume the transistor is in the active region and that  $V_{db} = 0$ .

b) If  $V_{ov} = 0.15\text{V}$ , find the unity gain frequency of the transistor in  $\text{Hz}$  (include the effect of  $C_{gd}$ )

c) Describe in words what is the unity gain frequency for a transistor?

---

## Solution

a)

$$C_{ox} = 8.5\text{e-}15\text{F}/\mu\text{m}^2 = 8.5\text{e-}3\text{F}/\text{m}^2$$

$$C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox} = ((2/3)L + L_{ov})(WC_{ox})$$

$$C_{gs} = ((2/3)(200\text{e-}9) + (40\text{e-}9))(3\text{e-}6)(8.5\text{e-}3)$$

$$C_{gs} = 4.42\text{fF}$$

$$C_{gd} = W * L_{ov} * C_{ox} = (3\text{e-}6) * (40\text{e-}9) * (8.5\text{e-}3) = 1.02\text{fF}$$

$$C_{db0}/W = 300\text{e-}18\text{F}/\mu\text{m} = 300\text{e-}12\text{F}/\text{m}$$

$$C_{db} = C_{db0}/W * W = (300\text{e-}12) * (3\text{e-}6) = 900\text{aF}$$

b)

$$g_m = \mu_n C_{ox} * (W/L) * V_{ov} = (240\text{e-}6) * ((3\text{e-}6)/(200\text{e-}9)) * (0.15) = 540\mu\text{A}/\text{V}$$

$$\omega_t = g_m / (C_{gs} + C_{gd}) = (540\text{e-}6) / ((4.42\text{e-}15) + (1.02\text{e-}15)) = 99.26\text{Grad}/\text{s}$$


$$f_t = \omega_t / (2 * \pi) = (99.26\text{e}9) / (2 * (3.142)) = 15.8\text{GHz}$$

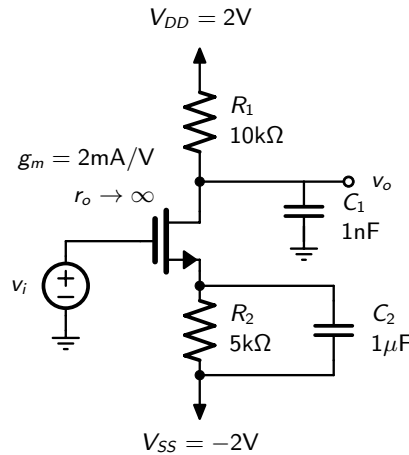c) The unity gain frequency of a transistor is the frequency at which the magnitude of the drain current equals the magnitude of the gate current assuming the transistor is in the active region.



[5] **Q3.** Consider the circuit shown below where the only capacitors in the circuit are  $C_1$  and  $C_2$ .

Sketch the small-signal freq response  $v_o/v_i$  showing all values (gains in V/V and freq in rad/s).



## Solution

First we find the dc gain

$$(G_m)_{dc} = -1/((1/g_m) + R_2) = -1/((1/(2e-3)) + (5e3)) = -181.8 \mu A/V$$

$$R_{out} = R_1 = (10e3) = 10k\Omega$$

$$(v_o/v_i)_{dc} = (G_m)_{dc} * R_{out} = (-181.8e-6) * (10e3) = -1.818V/V$$

Next, we find the high freq gain

$$(G_m)_{hf} = -1/((1/g_m)) = -1/((1/(2e-3))) = -2mA/V$$

$$R_{out} = R_1 = (10e3) = 10k\Omega$$

$$(v_o/v_i)_{hf} = (G_m)_{hf} * R_{out} = (-2e-3) * (10e3) = -20V/V$$

For the freq response, we see that a zero occurs when the parallel combination of  $R_2$  and  $C_2$  go to infinity (the short circuit current will go to zero at this freq). So we have


$$\omega_z = 1/(R_2 * C_2) = 1/((5e3) * (1e-6)) = 200rad/s$$

and then for  $C_2$  a pole occurs at

$$\omega_{p1} = 1/(C_2 * (R_2 || 1/g_m)) = 1/((1e-6) * ((5e3) || (1/(2e-3)))) = 2.2krad/s$$

Finally, for  $C_1$ , a pole occurs at
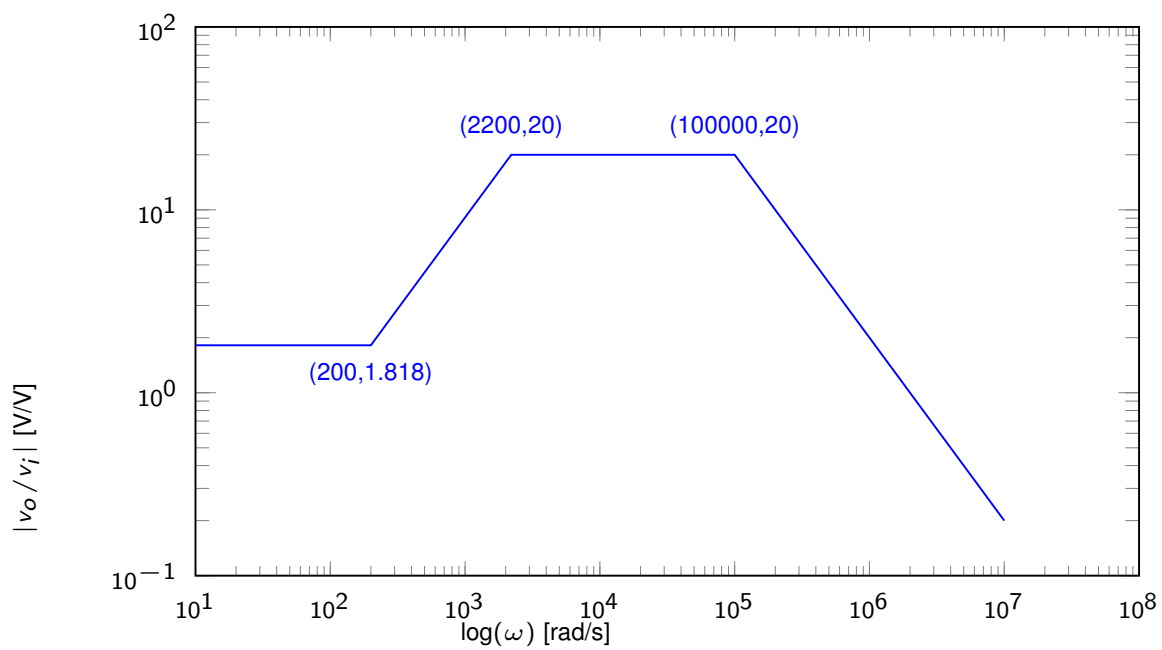
$$\omega_{p2} = 1/(R_1 * C_1) = 1/((10e3) * (1e-9)) = 100krad/s$$










## Equation Sheet

Constants:  $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26\text{mV}$  at  $300 \text{ K}$ ;  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ ;  $k_{ox} = 3.9$ ;  
 $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$ ;  $\omega = 2\pi f$

NMOS:  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{tn} > 0$ ;  $v_{DS} \geq 0$ ;  $V_{ov} = V_{GS} - V_{tn}$   
 (triode)  $v_{DS} \leq V_{ov}$ ;  $v_D < v_G - V_{tn}$ ;  $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{DS} \geq V_{ov}$ ;  $i_D = 0.5k_n V_{ov}^2(1 + \lambda_n v_{DS}')$ ;  $v_{DS}' = v_{DS} - V_{ov}$ ;  
 $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_n'|I_D)$

PMOS:  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{tp} < 0$ ;  $v_{SD} \geq 0$ ;  $V_{ov} = V_{SG} - |V_{tp}|$   
 (triode)  $v_{SD} \leq V_{ov}$ ;  $v_D > v_G + |V_{tp}|$ ;  $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{SD} \geq V_{ov}$ ;  $i_D = 0.5k_p V_{ov}^2(1 + |\lambda_p|v_{SD}')$ ;  $v_{SD}' = v_{SD} - V_{ov}$   
 $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_p'|I_D)$

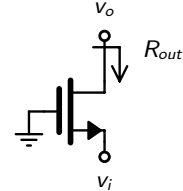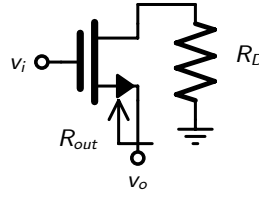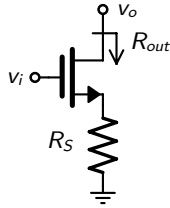

Accurate:  $R_{out} = r_o + (1 + g_m r_o)R_S$   
 $i_{sc} = (-g_m r_o v_i)/(r_o + (1 + g_m r_o)R_S)$   
 $v_{oc} = -g_m r_o v_i$

$g_m r_o \gg 1$   $R_{out} = (1 + g_m R_S)r_o$   
 $i_{sc} = -v_i/((1/g_m) + R_S)$   
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (r_o + R_D)/(1 + g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = (g_m r_o v_i)/(1 + g_m r_o)$

$R_{out} = (1/g_m) + (R_D/g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = v_i$

$R_{out} = r_o$   
 $i_{sc} = ((1 + g_m r_o)/r_o)v_i$   
 $v_{oc} = (1 + g_m r_o)v_i$

$R_{out} = r_o$   
 $i_{sc} = g_m v_i$   
 $v_{oc} = g_m r_o v_i$

Diff Pair:  $A_d = g_m R_D$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$ ;  
 $V_{OS} = \Delta V_t$ ;  $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$ ;  $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$   
 Large signal:  $i_{D1} = (I/2) + (I/V_{ov})(v_{id}/2)(1 - (v_{id}/2V_{ov})^2)^{1/2}$

1st order: step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ ;  
 unity gain freq for  $T(s) = A_M/(1 + (s/\omega_{3dB}))$  for  $A_M \gg 1 \Rightarrow \omega_t \simeq |A_M|\omega_{3dB}$

Freq: for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$   
 OTC estimate  $\omega_H \simeq 1/(\sum \tau_i)$ ; dominant pole estimate  $\omega_H \simeq 1/(\tau_{max})$   
 STC estimate  $\omega_L \simeq \sum 1/\tau_i$ ; dominant pole estimate  $\omega_L \simeq 1/(\tau_{min})$

Miller:  $Z_1 = Z/(1 - K)$ ;  $Z_2 = Z/(1 + 1/K)$

Mos caps:  $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$ ;  $C_{gd} = WL_{ov}C_{ox}$ ;  $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$ ;  
 $\omega_t = g_m/(C_{gs} + C_{gd})$ ; for  $C_{gs} \gg C_{gd} \Rightarrow f_t \simeq (3\mu V_{ov})/(4\pi L^2)$

SEE NEXT PAGE ...

Feedback:  $A_f = A/(1 + A\beta)$ ;  $x_i = (1/(1 + A\beta))x_s$ ;  $dA_f/A_f = (1/(1 + A\beta))dA/A$ ;  $\omega_{Hf} = \omega_H(1 + A\beta)$ ;  $\omega_{Lf} = \omega_L/(1 + A\beta)$ ;

Loop Gain  $L \equiv -s_r/s_t$ ;  $A_f = A_{\infty}(L/(1 + L)) + d/(1 + L)$ ;  $Z_{port} = Z_{pe}((1 + L_s)/(1 + L_o))$ ;  $PM = \angle L(j\omega_t) + 180$ ;  
 $GM = -|L(j\omega_{180})|_{db}$ ;

Pole splitting  $\omega'_{p1} \simeq 1/(g_m R_2 C_f R_1)$ ;  $\omega'_{p2} \simeq (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair:  $s^2 + (\omega_o/Q)s + \omega_o^2$ ;  $Q \leq 0.5 \Rightarrow$  real poles;  $Q > 1/\sqrt{2} \Rightarrow$  freq resp peaking

Power Amps: Class A :  $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$ ; Class B :  $\eta = (\pi/4)(\hat{V}_O/V_{CC})$ ;  $P_{DN,max} = V_{CC}^2/(\pi^2 R_L)$ ;

Class AB :  $i_n i_p = I_Q^2$ ;  $I_Q = (I_S/\alpha)e^{V_{BB}/(2V_T)}$ ;  $i_n^2 - i_L i_n - I_Q^2 = 0$

2-stage opamp:  $\omega_{p1} \simeq (R_1 G_{m2} R_2 C_c)^{-1}$ ;  $\omega_{p2} = G_{m2}/C_2$ ;  $\omega_z = (C_c(1/G_{m2} - R))^{-1}$ ;

$SR = I/C_c = \omega_t V_{ov1}$ ; will not SR limit if  $\omega_t \hat{V}_O < SR$