

# University of Toronto

## Final Exam

Date - Dec 13, 2012 (9:30am to 12pm)

Duration: 2.5 hrs

ECE331 — Analog Electronics

Lecturer - D. Johns

**ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY**

1. Equation sheet is on last page of test.
  2. Unless otherwise stated, use transistor parameters on equation sheet.
  3. Non-programmable calculator allowed; No other aids allowed
  4. Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.
- 

Last Name: SOLUTIONS


First Name: \_\_\_\_\_

Student #: \_\_\_\_\_

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

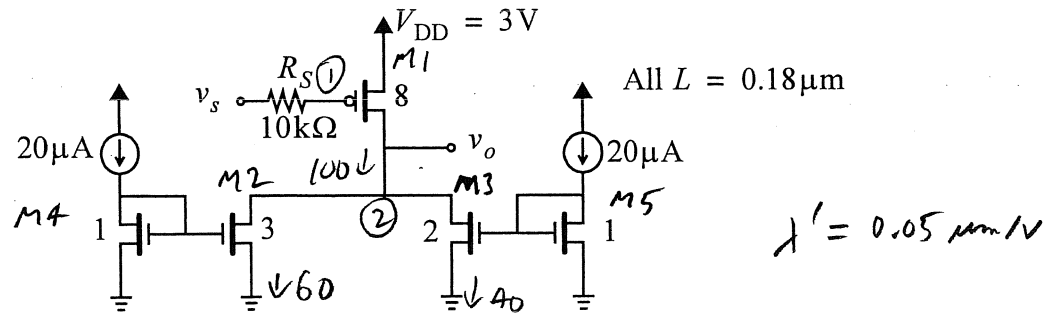**(max grade = 36)**

[6] Question 1: Consider the circuit below where all transistors are in the active region. The numbers beside the transistors indicate the transistor width (in  $\mu\text{m}$ ).



a) Find the small-signal gain  $v_o/v_s$

$$r_o = \frac{L}{\lambda' I_D} = \frac{3.6}{I_D} \quad r_{o1} = 36\text{k} \quad r_{o2} = 60\text{k}$$

$$r_{o3} = 90\text{k} \quad r_{o1} \parallel r_{o2} \parallel r_{o3} = 18\text{k}$$

$v_o/v_s = -13.1 \text{ V/V}$

$$g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right) I_D} = \sqrt{2(60e-6) \left(\frac{8}{0.18}\right) (100e-6)} = 0.730 \text{ mA/V}$$

$$\frac{v_o}{v_s} = -g_{m1} (r_{o1} \parallel r_{o2} \parallel r_{o3}) = -(0.73e-3)(18\text{k}) = -13.14 \text{ V/V}$$

b) Estimate the 3db frequency cutoff,  $f_{3dB}$ . For  $C_{db}$  values assume  $V_{db} = 0$ .

NODE ①

$$C_{p1} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$$

$$= \left[ \left(\frac{2}{3}\right) (8)(0.18) + (8)(0.04) \right] (8.5e-15)$$

$f_{3dB} = 340 \text{ MHz}$

$$= 10.9 \text{ fF}$$

$$C_{gd1} = W L_{ov} C_{ox} = (8)(0.04)(8.5e-15) = 2.72 \text{ fF}$$

$$\omega_{p1} = \frac{1}{R_S [C_{p1} + (13.1)C_{gd1}]} = \frac{1}{(10\text{k})(46.5 \text{ fF})} = 2.15e9 \text{ RAD/S}$$

NODE ②


$$C_d \equiv C_{d1} + C_{d2} + C_{d3} = (W_1 + W_2 + W_3) \left(\frac{C_{db0}}{W}\right)$$

$$= (8 + 3 + 2)(0.3 \text{ fF}/\mu\text{m}) = 3.9 \text{ fF}$$

$$\omega_{p2} = \frac{1}{(r_{o1} \parallel r_{o2} \parallel r_{o3})(C_d)} = \frac{1}{(18\text{k})(3.9 \text{ fF})} = 1.42e10 \text{ RAD/S}$$

SO  $f_{p1} \approx \frac{\omega_{p1}}{2\pi} = 342 \text{ MHz}$

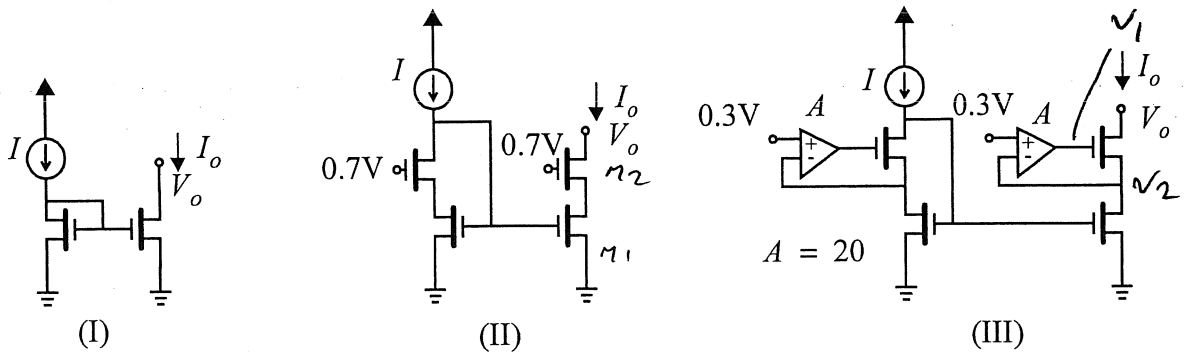[6] **Question 2:** Consider the 3 current mirrors shown below. For all transistors,  $L = 0.18\mu\text{m}$ ,  $W = 3\mu\text{m}$ . Also,  $I = 100\mu\text{A}$ .



a) For the current mirror in (I), estimate the **change** in the output current for an output voltage **change** of  $0.5\text{V}$ . Also, what is the minimum output voltage,  $V_{o(\text{min})}$ , while keeping transistors in the active region.

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{ov})^2 \Rightarrow V_{ov} = \sqrt{\frac{2I_D}{\mu_n C_{ox}} \left(\frac{L}{W}\right)}$$

$$V_{ov} = \sqrt{\frac{2 \times 100 \times 10^{-6}}{(2.4 \times 10^{-6})} \left(\frac{3}{0.18}\right)} = 0.224\text{V}$$

$$r_o = \frac{3.6}{I_D} = 36\text{k} \Rightarrow \Delta I = \frac{\Delta V}{r_o} = \frac{0.5}{36\text{k}} = 13.9\mu\text{A}$$

$$V_{o(\text{min})} = V_{ov} = 0.224\text{V}$$

$\Delta I = 13.9\mu\text{A}$
$V_{o(\text{min})} = 0.224\text{V}$

$$r_{o1} = r_{o2} = 36\text{k}$$

b) Repeat question a) for the mirror in (II)

$$V_{ov} = 0.224\text{V} \quad g_{m2} = \frac{2I_D}{V_{ov}} = 0.893\text{mA/V}$$

$$r_{out} = r_{o1} + r_{o2} + g_{m2} r_{o2} r_{o1} \approx g_{m2} r_{o2} r_{o1}$$

$$r_{out} \approx 11.6\text{M}\Omega$$

$$\Delta I = \frac{\Delta V}{r_{out}} = \frac{0.5}{11.6\text{M}} = 0.43\mu\text{A}$$

$$V_{o(\text{min})} = 0.7\text{V} - V_{T1} = 0.7 - 0.4 = 0.3\text{V}$$

$\Delta I = 0.43\mu\text{A}$
$V_{o(\text{min})} = 0.3\text{V}$

c) Repeat question a) for the mirror in (III)

$$\text{Loop Gain } L \approx 20$$

$$\text{SINCE } \frac{v_o}{v_i} \approx 1 \quad (\text{SOURCE FOLLOWER}) \\ \text{WITH } R_L = r_o$$

$\Delta I = 2$	mA
$V_{o(\min)} = 0.52$	V

$$\text{SO } R_{out} = (g_{m2} r_o^2)(1+L) = (11.6 \text{ M}) (21)$$


$$= 244 \text{ M}\Omega$$

$$\Delta I = \frac{\Delta v}{R_{out}} = \frac{0.5}{244 \text{ M}} = 2 \text{ mA}$$

$$V_{o(\min)} = V_2 + V_{ov} = 0.3 + 0.224$$

$$= 0.524$$

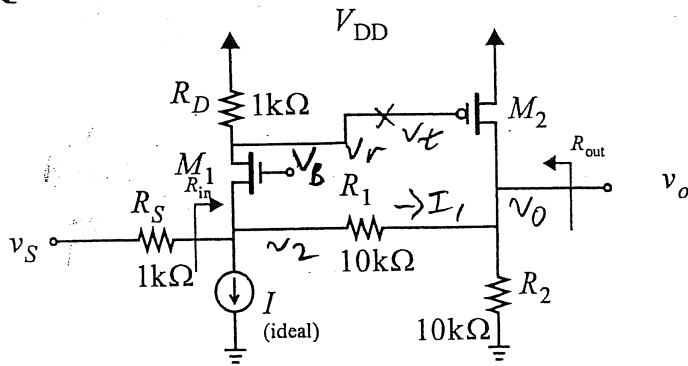[6] Question 3: Consider the circuit below.



$$g_{m1} = g_{m2} = 2 \text{ mA/V}$$

$$r_{o1} = r_{o2} \rightarrow \infty$$

a) Find  $L$ ,  $A_{\infty}$  and  $d$ .

$$L = -\left(\frac{v_o}{v_t}\right)\left(\frac{v_2}{v_o}\right)\left(\frac{v_r}{v_2}\right) \quad 333 \Omega$$

$$\frac{v_o}{v_t} = -g_{m2} \left( R_2 \parallel \left[ R_1 + \left( R_S \parallel \frac{1}{g_{m1}} \right) \right] \right)$$

$$= -(2 \text{e-}3) (10 \text{k} \parallel (10 \text{k} + 10.33 \text{k})) = -10.2 \text{ V/V}$$

$$\frac{v_2}{v_o} = \frac{333}{333 + 10 \text{k}} = 0.0322 \text{ V/V} \quad \frac{v_r}{v_2} = g_{m1} R_D = 2$$

$$L = (10.2) (0.0322) (2) = 0.657 \text{ V/V}$$

$A_{\infty} \Rightarrow$  SHUNT FEEDBACK so  $v_2 \rightarrow 0 \perp \frac{v_s}{R_S} = I_1 \Rightarrow v_o = -\frac{R_1}{R_S} \frac{v_s}{R_S}$

$$\frac{v_o}{v_s} = -10 \text{ V/V}$$

$$A_{\infty} = -10$$

$$d = \left(\frac{v_2}{v_s}\right)\left(\frac{v_o}{v_2}\right) = \left(\frac{20 \text{k} \parallel \left(\frac{1}{g_{m1}}\right)}{\left(20 \text{k} \parallel \frac{1}{g_{m1}}\right) + R_S}\right) \left(\frac{R_2}{R_1 + R_2}\right) = \left(\frac{487}{487 + 1 \text{k}}\right) (0.5)$$

$$= 0.164$$

$L = 0.657$	V/V
$A_{\infty} = -10$	V/V
$d = 0.164$	V/V

b) Find  $v_o/v_s$ ,  $R_{in}$  and  $R_{out}$ .

$$\frac{v_o}{v_s} = A_{\infty} \left(\frac{L}{1+L}\right) + \frac{d}{1+L} = -3.87 \text{ V/V}$$

$$R_{in}' = \left[ \frac{1}{g_{m1}} \parallel R_S \parallel (R_1 + R_2) \right] \left( \frac{1}{1+L} \right) \quad L_S = 0$$

$$L_O = L$$

$$R_{in}' = \frac{328}{1+0.657} = 198 \Omega$$


$$R_{out} = \left[ R_2 \parallel \left[ R_1 + \left( R_S \parallel \frac{1}{g_{m1}} \right) \right] \right] \left( \frac{1}{1+L} \right) = \frac{5.08 \text{k}}{1+0.657} = 3.07 \text{k}$$

But

$$R_{in}' = R_{in} \parallel R_S \Rightarrow R_{in} = \left( \frac{1}{R_{in}'} - \frac{1}{R_S} \right)^{-1} = 247 \Omega$$

$v_o/v_s = -3.9$	V/V
$R_{in} = 247$	$\Omega$
$R_{out} = 3.07$	k $\Omega$

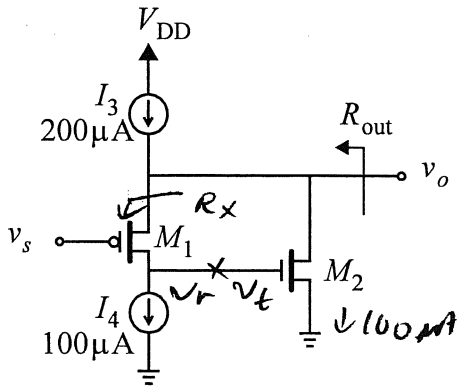[6] **Question 4:** The circuit below is called a "super source follower". Assume the current sources are realized using single transistors with  $L = 0.18\mu\text{m}$  (include their output resistances  $r_{o3}$  and  $r_{o4}$ ).



$$\text{All } L = 0.18\mu\text{m}$$

$$\text{All } |V_{ov}| = 200\text{mV}$$

$$r_o = \frac{3.6}{I_D}$$

$$r_{o1} = r_{o2} = r_{o4} = \frac{3.6}{100\mu\text{A}} = 36\text{k}$$

$$r_{o3} = 18\text{k}$$

$$g_{m1} = g_{m2} = \frac{2(100e-6)}{200e-3} = 1\text{mA/V}$$

Find the value for the output resistance,  $R_{out}$ , assuming  $g_m r_o \gg 1$ .

$$R_x = \frac{r_{o4} + r_{o1}}{1 + g_{m1} r_{o1}} \approx \frac{2}{g_{m1}} = 2\text{k}\Omega$$

$$R_{out} = 55\Omega$$

$$R_{out}(k=0) = r_{o2} \parallel r_{o3} \parallel R_x$$

$$= 36\text{k} \parallel 18\text{k} \parallel 2\text{k} = 1.71\text{k}$$

$$L = -\left(\frac{v_o}{v_t}\right) \left(\frac{v_r}{v_o}\right)$$


$$\frac{v_o}{v_t} = -g_{m2} (r_{o2} \parallel r_{o3} \parallel R_x) = -1.71 \sqrt{V}$$

$$\frac{v_r}{v_o} \approx g_{m1} (r_{o4} \parallel r_{o1}) = 18$$

$$L = 1.71 \times 18 = 30.9 \sqrt{V}$$

$$R_{out} = R_{out}(k=0) \left(\frac{1}{1+L}\right) = 55\Omega$$

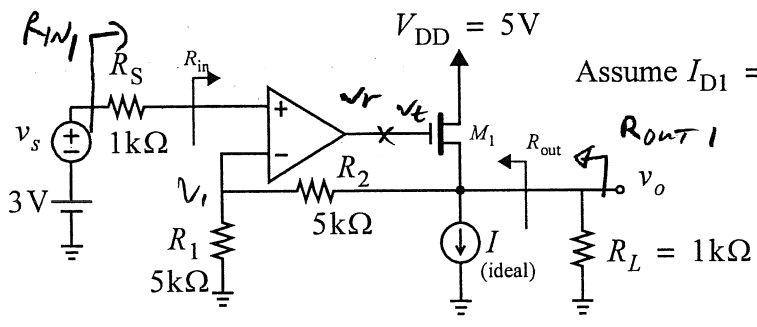[6] **Question 5:** Consider the circuit shown below. For the opamp,  $A_o = 40$ ,  $R_{id} = 10k\Omega$ ,  $R_o = 1k\Omega$ . For  $M_1$ ,  $V_{ov} = 200mV$  and  $L = 0.18\mu m$  (include  $r_o$ ).



Assume  $I_{D1} = 200\mu A$

$$r_{o1} = \frac{3.6}{I_{D1}} = 18k$$

$$g_{m1} = \frac{2I_{D1}}{V_{ov}} = 2mA/V$$

a) Find  $L$ ,  $A_{\infty}$  and  $d$ .

$$L = -\left(\frac{v_o}{v_t}\right)\left(\frac{v_1}{v_o}\right)\left(\frac{v_r}{v_1}\right)$$

LET  $R_x = R_L \parallel r_{o1} \parallel (R_2 + [R_1 \parallel (R_{id} + R_S)])$

$$= 852 \Omega$$

$$\frac{v_o}{v_t} = \frac{R_x}{R_x + r_{s1}} = 0.63 \frac{V}{V}$$

LET  $R_z = R_1 \parallel (R_{id} + R_S) = 3.44k$

$$\frac{v_1}{v_o} = \frac{R_z}{R_z + R_2} = 0.407 \frac{V}{V}$$

$$\frac{v_r}{v_1} = -\left(\frac{R_{id}}{R_{id} + R_S}\right) A = 36.4 \frac{V}{V}$$

$$L = 0.63 \times 0.407 \times 36.4 = 9.32 \frac{V}{V}$$

$$A_{\infty} = 1 + \frac{R_2}{R_1} = 2 \frac{V}{V}$$

$$d \approx 0$$

$L = 9.32$	$\frac{V}{V}$
$A_{\infty} = 2$	$\frac{V}{V}$
$d = 0$	

b) Find  $v_o/v_s$ ,  $R_{in}$  and  $R_{out}$ .

$v_o/v_s = 1.81$	$\frac{V}{V}$
$R_{in} = 139$	$k\Omega$
$R_{out} = 31.5$	$\Omega$

$$\frac{v_o}{v_s} = A_{\infty} \left( \frac{L}{1+L} \right) + \frac{d}{1+L} \quad (d=0)$$

$$= 2 \left( \frac{9.32}{1+9.32} \right) = 1.81 \frac{V}{V}$$

$$R_{in,1} = R_S + R_{id} + \underbrace{\left[ R_1 \parallel \left[ R_2 + \left( R_L \parallel \frac{1}{g_{m1}} \parallel r_{o1} \right) \right] \right]}_{2.58k}$$

$$= 13.58 k\Omega$$

$$R_{in,1} = R_{in,1}(k=0) (1+L) = 140.1 k\Omega$$

$$R_{in} = R_{in,1} - R_S = \underline{\underline{139.1 k\Omega}}$$

$$R_{out,1} = R_L \parallel \frac{1}{g_{m1}} \parallel r_{o1} \parallel \underbrace{\left( R_2 + \left[ R_1 \parallel (R_{id} + R_S) \right] \right)}_{8.44k}$$

$$(k=0) = 315 \Omega$$

$$R_{out,1} = R_{out,1}(k=0) / (1+L) = 30.5 \Omega$$

$$R_{out,1} = R_{out} \parallel R_L \Rightarrow \frac{1}{R_{out}} = \frac{1}{R_{out,1}} - \frac{1}{R_L}$$


$$R_{out} = 31.5 \Omega$$

[6] **Question 6:** Assume an opamp is ideal but has the following open-loop gain and will be used in a non-inverting configuration with 2 resistors.


$$A(s) = \frac{10^4}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})(1 + s/\omega_{p3})} \text{ where } \omega_{p1} = 10^5, \omega_{p2} = 10^7, \omega_{p3} = 10^8.$$

a) Draw the Bode plot for the above open-loop gain (both mag and phase)

dB  
= 80

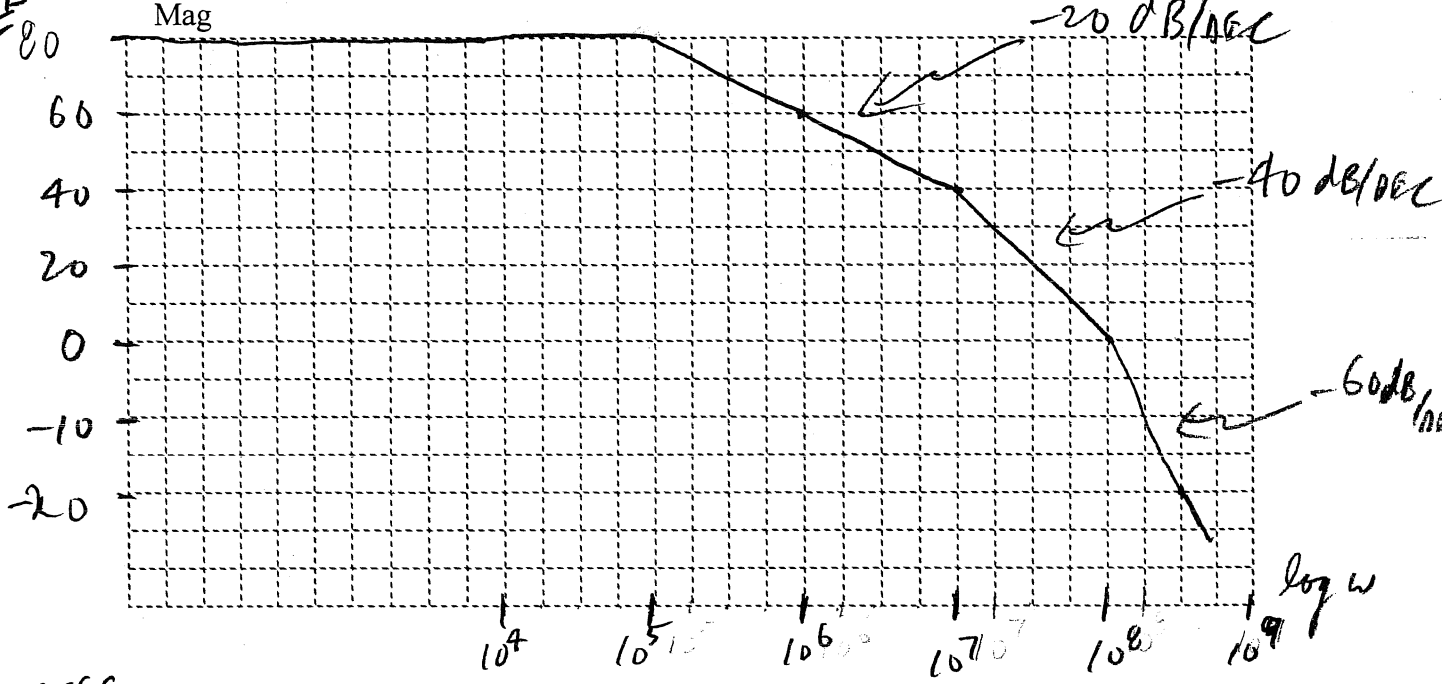

DEGREES

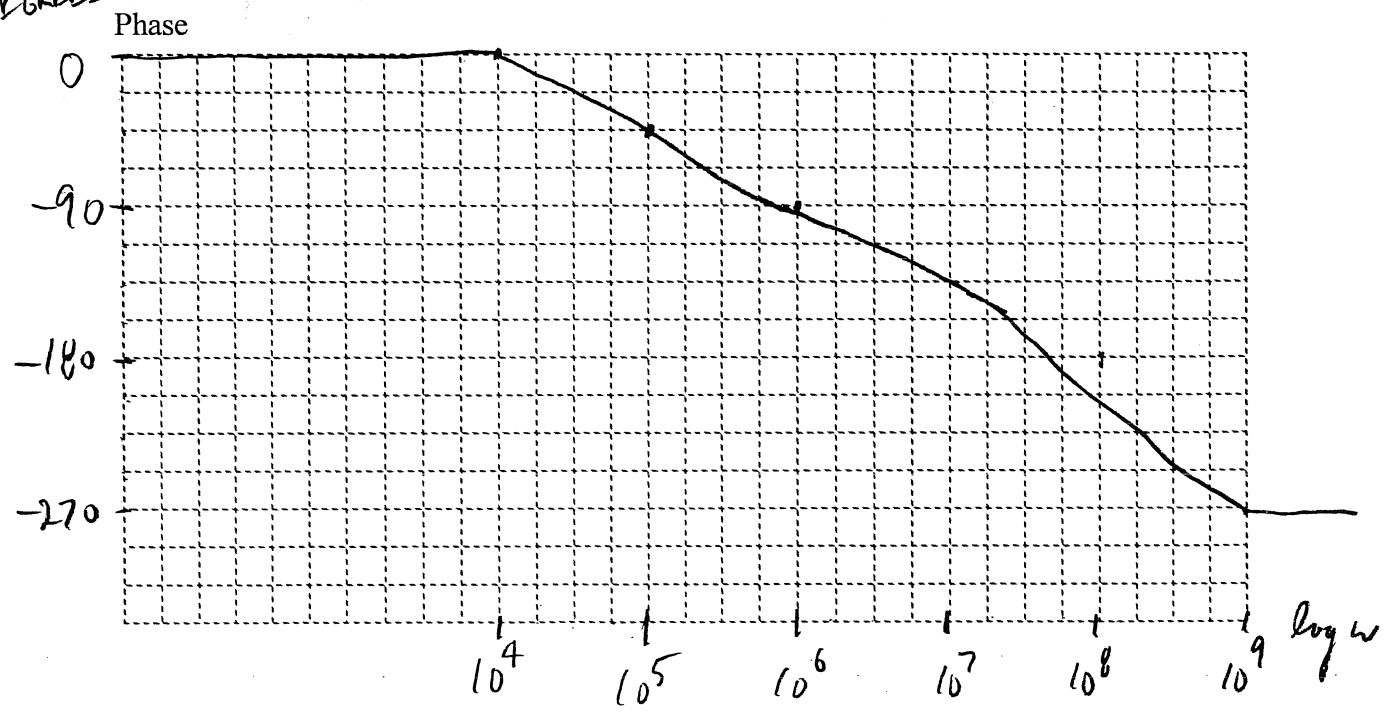

b) Estimate the minimum closed-loop gain,  $A_{\min}$ , that can be realized while having a phase margin about  $45^\circ$

$$\angle A(j\omega) \approx -135^\circ \text{ WHEN } \omega_1 \approx 10^7 \text{ RAD/S}$$

$$A_{\min} = 100 \text{ V/V}$$

$$\& |A(j\omega)| \approx 40 \text{ dB (OR } 100 \text{ V/V)}$$

$$\text{SO FOR LOOP GAIN} \approx 1 \Rightarrow \beta \approx 0.01$$

$$\& \text{FOR NON-INVERTING AMP, } A_{CL} \approx \frac{1}{\beta}$$

$$\therefore A_{\min} = 100 \text{ V/V (OR } 40 \text{ dB)}$$

c) If it is desired to have a closed-loop gain of 10 estimate the new value of  $\omega_{p1}$  if it is moved to a lower freq and a phase margin of about  $45^\circ$  is desired.

$$A_{CL} = 10 \Rightarrow \beta = 0.1$$

$$\omega_{p1}' = 10^4 \text{ RAD/S}$$

LOOP GAIN UNITY GAIN FREQ SHOULD OCCUR AT

$$\omega_{p2} |L(j\omega_{p2})| \approx 1$$

$$\beta |A(j\omega_{p2})| \approx 1 \Rightarrow |A(j\omega_{p2})| \approx 10 \text{ FOR } \omega \approx \omega_{p2}$$

$$|A(j\omega)| = \left| \frac{10^4}{\left(1 + \frac{j\omega}{\omega_{p1}'}\right) \left(1 + \frac{j\omega}{\omega_{p2}}\right)} \right| \approx \frac{10^4}{\left| \frac{j\omega}{\omega_{p1}'} \right|} \approx \frac{\omega_{p1}' 10^4}{\omega}$$

$$\omega_{p1}' \approx \frac{10 \omega_{p2}}{10^4} = \frac{\omega_{p2}}{10^3} = 10^4$$

Constants:  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26\text{mV}$  at  $300 \text{ }^\circ\text{K}$ ;  
 $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$ ;  $k_{ox} = 3.9$ ;  $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$

NMOS:  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{in} > 0$ ;  $v_{DS} \geq 0$ ;  $v_{ov} = v_{GS} - V_{in}$

(triode)  $v_{DS} \leq v_{ov}$  (or  $v_D < v_G - V_{in}$ );  $i_D = k_n((v_{ov})v_{DS} - (v_{DS}^2/2))$

(active)  $v_{DS} \geq v_{ov}$ ;  $i_D = 0.5k_n v_{ov}^2(1 + \lambda v_{DS})$ ;  $g_m = k_n v_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(\lambda' I_D)$

PMOS:  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{ip} < 0$ ;  $v_{SD} \geq 0$ ;  $v_{ov} = v_{SG} - |V_{ip}|$


(triode)  $v_{SD} \leq v_{ov}$  (or  $(v_D > v_G + |V_{ip}|)$ );  $i_D = k_p((v_{ov})v_{SD} - (v_{SD}^2/2))$

(active)  $v_{DS} \geq v_{ov}$ ;  $i_D = 0.5k_p v_{ov}^2(1 + |\lambda|v_{SD})$ ;  $g_m = k_p v_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(\lambda' I_D)$


BJT: (active)  $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$ ;  $g_m = \alpha/r_e = I_C/V_T$ ;  $r_\pi = \beta/g_m$ ;  $r_o = |V_A|/I_C$

$i_C = \beta i_B$ ;  $i_E = (\beta + 1)i_B$ ;  $\alpha = \beta/(\beta + 1)$ ;  $i_C = \alpha i_E$ ;  $R_b = (\beta + 1)(r_e + R_E)$ ;  $R_e = (R_B + r_\pi)/(\beta + 1)$

Cascode:

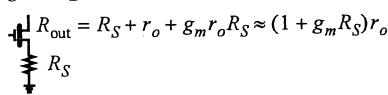
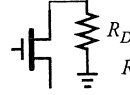
$$R_{out} = R_S + r_o + g_m r_o R_S \approx (1 + g_m R_S) r_o$$



$$R_{in} = (R_D + r_o)/(1 + g_m r_o) \approx R_D/(g_m r_o) + 1/g_m$$

Diff Pair:

$$A_d = g_m R_D$$

$$A_{CM} = -(R_D/(2R_{SS}))((\Delta R_D)/R_D)$$

$$V_{os} = \Delta V_t$$

$$V_{os} = (V_{ov}/2)((\Delta R_D)/R_D)$$

$$V_{os} = (V_{ov}/2)((\Delta(W/L))/(W/L))$$

1st order:

step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$  unity gain freq for  $T(s) = \frac{A_M}{1 + s/\omega_{3dB}}$   $f_t \approx |A_M|\omega_{3dB}$  when  $A_M \gg 1$

Freq:

for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2)...(1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2)...(1 + s/\omega_n)}$

OTC estimate  $f_H = 1/(2\pi \sum \tau_i)$ ; dominant pole estimate  $f_H = 1/(2\pi \tau_{max})$

Miller:

$$Z_1 = Z/(1 - K)$$

$$Z_2 = Z/(1 + K)$$

Mos caps:

$$C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$$

$$C_{gd} = WL_{ov}C_{ox}$$

$$C_{db} = C_{db0}/(\sqrt{1 + V_{db}/V_0})$$

$$f_t = g_m/(2\pi(C_{gs} + C_{gd}))$$

assuming  $C_{gd} \ll C_{gs}$   $f_t = (3\mu V_{ov})/(4\pi L^2)$

Feedback:

$$A_f = A/(1 + A\beta)$$

$$x_i = (1/(1 + A\beta))x_s$$

$$dA_f/A_f = (1/(1 + A\beta))dA/A$$

$$\omega_{Hf} = \omega_H(1 + A\beta)$$

$$\omega_{Lf} = \omega_L/(1 + A\beta)$$

$$\text{Loop Gain } L = -s_r/s$$

$$A_f = A_\infty(L/(1 + L)) + d/(1 + L)$$

$$Z_{port} = Z_{port(k=0)}((1 + L_S)/(1 + L_O))$$

$$\text{PM} = \angle L(j\omega_1) + 180$$

$$\text{GM} = -\angle L(j\omega_{180})|_{\text{dB}}$$

$$\text{Pole Splitting } \omega_{p1}' \approx 1/(g_m R_2 C_f R_1)$$

$$\omega_{p2}' \approx (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$$

Pole Pair

$$s^2 + (\omega_o/Q)s + \omega_o^2 = 0$$

$$Q \leq 0.5 \Rightarrow \text{real poles}$$

$$Q > 1/\sqrt{2} \Rightarrow \text{freq resp peaking}$$

**MOS Transistor;** CMOS basic parameters. Channel length = 0.18μm

	$V_t$ (V)	$\mu C_{ox}$ ( $\mu\text{A}/\text{V}^2$ )	$\lambda'$ ( $\mu\text{m}/\text{V}$ )	$C_{ox}$ ( $\text{fF}/\mu\text{m}^2$ )	$t_{ox}$ (nm)	$L_{ov}$ ( $\mu\text{m}$ )	$\frac{C_{db0}}{W}$ ( $\frac{\text{fF}}{\mu\text{m}}$ )
NMOS	0.4	240	0.05	8.5	4	0.04	0.3
PMOS	-0.4	60	-0.05	8.5	4	0.04	0.3