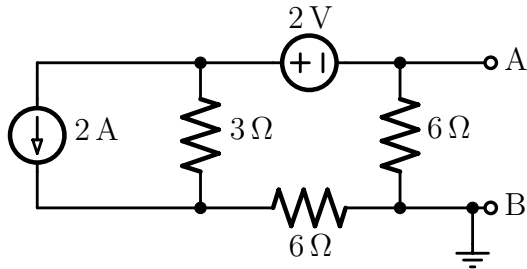



## Problem Set 1

**Q1.** Find the voltage source equivalent and current source equivalent circuits for the following circuits between the nodes A and B. Use  $I_{sc}$  for the short circuit output current,  $V_{oc}$  for the open circuit output voltage and  $R_{th}$  for the output resistance.


(a)



(b)

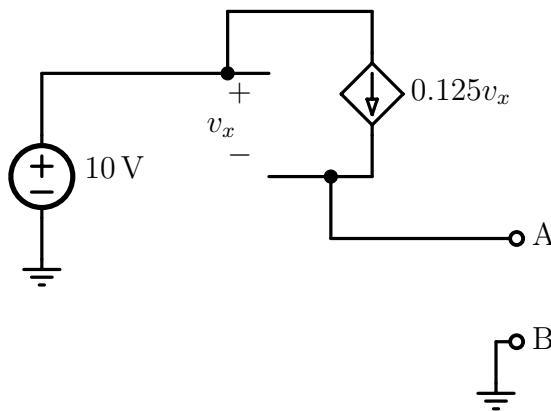

(c)

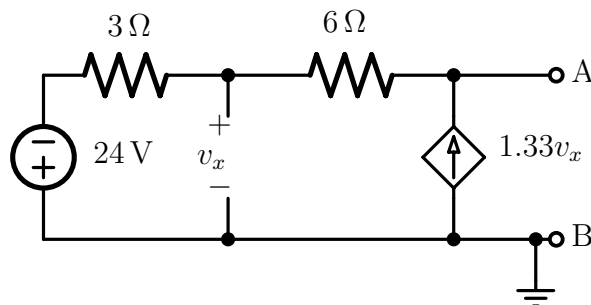

- Q2.** An NMOS transistor that is operated with a small  $v_{DS}$  is found to exhibit a resistance  $r_{DS}$ . By what factor will  $r_{DS}$  change in each of the following situations?
- Overdrive is multiplied by a factor of 2.
  - The device is replaced with another fabricated in the same technology but width multiplied by a factor of 2.
  - The device is replaced with another fabricated in the same technology but with both the width and length are multiplied by a factor of 2.
  - The device is replaced with another fabricated in a more advanced technology for which the oxide thickness is multiplied by a factor of 0.5 and both  $W$  and  $L$  are each multiplied by a factor of 0.5 (assume  $\mu_n$  remains unchanged).
- Q3.** An NMOS transistor with  $k_n = 1 \text{ mA/V}^2$  and  $V_t = 1 \text{ V}$  is operated with  $V_{GS} = 2.5 \text{ V}$ . At what value of  $V_{DS}$  does the transistor enter the saturation region? What value of  $I_D$  is obtained in saturation?
- Q4.** With the knowledge that  $\mu_p \approx 0.4 \mu_n$ , what must be the relative width of n-channel and p-channel devices if they are to have equal drain currents when operated in the saturation mode with overdrive voltages of the same magnitude?
- Q5.** An NMOS transistor is fabricated in a  $0.8\text{-}\mu\text{m}$  process having  $k'_n = 130 \mu\text{A/V}^2$  and  $V'_A = 20 \text{ V}/\mu\text{m}$  of channel length. If  $L = 1.6 \mu\text{m}$  and  $W = 16 \mu\text{m}$ , find  $V_A$  and  $\lambda$ . Find the value of  $I_D$  that results when the device is operated with an overdrive voltage of  $0.5 \text{ V}$  and  $V_{DS} = 2 \text{ V}$ . Also, find the value of  $r_o$  at this operating point. If  $V_{DS}$  is increased by  $1 \text{ V}$ , what is the corresponding change in  $I_D$ ?
- Q6.** A p-channel transistor for which  $|V_t| = 1 \text{ V}$  and  $|V_A| = 50 \text{ V}$  operates in saturation with  $|V_{GS}| = 3 \text{ V}$ ,  $|V_{DS}| = 4 \text{ V}$ ,  $i_D = 3 \text{ mA}$ . Find the corresponding signed values for  $V_{GS}$ ,  $V_{SG}$ ,  $V_{DS}$ ,  $V_{SD}$ ,  $V_t$ ,  $\lambda$ , and  $k'_p(W/L)$ .
- Q7.** For the NMOS amplifier below, replace the transistor with its T equivalent circuit, assuming  $\lambda = 0$ . Derive the expressions for the voltage gains  $v_s/v_i$  and  $v_d/v_i$ .

