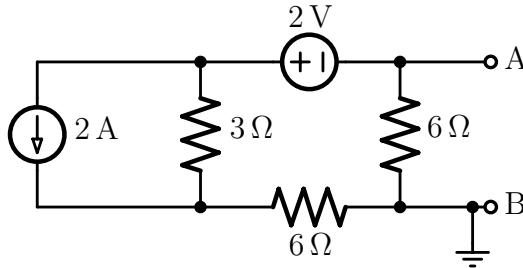



Problem Set 1

Q1. Find the voltage source equivalent and current source equivalent circuits for the following circuits between the nodes A and B. Use I_{sc} for the short circuit output current, V_{oc} for the open circuit output voltage and R_{th} for the output resistance.


(a)




Solution

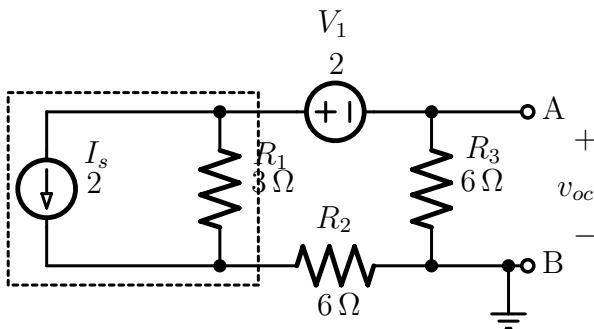

Using source transformation:

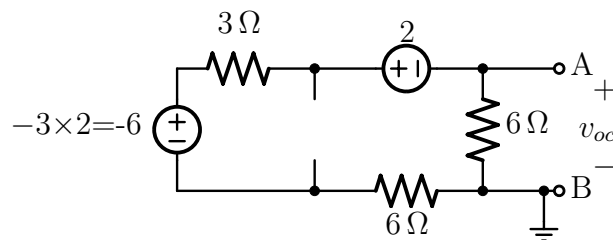

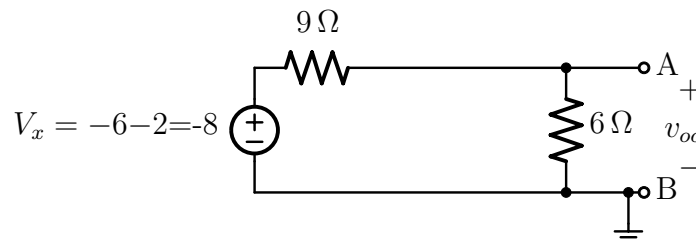Simplifying Voltage source and resistor in series:




Then, we calculate: $V_x = -(R_1 * I_s) - V_1 = -((3) * (2)) - (2) = -8 \text{ V}$

$V_{oc} = V_x * (R_3) / (R_3 + R_1 + R_2) = (-8) * ((6)) / ((6) + (3) + (6)) = -3.2 \text{ V}$



$$R_{th} = R_3 || R_1 + R_2 = (6) || (3) + (6) = 3.6 \Omega$$

$$I_{sc} = V_{oc} / R_{th} = (-3.2) / (3.6) = -0.8889 \text{ A}$$

(b)

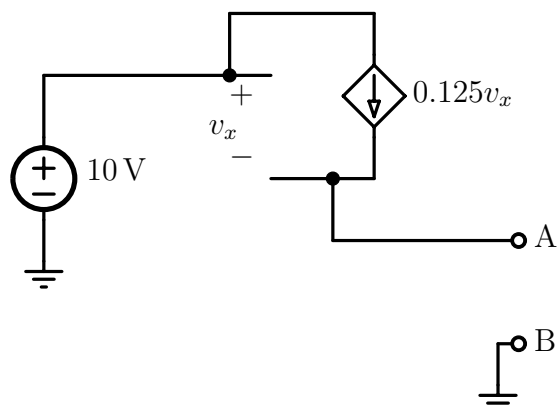

Solution

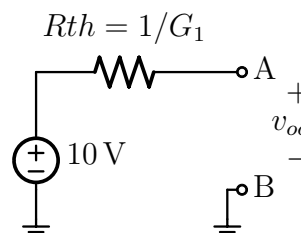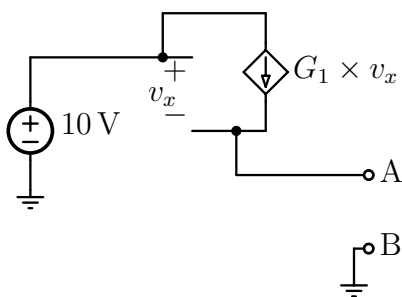


We calculate: $V_{oc} = V_2 = (10) = 10 \text{ V}$


$$R_{th} = 1/G_1 = 1/(0.125) = 8 \Omega$$

$$I_{sc} = V_{oc} / R_{th} = (10) / (8) = 1.25 \text{ A}$$

(c)

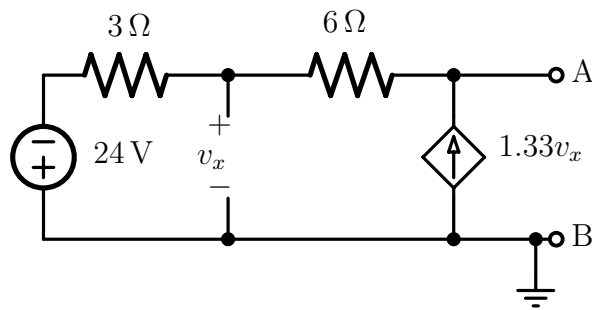

Solution

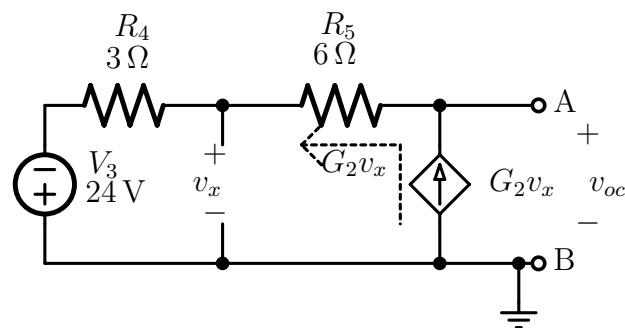


KVL:

$$-V_3 + v_x + G_2 v_x R_4 = 0$$

$$v_x = V_3 / (G_2 * R_4 - 1) = (24) / ((1.33) * (3) - 1) = 8.027 \text{ V}$$
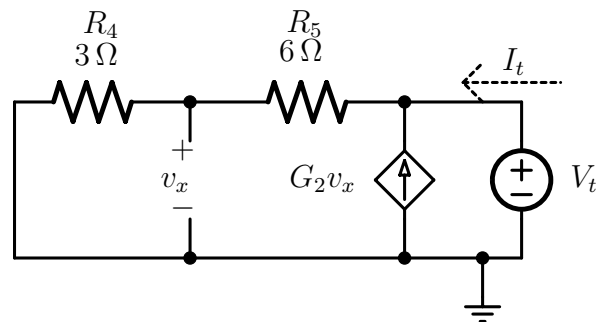
$$v_{oc} = -V_3 + (R_4 + R_5) * G_2 * v_x = -(24) + ((3) + (6)) * (1.33) * (8.027) = 72.08 \text{ V}$$



$$v_x = V_t * R_4 / (R_4 + R_5) = (1) * (3) / ((3) + (6)) = 0.3333 \text{ V}$$

$$I_{sc} = v_x / R_4 - G_2 * v_x = (0.3333) / (3) - (1.33) * (0.3333) = -0.3322 \text{ A}$$

$$R_{th} = V_t/I_{sc} = (1)/(-0.3322) = -3.01 \Omega$$

Q2. An NMOS transistor that is operated with a small v_{DS} is found to exhibit a resistance r_{DS} . By what factor will r_{DS} change in each of the following situations?

- Overdrive is multiplied by a factor of 2.
- The device is replaced with another fabricated in the same technology but width multiplied by a factor of 2.
- The device is replaced with another fabricated in the same technology but with both the width and length are multiplied by a factor of 2.
- The device is replaced with another fabricated in a more advanced technology for which the oxide thickness is multiplied by a factor of 0.5 and both W and L are each multiplied by a factor of 0.5 (assume μ_n remains unchanged).

Solution

With V_{DS} small compared to V_{OV} , The drain to source resistance r_{DS} can be approximated with

$$r_{DS} = \frac{1}{\mu_n C_{ox} (W/L) V_{OV}}$$

- If $V'_{OV} = 2V_{OV}$, then $r'_{DS} = r_{DS}/2$.
- If $W' = 2W$, then $r'_{DS} = r_{DS}/2$.
- If $W' = 2W$ and $L' = 2L$, then $r'_{DS} = r_{DS}$.
- If oxide thickness $t'_{ox} = 0.5t_{ox}$, then $C_{ox} = \epsilon_{ox}/t_{ox}$ is multiplied by a factor of 2. If W and L are scaled by the same factor, then $r'_{DS} = r_{DS}/0.5$.

Q3. An NMOS transistor with $k_n = 1 \text{ mA/V}^2$ and $V_t = 1 \text{ V}$ is operated with $V_{GS} = 2.5 \text{ V}$. At what value of V_{DS} does the transistor enter the saturation region? What value of I_D is obtained in saturation?

Solution

$$V_{OV} = V_{GS} - V_t = (2.5) - (1) = 1.5 \text{ V}$$

The minimum drain to source voltage to keep the device in saturation is:

$$V_{DSAT} = V_{OV} = (1.5) = 1.5 \text{ V}$$

In Saturation, the Drain current is:

$$I_D = 0.5 * k_n * V_{OV}^2 = 0.5 * (1e - 3) * (1.5)^2 = 1.125 \text{ mA}$$

Q4. With the knowledge that $\mu_p \approx 0.4\mu_n$, what must be the relative width of n-channel and p-channel devices if they are to have equal drain currents when operated in the saturation mode with overdrive voltages of the same magnitude?

Solution

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_{th})^2, \text{ where } k'_n = \mu_n C_{ox}.$$

for equal drain currents:

$$\mu_n C_{ox} \frac{W_n}{L} = \mu_p C_{ox} \frac{W_p}{L} \Rightarrow \mu_n W_n = \mu_p W_p \Rightarrow W_p/W_n = \mu_n/\mu_p = 2.5$$

Q5. An NMOS transistor is fabricated in a $0.8\text{-}\mu\text{m}$ process having $k'_n = 130 \mu\text{A/V}^2$ and $V'_A = 20 \text{ V}/\mu\text{m}$ of channel length. If $L = 1.6 \mu\text{m}$ and $W = 16 \mu\text{m}$, find V_A and λ . Find the value of I_D that results when the device is operated with an overdrive voltage of 0.5 V and $V_{DS} = 2 \text{ V}$. Also, find the value of r_o at this operating point. If V_{DS} is increased by 1 V , what is the corresponding change in I_D ?

Solution

$$V_A = V'_A L = 32 \text{ V}$$

$$\lambda = (31.25e - 3)V^{-1}$$

$$V_{DS} = 2 \text{ V} > V_{ov} = 0.5 \text{ V} \Rightarrow \text{Saturation}$$

$$i_D = 0.5 * k'_n * W/L * V_{ov}^2 = 162.5 \mu\text{A}$$

$$r_o = V_A/i_D = (32)/(162.5e - 6) = 196.9 \text{ k}\Omega = \frac{\Delta V_{DS}}{\Delta i_D} = \frac{1}{\Delta i_D} \Rightarrow \Delta i_D = 5.078 \mu\text{A}$$

- Q6.** A p-channel transistor for which $|V_t| = 1 \text{ V}$ and $|V_A| = 50 \text{ V}$ operates in saturation with $|V_{GS}| = 3 \text{ V}$, $|V_{DS}| = 4 \text{ V}$, $i_D = 3 \text{ mA}$. Find the corresponding signed values for V_{GS} , V_{SG} , V_{DS} , V_{SD} , V_t , λ , and $k'_p(W/L)$.

Solution

$$V_{SG} = 3 \text{ V}$$

$$V_{GS} = -3 \text{ V}$$

$$V_{SD} = 4 \text{ V}$$

$$V_{DS} = -4 \text{ V}$$

$$V_t = -1 \text{ V}$$


$$\lambda = 1/V_A = 1/(50) = 20 \text{ mV}^{-1}$$

$$i_D = 1/2 k'_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$


$$\Rightarrow 3e - 3 = 1/2 k'_p \frac{W}{L} (-3 - (-1))^2 (1 + 20e - 3(-4))$$

$$\Rightarrow k'_p \frac{W}{L} = 1.389 \text{ mA/V}^2$$

- Q7.** For the NMOS amplifier below, replace the transistor with its T equivalent circuit, assuming $\lambda = 0$. Derive the expressions for the voltage gains v_s/v_i and v_d/v_i .

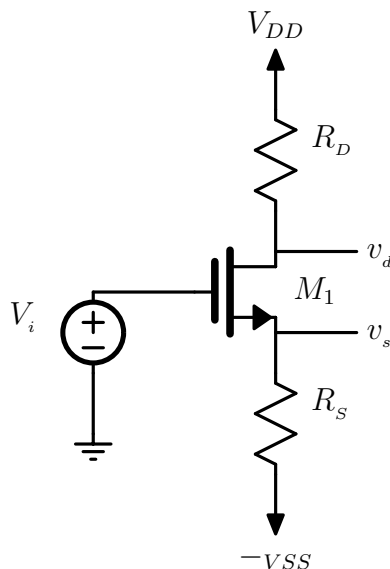**Solution**

The equivalent T model is:

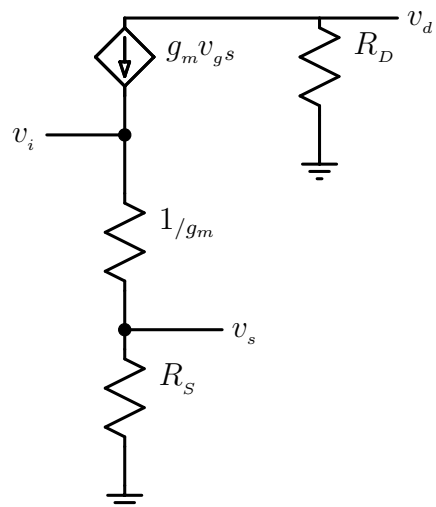

$$\lambda = 0 \Rightarrow r_o = \infty$$

$$v_i = g_m v_{gs} \left(\frac{1}{g_m} + R_S \right)$$

$$v_d = -g_m v_{gs} R_D$$

$$v_s = g_m v_{gs} R_S$$

Note the voltage divider:

$$\frac{v_s}{v_i} = \frac{R_S}{1/g_m + R_S} = \frac{g_m R_S}{1 + g_m R_S} \approx 1$$

$$\frac{v_d}{v_i} = -\frac{R_D}{1/g_m + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$