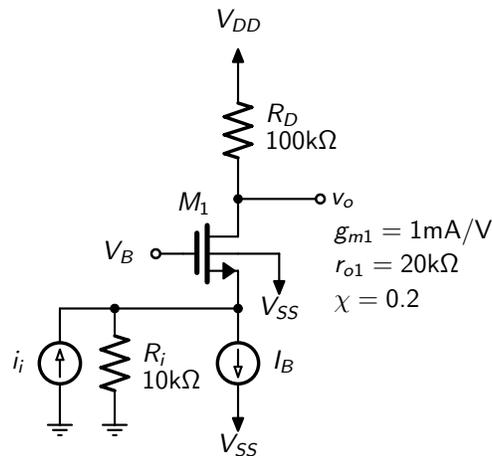


Problem Set 3C - Body Effect

Question 1

It is desired to create a voltage output from a small current source input (say from a photodetector). Shown below, the small current source input and its output impedance is shown as i_i and R_i , respectively. V_B is a dc bias voltage and assume the current source I_B is ideal.



- (a) Find the small-signal gain, v_o/i_i assuming no body effect (in other words, $\chi = 0$).
- (b) Find the small-signal gain, v_o/i_i assuming $\chi = 0.2$.

Solution

(a) We can start by finding the output impedance, R_o


Define R_{dx} to be the small signal resistance looking into the drain of M_1

$$R_{dx} = r_{o1} + (1 + g_{m1} * r_{o1}) * R_i = (20e3) + (1 + (1e-3) * (20e3)) * (10e3) = 230k\Omega$$

$$R_o = R_{dx} || R_D = (230e3) || (100e3) = 69.7k\Omega$$

Next, we find the short circuit current, i_{sc}

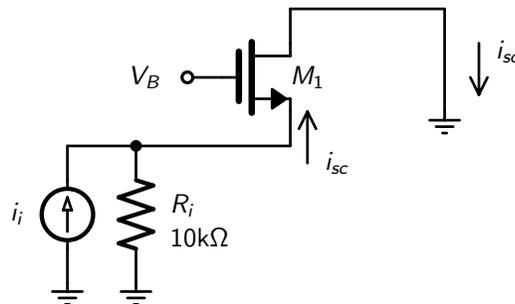We have the following small circuit circuit



Defining R_{sx} to be the impedance looking in to the source of M_1 we have

$$R_{sx} = (1/g_{m1}) || r_{o1} = (1/(1e-3)) || (20e3) = 952.4\Omega$$

and we see a current divider, so we have

$$i_{sc}/i_i = R_i/(R_i + R_{sx}) = (10e3)/((10e3) + (952.4)) = 0.913A/A \text{ leading to}$$

$$(v_o/i_i)_a = i_{sc}/i_i * R_o = (0.913) * (69.7e3) = 63.64k\Omega$$

(b) We go through the same analysis as in (a) except that we have

$$g'_{m1} = g_{m1} * (1 + \chi) = (1e-3) * (1 + (0.2)) = 1.2e-3$$

Define R_{dx} to be the small signal resistance looking into the drain of M_1

$$R_{dx} = r_{o1} + (1 + g'_{m1} * r_{o1}) * R_i = (20e3) + (1 + (1.2e-3) * (20e3)) * (10e3) = 270k\Omega$$

$$R_o = R_{dx} || R_D = (270e3) || (100e3) = 72.97k\Omega$$

Next, we find the short circuit current, i_{sc}

Defining R_{sx} to be the impedance looking in to the source of M_1 we have


$$R_{sx} = (1/g'_{m1}) || r_{o1} = (1/(1.2e-3)) || (20e3) = 800\Omega$$

and we see a current divider, so we have

$$i_{sc}/i_i = R_i/(R_i + R_{sx}) = (10e3)/((10e3) + (800)) = 0.9259A/A \text{ leading to}$$

$$(v_o/i_i)_b = i_{sc}/i_i * R_o = (0.9259) * (72.97e3) = 67.57k\Omega$$

Question 2

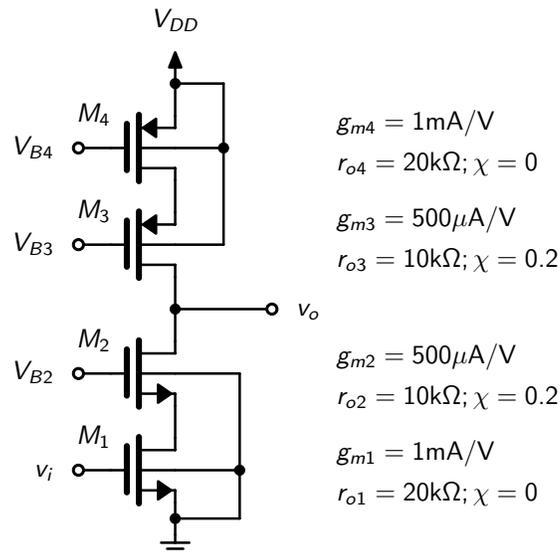

For the circuit above

(a) Find v_o/v_i ignoring body effect (all $\chi = 0$).

(b) Find v_o/v_i including body effect where for $M2, M3, \chi = 0.2$.

Solution

(a) Define R_{op} to be the impedance looking up into the drain of M_3 and define R_{on} to be the impedance looking down into the drain of M_2


$$R_{op} = r_{o3} + (1 + g_{m3} * r_{o3}) * r_{o4} = (10e3) + (1 + (500e-6) * (10e3)) * (20e3) = 130k\Omega$$

$$R_{on} = r_{o2} + (1 + g_{m2} * r_{o2}) * r_{o1} = (10e3) + (1 + (500e-6) * (10e3)) * (20e3) = 130k\Omega$$

Define R_o to be the impedance to ground at node v_o

$$R_o = R_{op} || R_{on} = (130e3) || (130e3) = 65k\Omega$$

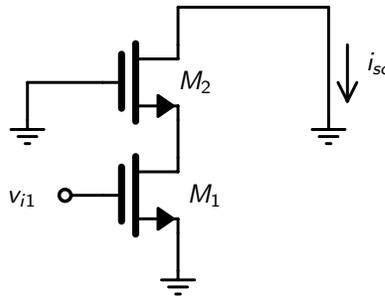For i_{sc} , we have the following circuit



Define R_{S2} to be the impedance looking up into the source of M_2

$$R_{S2} = (1/g_{m2}) || r_{o2} = (1/(500e-6)) || (10e3) = 1.667k\Omega$$

The drain current of M_1 current divides between R_{S2} and r_{o1} resulting in

$$G_{Ma} = -g_{m1} * (r_{o1}) / (r_{o1} + R_{S2}) = -(1e-3) * ((20e3)) / ((20e3) + (1.667e3)) = -923.1e-6$$

and $i_{sc} = G_{Ma} * v_i$. The resulting gain is

$$(v_o/v_i)_a = G_{Ma} * R_o = (-923.1e-6) * (65e3) = -60V/V$$

(b) To include the body effect, we have

$$g'_m2 = g_{m2} * (1 + \chi) = (500e-6) * (1 + (0.2)) = 600e-6$$

$$g'_m3 = g_{m3} * (1 + \chi) = (500e-6) * (1 + (0.2)) = 600e-6$$

Define R_{op} to be the impedance looking up into the drain of M_3 and define R_{on} to be the impedance looking down into the drain of M_2

$$R_{op} = r_{o3} + (1 + g'_m3 * r_{o3}) * r_{o4} = (10e3) + (1 + (600e-6) * (10e3)) * (20e3) = 150k\Omega$$

$$R_{on} = r_{o2} + (1 + g'_m2 * r_{o2}) * r_{o1} = (10e3) + (1 + (600e-6) * (10e3)) * (20e3) = 150k\Omega$$

Define R_o to be the impedance to ground at node v_o

$$R_o = R_{op} || R_{on} = (150e3) || (150e3) = 75k\Omega$$

For i_{sc} , we define R_{S2} to be the impedance looking up into the source of M_2 when the drain of M_2 is grounded

$$R_{S2} = (1/g'_m2) || r_{o2} = (1/(600e-6)) || (10e3) = 1.429k\Omega$$

The drain current of M_1 current divides between R_{S2} and r_{o1} resulting in


$$G_{Ma} = -g_{m1} * (r_{o1}) / (r_{o1} + R_{S2}) = -(1e-3) * ((20e3)) / ((20e3) + (1.429e3)) = -933.3e-6$$

and $i_{sc} = G_{Ma} * v_i$. The resulting gain is

$$(v_o/v_i)_b = G_{Ma} * R_o = (-933.3e-6) * (75e3) = -70V/V$$

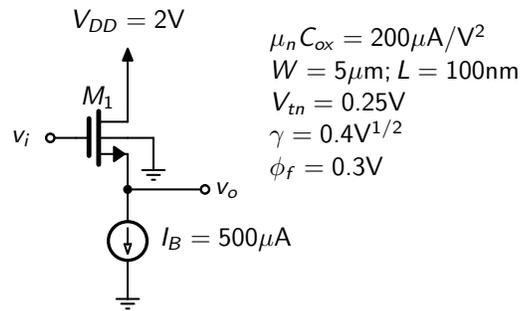Question 3

Consider the common-drain (or source follower) shown below.



- (a) Ignoring the body effect, find the voltage at v_o when $v_i = V_{DD}$
 (b) Repeat (a) but include the body effect and find the output voltage (an iterative approach is needed here).

Solution

(a) First find V_{ov} using the equation

$$I_D = 0.5 \mu_n C_{ox} (W/L) V_{ov}^2$$

and we see that $I_D = I_B = (500e-6) = 500 \mu A$

$$V_{ov} = \sqrt{2 * I_D / (\mu_n C_{ox} * (W/L))} = \sqrt{2 * (500e-6) / ((200e-6) * ((5e-6) / (100e-9)))} = 0.3162V$$

So we have

$$V_{GS} = V_{ov} + V_{tn} = (0.3162) + (0.25) = 0.5662V$$

and when $v_i = V_{DD}$, we have

$$v_{o,a} = V_{DD} - V_{GS} = (2) - (0.5662) = 1.434V$$

Note that $v_o = V_{SB}$ since v_o is at the source voltage and $V_B = 0$

(b) When including the body effect, V_{tn} will change. So we define

$$V_{tn0} = 0.25V$$

V_{tn0} is the threshold voltage with $V_{SB} = 0$

Also, the value for V_{ov} is the same we found in (a)

$$V_{ov} = 0.3162V$$

Now, we make use of the body equation for the threshold voltage

$$V_{tn} = V_{tn0} + \gamma [\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}]$$

as well as the equation

$$V_{SB} = v_o = V_{DD} - (V_{ov} + V_{tn})$$

Now we use an iterative approach to find the value of V_{tn} and therefore the value for $v_o = V_{SB}$

Our first guess for V_{SB} can be any value but lets start with the value we found when we ignored the body effect.

$$V_{SB0} = 1.434V$$

$$V_{tn1} = V_{tn0} + \gamma * (\sqrt{2\phi_f + V_{SB0}} - \sqrt{2\phi_f}) = (0.25) + (0.4) * (\sqrt{2 * (0.3) + (1.434)} - \sqrt{2 * (0.3)}) = 0.5106V$$

$$V_{SB1} = V_{DD} - (V_{ov} + V_{tn1}) = (2) - ((0.3162) + (0.5106)) = 1.173V$$

$$V_{tn2} = V_{tn0} + \gamma * (\sqrt{2\phi_f + V_{SB1}} - \sqrt{2\phi_f}) = (0.25) + (0.4) * (\sqrt{2 * (0.3) + (1.173)} - \sqrt{2 * (0.3)}) = 0.4728V$$

$$V_{SB2} = V_{DD} - (V_{ov} + V_{tn2}) = (2) - ((0.3162) + (0.4728)) = 1.211V$$

$$V_{tn3} = V_{tn0} + \gamma * (\sqrt{2\phi_f + V_{SB2}} - \sqrt{2\phi_f}) = (0.25) + (0.4) * (\sqrt{2 * (0.3) + (1.211)} - \sqrt{2 * (0.3)}) = 0.4785V$$

$$V_{SB3} = V_{DD} - (V_{ov} + V_{tn3}) = (2) - ((0.3162) + (0.4785)) = 1.205V$$

Since V_{SB} is now changing very little, we can say our answer for v_o when the body effect is taken into account is

$$v_{o,b} = V_{SB3} = (1.205) = 1.205V$$