

$$9.17 \quad g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.1}{0.2} = 1 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{1 \times 10^{-3}}{2\pi(20 + 5) \times 10^{-15}} = 6.3 \text{ GHz}$$

9.20 The intrinsic gain A_O is

$$= g_m \cdot r_o = \left(\frac{2I_D}{V_{OV}}\right) \cdot \left(\frac{V_A}{I_D}\right) = \frac{2V_A}{V_{OV}} \text{ and}$$

$$V_A = V_A' \cdot L = 5 \text{ V}/\mu\text{m} \cdot L$$

$$A_O = \frac{2 \times 5[\text{V}/\mu\text{m}] \cdot L}{0.2[\text{V}]} = 50 \times L \text{ V/V with } L \text{ in mm.}$$

* From problem 9.19

$$f_T = \frac{3\mu_n V_{OV}}{4\pi \cdot L^2} = \frac{3 \times 450 \left[\frac{\text{cm}^2}{\text{V} \cdot \text{S}} \right] \cdot 0.2[\text{V}]}{4\pi L^2} = \frac{2.15 \times 10^{-3}}{L^2}$$

$$L_{\min} = 0.18 \times 10^{-6} \text{ m}$$

	1 L_{\min}	2 L_{\min}	3 L_{\min}	4 L_{\min}	5 L_{\min}
$A_O [\text{V/V}]$	9	18	27	36	45
$f_T[\text{GHz}]$	66.35	16.59	7.37	4.14	2.65

$$9.29 \quad C_{in} = C_{gs} + C_{eq}$$

$$= C_{gs} + C_{gd} (1 + g_m R_L)$$

$$= 0.5 + 0.1(1 + 29) = 3.5 \text{ pF}$$

Neglecting R_G :

$$f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}} \text{ i.e. } R_G \text{ is very large if}$$

$$f_H > 10 \text{ MHz} \Rightarrow \frac{1}{2\pi \cdot 3.5 \times 10^{-12} \times 10^6} > R_{sig}$$

$$\Rightarrow R_{sig} < 4.55 \text{ k}\Omega$$

$$9.33 \quad R_G = 1 \text{ M}\Omega, g_m = 5 \frac{\text{mA}}{\text{V}},$$

$$r_o = 100 \text{ k}\Omega, R_D = 10 \text{ k}\Omega$$

$$C_{gs} = 2 \text{ pF}, C_{gd} = 0.4 \text{ pF}, R_{sig} = 500 \text{ k}\Omega, R_L = 10 \text{ k}\Omega$$

a) Using Eq. 9.44 where $R_L' = r_o \parallel R_D \parallel R_L$

$$A_M = \frac{-R_G}{R_G + R_{sig}} \cdot g_m(r_o \parallel R_D \parallel R_L)$$

$$= \frac{-1 \times 5}{1 + 0.5} (100 \text{ K} \parallel 10 \text{ K} \parallel 10 \text{ K})$$

$$A_M = -15.9 \text{ V/V}$$

b) Eq. 9.54: $f_H = \frac{1}{2\pi \cdot C_{in} \cdot R_{sig}}$ where

$$C_{in} = C_{gs} + C_{gd}(1 + g_m(r_o \parallel R_D \parallel R_L))$$

$$= 2 + 0.4(1 + 5(100 \parallel 10 \parallel 10)) = 11.9 \text{ pF}$$

$$R_{sig}' = R_{sig} \parallel R_G = 0.5 \text{ M} \parallel 1 \text{ M} = 333.3 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi \cdot 11.9 \times 10^{-12} \times 333.3 \times 10^3}$$

$$= 40.1 \text{ kHz}$$

9.35 If $g_m = 1 \frac{\text{mA}}{\text{V}}$ and $r_o = 100 \text{ k}\Omega$:

$$A_M = \frac{R_G}{R_G + R_{sig}} g_m(r_o \parallel R_D \parallel R_L) \text{ where}$$

$$R_G = 10 \text{ M} \parallel 47 \text{ M}$$

$$R_G = 8.25 \text{ M}\Omega$$

$$A_M = -\frac{8.25}{8.25 + 0.1} 1(100 \text{ K} \parallel 4.7 \text{ K} \parallel 10 \text{ K})$$

$$= -3.06 \text{ V/V}$$

$$f_H = \frac{1}{2\pi C_{in} R_{sig}'} \text{ where}$$

$$R_{sig}' = R_{sig} \parallel R_G = 0.1 \text{ M} \parallel 8.25 \text{ M}\Omega$$

$$R_{sig}' \equiv 0.1 \text{ M}\Omega$$

$$C_{in} = C_{gs} + C_{gd}(1 + g_m(r_o \parallel R_D \parallel R_L))$$

$$C_{in} = 1 + 0.2(1 + 1(100 \text{ K} \parallel 4.7 \text{ K} \parallel 10 \text{ K}))$$

$$= 1.82 \text{ pF}$$

$$f_H = \frac{1}{2\pi \times 1.82 \times 10^{-12} \times 0.1 \times 10^6}$$


$$= 875 \text{ kHz}$$

9.44

a) Gain $A = 60 \text{ dB} = 1000$

$$A(s) = \frac{1000}{\left(1 + \frac{1}{2\pi \times 10 \times 10^3}\right)} = \frac{1000}{\left(1 + \frac{1}{2\pi \times 10^4}\right)}$$

(b)

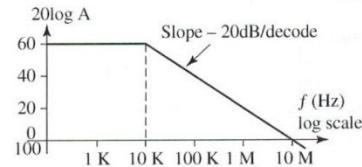


$$\text{(c) Gain-bandwidth product} = 1000 \times 10 \text{ K}$$

$$= 10 \text{ MHz}$$

(d) From the gain plot, unity gain frequency = 10 MHz

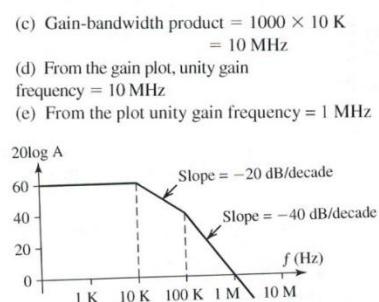(e) From the plot unity gain frequency = 1 MHz




9.57 Using Miller's theorem Eq. 9.76

$$Z_1 = \frac{Z}{1 - K} \Rightarrow C_I = 0.2 \times (1 - (-1000))$$

$$\Rightarrow C_I = 200.2 \text{ pF}$$

$$C_O = 0.2 \times \left(\frac{-1}{1000} + 1 \right)$$

$$= 199.8 \text{ fF}$$

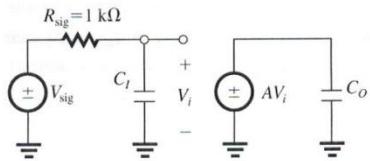

$$v_O = A v_i = A \cdot v_{\text{sig}} \frac{1/C_I s}{R_{\text{sig}} + \frac{1}{C_I \cdot s}}$$

$$\Rightarrow \frac{v_O}{v_{\text{sig}}} = \frac{A}{1 + C_I R_{\text{sig}} \cdot s}$$

$$\omega_H = \frac{1}{C_I R_{\text{sig}}} = \frac{1}{200.2 \text{ pF} \times 1 \text{ k}\Omega} = 4.99 \text{ M rad/s}$$

$$\Rightarrow f_H = 795 \text{ kHz}$$

$$\begin{aligned} \mathbf{9.60} \quad A_M &= -g_m \cdot R_L' = -4 \times 20 \\ &= -80 \text{ V/V} \end{aligned}$$

$$C_{\text{in}} = C_{gs} + C_{gd}(1 + g_m \cdot R_L')$$

(See Example 9.8)

$$C_{\text{in}} = 2 + 0.1(1 + 4 \times 20) = 10.1 \text{ pF}$$

$$f_H \approx \frac{1}{2\pi C_{\text{in}} \cdot R_{\text{sig}}'}$$


$$= \frac{1}{2\pi \times 10.1 \times 10^{-12} \times 20 \times 10^3} = 788 \text{ kHz}$$

Note : The Miller approximation consists on reflecting C_{sd} towards the input using the Miller theorem, but neglecting the effect of C_L and of C_{gd} reflected towards the load.

Question 9.60

$$A_m = -80$$

Using Miller's Theorem, we have:

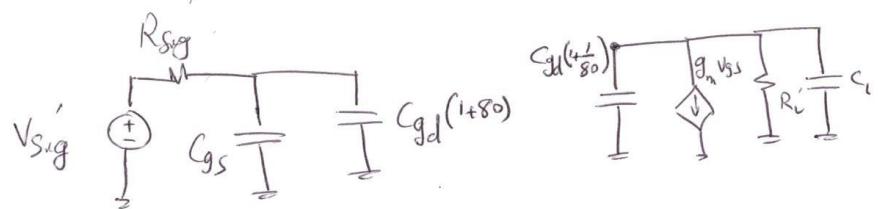

$$f_{in} = \frac{1}{2\pi C_{in} R_{sig}} = \frac{1}{2\pi (2 + (0.1)(1 + 80)) \times 20^k} = 788 \text{ Hz}$$

$$f_{out} = \frac{1}{2\pi (C_{out} \cdot R_o)} = \frac{1}{2\pi (2 + (0.1) \times (1 + \frac{1}{80})) \times 20^k} = 3.79 \text{ MHz}$$

$$\begin{aligned}
\mathbf{9.79} \quad R_O &= 2r_O + (g_m r_O) r_O = 2 \times 50 \text{ k}\Omega \\
&\quad + (1 \times 50) \times 50 \text{ k}\Omega = 2.6 \text{ M}\Omega \\
A_V &= -g_m(R_O \parallel R_L) = -1 \text{ m}(2.6 \text{ M} \parallel 2 \text{ M}) \\
&= -1130 \frac{\text{V}}{\text{V}}
\end{aligned}$$

$$\begin{aligned}
A_V &= -1130 \frac{\text{V}}{\text{V}} \\
R_{in2} &= \frac{r_O + R_L}{g_m r_O} = \frac{50 \text{ k}\Omega + 2 \text{ M}\Omega}{1 \times 50} = 41 \text{ k}\Omega \\
R_{d1} &= r_O \parallel R_{in2} = 50 \text{ k}\Omega \parallel 41 \text{ k}\Omega = 22.5 \text{ k}\Omega \\
\tau_H &= R_{sig}[C_{gs} + C_{gd}(1 + g_m R_{d1})] \\
&\quad + R_{d1}(C_{gd} + C_{db} + C_{gs}) \\
&\quad + (R_L \parallel R_o)(C_L + C_{db} + C_{gd}) \\
\tau_H &= 100 \text{ K} \times [30 \text{ f} + 10 \text{ f}(1 + 1 \times 22.5)] \\
&\quad + 22.5 \text{ K} \times [10 \text{ f} + 10 \text{ f} + 30 \text{ f}] \\
&\quad + (2 \text{ M} \parallel 2.6 \text{ M}) \times [40 \text{ f} + 10 \text{ f} + 10 \text{ f}] \\
\tau_H &= 26.5 \text{ ns} + 1.125 \text{ ns} + 67.8 \text{ ns} = 95.42 \text{ ns} \\
f_H &= \frac{1}{2\pi\tau_H} = 1.67 \text{ MHz}
\end{aligned}$$

$$\begin{aligned}
\mathbf{9.85} \quad R_O &= r_O \parallel \frac{1}{g_m} = 20 \text{ K} \parallel \frac{1}{5 \text{ m}} \\
&= 198 \text{ }\Omega \\
R'_L &= R_L \parallel r_o = 2 \text{ K} \parallel 20 \text{ K} = 1.82 \text{ k}\Omega \\
A_M &= \frac{g_m R'_L}{1 + g_m R'_L} = \frac{5 \times 1.82}{1 + 5 \times 1.82} = 0.9 \frac{\text{V}}{\text{V}} \\
f_Z &= \frac{g_m}{2\pi \cdot C_{gs}} = \frac{1}{2\pi} \times \frac{5 \text{ m}}{2 \text{ p}} = 398 \text{ MHz} \\
R_{gd} &= R_{sig} = 20 \text{ k}\Omega \\
R_{gs} &= \frac{R_{sig} + R'_L}{1 + g_m R'_L} = \frac{20 \text{ k}\Omega + 1.82 \text{ k}\Omega}{1 + 5 \times 1.82} = 2.16 \text{ k}\Omega \\
R_{CL} &= R_L \parallel R_O = 2 \text{ k}\Omega \parallel 198 \text{ k}\Omega = 180 \text{ }\Omega \\
\tau_{gd} &= R_{gd} \times C_{gd} = 20 \text{ k}\Omega \times 0.1 \text{ pF} = 2 \text{ ns} \\
\tau_{gs} &= R_{gs} \times C_{gs} = 2.16 \text{ k}\Omega \times 2 \text{ pF} = 4.32 \text{ ns} \\
\tau_{CL} &= R_{CL} \times C_L = 180 \times 1 \text{ p} = 0.18 \text{ ns} \\
\tau_H &= \tau_{gd} + \tau_{gs} + \tau_{CL} = 6.5 \text{ ns} \\
\Rightarrow f_H &= \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 6.5 \text{ ns}} = 24.5 \text{ MHz}
\end{aligned}$$