
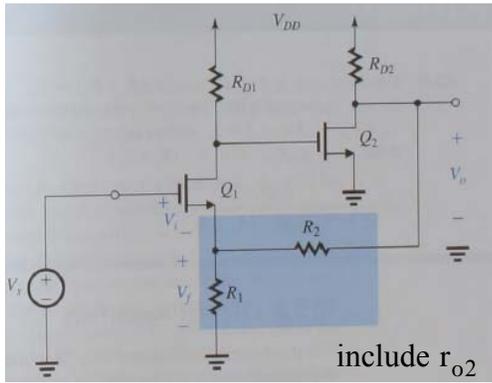


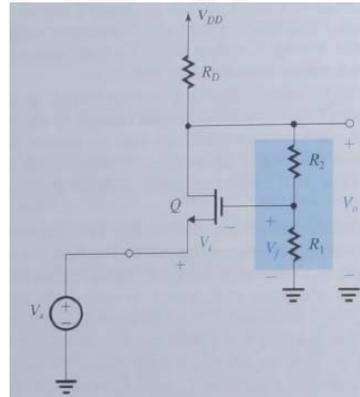For the following circuits, find the loop gain,  $L$ , asymptotic gain,  $A_{\infty}$ , and feedthrough term,  $d$ . For any transistors,  $Q_i$ , assume a transconductance of  $g_{mi}$ . Ignore  $r_{oi}$  unless the figure states "include  $r_{oi}$ ".




$$A_{cl} = \frac{V_o}{V_s}$$

(a)




$$A_{cl} = \frac{V_o}{V_s}$$

(b)

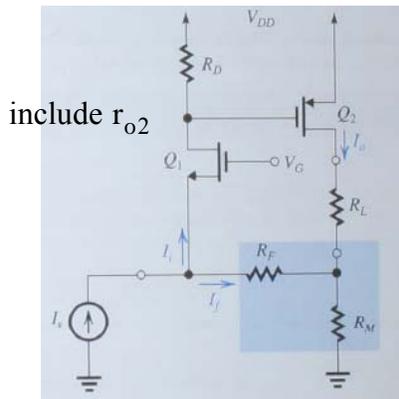


$$A_{cl} = \frac{I_o}{I_s}$$

(c)

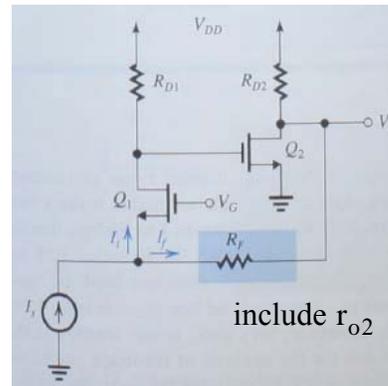


$$A_{cl} = \frac{V_o}{I_s}$$

(d)

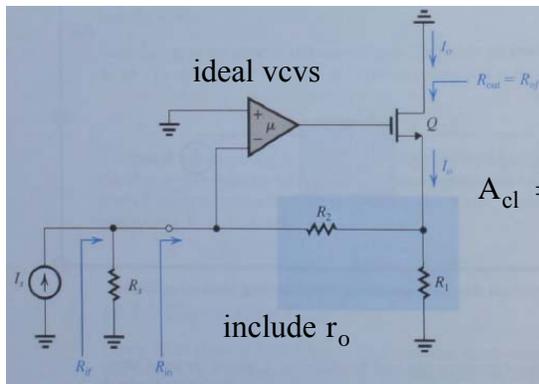

$$A_{cl} = \frac{I_o}{I_s}$$

(e)

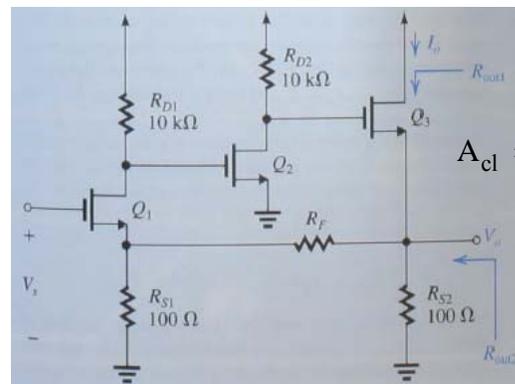

$$A_{cl} = \frac{V_o}{V_s}$$

(f) include  $r_{o2}, r_{o3}$   
ignore resistor values given