

Q1. For the circuit of Fig. P1, each transistor has $|V_{ov}| = 0.2V$ and $|V_A| = 10V$ (including the current sources where each are built with a single transistor).

- a) Find V_o/V_s assuming $d \approx 0$.
- b) Find R_{out} .

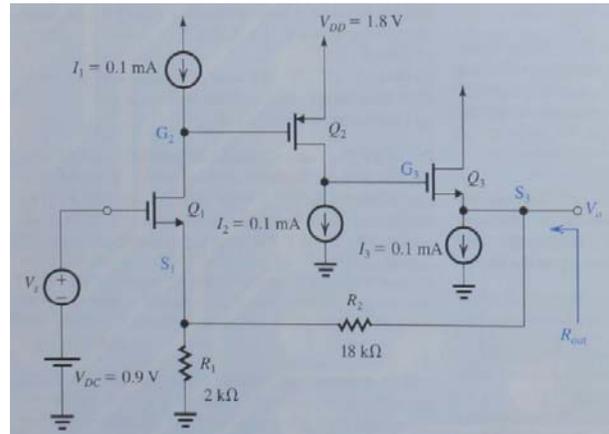


Fig P1

Q2. For the circuit of Fig. P2, assume $v_o = 0$ for $v_s = 0$, $|V_t| = 0.7V$, $|V_A'| = 24V/\mu m$

$$\mu_n C_{ox} = 2\mu_p C_{ox} = 120\mu A/V^2.$$

Assume bias currents are ideal.

- a) Find V_o/V_s .
- b) Find R_{out} .

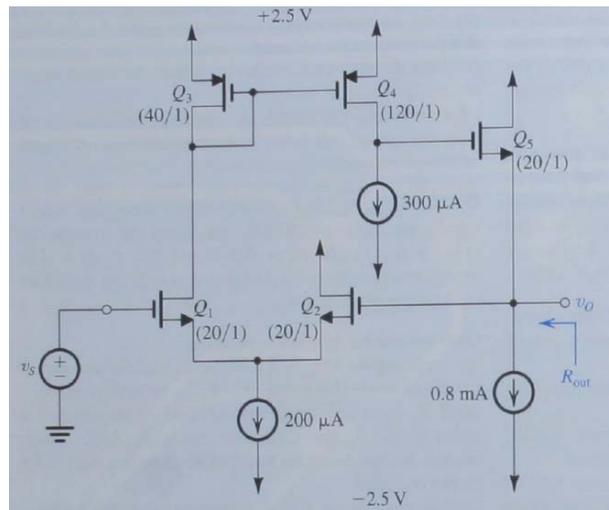


Fig P2

Q3. For the circuit of Fig. P3, $R_s = 9k$,

$R_L = 1k$, $R_1 = 10k$ and $R_2 = 90k$.

A1 has $82k\Omega$ diff R_{in} , $20V/V$ open circuit diff voltage gain and $3.2k\Omega$ R_{out} .

A2 has $5k\Omega$ R_{in} , $20mA/V$ short circuit transconductance and $20k\Omega$ R_{out} .

A3 has $20k\Omega$ R_{in} , $1V/V$ open circuit voltage gain and $1k\Omega$ R_{out} .

- a) Find V_o/V_s assuming $d \approx 0$.
- b) Find R_{in} and R_{out} .

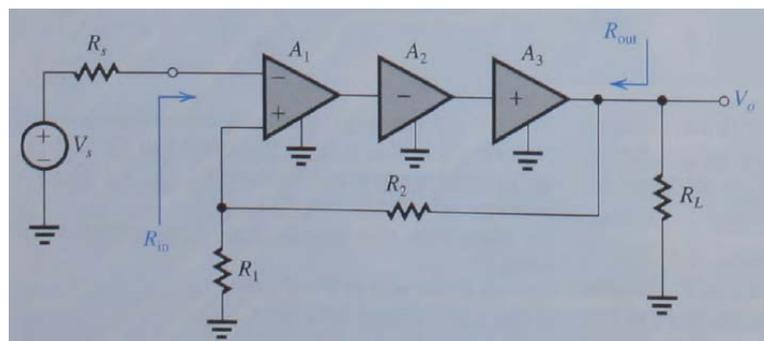


Fig P3