


DIGITAL MOSFET

2 CIRCUIT FAMILIES

- 1) STATIC CMOS
- 2) RATIOED CIRCUITS
- 3) CASCODE VOLTAGE SWITCH LOGIC (CVSL)
- 4) DYNAMIC CIRCUITS
- 5) PASS TRANSISTOR CIRCUITS

STATIC CMOS

BUBBLE PUSHING (DEMORGAN'S LAW)




 


EX COMPUTE  $F = AB + C$

USING NANDS & NORS


START ANDS & ORS

INSERT DOUBLE INVERSIONS

    

PUSH BUBBLES


INPUT ORDERING DELAY

 

DELAY FROM  
"A" TO "Y" LESS  
THAN "B" TO "Y"

A INPUT CAP = 4


ASYMMETRIC GATES

 


Y = A     RESET = 0  
Y = D     RESET = 1

ASSUMING "A" TO "Y" DELAY CRITICAL

⊥ RESET TO "Y" NOT CRITICAL AT ALL

 


 A INPUT CAP =  $\frac{4}{3} + 2$   
=  $3\frac{1}{3}$



(C-4)

## SYMMETRIC NAND

 


SAME DELAY  
FOR "A" AND  
"B" INPUTS

## - RATIOED CIRCUITS (PREVIOUSLY DISCUSSED)

- STATIC CURRENT DRAW
- MAKE PULL-UP "SMALL" SO SMALL CURRENT DRAW WHEN OUTPUT LOW

# CVSL (CASCODE VOLTAGE SWITCH LOGIC)

 


GENERATES BOTH  $Y + \bar{Y}$

- NO STATIC POWER

(RATIOED LOGIC)

## NAND

 

- INTERESTING APPROACH BUT PROCESS SENSITIVE MAKES SLOWER THAN CMOS

→ SLOW NMOS, FAST PMOS ⇒ MAKE PMOS SMALL SO NMOS CAN OVERCOME IT.

SLOW PMOS ⇒ SLOW PULL-UP


GENERALLY SLOWER THAN CMOS.  
+ MORE POWER HUNGRY.

# DYNAMIC CIRCUITS


C-6

- REQUIRES CLOCK  $\phi$  TO OPERATE
- HAS PRECHARGE PHASE AND EVALUATION PHASE
- OUTPUT ONLY VALID DURING EVAL PHASE
- OUTPUT PRECHARGED TO  $V_{DD}$  DURING PRECHARGE PHASE
- FAST, NO STATIC POWER, HIGH DYNAMIC POWER

## INVERTER

 


UNFOOTED

 

FOOTED

- FOOTED ALLOWS INPUT "A" TO BE "1" DURING PRECHARGE PHASE
- UNFOOTED REQUIRES "A" TO BE "0" DURING PRECHARGE PHASE

C-7

 

### STRICT REQUIREMENT ON INPUTS

- INPUTS MUST BE MONOTONIC RISING  
ONE OF ...


- LOW AND STAY LOW
  - LOW AND RISE HIGH
  - HIGH AND STAY HIGH
- ← (ALLOWED IF FOOTED)  
← (NOT IF UNFOOTED)

BUT NOT HIGH AND GO LOW


SINCE INPUT IS PRECHARGED HIGH AND CANNOT GO HIGH AGAIN IF DISCHARGED

- FOOTED ALLOWS CMOS GATES TO DRIVE DYNAMIC GATES

NAND 2

 


UNFOOTED

 


FOOTED

NOR 2

 

UNFOOTED

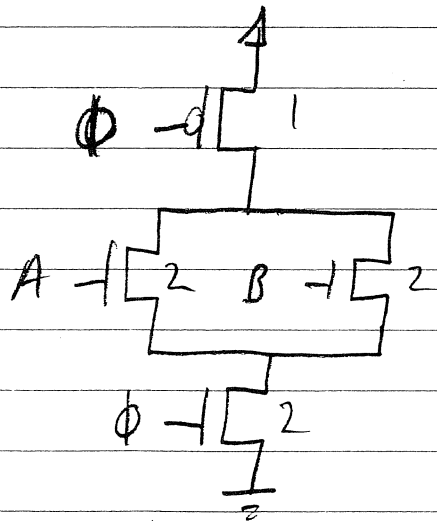

FOOTED





(C-9)

- CANNOT CONNECT Y DIRECTLY TO ANOTHER GATE AS IT VIOLATES ABOVE CONDITION.

- INSERT CMOS INVERTER BETWEEN GATES


⇒ DOMINO LOGIC (USES DYNAMIC GATES)

 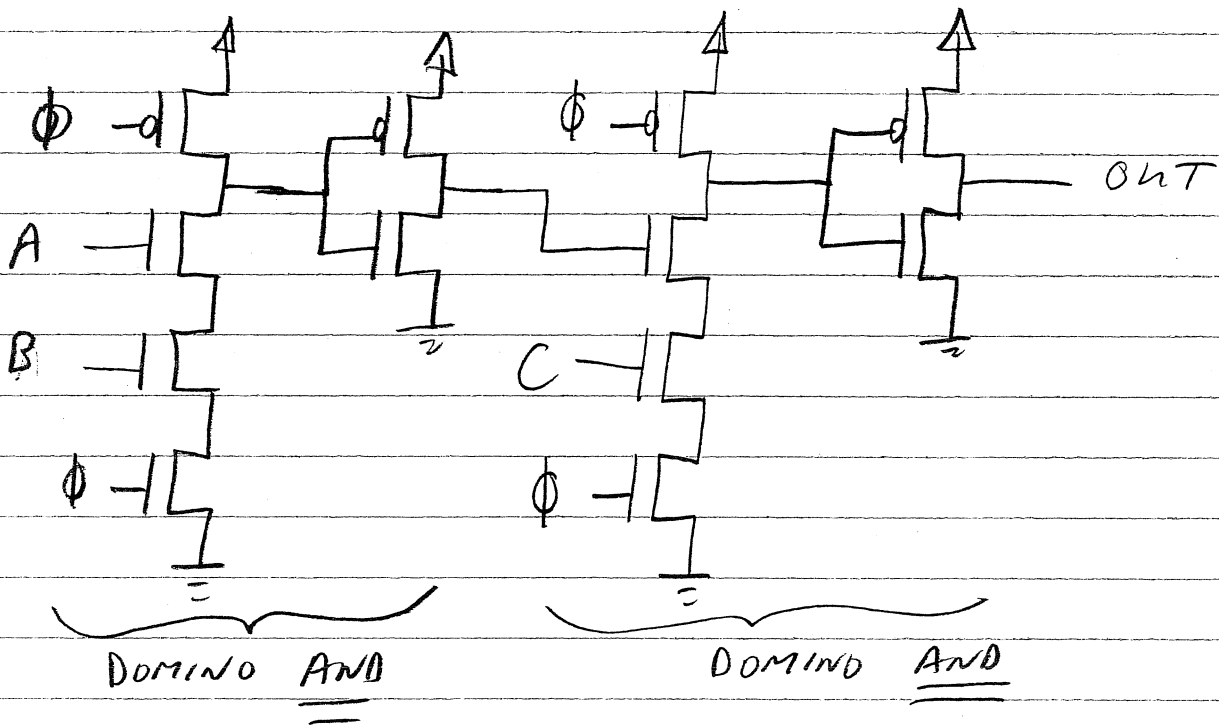

C-9A
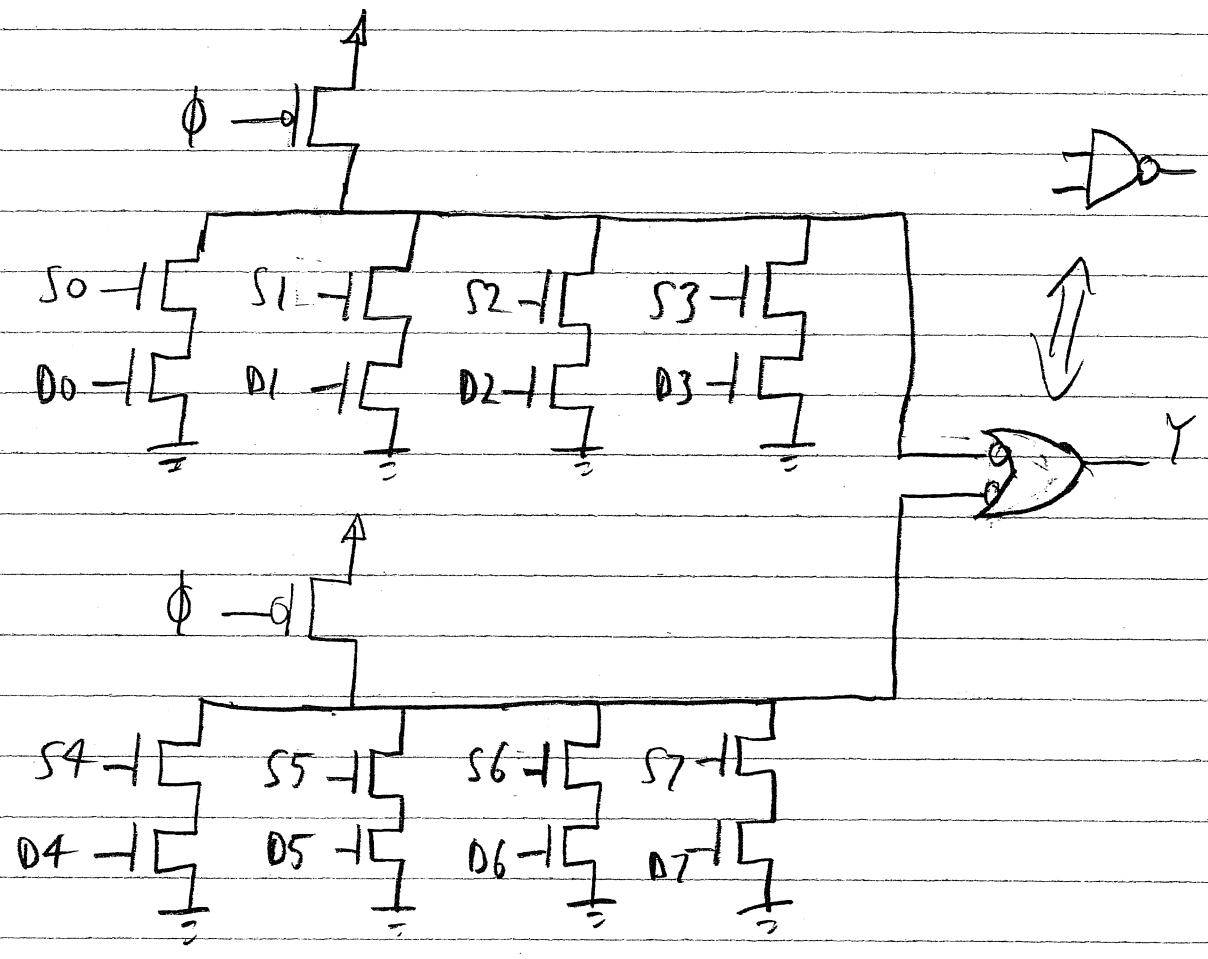
# CAN BUILD MORE COMPLEX GATES

8 - INPUT MULTIPLEXER USING 2  
4 - INPUT MUXES



ONE OF  $S_0 \rightarrow S_7$  HIGH

(C-10)

DOMINO GATES INHERENTLY NON-INVERTING


- IF LAST GATE, CAN USE CMOS INVERTER

- IF WITHIN DOMINO GATES, USE DUAL-RAIL  
DOMINO LOGIC

ALL INPUT/OUTPUT SIGNALS ENCODED AS A  
PAIR OF SIGNALS

<u>SIG_H</u>	<u>SIG_L</u>	<u>MEANING</u>
0	0	PRECHARGE
0	1	"0"
1	0	"1"
1	1	INVALID

SIMILAR TO CVSL

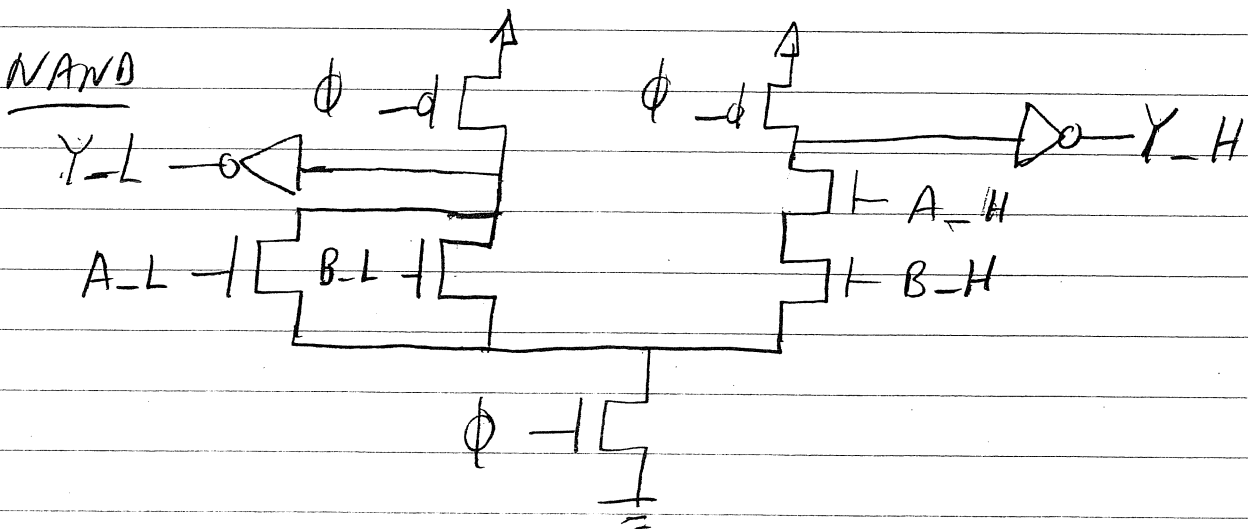


- CLOCK  $\phi$  NEEDS TO ALWAYS RUN FOR LOGIC TO OPERATE

- DYNAMIC POWER HIGH DUE TO DUAL-RAIL AND ACTIVITY FACTOR HIGH DUE TO PRECHARGE PHASE

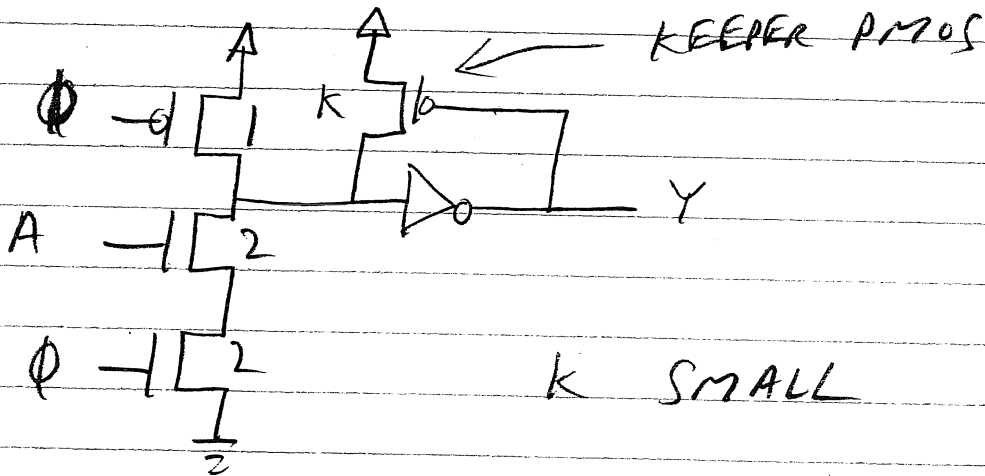
### KEEPERS

- IF  $\phi$  STOPPED, CHARGE LEAKAGE ON DYNAMIC NODE CAN CHANGE LOGIC VALUE ON EVAL PHASE

- USE SMALL  $\frac{W}{L}$  PMOS TRANSISTOR TO OVERCOME LEAKAGE



CHARGE - SHARING ERRORS

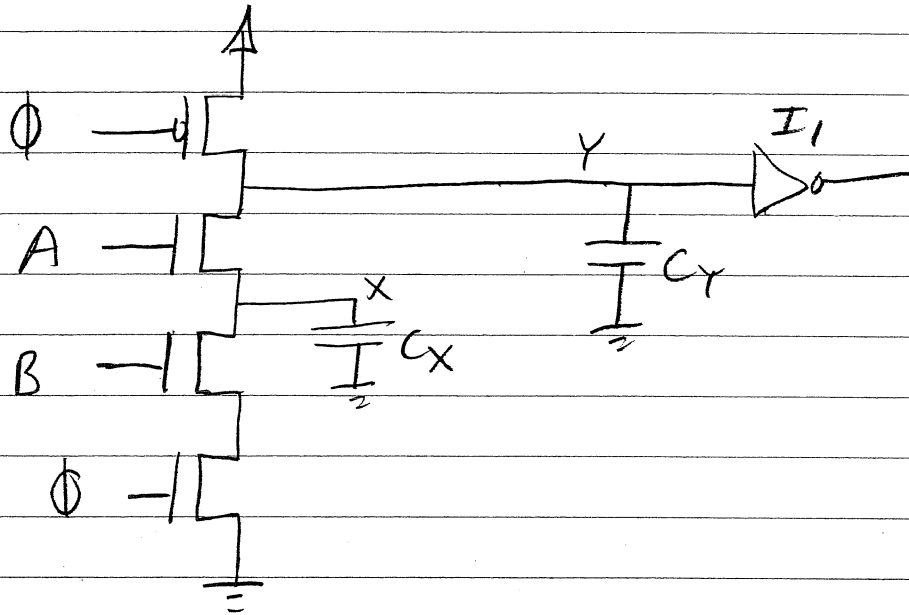

IF NODE X NOT PRECHARGED BUT

$V_x \approx 0$  + NODE  $V_y$  PRECHARGED TO  $V_{DD}$

CHARGE SHARING OCCURS IF  $B = 0$   
 $A = 1$

$$V_x = V_y = \frac{C_y}{C_y + C_x} V_{DD}$$

MIGHT DROP  $V_y$  BELOW  $V_{TH}$  OF  $I_1$   
AND ERROR OCCURS

- MIGHT PRECHARGE ALL OR SOME  
INTERNAL NODES TO REDUCE THIS EFFECT.