
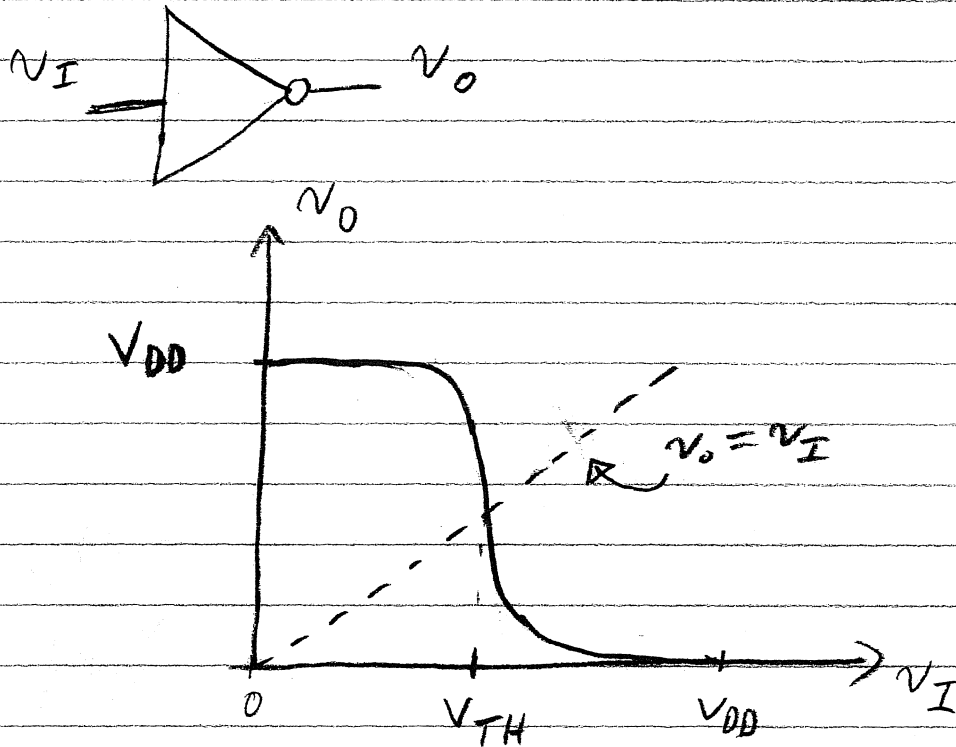


INVERTER DC TRANSFER CHARACTERISTICS

BY DEFINITION, THE THRESHOLD OF THE
INVERTER IS WHERE $V_O = V_I$


V_{TH} IS INVERTER THRESHOLD
 (OR INPUT THRESHOLD)

CMOS INVERTER

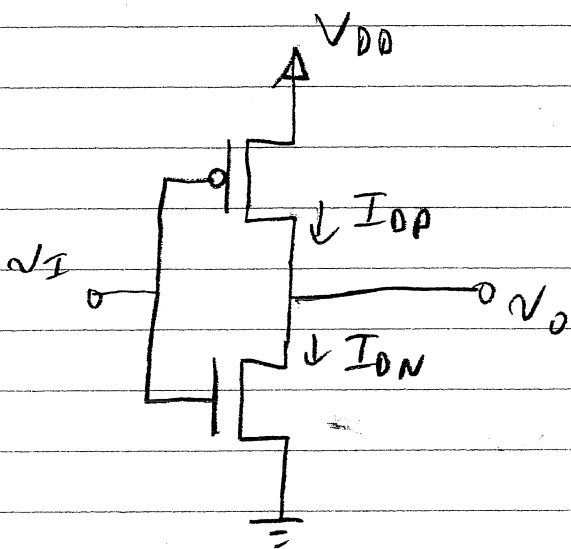

PMOS: $\mu_p, V_{tp}, \left(\frac{W}{L}\right)_p$

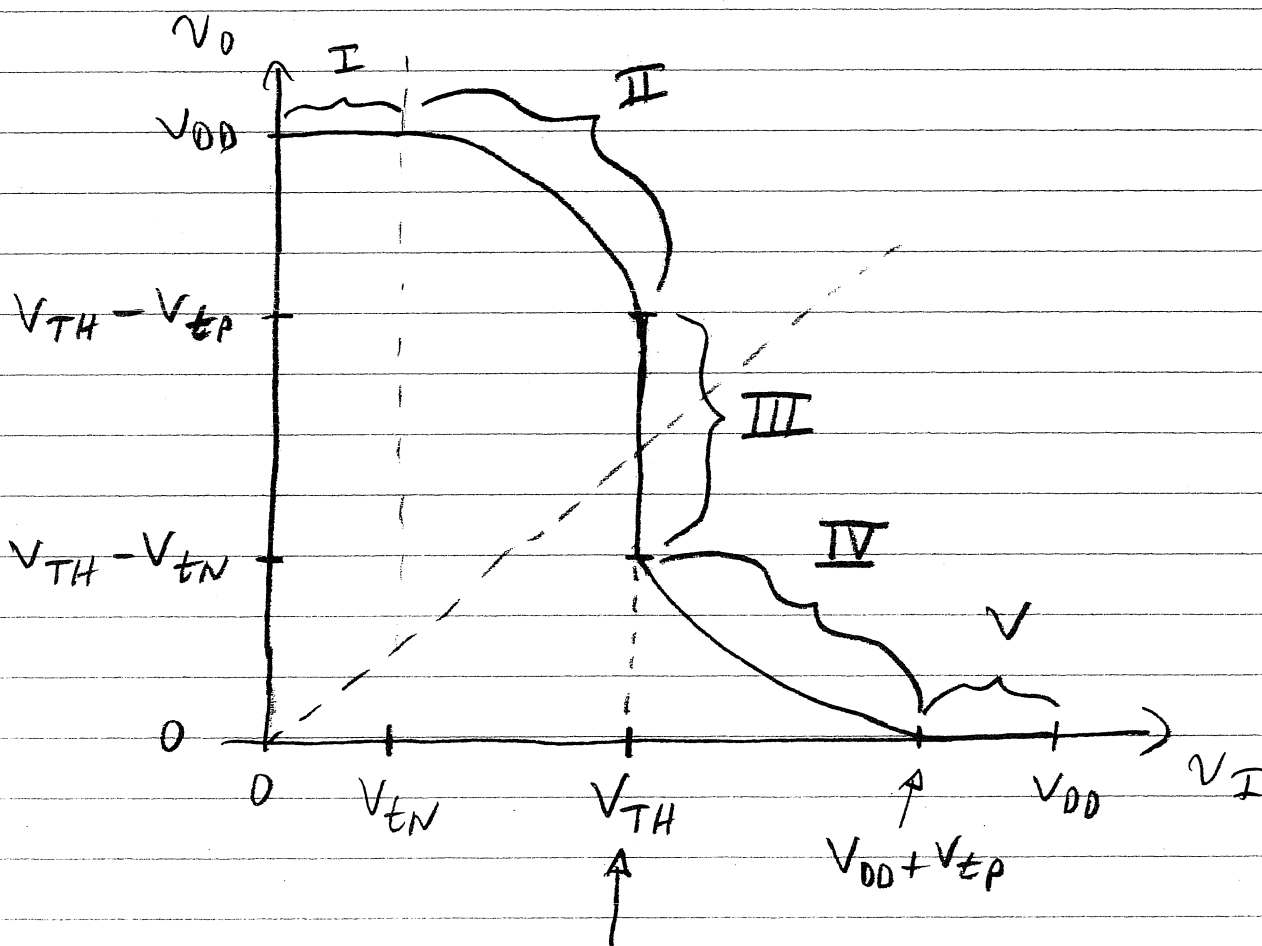NMOS: $\mu_n, V_{tn}, \left(\frac{W}{L}\right)_n$



INVERTER THRESHOLD

<u>REGION</u>	<u>NMOS</u>	<u>PMOS</u>
I	CUTOFF	TRIODE
II	ACTIVE	TRIODE
III	ACTIVE	ACTIVE
IV	TRIODE	ACTIVE
V	TRIODE	CUTOFF

IN ALL REGIONS $I_{DN} = I_{DP}$ SINCE
 WE ARE LOOKING AT DC CURVE
 SO NO CURRENT FLOWS OUT OF V_0

V_{TH} OCCURS WHEN BOTH NMOS & PMOS
ACTIVE (SINCE $V_{DS} = V_{GS}$ FOR
BOTH NMOS & PMOS)

$$I_{DN} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_N (V_{TH} - V_{tN})^2 \quad (1)$$

$$I_{DP} = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_P (V_{TH} - V_{DD} - V_{tP})^2 \quad (2)$$

(1) = (2) AND SOLVE FOR V_{TH}

$$V_{TH} = \frac{V_{DD} + V_{tP} + V_{tN} r}{1 + r}$$

WHERE $r = \sqrt{\frac{\mu_n \left(\frac{W}{L}\right)_N}{\mu_p \left(\frac{W}{L}\right)_P}}$

EXAMPLE $V_{tN} = 0.7 \text{ V}$ $V_{tP} = -0.8 \text{ V}$

$$\mu_n C_{ox} = 190 \mu\text{A}/\text{V}^2 \quad \mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$$

$$\left(\frac{W}{L}\right)_N = 2$$

$$\left(\frac{W}{L}\right)_P = 4$$

$$V_{DD} = 3.3 \text{ V}$$

$$\Gamma = \sqrt{\frac{(190)(2)}{(50)(4)}} = 1.38$$

$$V_{TH} = \frac{3.3 - 0.8 + 0.7(1.38)}{1 + 1.38}$$

$$= 1.46 \text{ V}$$


NOTE THAT $V_{DD}/2 = 1.65 \text{ V}$

SO $V_{TH} < \frac{V_{DD}}{2}$

TO HAVE $V_{TH} = \frac{V_{DD}}{2}$ WHEN $V_{tN} = -V_{tP}$

LET $\Gamma = 1 \Rightarrow \mu_n \left(\frac{W}{L}\right)_N = \mu_p \left(\frac{W}{L}\right)_P$

HOWEVER THIS CHOICE OF V_{TH} IS NOT
USUALLY BEST CHOICE FOR SPEED
(DISCUSSED LATER)

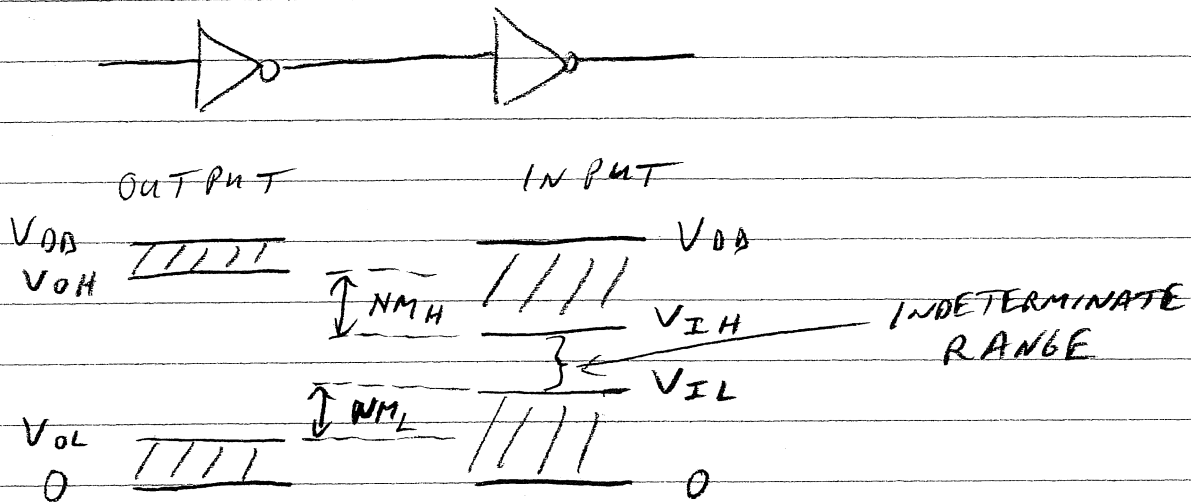NOISE MARGIN

$$NM_H = V_{OH} - V_{IH}$$


$$NM_L = V_{IL} - V_{OL}$$

$V_{IH} \Rightarrow$ MIN HIGH INPUT VOLTAGE

$V_{IL} \Rightarrow$ MAX LOW INPUT VOLTAGE

$V_{OH} \Rightarrow$ MIN HIGH OUTPUT VOLTAGE



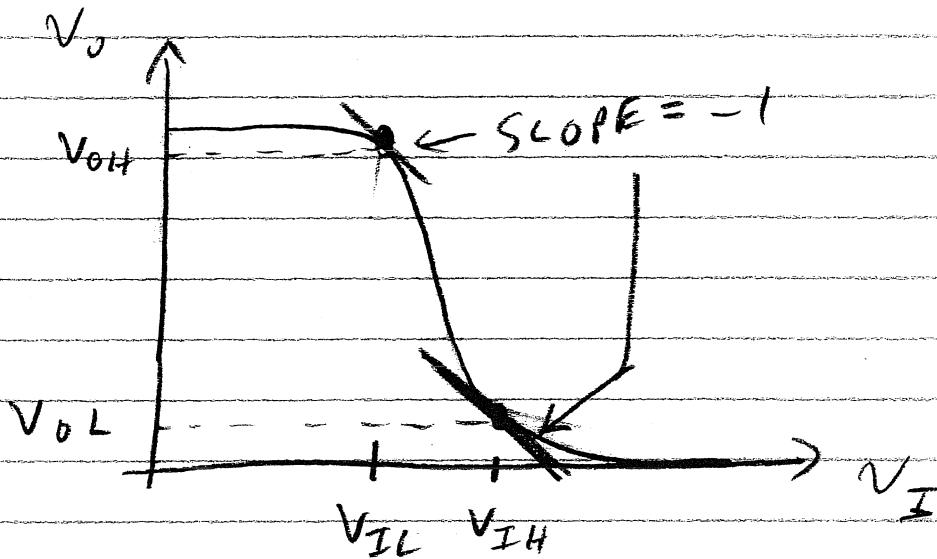
$V_{OL} \Rightarrow$ MAX LOW OUTPUT VOLTAGE



- CONSERVATIVE ESTIMATE OF NOISE MARGINS

- NOT USED IN INDUSTRY MUCH

RATIOED INVERTER LOGIC

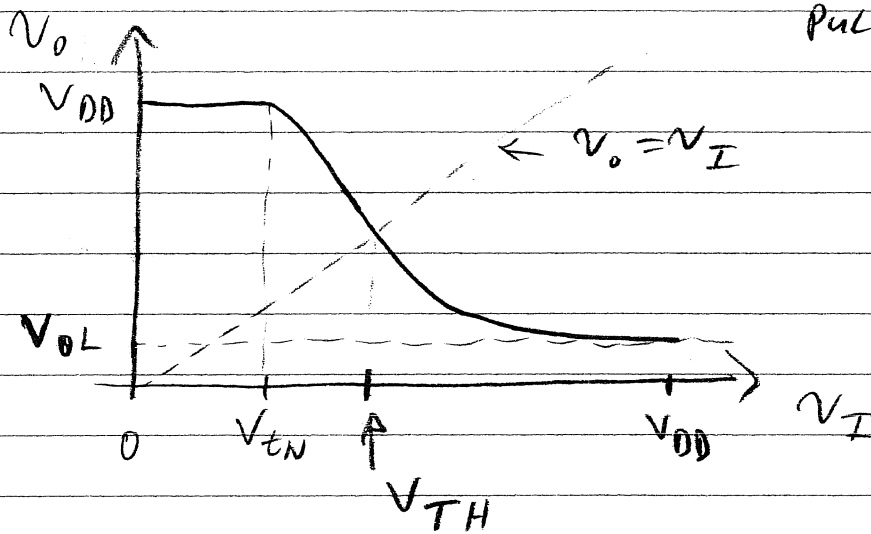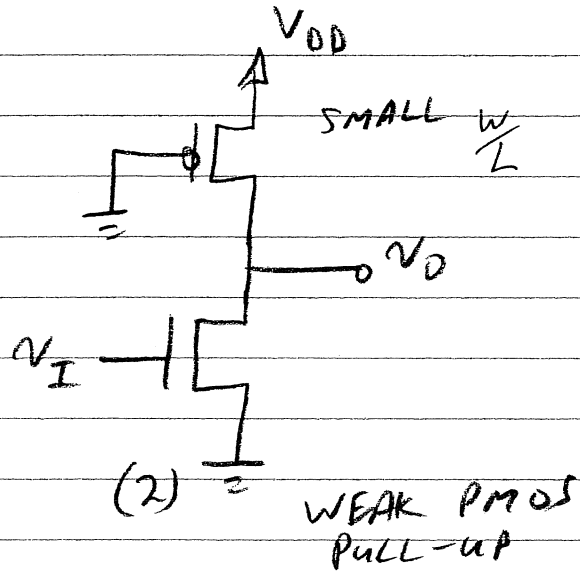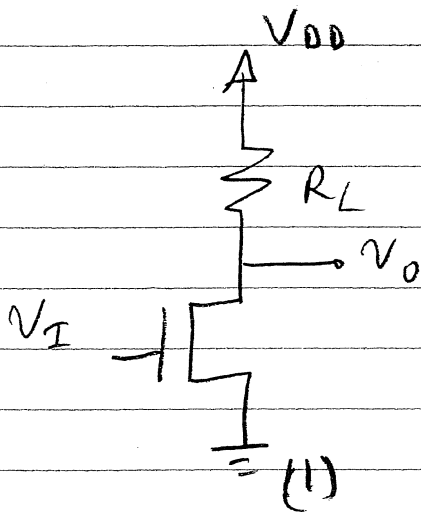

EXAMPLE FIND V_{OL} & V_{TH} FOR CIRCUIT (1)

WHEN $R = 10\text{K}\Omega$, $\mu_n C_{ox} = 200\text{mA/V}^2$

$$\left(\frac{W}{L}\right)_N = 10$$

$$V_{TN} = 0.5\text{V}, \quad V_{DD} = 3\text{V}$$

FOR V_{OL} , NMOS IN TRIODE

$$I_D = \mu_N C_{ox} \left(\frac{W}{L}\right)_N \left[(V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$I_D = \mu_N C_{ox} \left(\frac{W}{L}\right)_N \left[(V_{DD} - V_{TN}) V_{OL} - \frac{V_{OL}^2}{2} \right]$$

$$I_D = (2e-3) \left[(2.5) V_{OL} - \frac{V_{OL}^2}{2} \right] \quad (1)$$

ALSO

$$I_D = \frac{V_{DD} - V_{OL}}{R} = \frac{3 - V_{OL}}{1e4} \quad (2)$$

$$(1) = (2)$$

$$\frac{3 - V_{OL}}{1e4} = (2e-3) \left[2.5 V_{OL} - \frac{V_{OL}^2}{2} \right]$$

$$10 V_{OL}^2 - 51 V_{OL} + 3 = 0$$

$$V_{OL} = 5.04 \quad \text{OR} \quad \underline{\underline{0.06 V}}$$

↑
NOT POSSIBLE

V_{TH} NMOS IN ACTIVE SINCE $V_{DS} = V_{GS}$

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_N (V_{GS} - V_{tn})^2$$

$$I_D = (1e-3)(V_{TH} - 0.5)^2 \quad (1)$$

$$I_D = \frac{V_{DD} - V_{TH}}{R} = \frac{3 - V_{TH}}{1e4} \quad (2)$$

$$(1) = (2)$$

$$\frac{3 - V_{TH}}{1e4} = (1e-3)(V_{TH} - 0.5)^2$$

$$3 - V_{TH} = 10(V_{TH}^2 - V_{TH} + 0.25)$$

$$10V_{TH}^2 - 9V_{TH} - 0.5 = 0$$

$$V_{TH} = \underline{\underline{0.95}} \quad \text{OR} \quad \cancel{-0.05} \quad \text{NOT POSSIBLE}$$

STATIC POWER DISSIPATION WHEN $v_o = v_{OL}$

$$I_D = \frac{V_{DD} - v_{OL}}{R} = \frac{3 - 0.06}{1e4} = 29.4 \text{ mA}$$


$$P_{DISS} = I_D V_{DD} = (29.4e-3)(3) = \underline{\underline{88.2 \text{ mW}}}$$

STATIC

POWER DISSIPATION WHEN $V_o = V_{DD}$

$$I_D = \frac{V_{DD} - V_{DD}}{R} = 0$$

$$P_{Diss} = (0)(3) = \underline{\underline{0 \text{ W}}}$$

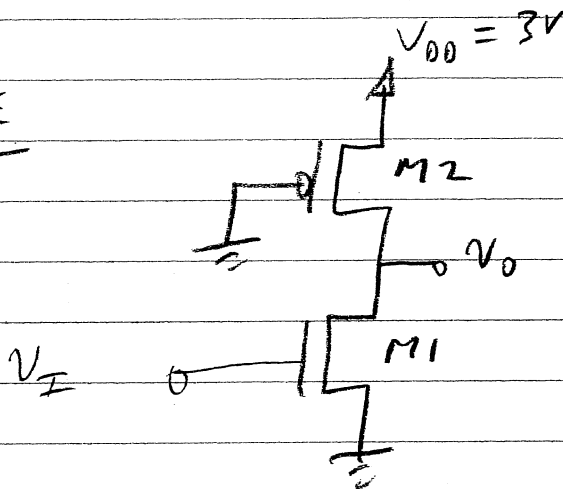EXAMPLE

$$\text{PMOS: } \mu_p C_{ox} = 50 \mu\text{A/V}^2$$

$$V_{tp} = -0.5\text{V}$$

$$\left(\frac{W}{L}\right)_p = ?$$

$$\text{NMOS: } \mu_n C_{ox} = 200 \mu\text{A/V}^2$$

$$\left(\frac{W}{L}\right)_n = 10$$

$$V_{tn} = 0.5\text{V}$$

FIND SIZE OF $\left(\frac{W}{L}\right)_p$ SUCH THAT $V_{OL} = 0.3\text{V}$ ALSO FIND V_{TH} FOR INVERTER.

$$\underline{V_{OL}} \quad \text{M1 IN TRIODE SINCE } V_I = V_{DD} = 3\text{V}$$

$$\text{AN } V_D = 0.3\text{V} \quad \Rightarrow V_{GS} = 3\text{V}$$

$$\Rightarrow V_{DS} = 0.3\text{V}$$

$$V_{DS} = 0.3\text{V} < V_{GS} - V_{tn} = 3 - 0.5 = 2.5\text{V}$$

$$I_{DN} = \mu_N C_{ox} \left(\frac{W}{L}\right)_N \left((V_{GS} - V_{thN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$= (200) (10) \left((3 - 0.5) V_{OL} - \frac{V_{OL}^2}{2} \right)$$

$$I_{DN} = 2000 \left(2.5 (0.3) - \frac{0.3^2}{2} \right)$$

$$I_{DN} = 1410 \mu A = 1.4 \text{ mA} \quad \textcircled{1}$$

M2 IS IN ACTIVE SINCE

$$V_{GS} = 0 - V_{DD} = -3V$$

$$V_{DS} = V_{OL} - V_{DD} = 0.3 - 3V = -2.7V$$

$$\therefore V_{DS} < V_{GS} - V_{thP} = -3V + 0.5 = -2.5V$$

$$I_{DP} = \frac{\mu_P C_{ox}}{2} \left(\frac{W}{L}\right)_P (V_{GS} - V_{thP})^2$$

$$= \frac{50}{2} \left(\frac{W}{L}\right)_P (-3 + 0.5)^2$$

$$= 156.25 \left(\frac{W}{L}\right)_P \quad \textcircled{2}$$

$$\textcircled{1} = \textcircled{2} \Rightarrow \left(\frac{W}{L}\right)_P = \frac{1410}{156.25} = 9.0$$

$$\left(\frac{W}{L}\right)_P = 9.0$$

V_{TH}

M1 ACTIVE SINCE $V_{DS} = V_{GS}$
 SINCE $V_D = V_I$ BY DEFINITION

$$I_{DN} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_N (V_{GS} - V_{thN})^2$$

$$I_{DN} = 1000 (V_{TH} - 0.5)^2 \quad (1)$$

M2 TRIODE IF $V_{TH} > 0.5 V$ (TRUE SINCE I_{DN} ON)

$$I_{DP} = \mu_p C_{ox} \left(\frac{W}{L}\right)_P \left((V_{GS} - V_{thP}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$



$$I_{DP} = (50)(9) \left[(-3 + 0.5)(V_{TH} - 3) - \frac{(V_{TH} - 3)^2}{2} \right] \quad (2)$$

(1) = (2) SOLVE FOR V_{TH}

$$V_{TH} = \underline{\underline{1.57}} \quad \text{OR} \quad \cancel{-0.57} \quad \text{NOT POSSIBLE}$$

RATIOED INVERTER LOGIC

WITH PULL-UP CURRENT SOURCE

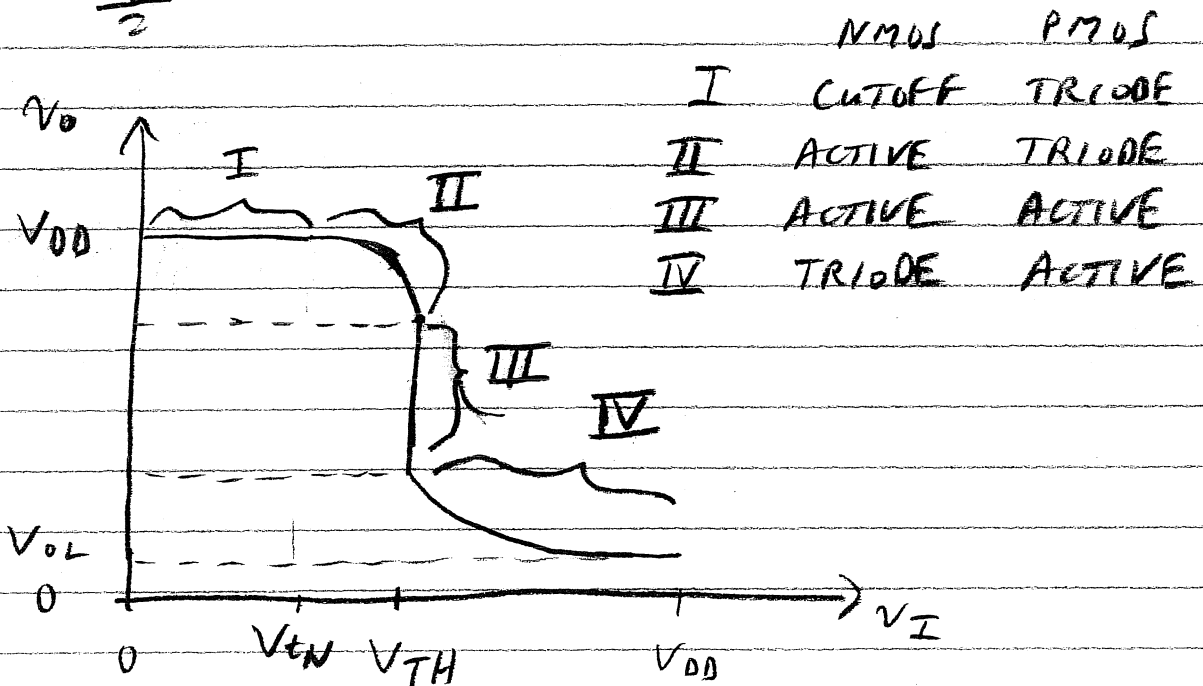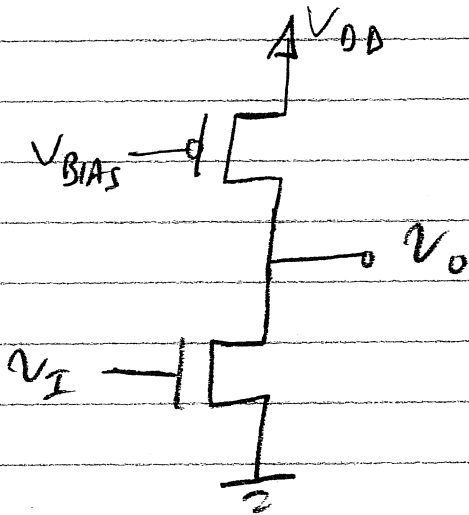

EXAMPLE PMOS $(\frac{W}{L})_P = 20$ $\mu_p C_{ox} = 50 \mu A/V^2$
 $V_{DD} = 3V$ $V_{tp} = -0.5V$ $V_{BIAS} = 1.5V$

NMOS $(\frac{W}{L})_N = ?$ $\mu_n C_{ox} = 200 \mu A/V^2$
 $V_{tn} = 0.5V$

2-(39)

FIND $\left(\frac{W}{L}\right)_N$ SUCH THAT $V_{TH} = 1.5V$ BOTH ACTIVE $(V_{TH} - V_{DD})$


$$I_{OP} = \left(\frac{50}{2}\right)(20) \left(-1.5 + 0.5\right)^2 = 500 \mu A \quad (1)$$

$$I_{ON} = \left(\frac{200}{2}\right) \left(\frac{W}{L}\right)_N \left(1.5 - 0.5\right)^2 = (2)$$


$$(1) = (2) \Rightarrow \left(\frac{W}{L}\right)_N = 5$$

PASS TRANSISTOR AT DC

RECALL

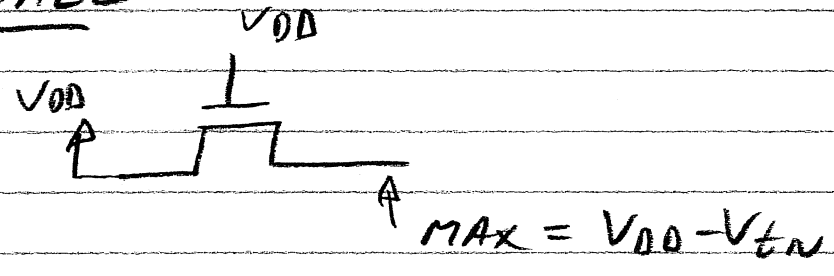


BAD DESIGN

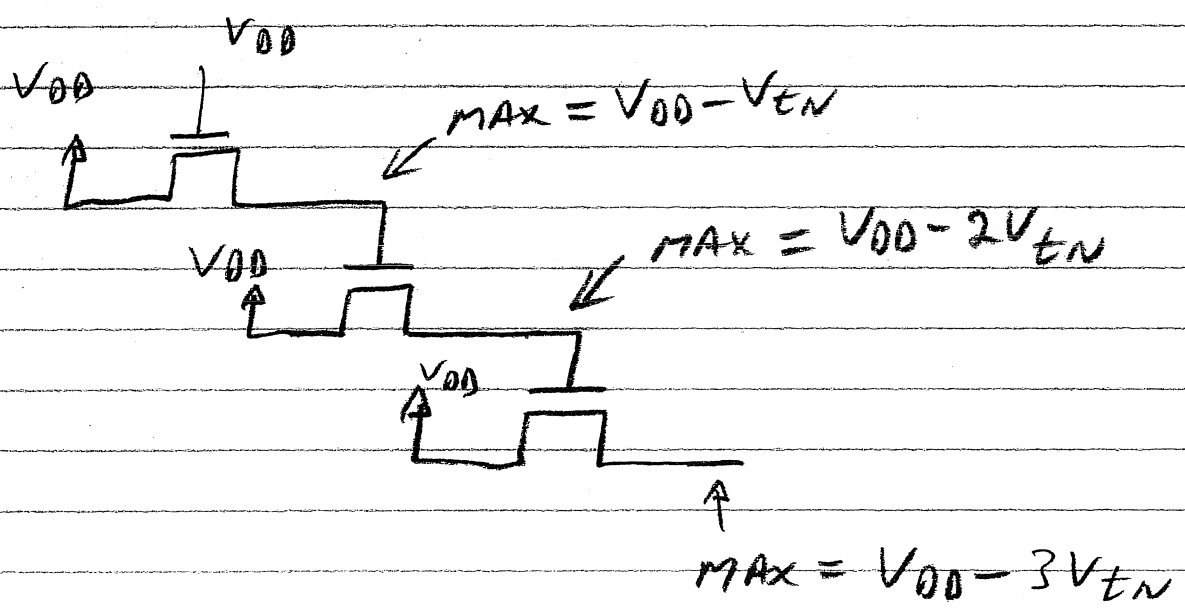

X

OKAY DESIGN (BUT SLOW)

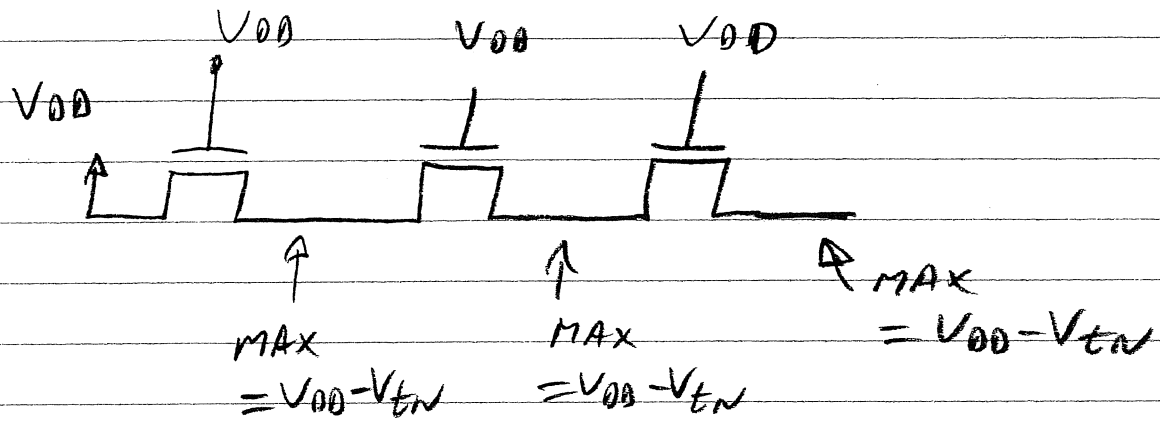

BUT SIGNAL AT LEFT END
HAS TO GO THROUGH MULTIPLE
TRANSISTORS AS THEY TURN OFF.