 


POWER DISSIPATION

PW-①


CAPACITORS DO NOT DISSIPATE ENERGY BUT...



$$\text{ENERGY, } E = \frac{1}{2} C V_x^2$$

$$\text{CHARGE, } Q = C V_x$$


CONSIDER

 

$$E_{\text{TOTAL}} = \frac{1}{2} C V_x^2$$

$$Q_{\text{TOTAL}} = C V_x$$

CLOSE SWITCH

 

USING CHARGE
CONSERVATION

$$Q_{\text{TOTAL}} = C \frac{V_x}{2} + C \frac{V_x}{2} \\ = C V_x \quad \checkmark$$

BUT NOW $E_{\text{TOTAL}} = \frac{1}{2} (2C) \left(\frac{V_x}{2}\right)^2 = \frac{1}{4} C V_x^2$

WHERE DID $\frac{1}{4} C V_x^2$ JOULES GO??


PW - (2)

ENERGY IS DISSIPATED ACROSS SWITCH RESISTANCE, R_S

IF R_S SMALL THEN CURRENT IS LARGE

BUT FOR SHORT TIME, IF R_S LARGE

CURRENT IS SMALL BUT FOR LONG TIME.

 

SWITCH CLOSED AT $t=0$

$$i_{R_S}(0) = \frac{V_x}{R_S}$$

$$\tau = R_S \frac{C}{2}$$

SAME ENERGY DISSIPATED INDEPENDENT OF R_S (R_S CAN EVEN BE NON-LINEAR) AS IN CASE OF A TRANSISTOR

POWER DISSIPATION FOR A DIGITAL CHIP CONSISTS OF BOTH

- DYNAMIC POWER \leftarrow OCCURS ON TRANSITIONS
- STATIC POWER \leftarrow OCCURS EVEN IF HELD HIGH OR LOW

DYNAMIC POWER DISSIPATION

CONSISTS OF BOTH

- CAPACITOR CHARGE/DISCHARGE POWER
- DIRECT PATH POWER


TYPICALLY CAPACITIVE POWER $\approx 80\%$
 DIRECT PATH $\approx 20\%$

OF DYNAMIC POWER DISSIPATION


BUT SLOW CLOCK/DATA EDGES CAN

INCREASE DIRECT-PATH POWER DISSIPATION.

DYNAMIC CAPACITIVE POWER

 

LOW TO HIGH

 

ENERGY DELIVERED FROM V_{DD} , E_{DD}

$$E_{DD} = \int_0^{\infty} V_{DD} i_{DD} dt = V_{DD} \int_0^{\infty} i_{DD} dt \quad (1)$$

RECALL $q = CV$ AND $i = \frac{dq}{dt}$

$$\Rightarrow q = \int i dt + \text{CONSTANT}$$

PLW - (5)

SO ① $\Rightarrow E_{DD} = V_{DD} q$

$$= V_{DD} C_L V_{DD} = C_L V_{DD}^2$$

SO ENERGY DELIVERED BY V_{DD} EQUALS $C_L V_{DD}^2$

BUT ENERGY STORED ON C_L , E_{CL}


$$E_{CL} = \frac{1}{2} C_L V_{DD}^2$$

SO ENERGY DISSIPATED IN RESISTOR R_S

$$E_{DISS} = E_{DD} - E_{CL} = \underline{\underline{\frac{1}{2} C_L V_{DD}^2}}$$

INDEPENDENT OF R_S VALUE OR WHETHER IT IS LINEAR OR NOT.

HIGH TO LOW

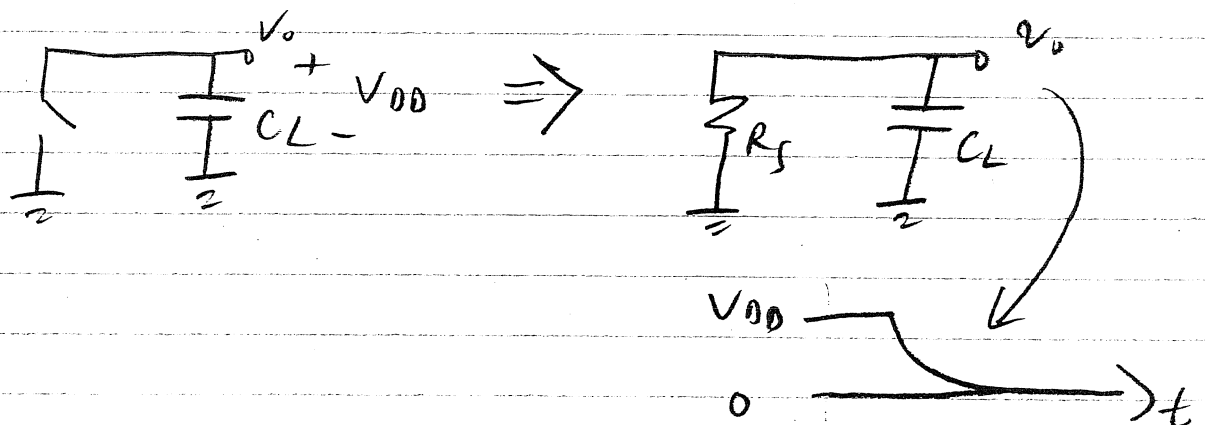

PW - (6)

ENERGY BEFORE IN CAP

$$E_{CL} = \frac{1}{2} C_L V_{DD}^2$$

AFTER $E_{CL} = 0$

$$\Rightarrow E_{DISS} = \frac{1}{2} C_L V_{DD}^2$$

THEREFORE OVER 1 COMPLETE CYCLE

$$E_{DISS} = C_L V_{DD}^2$$

IF f CYCLES PERFORMED EACH

SECOND

$$P_{DISS} = f C_L V_{DD}^2$$

FOR A CLOCK
SIGNAL OF
FREQ f


HOWEVER FOR A DATA SIGNAL

$$P_{DISS} = P_{1 \rightarrow 0} f C_L V_{DD}^2$$

WHERE $P_{1 \rightarrow 0}$ IS PROBABILITY OF A 1 \rightarrow 0
TRANSITION

EXAMPLE 1


$V_{DD} = 3.3V$

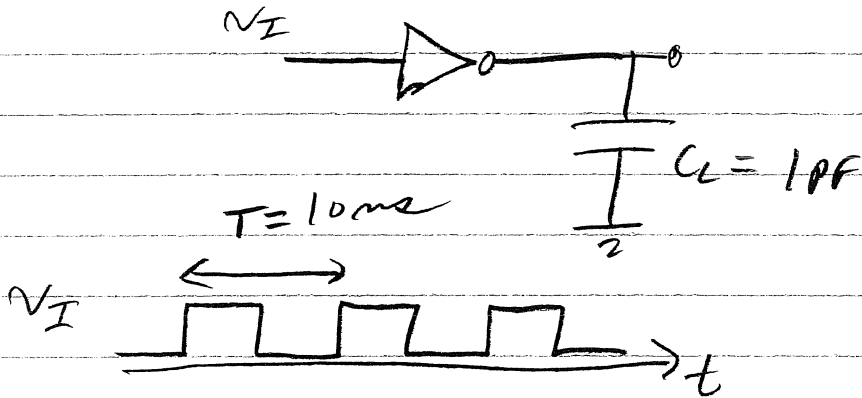

$f = \frac{1}{T} = 100 MHz$

$P_{Diss} = (100 \times 10^6)(1 \times 10^{-12})(3.3^2) = 1.1 mW$

EXAMPLE 2

 


$P_{1 \rightarrow 0}$ AT EACH TRANSITION

$$P_{1 \rightarrow 0} = 0.5$$

$$\begin{aligned} P_{\text{DISS}} &= P_{1 \rightarrow 0} f C_L V_{DD}^2 \\ &= (0.5) (100e6) (1e-12) (3.3)^2 \\ &= 0.54 \text{ mW} \end{aligned}$$

EXAMPLE 3


RANDOM WITH $P(1) = 0.5$

 

$$P_{1 \rightarrow 0} = P(1) P(0) = (0.5)(0.5) = \frac{1}{4}$$

$$\begin{aligned} P_{\text{DISS}} &= P_{1 \rightarrow 0} f C_L V_{DD}^2 = \left(\frac{1}{4}\right) (100e6) (1e-12) (3.3)^2 \\ &= 0.27 \text{ mW} \end{aligned}$$

EXAMPLE 4

 

A, B EACH RANDOM DATA CLOCKED AT 100 MHz. EACH $P(1) = 0.5$

A	B	V_o
0	0	1
0	1	1
1	0	1
1	1	0

FOR V_o

$$P(1) = \frac{3}{4}$$

$$P(0) = 1 - P(1) = \frac{1}{4}$$


$$P_{1 \rightarrow 0} = P(1) P(0) = \left(\frac{3}{4}\right) \left(\frac{1}{4}\right) = \frac{3}{16}$$

$$P_{\text{DISS}} = P_{1 \rightarrow 0} f C_L V_{DD}^2 = \left(\frac{3}{16}\right) (100 \times 10^6) (1 \times 10^{-12}) (3.3)^2$$


$$= 0.20 \text{ mW}$$

WE ONLY ACCOUNT FOR 1-0 TRANSITIONS
 SINCE EVERY 1-0 TRANSITION IS FOLLOWED
 BY A 0-1 TRANSITION.

DYNAMIC DIRECT-PATH POWER

 

 I_{DP} IS CURRENT THAT FLOWS DIRECTLY FROM V_{DD} TO GND WHEN BOTH NMOS & PMOS ON AS V_I IS SWITCHING DOES NOT CHARGE/DISCHARGE C_L



ACTUALLY, I_{DP} NOT TRIANGULAR BUT IT IS A GOOD APPROXIMATION.

RECALL V_{TH} IS INVERTER THRESHOLD

$$I_{PEAK} = \frac{\mu_N C_{ox} (W/L)_N}{2} [V_{TH} - V_{EN}]^2$$

ENERGY DIRECT PATH, E_{DP}

$$E_{DP} = V_{DD} (Q_r + Q_f)$$

Q_r / Q_f ARE CHARGE DELIVERED FOR RISING / FALLING EDGES

$$Q_r = I_{AVERAGE} \times \Delta t = \frac{I_{PEAK}}{2} t_r$$

$$Q_f = \frac{I_{PEAK}}{2} t_f$$

So

$$E_{DP} = V_{DD} \frac{I_{PEAK}}{2} (t_r + t_f)$$

DIRECT PATH

POWER DISSIPATION, P_{DP}

$$P_{DP} = V_{DD} \frac{I_{PEAK}}{2} (t_r + t_f) (f) (P_{1 \rightarrow 0})$$

EXAMPLE

LET P_{DP} \Rightarrow DIRECT PATH POWER DISSIPATION

P_{DYN} \Rightarrow CAPACITIVE " "

$$\mu_n C_{ox} = 190 \mu A/V^2 \quad \mu_p C_{ox} = 50 \mu A/V^2$$

$$V_{thn} = 0.7V \quad V_{thp} = -0.8V \quad V_{DD} = 3.3V$$

$$\text{INVERTER WITH } \left(\frac{W}{L}\right)_N = \frac{0.7}{0.35} \quad \left(\frac{W}{L}\right)_P = \frac{1.4}{0.35}$$

ASSUME $t_r \approx t_{dr}$ & $t_f \approx t_{df}$

FIND RATIO OF $\frac{P_{DP}}{P_{DYN}}$

$$\frac{P_{DP}}{P_{DYN}} = \frac{(V_{DD}) \left(\frac{I_{PEAK}}{2}\right) (t_r + t_f) (f) (P_{1 \rightarrow 0})}{P_{1 \rightarrow 0} f C_L V_{DD}^2}$$

$$= \frac{\left(\frac{I_{PEAK}}{2}\right) (1.2 C_L) (R_{EQN} + R_{EQP})}{C_L V_{DD}}$$

TO FIND I_{PEAK} , FIRST FIND V_{TH}

$$V_{TH} = \frac{V_{DD} + V_{tp} + V_{tn} r}{1+r} \quad r = \sqrt{\frac{M_n \left(\frac{W}{L}\right)_n}{M_p \left(\frac{W}{L}\right)_p}} \quad \text{Plw - (13)}$$

$$= 1.46 \text{ V}$$

$$I_{PEAK} = \frac{M_n \mu_{ox} \left(\frac{W}{L}\right)_n}{2} (V_{TH} - V_{tn})^2$$

$$= \left(\frac{190 \text{ e-6}}{2}\right) (2) (1.46 - 0.7)^2 = 109.7 \mu\text{A}$$

$$R_{EAn} = \frac{2.5}{\mu_n \mu_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{tn})} = 2.53 \text{ k}$$

$$R_{EAp} = \frac{2.5}{\mu_p \mu_{ox} \left(\frac{W}{L}\right)_p (V_{DD} + V_{tp})} = 5 \text{ k}$$

$$\frac{P_{OP}}{P_{OYN}} = \frac{\left(\frac{109.7 \text{ e-6}}{2}\right) (1.2) (2.53 \text{ k} + 5 \text{ k})}{3.3}$$

$$= 0.15 \quad \text{OR} \quad \underline{\underline{15\%}}$$

STATIC POWER DISSIPATION

PW-(1A)

POWER DISSIPATION WHEN LOGIC IS
NOT SWITCHING.

IN CMOS, DUE TO

- 1) SUBTHRESHOLD CURRENT
- 2) GATE LEAKAGE
- 3) REVERSE BIAS JUNCTION LEAKAGE


SUBTHRESHOLD CURRENT GENERALLY DOMINATES
IN ADVANCED PROCESSES (130nm OR LESS)

GATE LEAKAGE IS NEXT WITH REVERSE BIAS
JUNCTIONS BEING LOWEST AMOUNT

IN OLDER TECHNOLOGIES, REVERSE BIAS
JUNCTIONS DOMINATE,

IN PSEUDO NMOS, STATIC POWER DISSIPATION
IS HIGH WHEN OUTPUT IS LOW BUT
NEAR ZERO WHEN OUTPUT IS HIGH


IN GENERAL

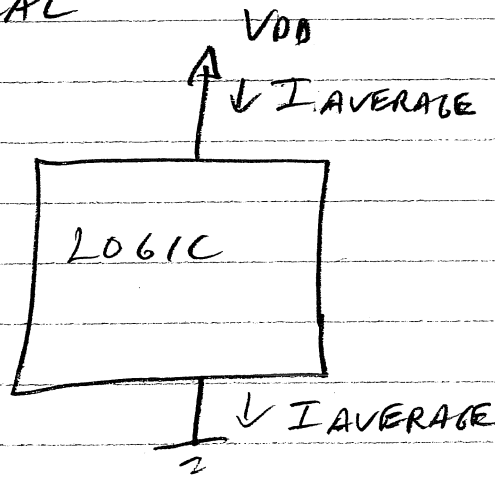

$$P_{DISS} = V_{DD} I_{AVERAGE}$$

(NOT I_{RMS})

WHY?

 

POWER DISSIPATED
IN LOAD

$$P_{DISS} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T v(t) i(t) dt$$

IF $v(t) = V_{DD}$ (A FIXED DC VALUE)

$$P_{DISS} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T V_{DD} i(t) dt$$

$$P_{DISS} = V_{DD} \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T i(t) dt$$

$$P_{DISS} = V_{DD} I_{AVERAGE}$$

$$\text{WHERE } I_{AVERAGE} \equiv \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T i(t) dt$$

ASIDE

RMS IS USEFUL WHEN LOAD IS
PURELY RESISTIVE \Rightarrow LOAD = R

$$V(t) = i(t) R$$

$$\begin{aligned} P_{DISS} &= \lim_{T \rightarrow \infty} \int_0^T R i^2(t) dt = R \lim_{T \rightarrow \infty} \int_0^T i^2(t) dt \\ &= I_{RMS}^2 R \quad \text{WHERE } I_{RMS}^2 \equiv \lim_{T \rightarrow \infty} \int_0^T i^2(t) dt \end{aligned}$$

SAME POWER AS A DC CURRENT OF I_{RMS}
APPLIED TO RESISTOR

CAN ALSO USE RMS WITH POWER
FACTORS FOR COMPLEX IMPEDANCE LOADS