

University of Toronto

Term Test 2

Date - Mar 17, 2010

Duration: 1.5 hrs

ECE334 — Digital Electronics

Lecturer - D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Equation sheet is on last page of test.
 2. Only tests written in pen will be considered for a re-mark.
 3. Calculator type unrestricted
 4. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.
-

Question	Mark
1	
2	
3	
4	
5	
Total	

Last Name: SOLUTIONS

First Name: _____

Student #: _____

(max grade = 29)

[5] **Question 1:** Answer the True [T] or False [F] questions below by **circling** the correct answer. Each correct answer is worth 0.5 marks.

T F When creating metal wires on a chip, first silicon dioxide is grown and photoresist is used to etch where wires should exist. Next, aluminum is sprayed on using silicon dioxide as a mask.

T F When creating metal wires on a chip, first aluminum is sprayed on the entire microchip, then photoresist and silicon oxide is used to mask where wires should exist and the rest is etched off.

T F In a self-aligned process, the drain/source junctions are first formed and then the gate is formed above the drain/source junctions so that it is self-aligned.

T F The silicon dioxide layer formed under the gate region is grown using wet oxidation instead of dry oxidation.

T F Tungsten is used in via and contact holes due to its low resistance.

T F P-type silicon is made by doping pure silicon with boron.


T F The dynamic power of a digital chip is due to the energy being dissipated across capacitors in the chip.

T F In CMOS circuits, to keep all the drain/source diodes reverse biased, the substrate (or bulk) of all NMOS transistors should be tied to V_{dd} while the substrate (or bulk) of all PMOS transistors should be tied to ground.

T F A pseudo-NMOS gate with power supplies 0 and V_{dd} has its output high level equal to V_{dd} while its output low level is a value greater than 0.

T F V_{TH} for an inverter is defined to be the input voltage where the inverter's gain is largest.

 [6] Question 2: Consider the following cross-section of a p-well process (not n-well)



- On the above diagram, label all the “???” signs with the material name (i.e. polysilicon, silicon dioxide, metal, p+, n+, p-, n-, etc.).
- What is the purpose of the p+ in the p-well and the n+ in the n- substrate?

THESE ARE SUBSTRATE CONTACTS TO BIAS THE P-WELL AND N-SUBSTRATE. IF METAL DIRECTLY CONNECTED TO LIGHTLY DOPED MATERIAL SCHOTTKY DIODE IS FORMED SO HEAVILY DOPED MATERIAL IS USED.

- What is the purpose of field-implants?

SO THAT THE SUBSTRATE DOES NOT INVERT DUE TO VOLTAGES ABOVE IT.


- Explain clearly why metal is not used as the gate material in a self-aligned process.

IT WOULD MELT DURING ANNEALING PROCESS STEP. POLYSILICON CAN WITHSTAND HIGHER TEMPERATURES.

[6] Question 3: Find the dynamic power dissipation, P_{dyn} , for the following CMOS circuit

assuming the clock is 1GHz, $V_{\text{DD}} = 2.5\text{V}$ and the inputs have the following probability values that change on the rising edge of the clock.
 
$$P(A=1) = 0.5, P(B=1) = 0.4, P(C=1) = 0.7$$



$$P_{\text{dyn}} = 23.4 \mu\text{W}$$

$$P_{\text{dyn}-1} = P_{1 \rightarrow 0} f C_1 V_{\text{DD}}^2$$

$$P_{X=1} = P_{A=0} P_{B=0} = (0.5)(0.6) = 0.3$$

$$P_{X=0} = 1 - P_{X=1} = 0.7$$

$$P_{X(1 \rightarrow 0)} = (0.3)(0.7) = 0.21$$

$$P_{\text{dyn}-1} = (0.21)(1e9)(5e-15)(2.5)^2 = 6.6 \mu\text{W}$$

$$P_{\text{dyn}-2} = P_{1 \rightarrow 0} f C_2 V_{\text{DD}}^2 = (0.3)(0.7)(1e9)(5e-15)(2.5^2)$$

$$= 6.6 \mu\text{W}$$

$$P_{\text{dyn}-3} = P_{1 \rightarrow 0} f C_3 V_{\text{DD}}^2$$

$$P_{Z=0} = P_{X=1} P_{Y=0} = (0.3)(0.3) = 0.09$$

$$P_{Z=1} = 1 - P_{Z=0} = 0.91$$

$$P_{\text{dyn}-3} = (0.91)(0.09)(1e9)(20e-15)(2.5^2)$$

$$= 10.2 \mu\text{W}$$

$$P_{\text{dyn}} = P_{\text{dyn}-1} + P_{\text{dyn}-2} + P_{\text{dyn}-3} = 6.6 + 6.6 + 10.2$$

$$= \underline{\underline{23.4 \mu\text{W}}}$$

[6] Question 4: Consider a metal 1 (first layer of metal) aluminum wire that is $0.8 \mu\text{m}$ above the substrate, is $0.5 \mu\text{m}$ in height and has a width of $0.25 \mu\text{m}$ and has a length of 5 mm . Recall that the resistivity of aluminum is $2.8 \mu\Omega \cdot \text{cm}$

a) Find the resistance per μm , R_w and the capacitance per μm , C_w .

$$R_{\square} = \frac{\sigma}{t} = \frac{2.8e-8 \Omega \cdot \text{m}}{0.5e-6 \text{ m}} = 0.056 \Omega/\square$$

$$R_w = R_{\square} \frac{1 \mu\text{m}}{0.25 \mu\text{m}} = 4R_{\square} = 0.224 \Omega/\mu\text{m}$$

$$C_w = \epsilon_{ox} \left[\left(\frac{w}{h} \right) + 0.77 + 1.06 \left(\frac{w}{h} \right)^{0.25} + 1.06 \left(\frac{t}{h} \right)^{0.5} \right]$$

$$= 3.9 \times 8.854e-12 [2.71]$$

$$= 93.7 \text{ pF/m} = 0.094 \text{ fF}/\mu\text{m}$$

$$R_w = 0.224 \Omega/\mu\text{m}$$

$$C_w = 0.094 \text{ fF}/\mu\text{m}$$

a) Estimate the delay, t_d , of this wire assuming the delay is 1.2τ .

$$\tau = \frac{RC}{2} = \frac{(0.224)(5000)(0.094)(5000)}{2}$$

$$= \frac{(1120)(470 \text{ fF})}{2} = 263 \text{ pS}$$

$$t_d = 316 \text{ pS}$$

$$t_d = 1.2\tau = 316 \text{ pS}$$

b) Estimate the delay of this wire if the width is increased to $1 \mu\text{m}$ and other parameters are unchanged.

$$w_2 = 4w \Rightarrow R_2 = \frac{R}{4} = 280 \Omega$$

$$t_d = 116 \text{ pS}$$

$$C_{w2} = \epsilon_{ox} \left[\left(\frac{w_2}{h} \right) + 0.77 + 1.06 \left(\frac{w_2}{h} \right)^{0.25} + 1.06 \left(\frac{t}{h} \right)^{0.5} \right]$$

$$= \epsilon_{ox} [3.98] = 0.138 \text{ fF}/\mu\text{m}$$

$$C_2 = C_{w2} (5000) = 690 \text{ fF}$$

$$t_{d2} = 1.2 \frac{R_2 C_2}{2} = 116 \text{ pS}$$


[6] **Question 5:** It is desired to drive a 1pF capacitive load given that a minimum size inverter has a gate capacitance of 4fF and its inherent delay is 15ps.

a) Find the delay if a single inverter is used.

$$t_d = \tau_{inv} \frac{C_{out}}{C_{in}} = (15 \text{ ps}) \left(\frac{1 \text{ pF}}{4 \text{ fF}} \right)$$

$$= \underline{\underline{3.75 \text{ ns}}}$$

 b) Find the delay if an inverter chain is used where a fanout factor of 4 is used for inverter sizing.



$$t_d = 3 \tau_{inv} (4) + \tau_{inv} \left(\frac{1 \text{ pF}}{256 \text{ fF}} \right) = 12 \tau_{inv} + 3.9 \tau_{inv}$$

$$= 15.9 \tau_{inv} = (15.9) (15 \text{ ps}) = \underline{\underline{238 \text{ ps}}}$$

c) Explain why a fanout factor of 4 is generally used for inverter sizing in an inverter chain instead of a factor of e which was derived in class to be optimum. (hint: what was overlooked in the class derivation?)

CLASS DERIVATION DID NOT ACCOUNT FOR OUTPUT CAPACITANCE OF AN INVERTER WHICH ROUGHLY SCALES WITH SIZE OF INVERTER ALSO FACTOR OF 4 IS SIMPLE TO DO.

Constants: $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \approx 26 \text{ mV}$ at $300 \text{ }^\circ\text{K}$;

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}; k_{\text{ox}} = 3.9; \text{caps: } C_{\text{ox}} = (k_{\text{ox}} \epsilon_0) / t_{\text{ox}}; C_j = C_{j0} / (1 + V_R / \phi_0)^{M_j};$$

NMOS: $\beta_n = \mu_n C_{\text{ox}} (W/L)$; $V_{tn} > 0$; $V_{DS} \geq 0$; (triode) $I_D = \beta_n ((V_{GS} - V_{tn}) V_{DS} - (V_{DS}^2 / 2))$; (active) $I_D = 0.5 \beta_n (V_{GS} - V_{tn})^2$;

$$\text{(triode)} V_{DS} \leq (V_{GS} - V_{tn}); \text{(active)} V_{DS} \geq (V_{GS} - V_{tn}); V_{tn} = V_{tn0} + \gamma (\sqrt{V_{SB} + \phi_s} - \sqrt{\phi_s});$$

$$\text{(subthreshold)} I_D = I_{D0} e^{\frac{(V_{GS} - V_{tn}) / (n V_T)}{(1 - e^{-V_{DS} / V_T})}};$$

PMOS: $\beta_p = \mu_p C_{\text{ox}} (W/L)$; $V_{tp} < 0$; $V_{DS} \leq 0$; (triode) $I_D = \beta_p ((V_{GS} - V_{tp}) V_{DS} - (V_{DS}^2 / 2))$; (active) $I_D = 0.5 \beta_p (V_{GS} - V_{tp})^2$;

$$\text{(triode)} V_{DS} \geq (V_{GS} - V_{tp}); \text{(active)} V_{DS} \leq (V_{GS} - V_{tp});$$

Simple cap model: $C_g = C_{\text{ox}} W L$; if L_{min} ; $C_{gu} \equiv C_{\text{ox}} L_{\text{min}}$; $C_g = C_{gu} W$; $C_d = C_s = C_{du} W$;

CMOS inverter: $V_{TH} = (V_{DD} + V_{tp} + V_{tn} r) / (1 + r)$; $r = \sqrt{(\mu_n (W/L)_n) / (\mu_p (W/L)_p)}$;

RC delay est: $t_{dr} = t_{df} = 1.2 \tau$; $\tau = R_{\text{eq}} C$; $R_{\text{eqn}} = 2.5 / (\mu_n C_{\text{ox}} (W/L)_n (V_{DD} - V_{tn}))$; $R_{\text{eqp}} = 2.5 / (\mu_p C_{\text{ox}} (W/L)_p (V_{DD} + V_{tp}))$;

$$(W_p / W_n)_{\text{opt}} = \sqrt{\mu_n / \mu_p} \quad \text{Unit delay est: } t_{dP2} / t_{dF1} = (C_{L2} / C_{L1}) \times ((W/L)_{n1} / (W/L)_{n2})$$

Min delay: $t_{\text{delay}} = \tau_{\text{inv}} (C_{\text{out}} / C_{\text{in}})$; $\text{total}_{\text{delay}} = N f \tau_{\text{inv}}$; $f^N = C_{\text{out}} / C_{\text{in}}$; usually $f = 4$

Power diss: $P_{\text{dyn}} = P_{1 \rightarrow 0} f C_L V_{DD}^2$; $P_{\text{dp}} = 0.5 P_{1 \rightarrow 0} f V_{DD} I_{\text{peak}} (t_r + t_f)$; $I_{\text{peak}} = 0.5 \beta_n (V_{TH} - V_{tn})^2$;

Elmore Delay: $\tau_i \approx \sum C_k R_{ik}$; dist RC, $\tau \approx RC / 2$;

Interconnect: $R = \rho l / (t w)$; $R_{\square} = \rho / t$; $C = (\epsilon_{\text{ox}} w l) / t$; $C = \epsilon_{\text{ox}} l (w/h + 0.77 + 1.06 (w/h)^{0.25} + 1.06 (t/h)^{0.5})$;