

# **Bandgap Voltage Reference**

*David Johns, Ken Martin  
University of Toronto  
(johns@eecg.toronto.edu)  
(martin@eecg.toronto.edu)*



# Voltage Reference

## Basic Goal


- To create an on-chip voltage reference that does not vary with process, temperature, aging, etc.
- Bandgap voltage reference most common
- Cancels negative temp of pn diode with positive temp of PTAT (Proportional To Absolute Temp) circuit

## Approaches other than bandgap

- Zener diode (p+/n+) — usually too high a voltage nowadays, 6.7volts
- Threshold difference between enhance and depletion transistors — no depletion nowadays



## Basic Concept

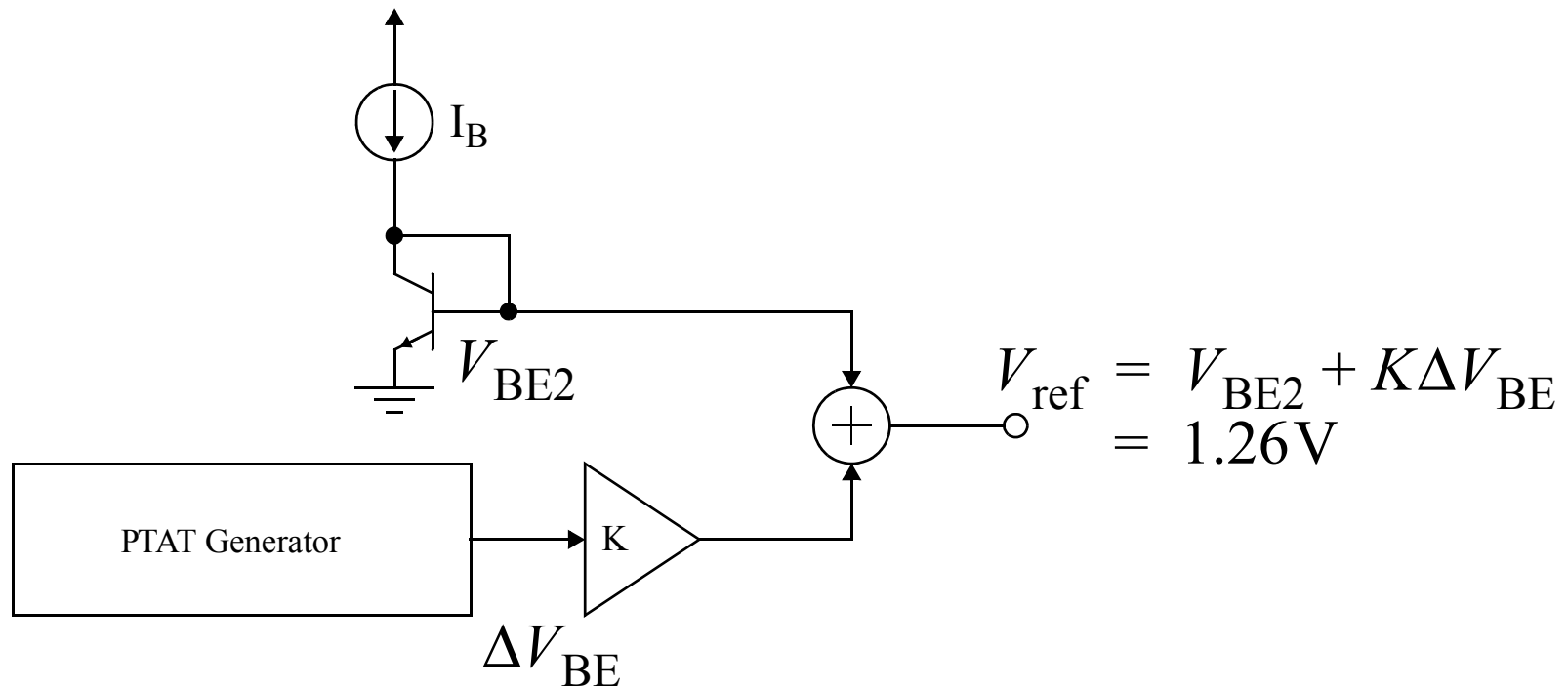

- $V_{BE2}$  has negative temperature coefficient
- $\Delta V_{BE}$  has positive temperature coefficient
- $K$  is a multiplying factor to get zero temp coeff



## Equations

$$I_C = I_s e^{V_{BE}/((kT)/q)} \quad (1)$$

- where for a constant  $I_C$ ,  $V_{BE}$  has a temperature coefficient of approximately

$$-2 \text{ mV}/^\circ\text{K} \quad (2)$$

- Also need to define collector current density,  $J_C$ , as

$$I_C = A_E J_C \quad (3)$$

- where  $A_E$  is the area of base-emitter junction
- Can write  $V_{BE}$  as a function of collector current and temperature.
- It has been shown to be ...



## Equations

$$V_{BE} = V_{G0} \left( 1 - \frac{T}{T_0} \right) + V_{BE0} \frac{T}{T_0} + \frac{mkT}{q} \ln \left( \frac{T_0}{T} \right) + \frac{kT}{q} \ln \left( \frac{J_C}{J_{C0}} \right) \quad (4)$$

- $V_{G0}$  is bandgap voltage of silicon at 0 °K (about 1.206 V)
- $T_0$  is a reference temperature,  $T$  is true temp
- $V_{BE0}$  is base-emitter voltage at temp  $T_0$
- $J_{C0}$  is collector current density at temp  $T_0$
- $J_C$  is collector current density at temp  $T$
- $m$  is a constant (approximately 2.3)



## Equations

$$\Delta V_{BE} = V_2 - V_1 = \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) \quad (5)$$

- while  $V_{BE}$  has negative temp coeff,  $\Delta V_{BE}$  has a positive temp coeff since ...
- $\Delta V_{BE}$  is *proportional to absolute temperature* (as long as ratio  $J_2/J_1$  remains constant) (PTAT voltage)



## Example

- Assuming ratio of  $J_2/J_1 = 10$  and  $T = 300\text{ }^\circ\text{K}$

$$\Delta V_{\text{BE}} = \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) = \frac{1.38 \times 10^{-23}(300)}{1.602 \times 10^{-19}} \ln(10) = 59.5\text{ mV} \quad (6)$$

- so temperature dependence is ...

$$59.5\text{ mV}/300\text{ }^\circ\text{K} = 0.198\text{ mV}/^\circ\text{K} \quad (7)$$

- Need  $K \cong 10$  to cancel temp dependence of  $V_{\text{BE}}$  which is  $-2\text{ mV}/^\circ\text{K}$



## Equations

- We now make the assumption that junction currents are PTAT (will be true if resistors are temp independent)

$$\frac{J_i}{J_{i0}} = \frac{T}{T_0} \quad (8)$$

- and we can now find

$$\begin{aligned} V_{\text{ref}} &= V_{\text{BE2}} + K \Delta V_{\text{BE}} \\ &= V_{\text{G0}} + \frac{T}{T_0} (V_{\text{BE0-2}} - V_{\text{G0}}) + (m - 1) \frac{kT}{q} \ln\left(\frac{T_0}{T}\right) + K \frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right) \end{aligned} \quad (9)$$





## Equations

- Take derivative of (9) wrt temperature to give

$$\frac{\partial V_{\text{ref}}}{\partial T} = \frac{1}{T_0} (V_{BE0-2} - V_{G0}) + K \frac{k}{q} \ln\left(\frac{J_2}{J_1}\right) + (m-1) \frac{k}{q} \ln\left(\frac{T_0}{T} - 1\right) \quad (10)$$

- and setting (10) equal to zero at  $T = T_0$  gives

$$V_{BE0-2} + K \frac{kT_0}{q} \ln\left(\frac{J_2}{J_1}\right) = V_{G0} + (m-1) \frac{kT_0}{q} \quad (11)$$

- Left side is output voltage  $V_{\text{ref}}$  at  $T = T_0$  so we need

$$V_{\text{ref-0}} = V_{G0} + (m-1) \frac{kT_0}{q} \quad (12)$$



## Equations

- In case where  $T_0 = 300\text{ }^\circ\text{K}$  and  $m = 2.3$

$$V_{ref-0} = 1.24\text{ V} \quad (13)$$

- Value is independent of current densities used --- thus the reason for name “**Bandgap** voltage reference”.
- From (11), we find  $K$  as

$$K = \frac{V_{G0} + (m-1)\frac{kT_0}{q} - V_{BE0-2}}{\frac{kT_0}{q} \ln\left(\frac{J_2}{J_1}\right)} = \frac{1.24 - V_{BE0-2}}{0.0258 \ln\left(\frac{J_2}{J_1}\right)} \quad (14)$$


- at  $T_0 = 300\text{ }^\circ\text{K}$



# Bipolar Circuit

$$A_{E1} = 8A_{E2}$$

$$\frac{J_2}{J_1} = 8$$

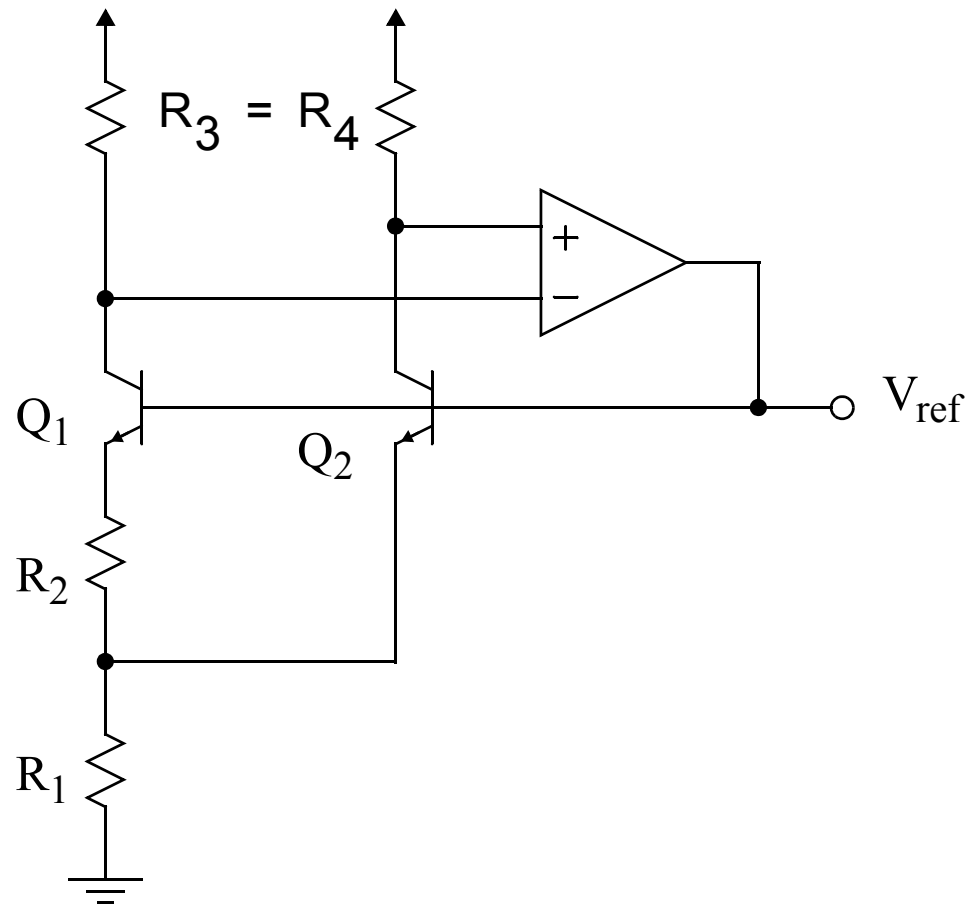

## Bipolar Circuit

$$V_{\text{ref}} = V_{BE2} + V_{R1} \quad (15)$$

$$\begin{aligned} V_{R1} &= I_{R1} R_1 \\ &= 2I_{R2} R_1 \end{aligned} \quad (16)$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{V_{BE2} - V_{BE1}}{R_2} = \frac{\Delta V_{BE}}{R_2} \quad (17)$$

$$V_{\text{ref}} = V_{BE2} + \frac{2R_1}{R_2} \Delta V_{BE} \quad (18)$$

$$K = \frac{2R_1}{R_2} \quad (19)$$



## Bipolar Circuit

- And if  $V_{BE2} = 0.65$  at ref temp



$$\frac{R_1}{R_2} = \frac{1}{2} \times \frac{1.24 - 0.65}{0.0258 \times \ln(8)} = 5.5 \quad (20)$$

- If possible,  $R_1$  or  $R_2$  would be trimmed to obtain correct reference voltage
- Note that as assumed, we have

$$I_{E1} = I_{E2} = I_{R2} = \frac{\Delta V_{BE}}{R_2} = \frac{\frac{kT}{q} \ln\left(\frac{J_2}{J_1}\right)}{R_2} \quad (21)$$




# CMOS Circuit

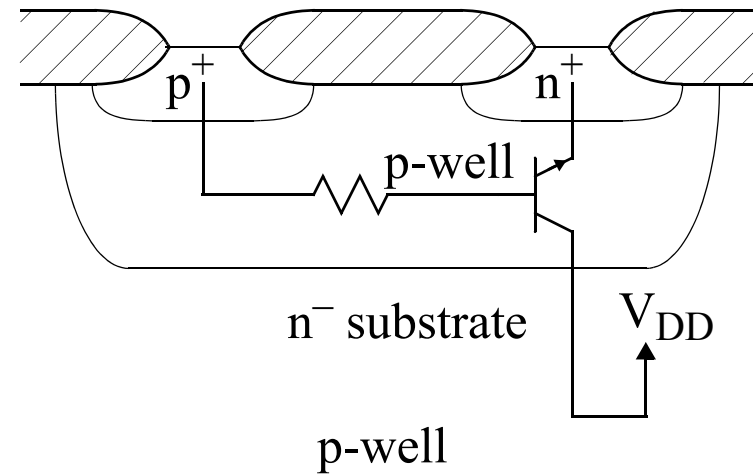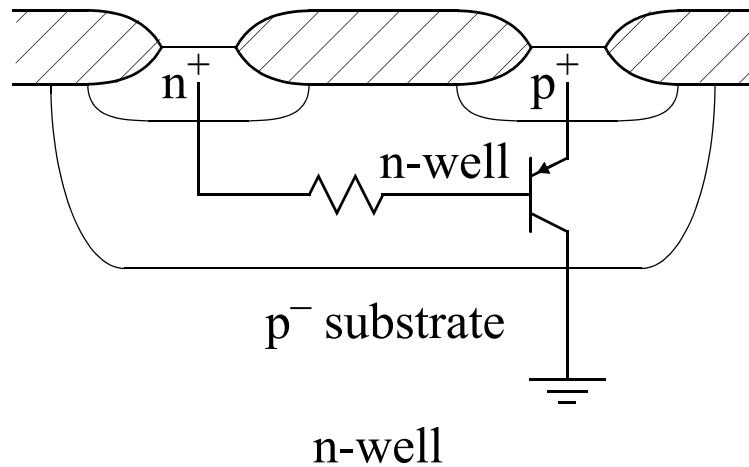


- Parasitic vertical bipolar transistors exist in CMOS



# CMOS Circuit

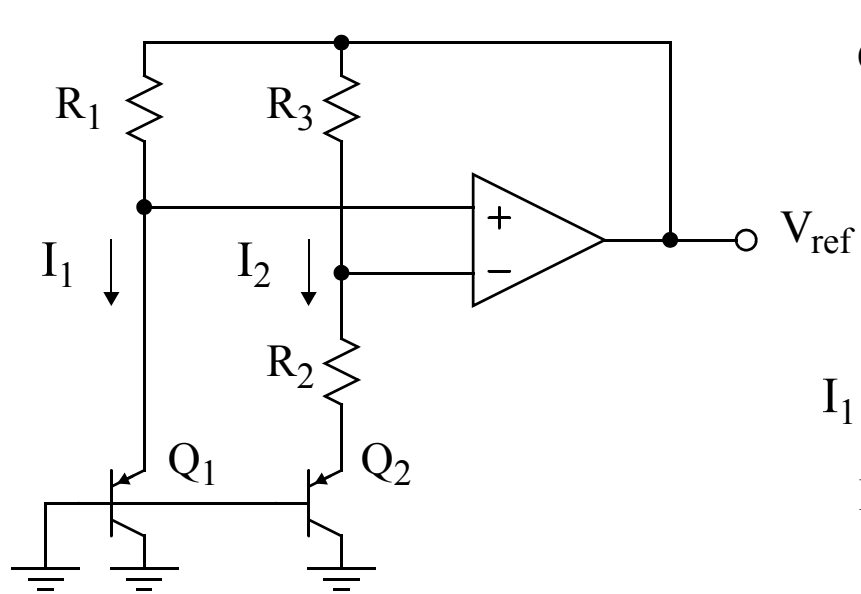

n-well

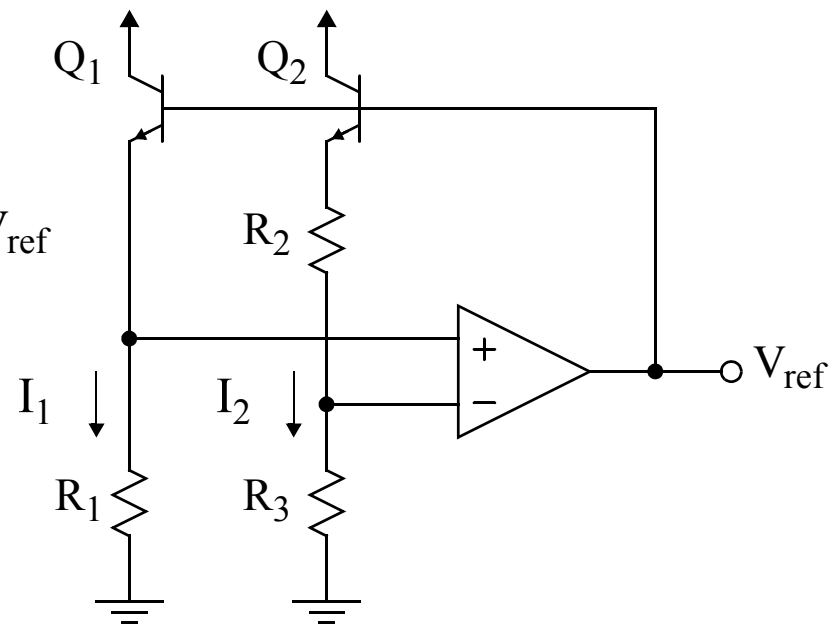

p-well



# CMOS Circuit

- Equations for n-well circuit

$$V_{\text{ref}} = V_{\text{EB1}} + V_{\text{R1}} \quad (22)$$

$$V_{\text{R2}} = V_{\text{EB1}} - V_{\text{EB2}} = \Delta V_{\text{EB}} \quad (23)$$

$$V_{\text{R3}} = \frac{R_3}{R_2} V_{\text{R2}} = \frac{R_3}{R_2} \Delta V_{\text{EB}} \quad (24)$$

$$V_{\text{ref}} = V_{\text{EB1}} + \frac{R_3}{R_2} \Delta V_{\text{EB}} \quad (25)$$

$$\frac{J_1}{J_2} = \frac{R_3}{R_1} \quad (26)$$





## CMOS Circuit

$$\Delta V_{EB} = V_{EB1} - V_{EB2} = \frac{kT}{q} \ln\left(\frac{J_1}{J_2}\right) \quad (27)$$

$$V_{\text{ref}} = V_{EB1} + \frac{R_3}{R_2} \frac{kT}{q} \ln\left(\frac{R_3}{R_1}\right) \quad (28)$$

$$K = \frac{R_3}{R_2} \quad (29)$$



## CMOS Example

- Find resistances for above when  $I_1 = 80 \mu\text{A}$ ,  $I_2 = 8 \mu\text{A}$ , and  $V_{EB1-0} = 0.65 \text{ V}$  at  $T = 300^\circ\text{K}$ .
- First, we note that

$$V_{ref-0} = 1.24 \text{ V} \quad (30)$$

- which leads to

$$V_{R1} = V_{ref-0} - V_{EB1-0} = 0.59 \text{ V} \quad (31)$$

- This allows us to find  $R_1$  and  $R_3$

$$R_1 = \frac{V_{R1}}{I_1} = \frac{0.59 \text{ V}}{80 \mu\text{A}} = 7.38 \text{ k}\Omega \quad (32)$$

$$R_3 = \frac{V_{R3}}{I_2} = \frac{0.59 \text{ V}}{8 \mu\text{A}} = 73.8 \text{ k}\Omega \quad (33)$$



- To find  $R_2$ , we first find  $K$  to be

$$K = \frac{1.24 - 0.65 \text{ V}}{0.0258 \times \ln(10)} = 9.93 \quad (34)$$

$$R_2 = \frac{R_3}{K} = 7.43 \text{ k}\Omega \quad (35)$$

