

# Phase-Locked Loops

*David Johns, Ken Martin*  
*University of Toronto*



University of Toronto


1 of 26

# Common PLL Applications

- **Clock multiplier**
  - input is a fixed frequency clock
  - output is a higher frequency clock signal that is a multiple of input clock frequency
- **Frequency synthesizer**
  - input is a fixed frequency clock
  - output is a clock signal with arbitrary frequency
- **Clock and data recovery**
  - input is a data signal (from a serial link)
  - output is digital data as well as clock signal
  - phase detector is different than other applications
- **FM demodulation**
  - input is a radio signal
  - output is demodulated signal



# PLL Basic Architecture

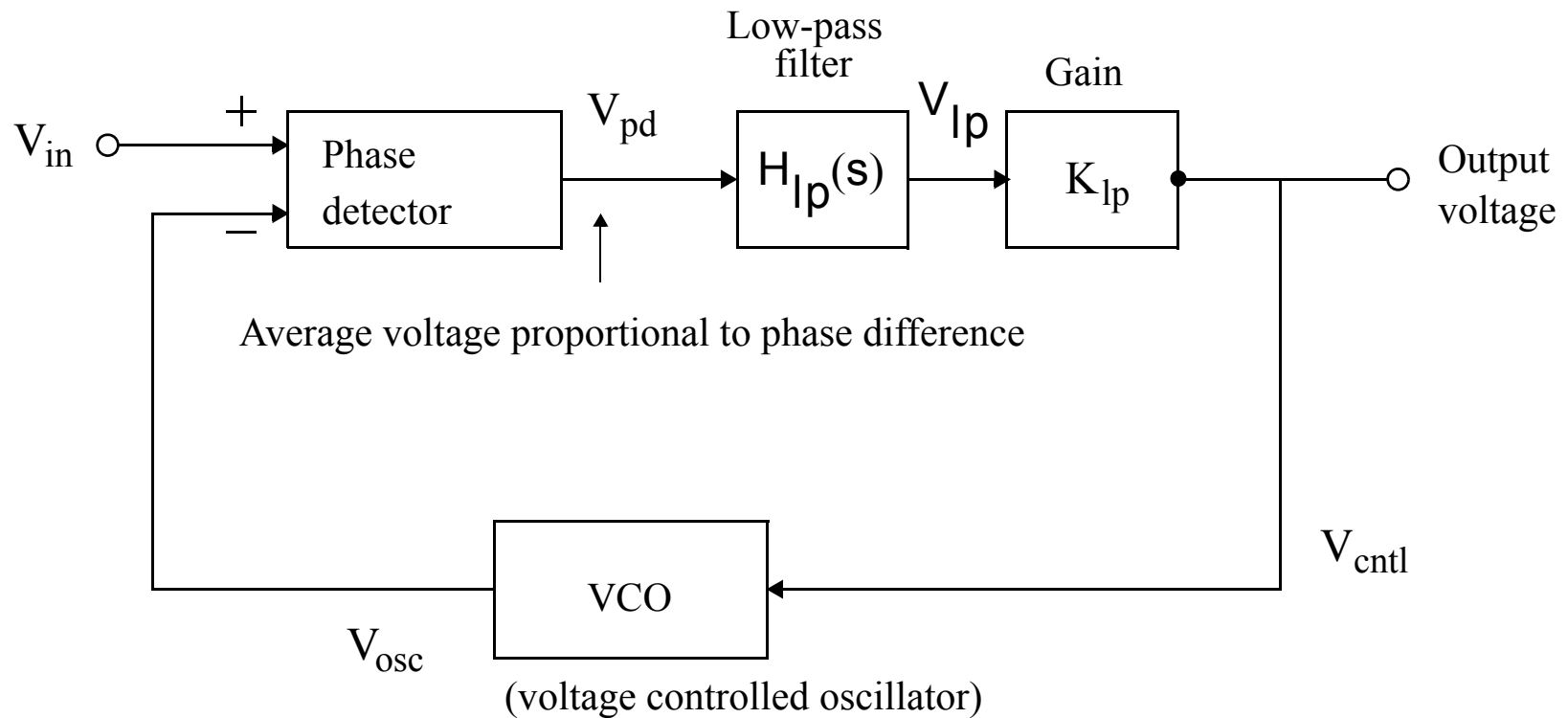

- In general, output may be  $V_{cntl}$  or  $V_{osc}$



## PLL Basics

- Feedback causes  $V_{in}$  to be phase locked to  $V_{osc}$
- We start with a simple phase detector of ...

$$V_{pd} = K_M V_{in} V_{osc} \quad (1)$$

$K_M$  is a multiplication constant


- Also assume filter is ...

$$H_{lp}(s) = \frac{1 + s\tau_z}{1 + s\tau_p} \quad (2)$$

which is a lead-lag filter. Usually  $\tau_z \ll \tau_p$



## Example Waveforms

 

$$V_{in} = E_{in} \sin(\omega t) \quad (3)$$

$$V_{osc} = E_{osc} \sin(\omega t - \phi_d + 90^\circ) = E_{osc} \cos(\omega t - \phi_d) \quad (4)$$

- Above shows an example of  $\phi_d \approx 90$  (slightly less)



## PLL Basics

- Can show

$$V_{pd} = K_M \frac{E_{in} E_{osc}}{2} [\sin(\phi_d) + \sin(2\omega t - \phi_d)] \quad (5)$$

- The lowpass filter removes second term and for small  $\phi_d$

...

$$V_{cntl} \cong K_{lp} K_M \frac{E_{in} E_{osc}}{2} \phi_d = K_{lp} K_{pd} \phi_d \quad (6)$$

where we define

$$K_{pd} = K_M \frac{E_{in} E_{osc}}{2} \quad (7)$$



## PLL Basics

- Oscillator frequency given by

$$\omega_{osc} = K_{osc} V_{cntl} + \omega_{fr} \quad (8)$$

$\omega_{fr}$  is the free running freq of oscillator


$K_{osc}$  is the VCO gain constant

- Feedback forces  $\omega_{osc}$  to equal  $\omega_{in}$
- However, if  $\omega_{in}$  does not equal  $\omega_{fr}$ , and loop filter does NOT have infinite gain at dc, then phase difference when in lock given by:

$$\phi_d = \frac{V_{cntl}}{K_{lp} K_{pd}} = \frac{\omega_{in} - \omega_{fr}}{K_{lp} K_{pd} K_{osc}} \quad (9)$$



# PLL Linear Model

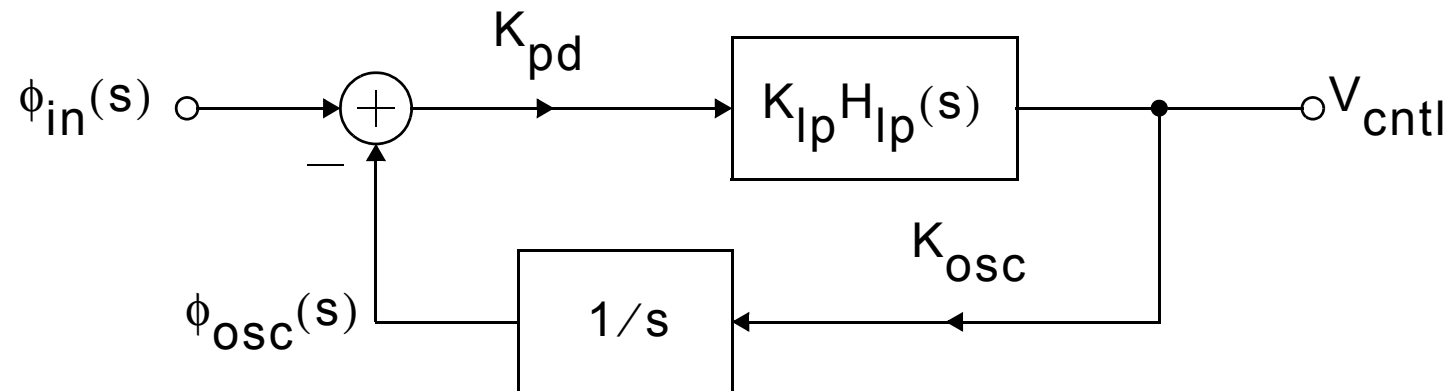

$$V_{cntl}(s) = K_{pd} K_{lp} H_{lp}(s) [\phi_{in}(s) - \phi_{osc}(s)] \quad (10)$$

$$\phi_{osc}(s) = \frac{K_{osc} V_{cntl}(s)}{s} \quad (11)$$





## PLL Equations

- Combining above 2 equations ...

$$\frac{V_{\text{cntl}}(s)}{\phi_{\text{in}}(s)} = \frac{sK_{pd}K_{lp}H_{lp}(s)}{s + K_{pd}K_{lp}K_{\text{osc}}H_{lp}(s)} \quad (12)$$


- This is a highpass response from input phase to control voltage
- Can also be written as

$$\frac{\phi_{\text{osc}}(s)}{\phi_{\text{in}}(s)} = \frac{K_{pd}K_{lp}K_{\text{osc}}H_{lp}(s)}{s + K_{pd}K_{lp}K_{\text{osc}}H_{lp}(s)} \quad (13)$$


- This is a lowpass response from input phase to output phase



# Charge Pump PLL

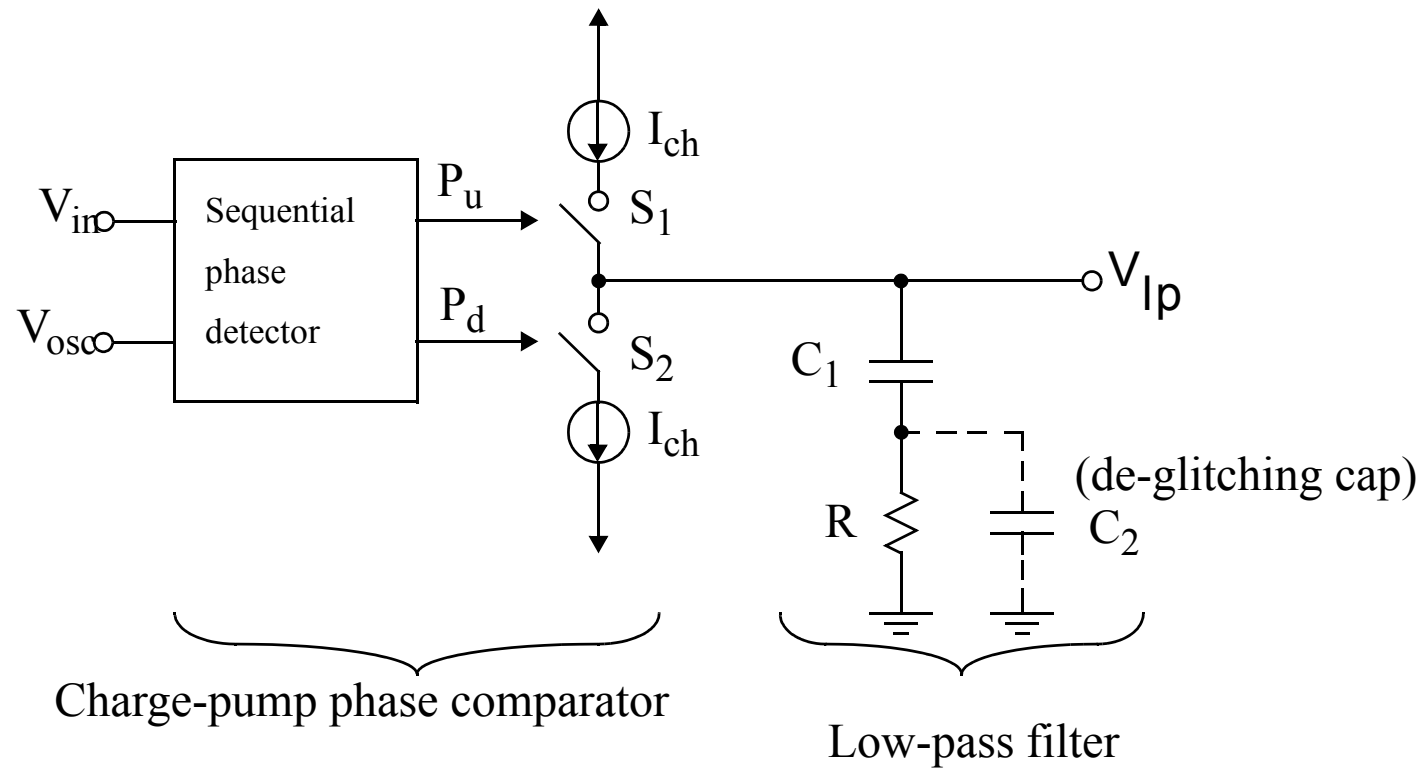

# Sequential Phase Detector

 

- If  $V_{in}$  leads  $V_{osc}$ ,  $P_u$  (pulse up) goes high for lead time
- If  $V_{osc}$  leads  $V_{in}$ ,  $P_d$  (pulse down) goes high for lead time.



## Charge Pump PLL Equations

- Average current flowing into lowpass filter is ...

$$I_{\text{avg}} = \frac{\Delta\phi_{in}}{2\pi} I_{ch} \quad (14)$$

- Lowpass filter is (ignoring  $C_2$ )...

$$H_{lp}(s) = \frac{V_{lp}(s)}{I_{\text{avg}}(s)} = R + \frac{1}{sC_1} = \frac{1 + sRC_1}{sC_1} \quad (15)$$

- which results in

$$\frac{\phi_{osc}(s)}{\phi_{in}(s)} = \frac{(1 + sRC_1)}{1 + sRC_1 + \frac{s^2 C_1}{K_{pd} K_{osc}}} \quad (16)$$



## Charge Pump PLL Equations

- The phase transfer curve is second-order (ignores de-glitching cap  $C_2$ ) so  $\omega_0$  and  $Q$  can be found as

$$\omega_0 = \frac{1}{\tau_{pll}} = \sqrt{\frac{I_{ch} K_{osc}}{2\pi C_1}} \quad (17)$$

$$Q = \frac{1}{RC_1 \omega_0} = \frac{1}{R} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}} \quad (18)$$



## Charge Pump Example

- Let  $K_{osc} = 2\pi \times 50 \text{ Mrad/V}$  and  $I_{ch} = 10 \mu\text{A}$ .
- $\omega_{fr} = 2\pi \times 50 \text{ Mrad/s}$ . Desired loop time constant of 100 cycles, or  $2 \mu\text{s}$ . Find loop filter components.

### SOLUTION

$$\omega_0 = \frac{1}{2 \mu\text{s}} = 500 \text{ krad/s} \quad (19)$$


$$C_1 = \frac{1}{\omega_0} \frac{I_{ch}}{2\pi} K_{osc} = 2 \text{ nF} \quad (20)$$

- Let  $C_2 = C_1/10 = 2.5 \text{ pF}$  and  $Q = 0.4$

$$R = \frac{1}{Q} \sqrt{\frac{2\pi}{C_1 I_{ch} K_{osc}}} = 31.4 \text{ k}\Omega \quad (21)$$




# Phase Frequency Detector

 

- Can be used for sequential phase detector but also works when large frequency differences between osc freq and input freq



# Phase Frequency Detector

 


- Above example is for osc freq much lower than input freq
- Note that  $P_u$  is high much longer than  $P_d$







# Oscillators

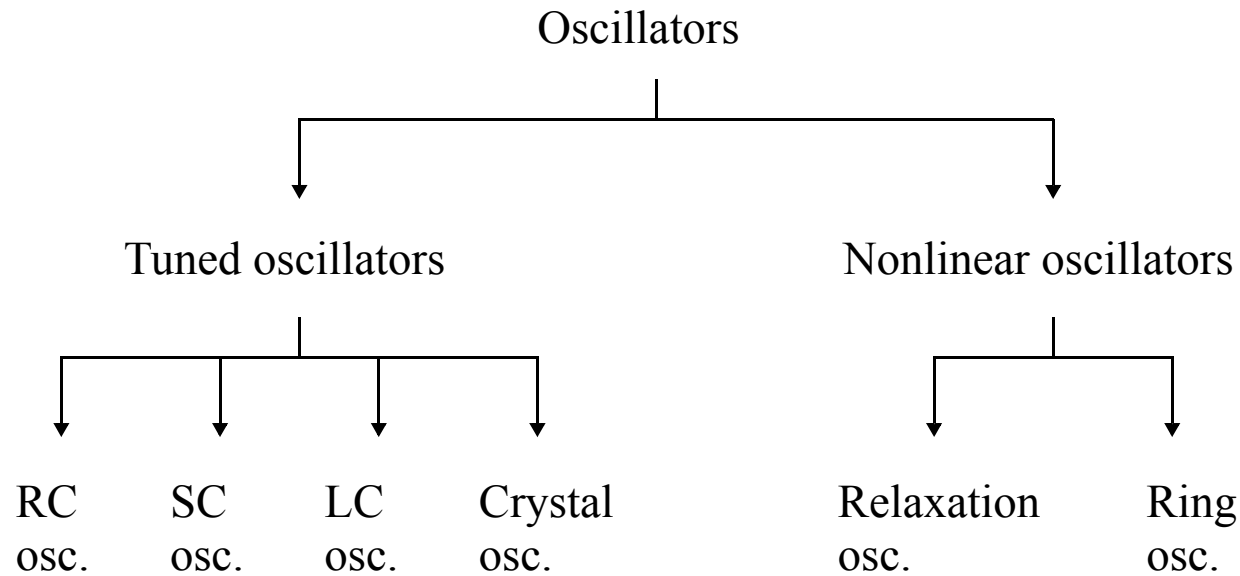

- Two main classes of oscillators
- Most common are LC osc and Ring osc (Crystal osc is good but difficult to tune away from center freq)



# Ring Oscillators

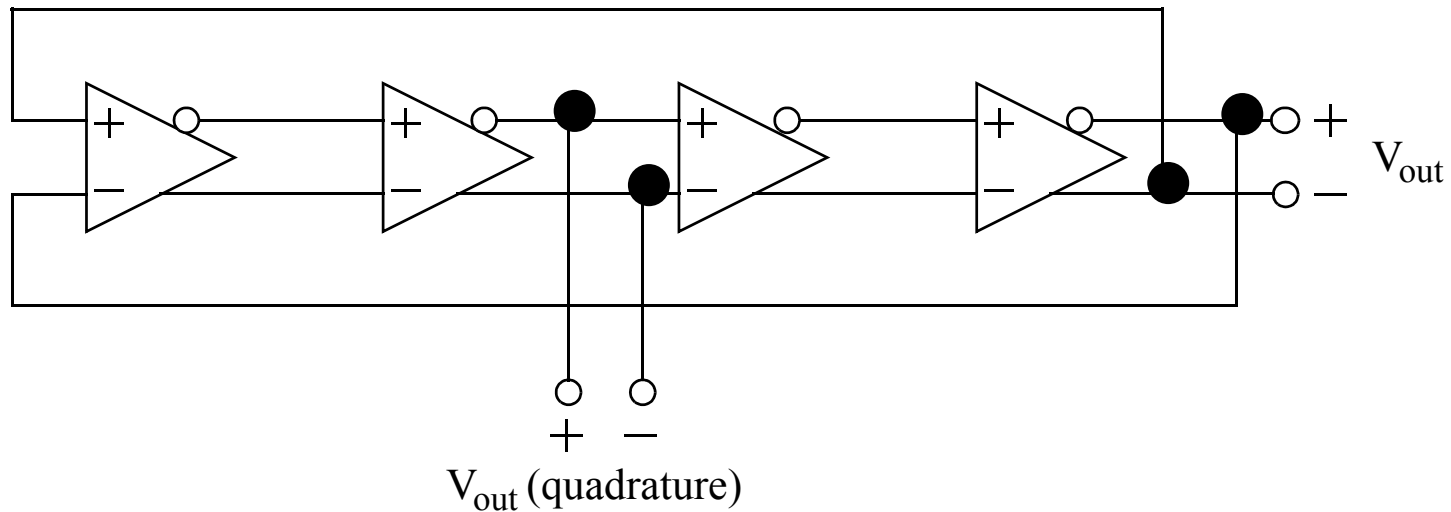 


$$f_{\text{osc}} = \frac{1}{T} = \frac{1}{2n\tau_{\text{inv}}} \quad (22)$$


where  $\tau_{\text{inv}}$  is delay of each inverter




# Fully Differential Delay Stage

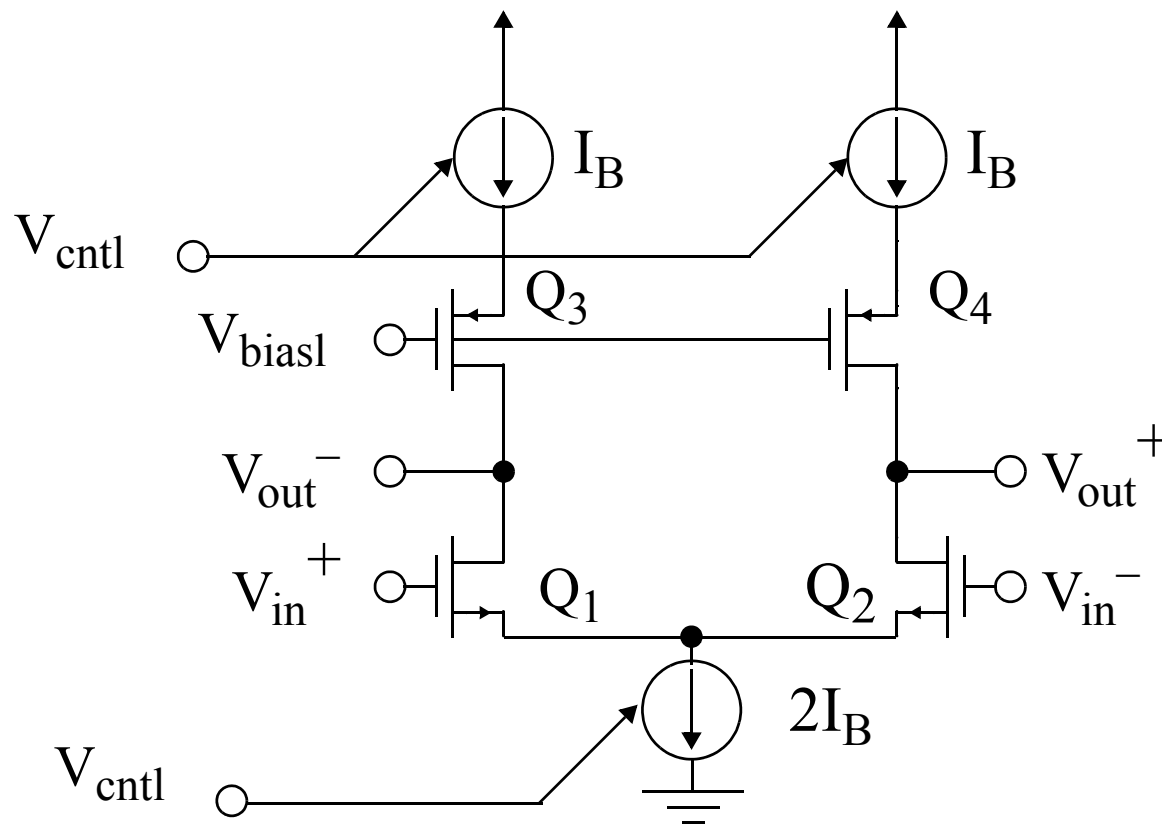

# V2I Conversion

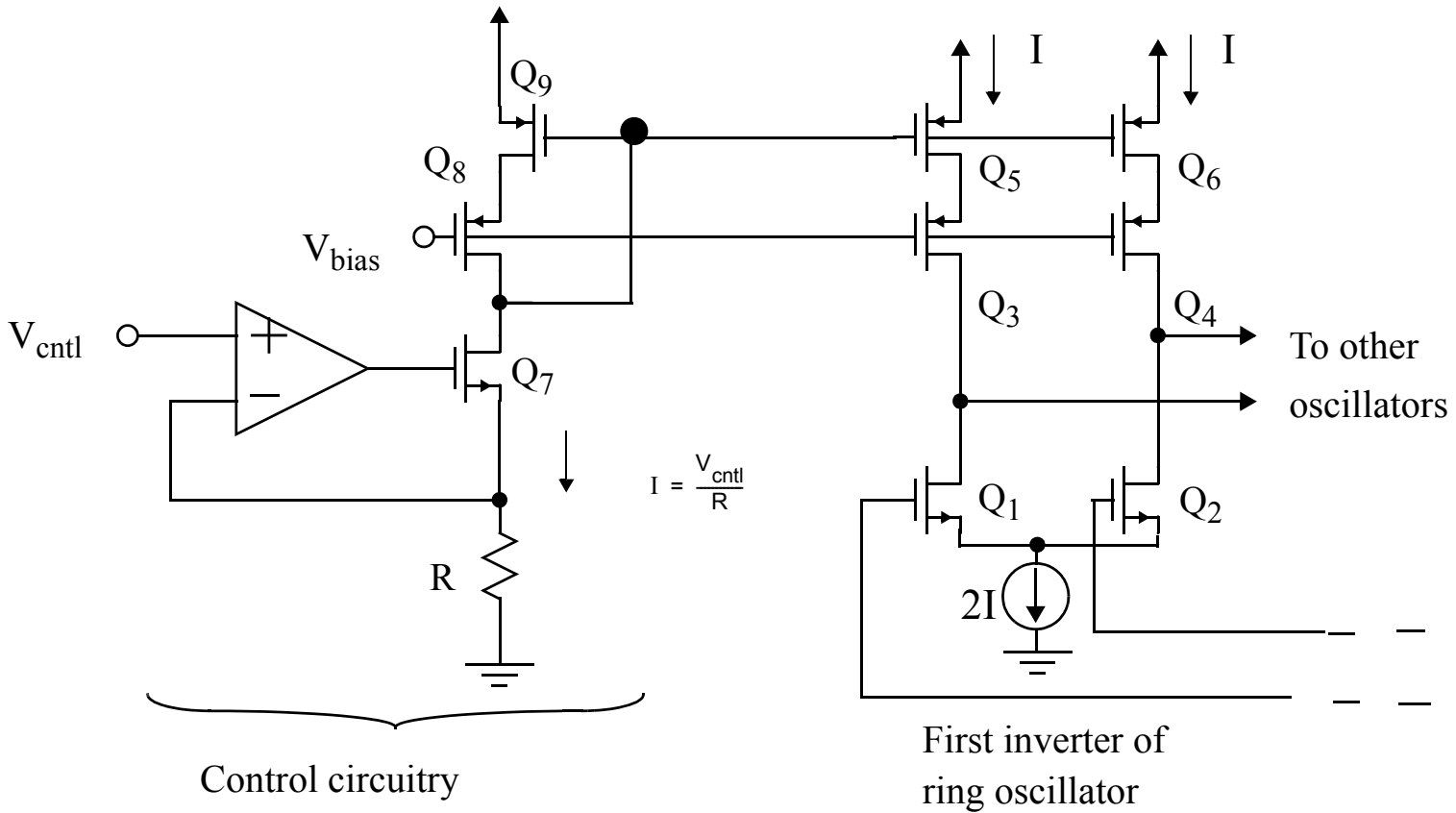

# Alternative Biasing

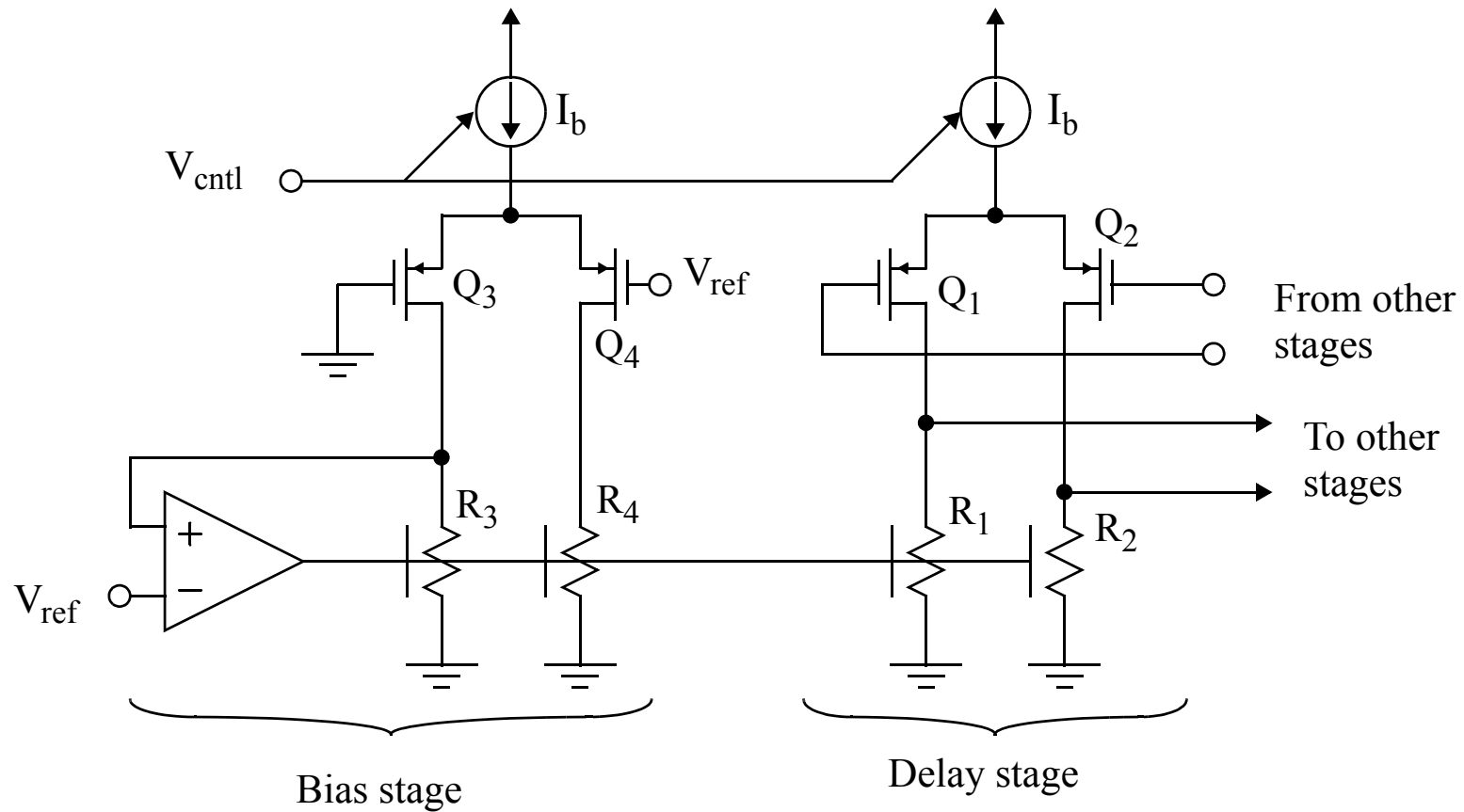

## Computer Simulation of PLLs

- Simulation times can be very long due to large variations in time-constants
- Make use of bilinear transform to simulate analog signals in discrete timesteps.
- Loop Filter example
- Impedance looking into loop filter is ... ( $G = 1/R$ )

$$Z_{lp}(s) = \frac{1}{sC_1} + \frac{1}{sC_2 + G} \quad (23)$$

- So voltage to charge relationship is ...

$$\frac{V_{lp}(s)}{Q_{lp}(s)} = \frac{G + s(C_1 + C_2)}{GC_1 + sC_1C_2} \quad (24)$$



## Discrete-time loop filter

- Use bilinear transform

$$s \leftarrow \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \quad (25)$$

- giving

$$M(z) = \frac{V_{lp}(z)}{Q_{lp}(z)} = \frac{2(1 - z^{-1})(C_1 + C_2) + GT(1 + z^{-1})}{2C_1C_2(1 - z^{-1}) + C_1GT(1 + z^{-1})} \quad (26)$$

which can be written as



$$\begin{aligned}
 P(z) &= \frac{V_{lp}(z)}{\Delta Q_{lp}(z)} = \frac{m_1 + m_2 z^{-1}}{1 + z^{-1}(k-2) + z^{-2}(1-k)} \\
 &= \left( \frac{1}{1 - z^{-1}} \right) \left( \frac{m_1 + m_2 z^{-1}}{1 - z^{-1} + k z^{-1}} \right)
 \end{aligned} \tag{27}$$

where

$$k = \frac{2GC_1T}{D} \tag{28}$$

$$m_1 = \frac{2(C_1 + C_2) + GT}{D} \tag{29}$$


$$m_2 = \frac{-2(C_1 + C_2) + GT}{D} \tag{30}$$

$$D = 2C_1C_2 + GC_1T \tag{31}$$





# Discrete-time Loop Filter

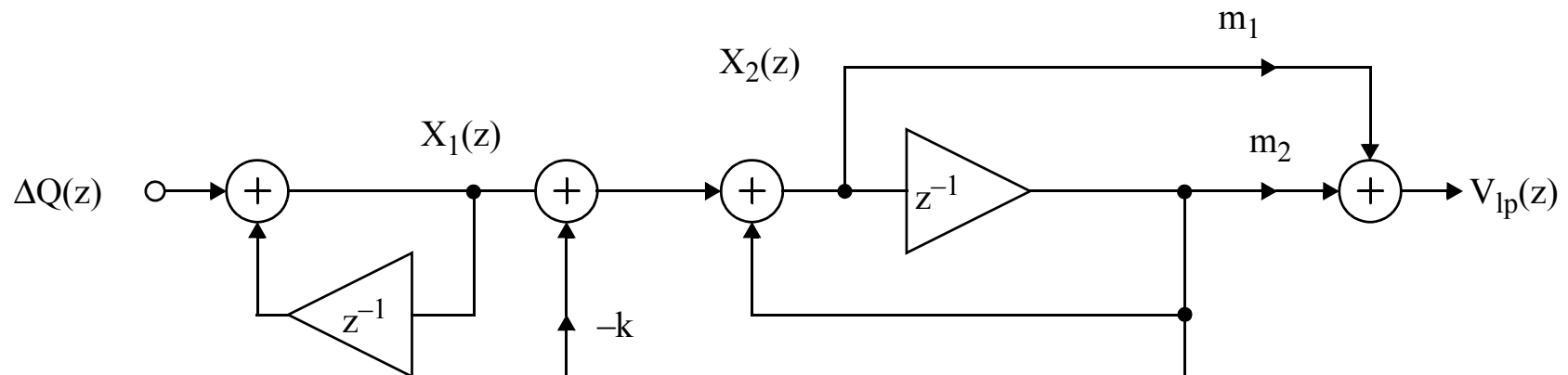


- Can use Matlab, Simulink, C, etc to simulate



# A Fractional-N Frequency Synthesizer

- Use oversampling within a PLL

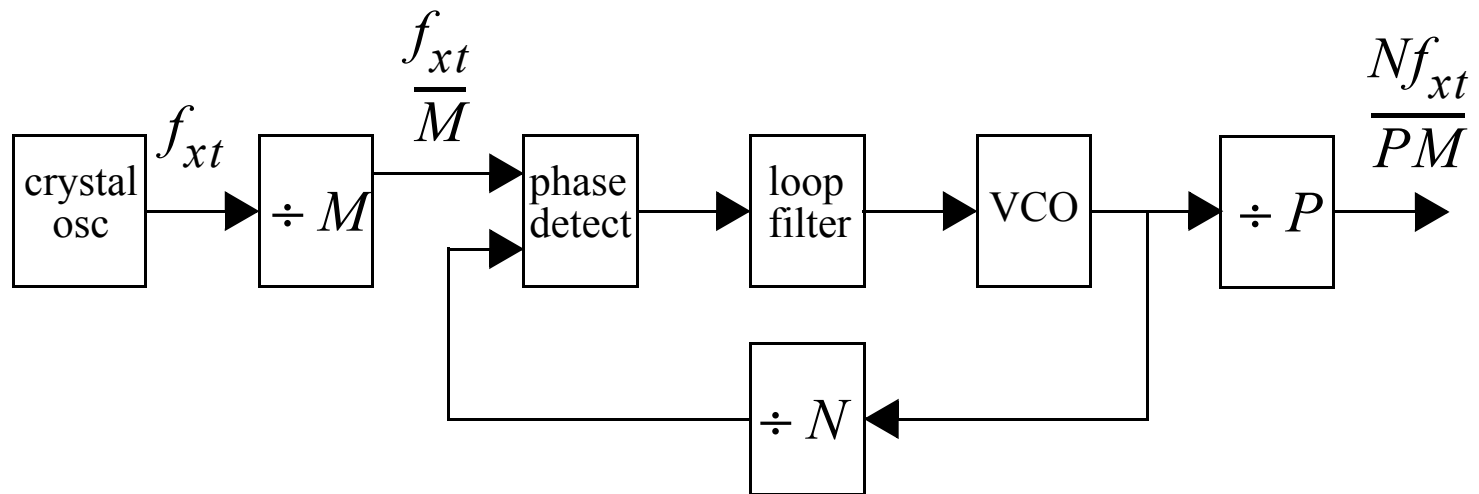

$$N = \{k-1, k, k+1\}$$

A digital controlled oscillator

