

Comparators


*David Johns and Ken Martin
University of Toronto
(johns@eecg.toronto.edu)
(martin@eecg.toronto.edu)*



University of Toronto

slide 1 of 13

Opamp does not work well!

 

Slow

- Compensation capacitor lowers slew-rate (should disconnect capacitor for higher speed)

Inaccurate


- Offset of input stage might be 2mV - 10mV

Limited input range

- Common-mode input range poor — not good if V_r is near one of power supplies (flash A/D converters)



Comparators — Offset Cancellation

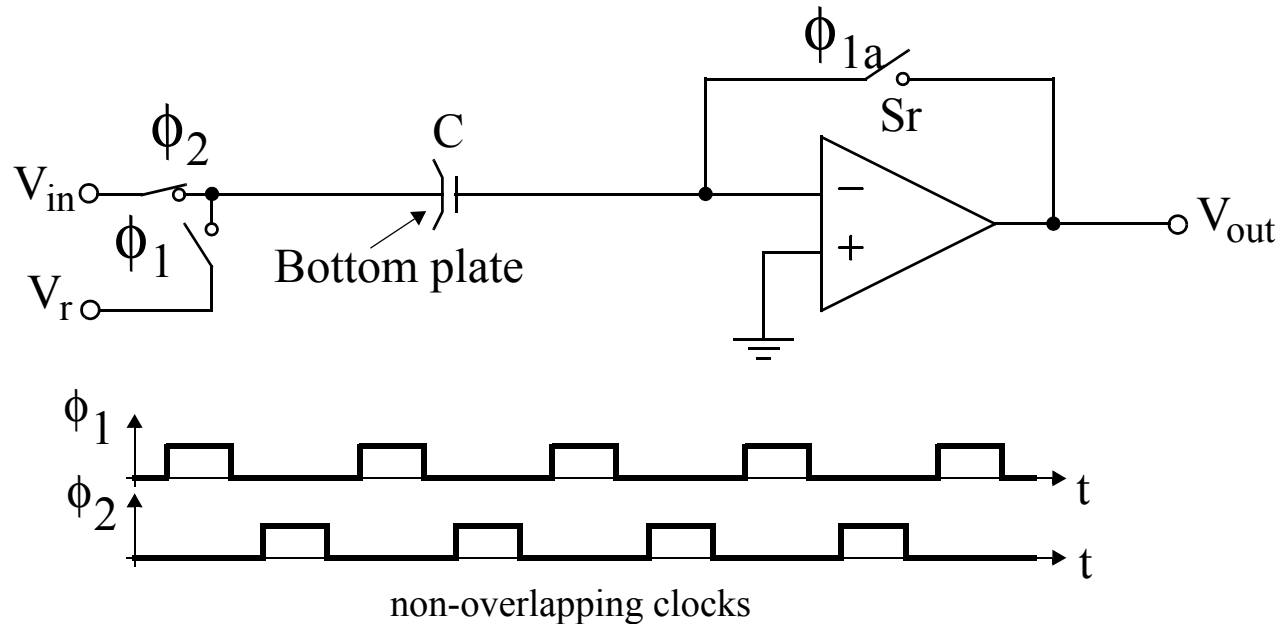

- On ϕ_1 , opamp offset stored on C as well as reference voltage, V_r — comparator set to “trigger point”.
- On ϕ_2 , evaluation phase — difference between V_r and V_{in} amplified



Comparators - Offset Cancellation

- Shown phases does not require charging of C (on ϕ_2 , capacitor is not charged)
- ϕ_{1a} is advanced version of ϕ_1 to reduce charge-injection effects (more below)
- Opamp compensation cap should be disconnected during evaluation phase for faster slew-rate

Advantages

- Very low offset possible
- Input common-mode range of amplifier near zero
- Also reduces 1/f noise

Disadvantages

- Requires floating capacitor and switches




Charge Injection Errors

- Channel charge for an ON transistor (with zero V_{ds})

$$Q_{CH} = WLC_{ox}V_{eff} = WLC_{ox}(V_{GS} - V_t) \quad (1)$$

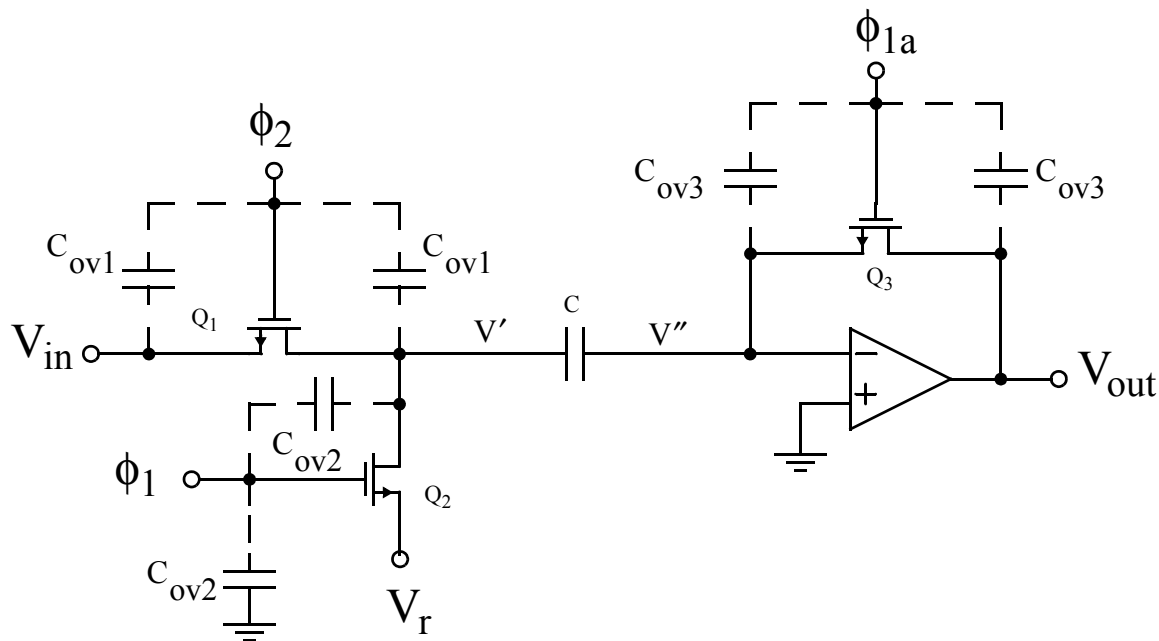- When turned off quickly, 1/2 charge flows out to each of source and drain
- Also overlap capacitances for each transistor




Making Charge Injection Signal Independent

- Advance Q3 so it turns off first [Haigh, 83]


Reasoning

 - Q3 off causes right side of C to be open circuited
- When Q2 turns off, charge injection cannot change charge on C
- When Q1 on, V' goes to V_{in} and V'' goes back to correct value (opamp offset voltage)



Minimizing Charge Injection Errors


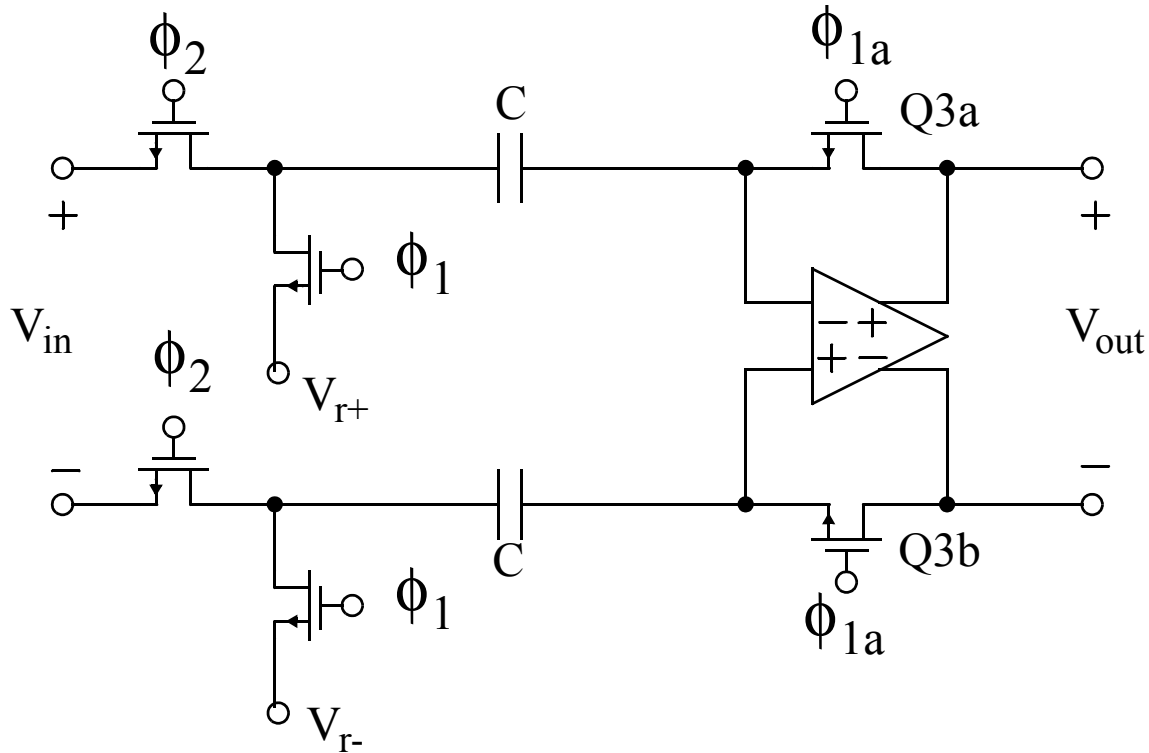
- Can use large C but slows down circuit
- Fully differential design



- Only mismatch in charge injection cause errors
- Likely 10 times smaller than single-ended case




Multi-Stage Comparator

 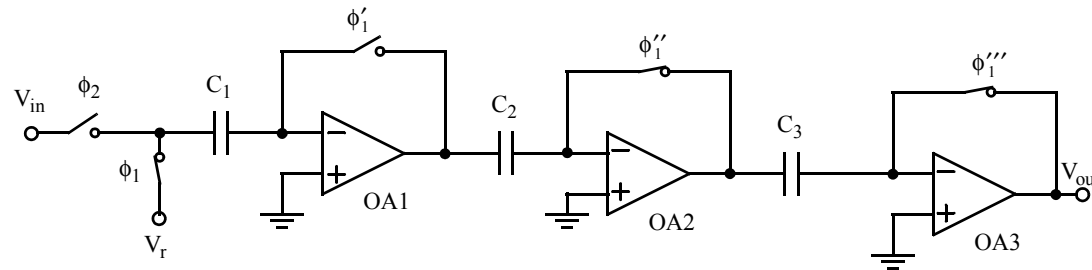

- [Poujois, 78] [Vittoz, 85]
- Clock feedthrough stored on coupling caps
- Used together with fully-diff design




Multi-Stage Comparator

 

- When ϕ'_1 goes low, charge OA1 output glitches but recovers
- OA1 input side goes negative causing OA1 output to go positive
- Since OA2 still being reset, error stored on C2



Latched Comparators

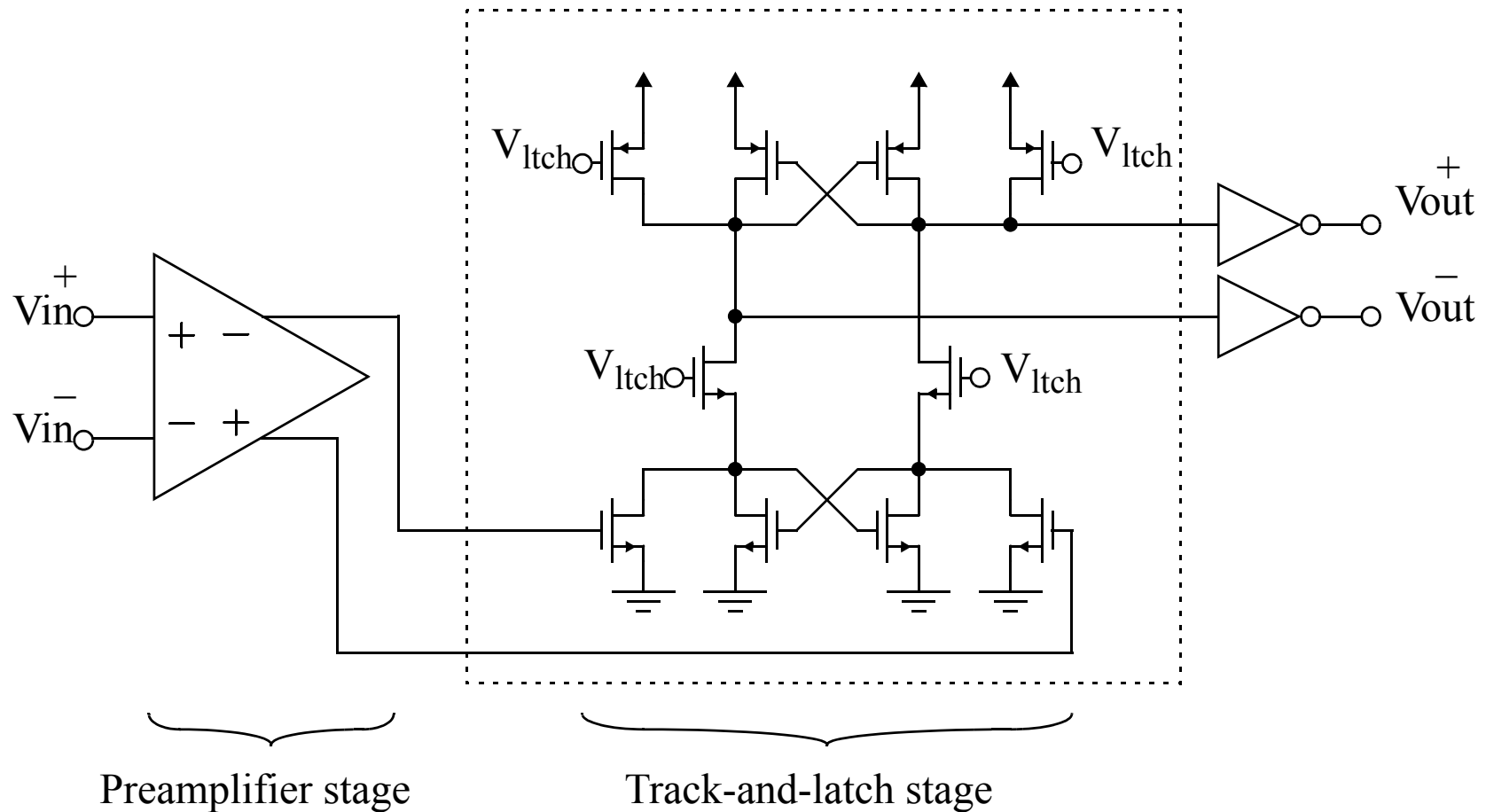

- 1 or 2 stages of preamp followed by track-and-latch




Latched Comparators

- Preamp used to improve resolution and reduce kickback
- Kickback result of charge transfer to inputs when going from track to latch mode
- Use preamp and match input impedances
- Preamp and track both have gain
- Positive feedback regenerates signal to logic levels
- Hysteresis effects reduced by setting internal nodes to known values each switching interval
- Known values likely setting latch to its trip point



Example CMOS Comparator

- [Song, 90]

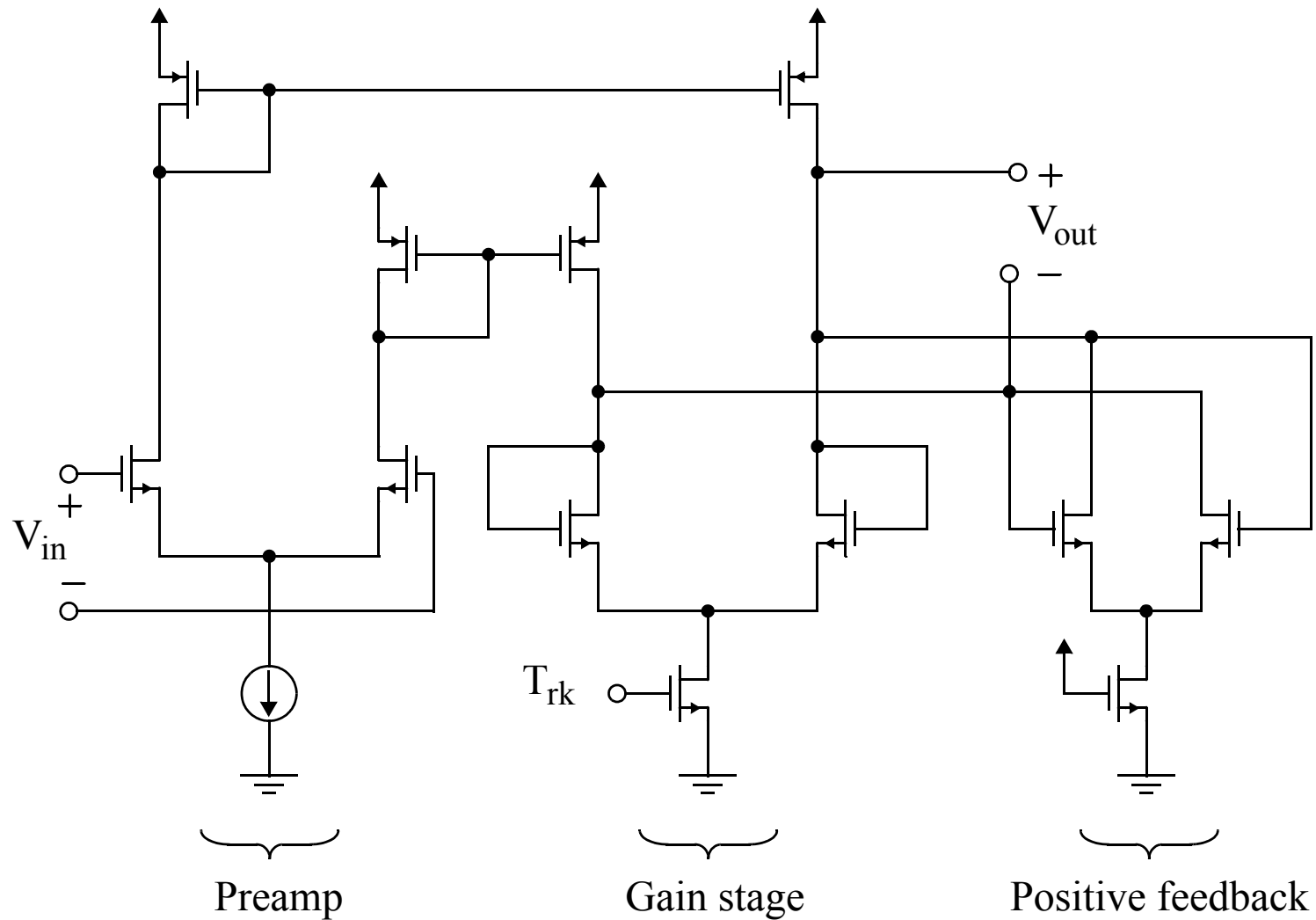

Example CMOS Comparator

- [Norsworthy, 89]

