

# **Basic Opamp Design and Compensation**

*David Johns and Ken Martin*  
*University of Toronto*  
*(johns@eecg.toronto.edu)*  
*(martin@eecg.toronto.edu)*



University of Toronto

slide 1 of 37

# Transistor Model Summary

## General Constants

Transistor charge —  $q = 1.602 \times 10^{-19} \text{ C}$

Boltzman constant —  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$

Intrinsic silicon carrier concentration (300 K)—  $n_i = 1.1 \times 10^{16} \text{ carriers/m}^3$

Relative permittivity of oxide —  $K_{ox} \cong 3.9$

Relative permittivity of silicon —  $K_s \cong 11.8$

## MOS Transistor Parameters

Electron mobility (typical) —  $\mu_n = 0.05 \text{ m}^2/\text{V} \cdot \text{s}$

Hole mobility (typical) —  $\mu_p = 0.02 \text{ m}^2/\text{V} \cdot \text{s}$

Oxide thickness (typical) —  $t_{ox} = 0.02 \text{ } \mu\text{m}$



## Transistor Model Summary

Gate capacitance per unit area —  $C_{ox} = \frac{K_{ox}\epsilon_o}{t_{ox}} \approx 1.9 \times 10^{-3} \text{ pF}/(\mu\text{m})^2$

Device parameters (typ) —  $\mu_n C_{ox} = 90 \text{ } \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 30 \text{ } \mu\text{A}/\text{V}^2$

Threshold voltages (typical) —  $V_{tn} = 0.8 \text{ V}$ ,  $V_{tp} = -0.9 \text{ V}$

Threshold voltage adjustment —  $V_{tn} = V_{tn-0} + \gamma(\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F})$

Body effect parameter (typical) —  $\gamma = 0.5 \text{ V}^{1/2}$

Fermi potential difference (typical) —  $\phi_F = 0.35 \text{ V}$


**Effective Gate-Source Voltage,  $V_{eff}$**

*Effective gate-source voltage* —  $V_{eff} \equiv V_{GS} - V_{tn}$


 
# Triode and Active Regions

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



- Cutoff Region:  $V_{GS} < V_{tn}$
- Triode Region:  $V_{GS} > V_{tn}$  ,  $V_{DS} \leq V_{eff}$
- Active Region:  $V_{GS} > V_{tn}$  ,  $V_{DS} \geq V_{eff}$




# MOS Triode Equations

Region of operation —  $V_{GS} > V_{tn}$  ,  $V_{DS} \leq V_{eff}$

Drain current — 
$$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right) \left[ (V_{GS} - V_{tn}) V_{DS} - 1.7 \frac{V_{DS}^2}{2} \right]$$

 1.7 typical term is due to body effect along channel

Small-Signal Model in Triode Region ( for  $V_{DS} \ll V_{eff}$  )



$$r_{ds} = \frac{1}{\mu_n C_{ox} \left( \frac{W}{L} \right) V_{eff}}$$



## MOS Active (or Pinch-Off) Equations

Region of operation —  $V_{GS} > V_{tn}$  ,  $V_{DS} \geq V_{eff}$

Drain current —  $I_D = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right) (V_{GS} - V_{tn})^2 [1 + \lambda(V_{DS} - V_{eff})]$

Output impedance constant —  $\lambda \propto \frac{1}{L \sqrt{V_{DG} + V_{tn} + 0.9}}$

0.9 term is due to built-in junction potential


Effective gate-source voltage —  $V_{eff} = V_{GS} - V_{tn} = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}}$

(ignoring output impedance)



# MOS Active Equations

## Small-Signal Model (Active Region)

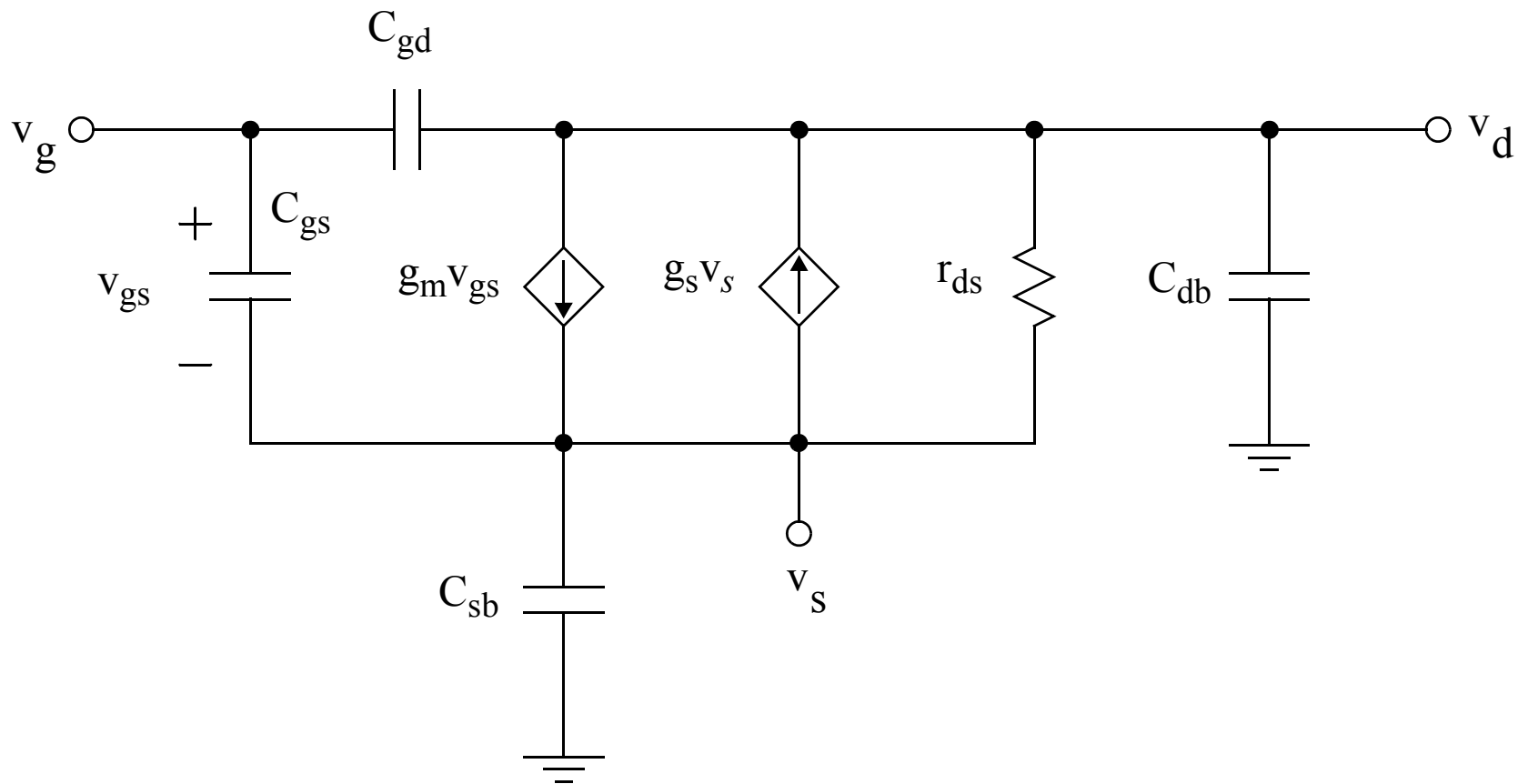

## MOS Active Equations

Transconductance —  $g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) V_{eff}$

Transconductance —  $g_m = \sqrt{2\mu_n C_{ox} (W/L) I_D}$

Transconductance —  $g_m = \frac{2I_D}{V_{eff}}$

Body effect transconductance —  $g_s = \frac{\gamma g_m}{2\sqrt{V_{SB} + |2\phi_F|}}$

Body effect transconductance (typical) —  $g_s \cong 0.2g_m$

Output impedance —  $r_{ds} = \frac{1}{\lambda I_D}$


Output impedance —  $r_{ds} \approx \alpha \frac{L}{I_D} \sqrt{V_{DG} + V_{tn}}$  where  $\alpha = 5 \times 10^6 \sqrt{V}/m$





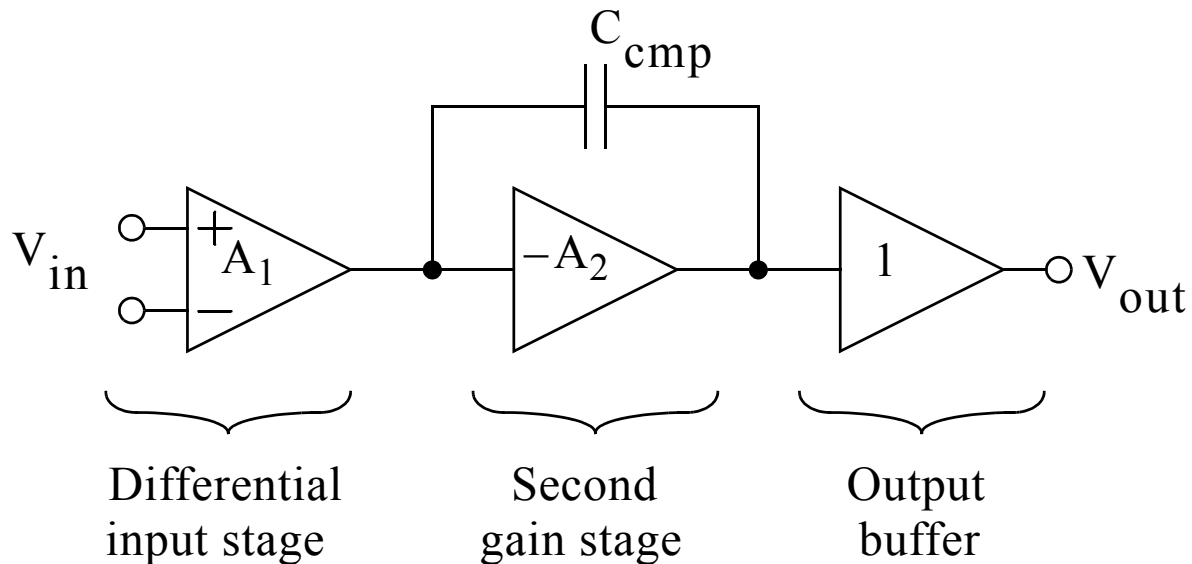
## Two-Stage CMOS Opamp

- Useful for describing many opamp design concepts
- Still used for low voltage applications



# Two-Stage CMOS Opamp

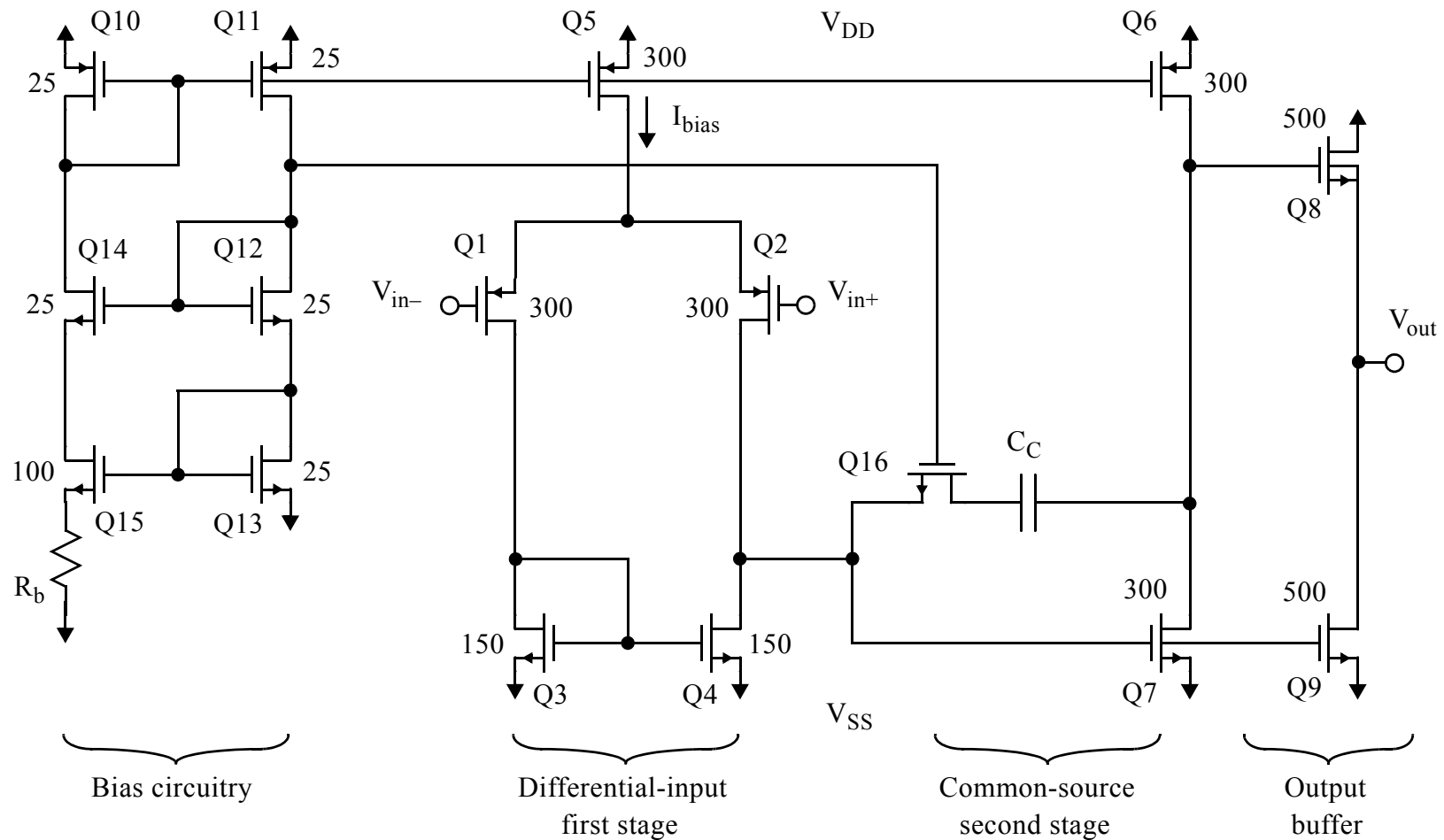

all transistor lengths = 1.6  $\mu\text{m}$



## Opamp Gain

- 3rd stage NOT included if driving capacitive loads
- Typical gains of 50-100 for each of stage 1 and 2

### First Stage

- Differential to single-ended

$$A_{v1} = g_{m1}(r_{ds2} \parallel r_{ds4}) \quad (1)$$

$$g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 \frac{I_{bias}}{2}} \quad (2)$$

### Second Stage

- Common-source gain

$$A_{v2} = -g_{m7}(r_{ds6} \parallel r_{ds7}) \quad (3)$$



# Opamp Gain

## Third Stage


- Source follower
- Typical gain — slightly less than 1 (say 0.9)
- Note —  $g_{ds} = 1/r_{ds}$  and  $G_L = 1/R_L$

$$A_{v3} \cong \frac{g_{m8}}{G_L + g_{m8} + g_{s8} + g_{ds8} + g_{ds9}} \quad (4)$$

- $g_s$  is body-effect conductance and equals zero if source tied to substrate
- $G_L$  is the load conductance at output



## Frequency Response

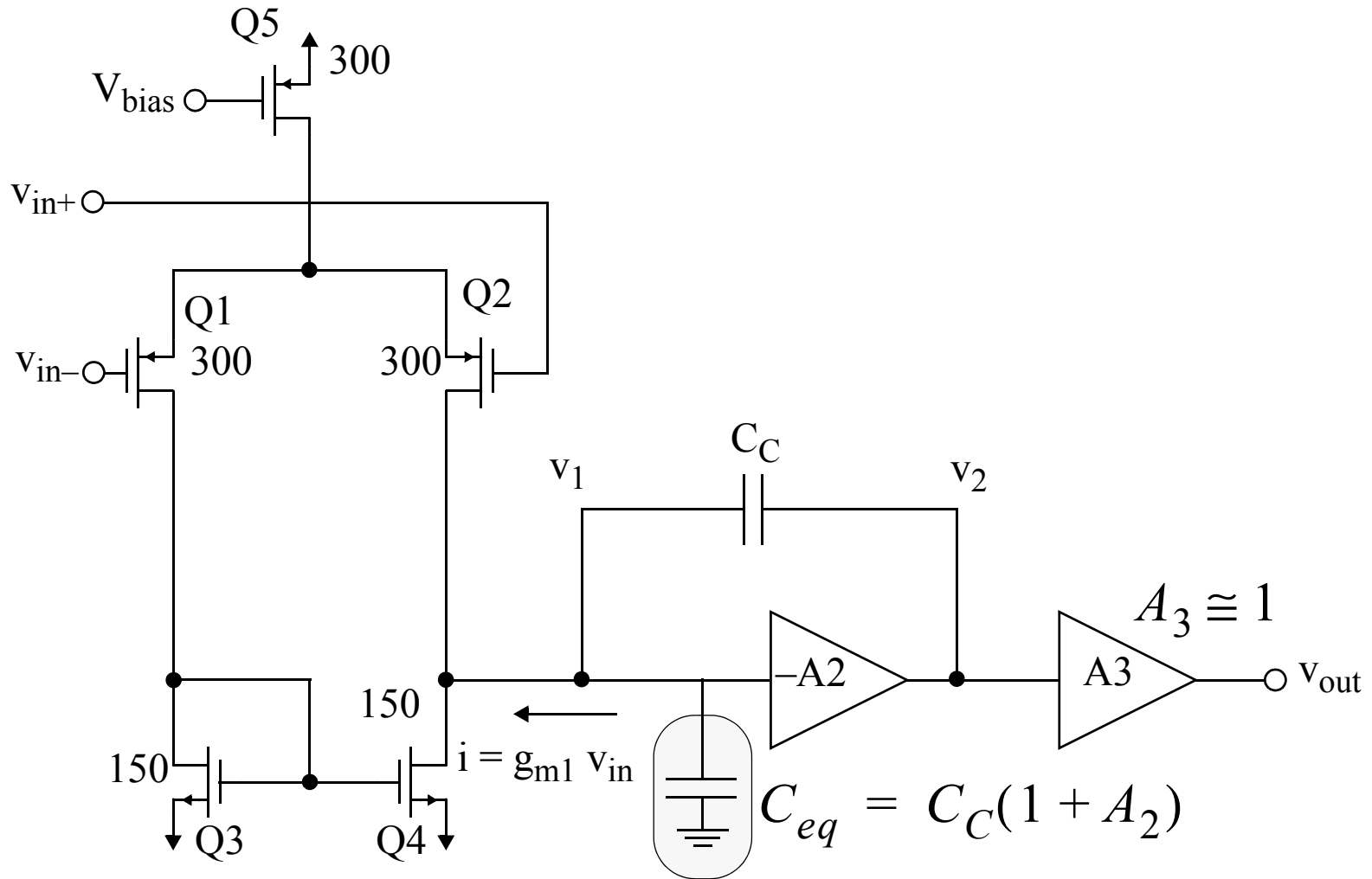

## Frequency Response

- $C_C$  dominates at all freq except unity-gain freq
- Ignore  $Q_{16}$  for now (used for lead compensation)
- Miller effect results in

$$(C_{eq} = C_C(1 + A_2)) \cong C_C A_2 \quad (5)$$

- At midband freq

$$A_1 = g_{m1} Z_{out} = g_{m1} / (s C_C A_2) \quad (6)$$

- Overall gain (assuming  $A_3 \cong 1$ )

$$A_v(s) = A_2 A_1 = g_{m1} / (s C_C) \quad (7)$$


resulting in a unity-gain frequency of

$$\omega_{ta} = g_{m1} / C_C \quad (8)$$



# Freq Response

- First-order model

 

## Slew Rate

- Max rate output changes when input signal large
- All Q5 bias current goes into Q1 or Q2

$$SR \equiv \left. \frac{dv_{out}}{dt} \right|_{\max} = \frac{I_{C_C}|_{\max}}{C_C} = \frac{I_{D5}}{C_C} = \frac{2I_{D1}}{C_C} \quad (9)$$

$I_{D1}$  is nominal bias current of input transistors

- Using  $C_C = g_{m1}/\omega_{ta}$  and  $g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}$





## Slew Rate

$$SR = \frac{2I_{D1}}{\sqrt{2\mu_p C_{ox}(W/L)_1 I_{D1}}} \omega_{ta} = V_{eff1} \omega_{ta} \quad (10)$$

where  $V_{eff1} = \sqrt{\frac{2I_{D1}}{\mu_p C_{ox}(W/L)_1}}$

- Normally, little control over  $\omega_{ta}$  for a given power diss
- Increase slew-rate by increasing  $V_{eff1}$
- This is one of main reasons for using p-channel input stage — higher slew-rate



## Systematic Offset Voltage

- To ensure inherent offset voltage does not exist, design should satisfy

$$\frac{(W/L)_7}{(W/L)_4} = 2 \frac{(W/L)_6}{(W/L)_5} \quad (11)$$

- Ensures nominal current through Q7 equals Q6
- Found by noting

$$I_{D5} = 2I_{D3} = 2I_{D4} \quad (12)$$

and

$$V_{GS7} = V_{DS3} = V_{GS4} \quad (13)$$

then setting  $I_{D7} = I_{D6}$



## N-Channel or P-Channel Input Stage

- Can also build complement opamp with an n-channel input diff pair and second-stage p-channel stage

### P-channel Advantages


- Higher slew-rate — For fixed bias current,  $V_{eff}$  is larger (assuming similar widths used for max gain)
- Higher unity-gain freq — higher transconductance of second stage which is proportional to unity-gain freq
- Lower 1/f noise — holes less likely to be trapped — p-channel transistors have lower 1/f noise

### N-channel Advantage


- Lower thermal noise — thermal noise is lowered by high transconductance of first stage



# Opamp Compensation

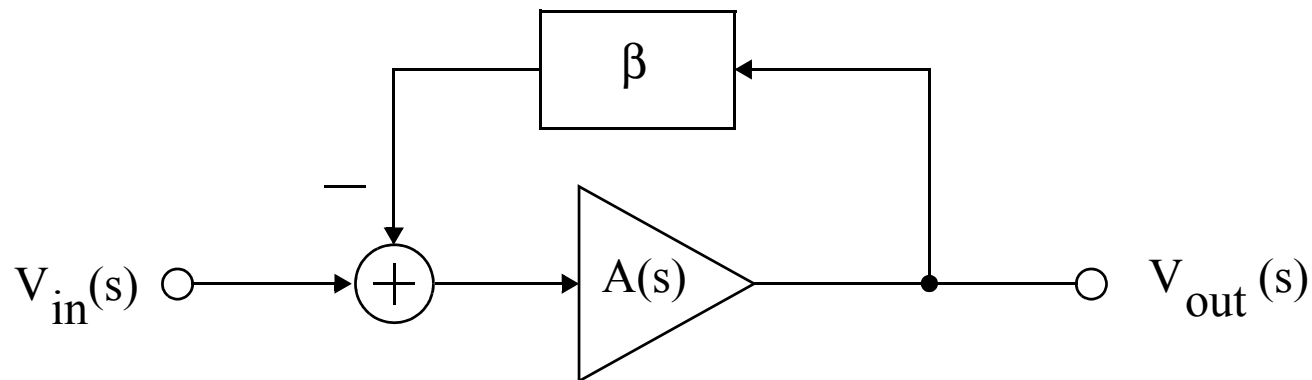

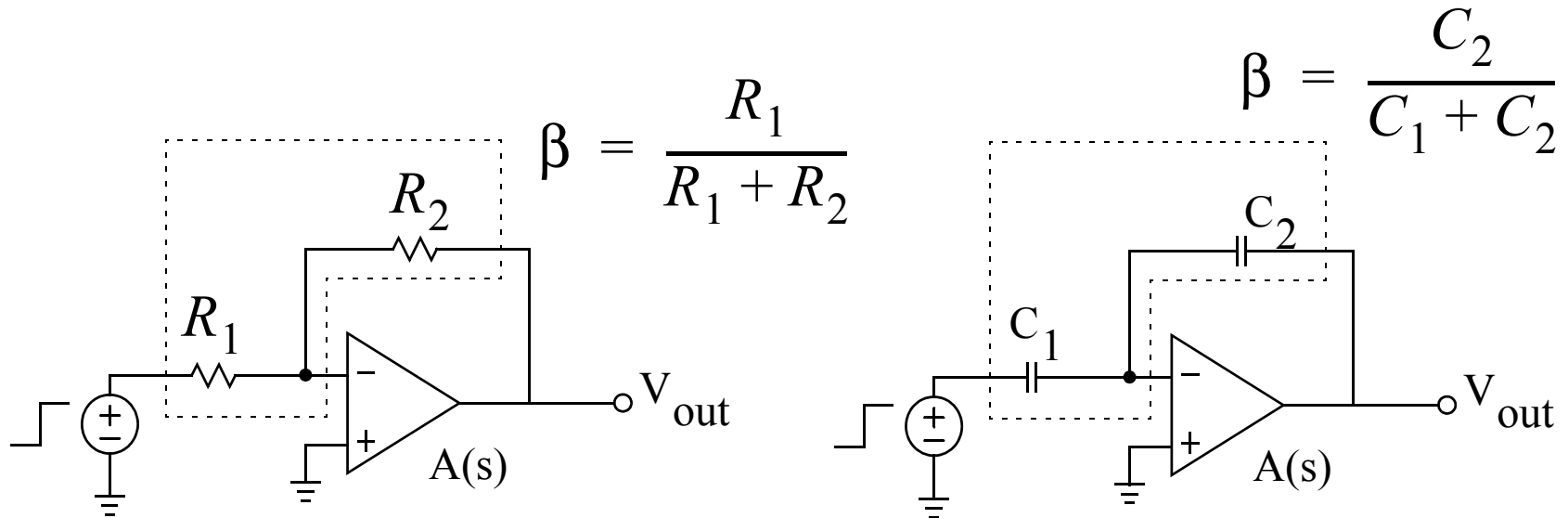- Feedback circuit  $\beta$  assumed to be freq independent



## General Opamp Compensation

- Model  $A(s)$  by

$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{eq})} \quad (14)$$

- $\omega_{p1}$  — first dominant-pole frequency
- $\omega_{eq}$  — pole frequency modelling higher-freq poles.
- $\omega_{eq}$  found from simulation — frequency with  $-135^\circ$  phase shift ( $-90^\circ$  due to  $\omega_{p1}$  and another  $-45^\circ$  due to higher-frequency poles and zeros)
- Closed loop gain given by

$$A_{CL}(s) = \frac{A(s)}{1 + \beta A(s)} \quad (15)$$



## General Opamp Compensation

$$A_{CL}(s) = \frac{A_{CL0}}{1 + \frac{s(1/\omega_{p1} + 1/\omega_{eq})}{1 + \beta A_0} + \frac{s^2}{(1 + \beta A_0)(\omega_{p1}\omega_{eq})}} \quad (16)$$

where  $A_{CL0} = A_0/(1 + \beta A_0) \cong 1/\beta$

- Compare to a general second-order equation

$$H_2(s) = \frac{K\omega_0^2}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2} = \frac{K}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}} \quad (17)$$

$$\% \text{ overshoot} = 100e^{\frac{-\pi}{\sqrt{4Q^2 - 1}}} \quad (18)$$



## General Opamp Compensation

- Equating 2 equations above results in

$$\omega_0 = \sqrt{(1 + \beta A_0)(\omega_{p1} \omega_{eq})} \cong \sqrt{\beta A_0 \omega_{p1} \omega_{eq}} \quad (19)$$

$$Q = \frac{\sqrt{(1 + \beta A_0)/\omega_{p1} \omega_{eq}}}{1/\omega_{p1} + 1/\omega_{eq}} \cong \sqrt{\frac{\beta A_0 \omega_{p1}}{\omega_{eq}}} \quad (20)$$

- To find relationship between  $Q$  and phase-margin we look at the loop gain,  $LG(s)$

$$LG(s) = \beta A(s) = \frac{\beta A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{eq})} \quad (21)$$

- To find a relationship for the loop-gain unity-gain freq

$$|LG(j\omega_t)| = 1 \quad (22)$$



## General Opamp Compensation

- And rearrange and use approx that  $\omega_t \gg \omega_{p1}$

$$\frac{\beta A_0 \omega_{p1}}{\omega_{eq}} = \left( \frac{\omega_t}{\omega_{eq}} \right) \sqrt{1 + \left( \frac{\omega_t}{\omega_{eq}} \right)^2} \quad (23)$$

so that


$$Q = \sqrt{\left( \frac{\omega_t}{\omega_{eq}} \right) \sqrt{1 + \left( \frac{\omega_t}{\omega_{eq}} \right)^2}} \quad (24)$$

- Would also like to relate ***phase-margin*** with  $\omega_t/\omega_{eq}$  and Q factor





# Phase-Margin

 

## General Opamp Compensation

$$PM = \angle LG(j\omega_t) - (-180^\circ) = 90^\circ - \tan^{-1}(\omega_t/\omega_{eq}) \quad (25)$$

where  $\omega_{p1}$  adds  $90^\circ$  phase shift

$$\omega_t/\omega_{eq} = \tan(90^\circ - PM) \quad (26)$$

- If non-dominant poles remains unchanged,  $\omega_t$  independent of  $\beta$  for optimally compensated circuit!


---

PM (Phase margin)	$\omega_t/\omega_{eq}$	Q factor	Percentage overshoot for a step input
$55^\circ$	0.700	0.925	13.3%
$60^\circ$	0.580	0.817	8.7%
$65^\circ$	0.470	0.717	4.7%
$70^\circ$	0.360	0.622	1.4%
$75^\circ$	0.270	0.527	0.008%


---



# Compensating the 2-Stage Opamp

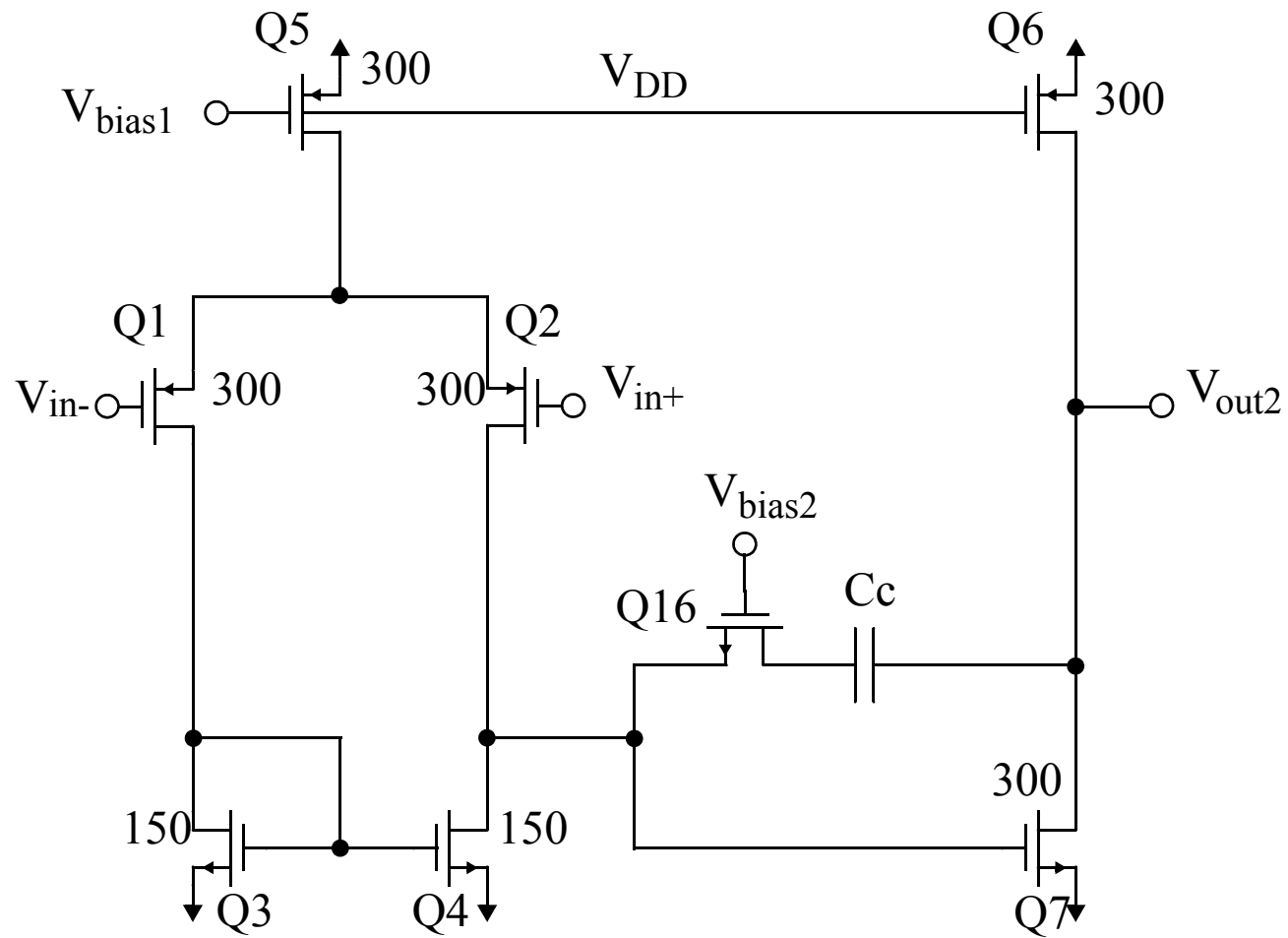

## Compensating the 2-Stage Opamp

 

- $Q_{16}$  has  $V_{DS16} = 0$  and is hard in the triode region.

$$R_C = r_{ds16} = \frac{1}{\mu_n C_{ox} \left( \frac{W}{L} \right)_{16} V_{eff16}} \quad (27)$$

- Small signal analysis — without  $R_C$  present, right-half plane zero occurs and worsens phase-margin



## Compensating the 2-Stage Opamp

- Including  $R_C$  (through Q16) places zero at

$$\omega_z = \frac{-1}{C_C(1/g_{m7} - R_C)} \quad (28)$$

- Zero moved to left-half plane to aid compensation
- Good practical choice is

$$\omega_z = 1.2\omega_t \quad (29)$$

satisfied by letting

$$R_C \cong \frac{1}{1.2g_{m1}} \quad (30)$$

since  $\omega_t \cong g_{m1}/C_C$  and  $\omega_z \cong 1/(R_C C_C)$  if  $R_C \gg 1/g_{m7}$



## Design Procedure

### 1) Find $C_C$ with $R_c=0$ for a $55^\circ$ phase margin

- Arbitrarily choose  $C'_C \cong 5$  pF and set  $R_C = 0$
- Using SPICE, find frequency  $\omega_t$  where a  $-125^\circ$  phase shift exists, define gain as  $A'$
- Choose new  $C_C$  so  $\omega_t$  becomes unity-gain frequency of the loop gain — results in a  $55^\circ$  phase margin.
- Achieved by setting  $C_C = C'_C A'$
- Might need to iterate on  $C_C$  a couple of times using SPICE



## Design Procedure

**2) Choose  $R_C$  according to**

$$R_C = \frac{1}{1.2\omega_t C_C} \quad (31)$$

— Increases  $\omega_t$  by about 20 percent, leaving zero near final  $\omega_t$

— Check that gain continues to decrease at frequencies above the new  $\omega_t$

**3) If phase margin not adequate, increase  $C_C$  while leaving  $R_C$  constant**



## Design Procedure

### 4) Replace $R_C$ by a transistor

$$R_C = r_{ds16} = \frac{1}{\mu_n C_{ox} \left( \frac{W}{L} \right)_{16} V_{eff16}} \quad (32)$$

— SPICE can be used again to fine-tune the device dimensions to optimize phase margin





## Process and Temperature Independence

- Can show non-dominant pole roughly given by

$$\omega_{p2} \cong \frac{g_{m7}}{C_1 + C_2} \quad (33)$$

- Recall zero given by

$$\omega_z = \frac{-1}{C_C(1/g_{m7} - R_C)} \quad (34)$$

- If  $R_C$  tracks inverse of  $g_{m7}$  then zero will track  $\omega_{p2}$


$$R_C = r_{ds16} = \frac{1}{\mu_n C_{ox}(W/L)_{16} V_{eff16}} \quad (35)$$

$$g_{m7} = \mu_n C_{ox}(W/L)_7 V_{eff7} \quad (36)$$


 
## Process and Temperature Independence

- Need to ensure  $V_{\text{eff}16}/V_{\text{eff}7}$  independent of process and temperature variations



- First set  $V_{\text{eff}13} = V_{\text{eff}7}$  which makes  $V_a = V_b$



## Process and Temperature Independence

$$\sqrt{\frac{2I_{D7}}{\mu_n C_{ox}(W/L)_7}} = \sqrt{\frac{2I_{D13}}{\mu_n C_{ox}(W/L)_{13}}} \quad (37)$$

$$\frac{I_{D7}}{I_{D13}} = \frac{(W/L)_7}{(W/L)_{13}} \quad (38)$$


- Since  $V_a = V_b$  and gates of Q12 and Q16 same

$$V_{eff12} = V_{eff16} \quad (39)$$

$$\frac{V_{eff7}}{V_{eff16}} = \frac{V_{eff13}}{V_{eff12}} = \frac{\sqrt{\frac{2I_{D13}}{\mu_n C_{ox}(W/L)_{13}}}}{\sqrt{\frac{2I_{D12}}{\mu_n C_{ox}(W/L)_{12}}}} = \sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} \quad (40)$$



# Stable Transconductance Biasing

 

- Can bias on-chip  $g_m$  to a resistor

$$V_{GS13} = V_{GS15} + I_{D15}R_B \quad (41)$$

$$\sqrt{\frac{2I_{D13}}{\mu_n C_{ox}(W/L)_{13}}} = \sqrt{\frac{2I_{D15}}{\mu_n C_{ox}(W/L)_{15}}} + I_{D15}R_B \quad (42)$$

- But  $I_{D13} = I_{D15}$  and rearrange

$$\frac{2}{\sqrt{2\mu_n C_{ox}(W/L)_{13}I_{D13}}} \left[ 1 - \sqrt{\frac{W/L_{13}}{W/L_{15}}} \right] = R_B \quad (43)$$

- Recall  $g_{m13} = \sqrt{2\mu_n C_{ox}(W/L)_{13}I_{D13}}$

$$g_{m13} = 2 \left[ 1 - \sqrt{\frac{(W/L)_{13}}{(W/L)_{15}}} \right] / R_B \quad (44)$$



## Stable Transconductance Biasing

- Transconductance of  $Q_{13}$  determined by geometric ratios only
- Independent of power-supply voltages, process parameters, temperature, etc.
- For special case  $(W/L)_{15} = 4(W/L)_{13}$

$$g_{m13} = \frac{1}{R_B} \quad (45)$$

- Note that high-temp will decrease mobility and hence increase effective gate-source voltages
- Roughly 25% increase for 100 degree increase
- Requires a start-up circuit (might have all 0 currents)

