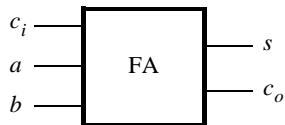



a) Full adder circuit



b) Full adder symbol

b	a	c_i	$c_o \ s$	
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

c) Full adder truth table

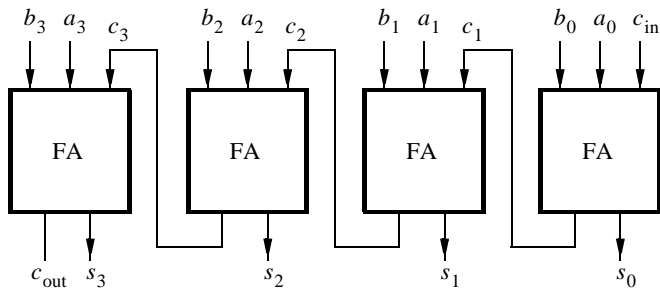

d) Four-bit ripple-carry adder circuit