

Laboratory Exercise 5

Clocks and Counters

The purpose of this exercise is to learn how to create counters and to be able to modify the speed of the 50MHz clock to be able to control circuits you build.

Preparation Before the Lab

You are required to complete Parts I to III of the lab by writing and testing Verilog code and compiling it with Quartus II. Show your Verilog, simulations and schematics for Parts I to III to the teaching assistants. You must simulate your circuit with ModelSim (using reasonable test vectors using the format shown in the previous lab).

In-lab Work

You are required to implement and test all of Parts I to III of the lab. You need to demonstrate both parts to the teaching assistants.

Part I

Consider the circuit in Figure 1. It is a 4-bit synchronous counter which uses four T-type flip-flops. The counter increments its value on each positive edge of the clock if the *Enable* signal is asserted. The counter is reset to 0 by setting the *Clear* signal low – it is an active-low asynchronous clear. You are to implement an 8-bit counter of this type.

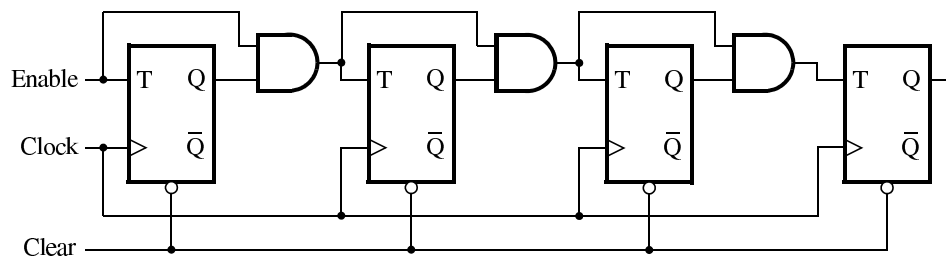


Figure 1: A 4-bit counter.

Perform the following steps:

1. Write a Verilog file that defines an 8-bit counter by using the structure depicted in Figure 1. Your code should include a T flip-flop module that is instantiated 8 times to create the counter (i.e. structural Verilog). Compile the circuit. How many logic elements (LEs) are used to implement your circuit? What is the maximum frequency, F_{max} , at which your circuit can be operated? (Use TimeQuest in Quartus to determine the maximum frequency F_{max} .)
2. Simulate your circuit to verify its correctness, draw the circuit and have both ready as prelab.
3. Augment your Verilog file to use the pushbutton KEY_0 as the *Clock* input, switches SW_1 and SW_0 as *Enable* and *Clear* inputs, and 7-segment displays $HEX0$ and $HEX1$ to display the hexadecimal count as your circuit operates. Make the necessary pin assignments needed to implement the circuit on the DE1-SoC board, and compile the circuit. For this part, you should re-use the hexadecimal-to-7-segment display decoder that you created for Lab 2.

- Download your circuit into the FPGA chip and test its functionality by operating the switches.
- Use the Quartus II RTL Viewer to see how Quartus II software synthesized your circuit. What are the differences in comparison with Figure 1?

Part II

Another way to specify a counter is by using a register and adding 1 to its value. This can be accomplished using the following Verilog statement:

$$Q \leq Q + 1;$$

Design and implement a circuit using the statement above that successively flashes the hexadecimal digits 0 through F on the 7-segment display *HEX0*. You will use two switches, SW_1 and SW_0 to determine the speed of flashing according to the following table:

SW[1]	SW[0]	Speed
0	0	Full
0	1	1 Hz
1	0	0.5 Hz
1	1	0.25 Hz

Full speed should use the 50-MHz clock signal provided on the DE1-SoC board. You must design a fully synchronous circuit, which means that every flip flop in your circuit should be clocked by the same 50 MHz clock signal. To derive the slower flashing rates you should use a counter, call it RateDivider, that is also clocked with the 50 MHz clock. The output of RateDivider can be used as part of a circuit to create pulses at the required rates. These pulses can be used to drive an *enable* signal on the counter, call it DisplayCounter, that is counting from 0 through F. Recall that an *enable* signal determines whether a flip flop, register, or counter will change on a clock pulse.

Perform the following steps.

- Write a Verilog file that realizes the behaviour described above. Your circuit should have the clock and the two switches as inputs.
- Simulate your circuit with ModelSim for a variety of input settings, ensuring the output waveforms are correct. You must show this to the TA as part of your prelab.
- Draw a schematic outlining the hierarchies you used and explain them to the TA as another part of your prelab.
- Compile the project.
- Download the compiled circuit into the FPGA chip. Test the functionality of the circuit.

Part III

In this part of the exercise you are to implement a Morse code encoder using a lookup table (hard coded multiplexer) (LUT) and a rate divider similar to Part II. The Morse code uses patterns of short and long pulses to represent a message. Each letter is represented as a sequence of dots (a short pulse), and dashes (a long pulse). For example, starting from A, eight letters of the alphabet have the following representation:

A	• —
B	— • • •
C	— • — •
D	— • •
E	•
F	• • — •
G	— — •
H	• • • •

Design and implement a Morse code encoder circuit a LUT and a rate divider. Your circuit should take as input one of the eight letters of the alphabet starting from A (as in the table above) and display the Morse code for it on a red LED, $LEDR_0$. Use switches SW_{2-0} and pushbuttons KEY_{1-0} as inputs. When a user presses KEY_1 , the circuit should display the Morse code for a letter specified by SW_{2-0} (000 for A, 001 for B, etc.), using 0.5-second pulses to represent dots, and 1.5-second pulses to represent dashes. The time between pulses is 0.5 seconds. Pushbutton KEY_0 should function as an asynchronous reset.

Hint: Since your minimum time is 0.5 second, set each 0 or 1 to be 0.5 seconds. This means that a 0 is a pause, a 1 is a dot, and 111 is a dash. Then read each 0 or 1 individually out of a shift register at 0.5 seconds per read.

Perform the following steps.

1. Write a Verilog file that realizes the behaviour described above.
2. Simulate your circuit with ModelSim for a variety of input settings, ensuring the output waveforms are correct. You must show this to the TA as part of your prelab.
3. Draw a schematic outlining the hierarchies you used and explain them to the TA as another part of your prelab.
4. Compile the project.
5. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit.