


**EUROPEAN
MICROWAVE
WEEK**
RAI Amsterdam
28 October – 2 November 2012
www.eumweek.com

**W04: Submillimetre-wave
Monolithic Integrated Circuits**

SiGe HBT Based S-MMICs

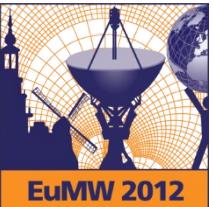Sorin P. Voinigescu
University of Toronto





Credits

Graduate students

- ◆ Yannis Sarkas
- ◆ Andreea Balteanu
- ◆ Alex Tomkins
- ◆ Eric Dacquay
- ◆ Katya Laskin

Collaborators

- ◆ Dr. Juergen Hasch
- ◆ Dr. Pascal Chevalier
- ◆ Prof. Thomas Zwick
- ◆ Mekdes Girma
- ◆ Stefan Beer

- NSERC, Robert Bosch GmbH for funding
- STMicroelectronics for chip donations
- Bernard Sautreuil and Patrick Cogez for technology access
- Jaro Pristupa and CMC for CAD and support

Outline



- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors

Applications


- Industrial range and Doppler sensors



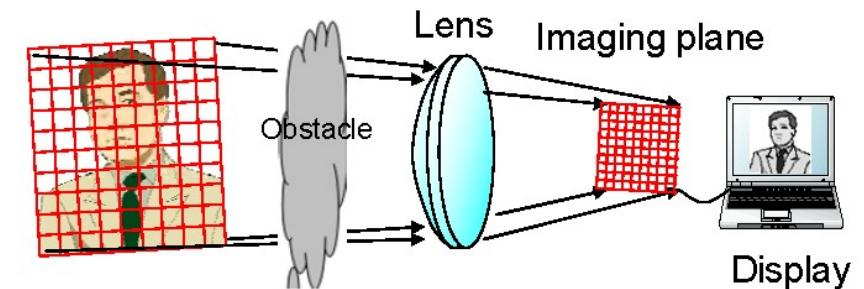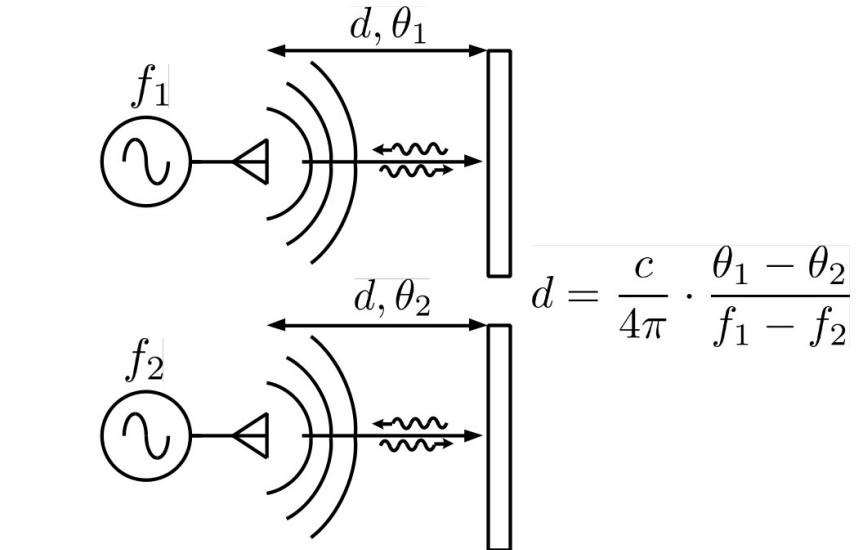- Active/passive imagers for security and remote sensing



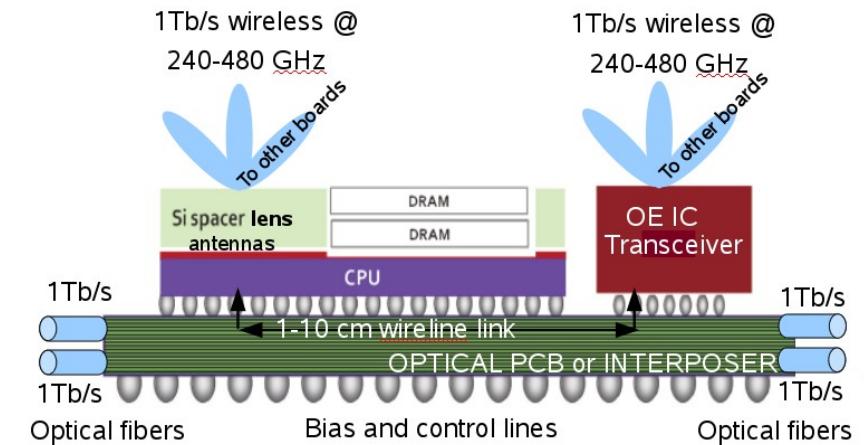- 100+Gb/s short-range reconfigurable wireless data transmission in the data center



Wish list for submillimeter radio/radar


- $P_{TX} = 10 \text{ dBm}$
- $PN < -90 \text{ dBc/Hz}$ in band, $<-140 \text{ dBc/Hz}$ beyond 50 MHz
- $NF < 12 \text{ dB}$
- $P_{DC} < 1\text{W}$
- $BW > 20\%$ (for passive imaging and 100+Gbs radio)
- QPSK, 16/64 QAM modulation schemes
- 50-100 Gb/s digital streams in TX
- 100 GS/s 8-10 bit ADC in receiver

Outline

- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors


STMicroelectronics' 130-nm SiGe BiCMOS

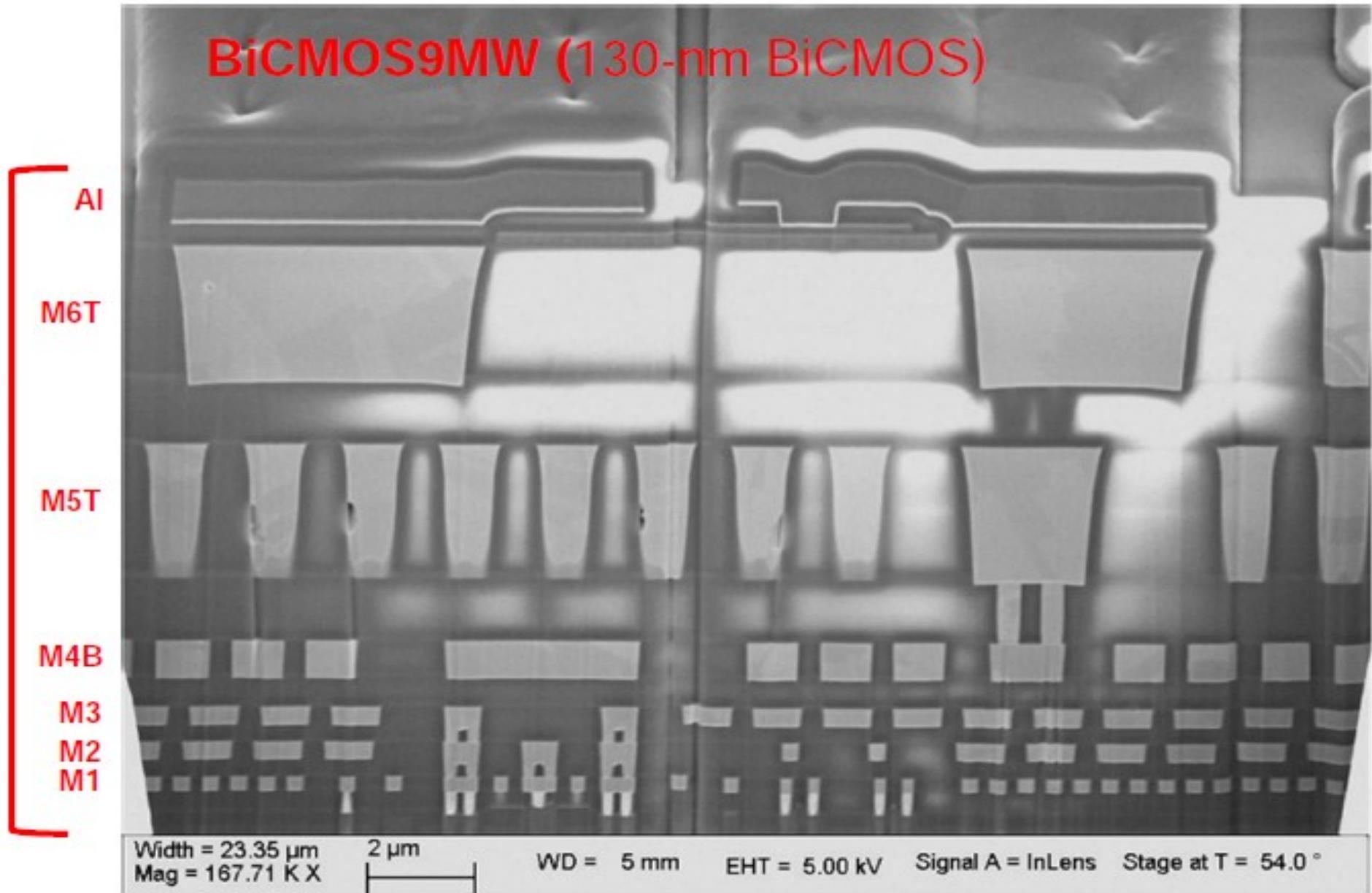6ML BEOL $\Rightarrow \alpha = 0.7$ dB/mm at 100 GHz
(Al+M6 with M1+M2 shield for $Z_C = 50 \Omega$)




[Pascal Chevalier, CSICS-2012]

CMOS, SiGe, ISS μ -strip lines: D-Band


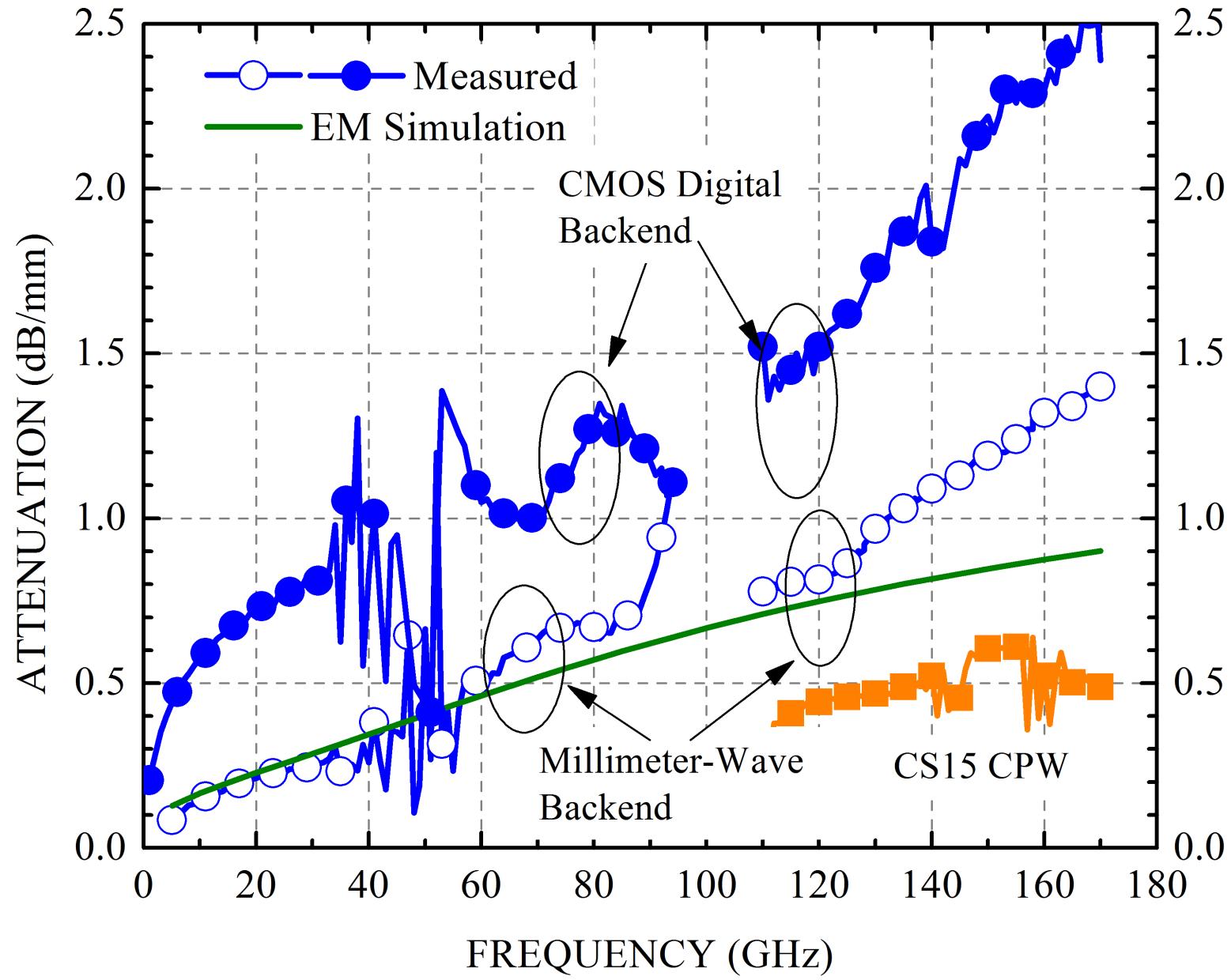


[Ken Yau, IEEE Micro Mag., Feb.-2012]


SiGe vs. ISS μ -strip lines: H-Band

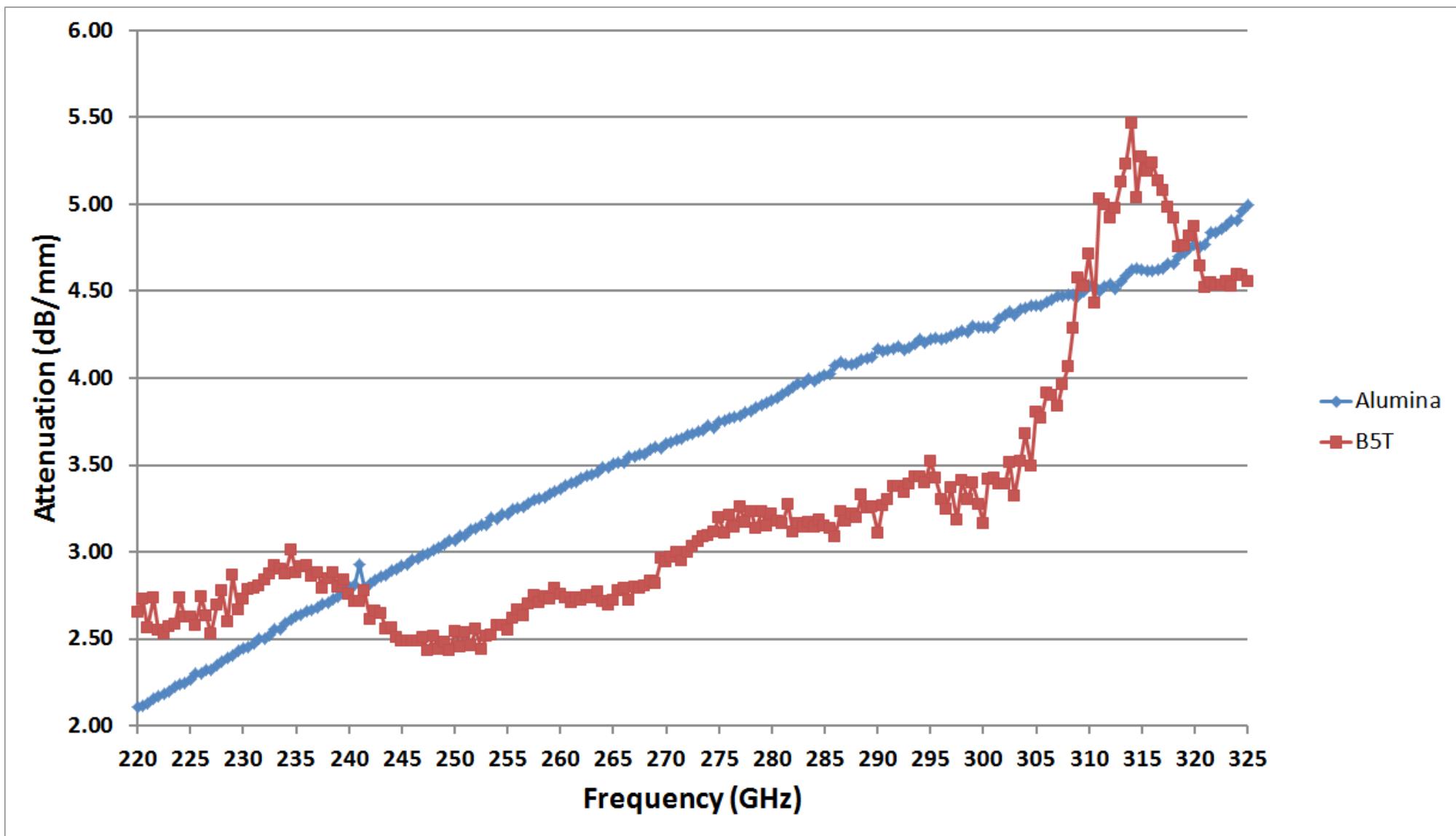

Si Transistor Performance at G-Band

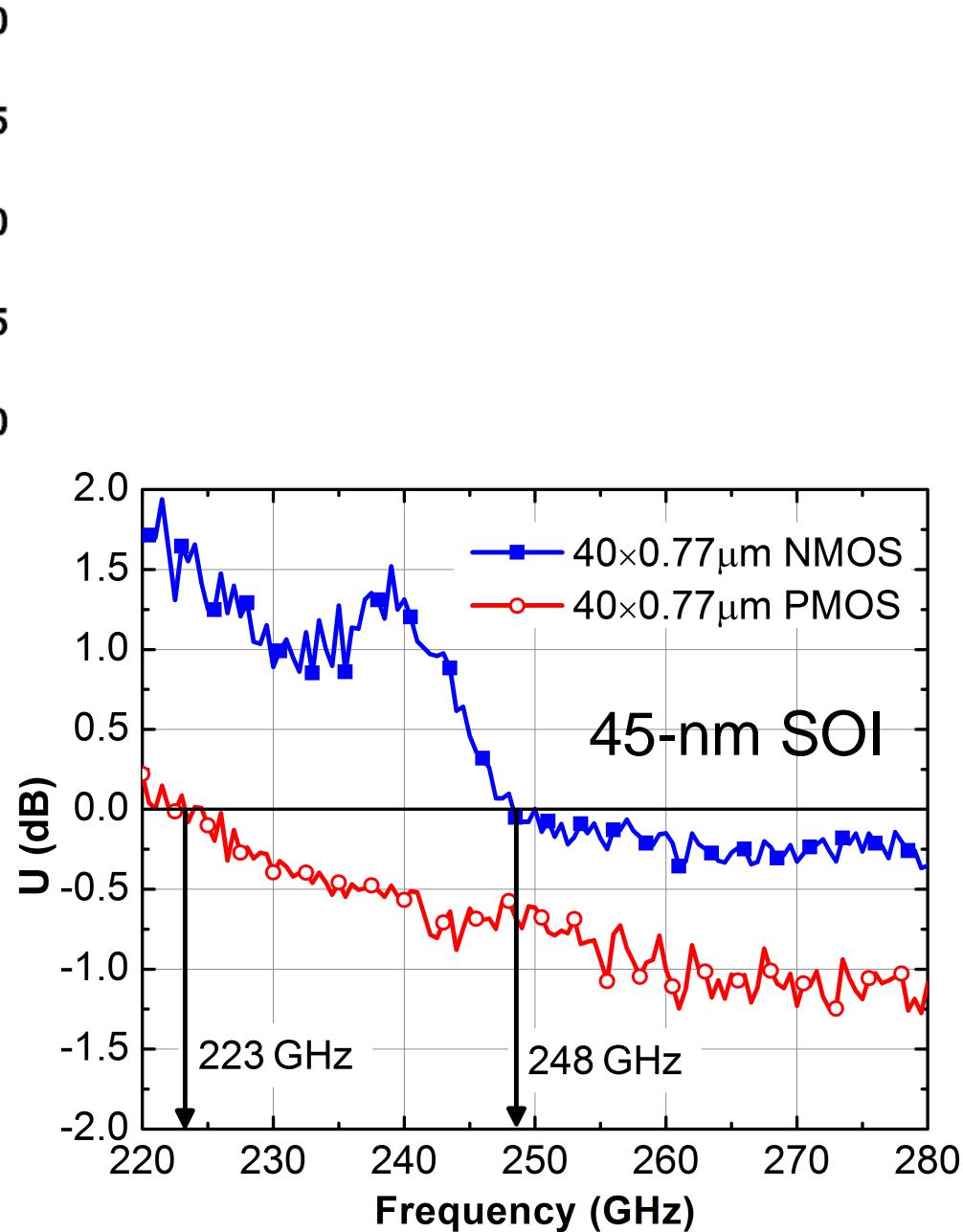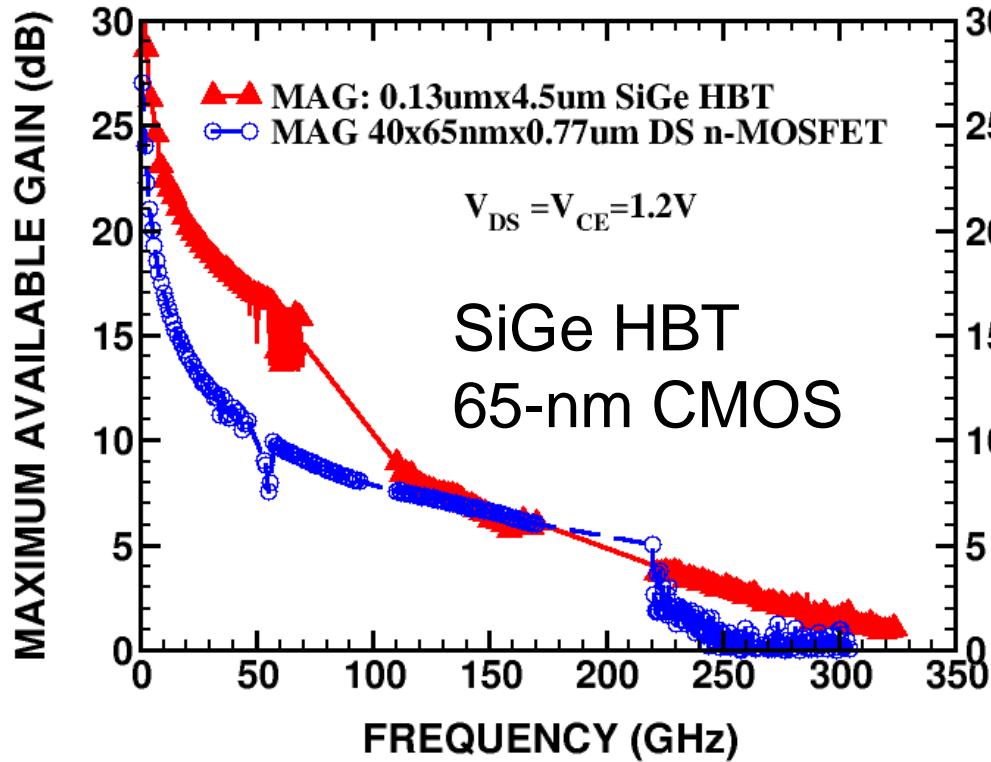


SiGe HBT: BC9MW vs. B5T

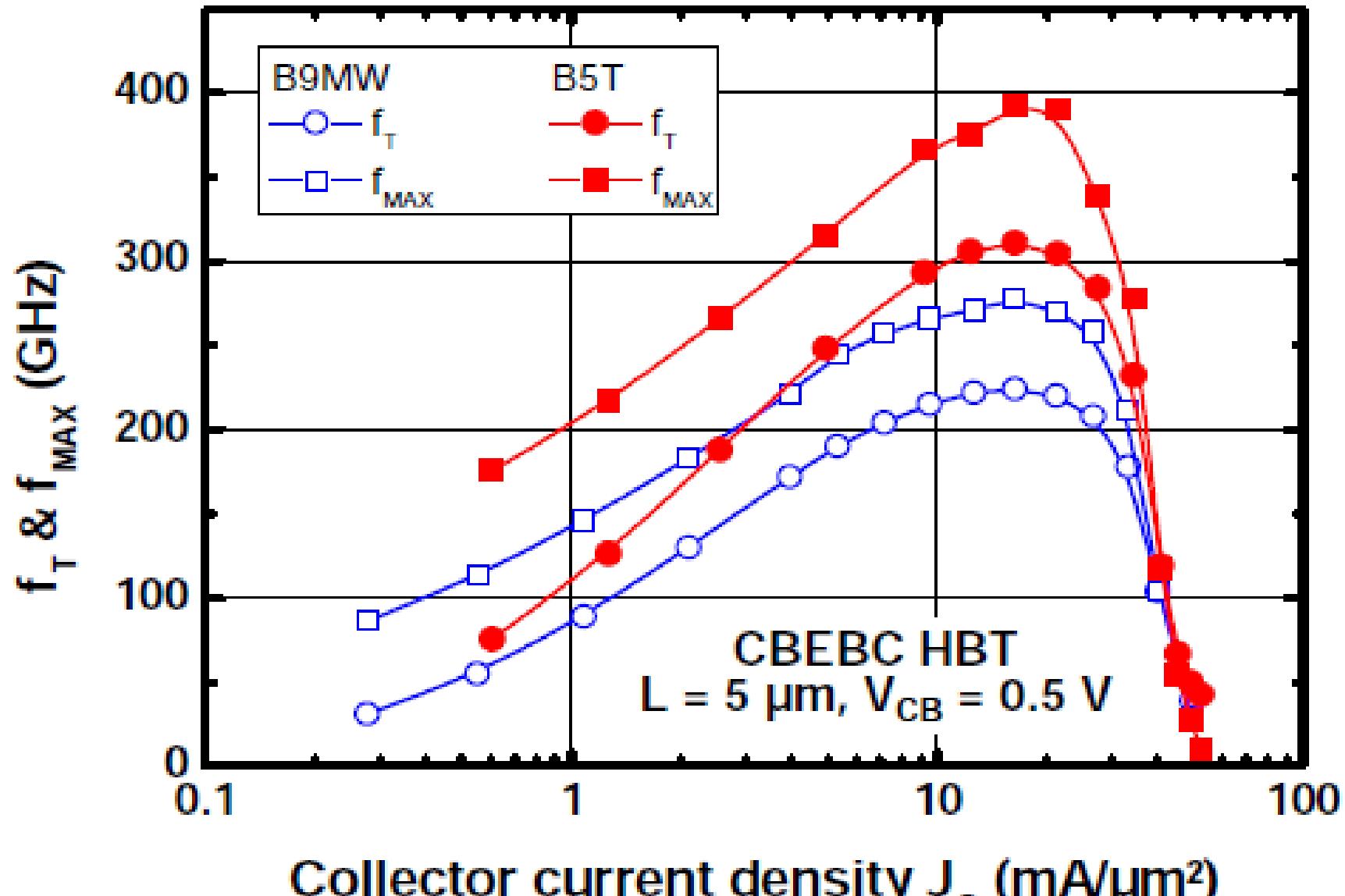

Outline

- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors

Dual Receive Channel Transceiver

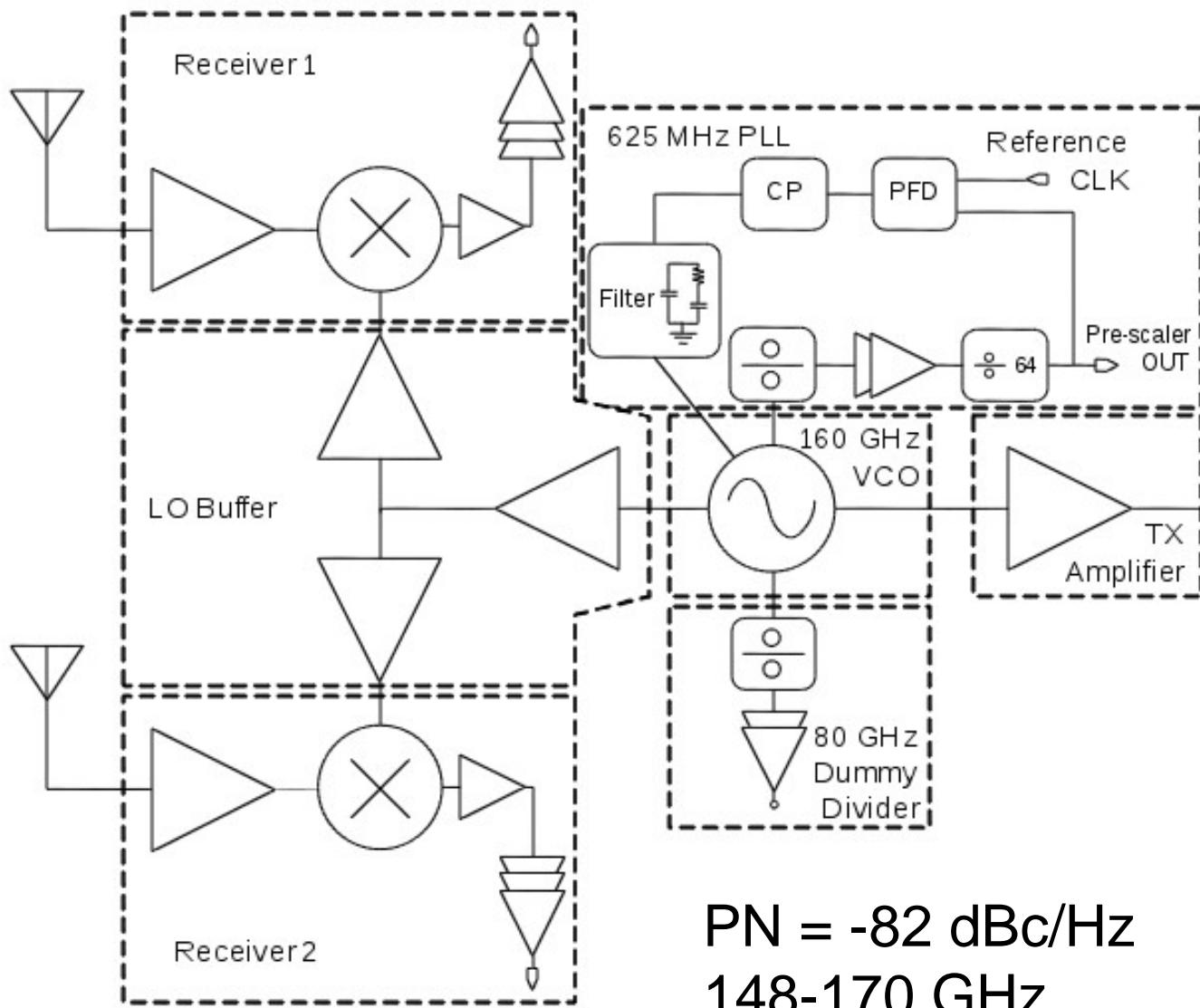

1.5/2.5/3/3.6V
 $P_D = 1.8 \text{ W}$


$P_{\text{out}} = 1 \text{ dBm}$

$\text{PN} = -82 \text{ dBc/Hz}$
148-170 GHz


RX Gain = 27 dB

NF = 12 dB

[I. Sarkas et al., MIKON-2012]

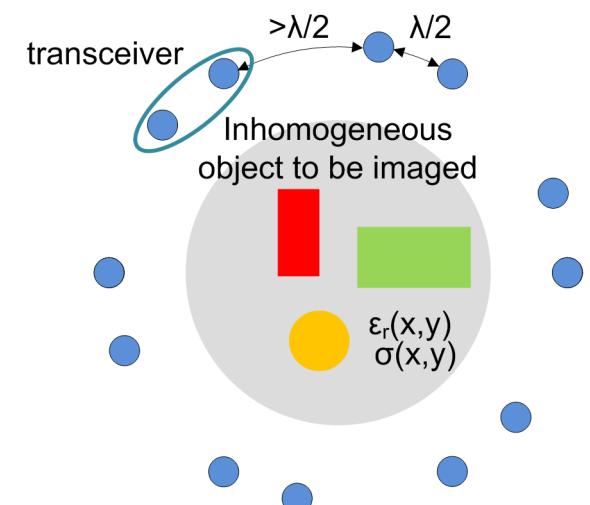


Push-Push 148-170 GHz VCO

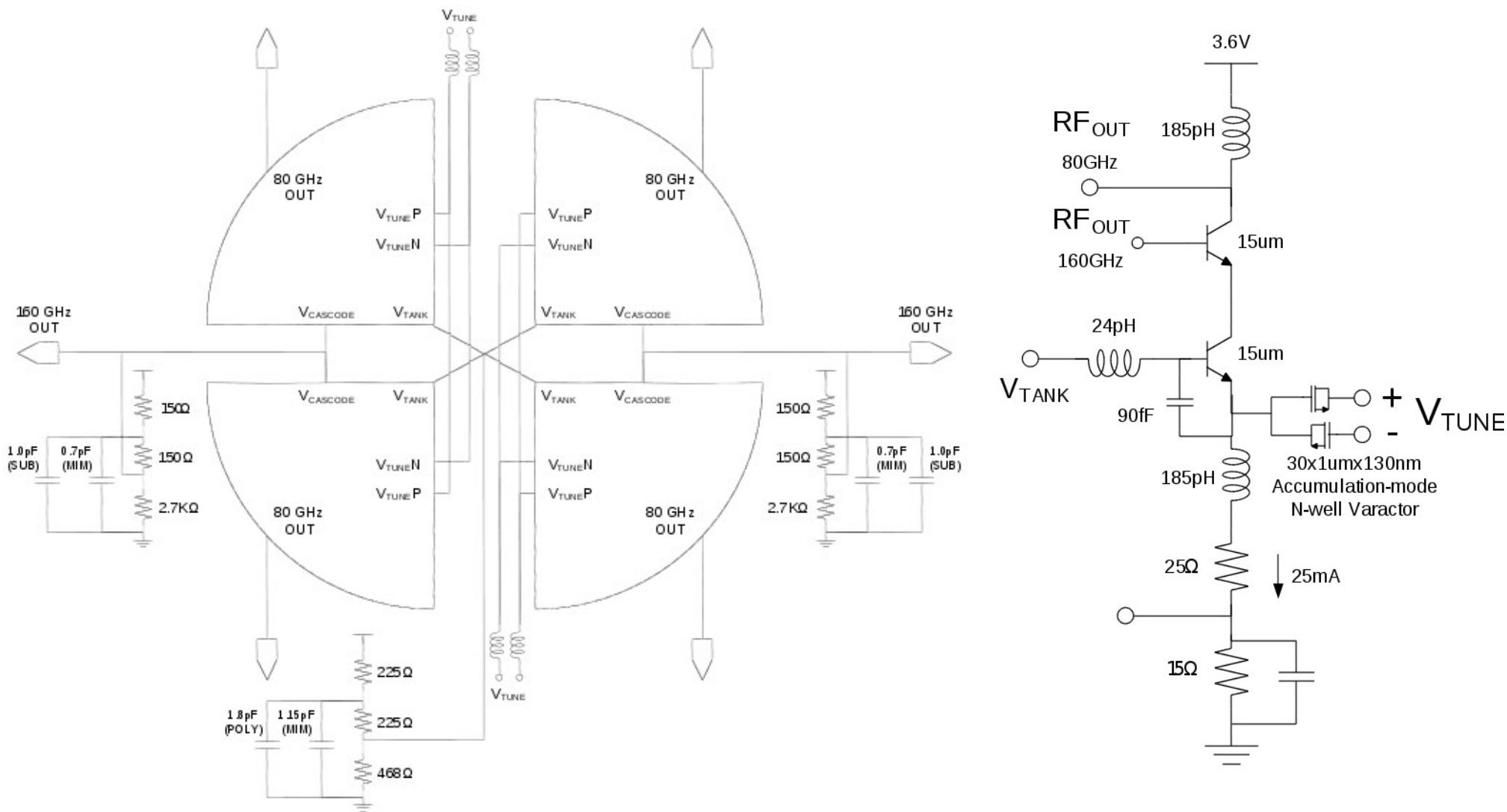


$$P_{DC} = 360 \text{ mW}, P_{OUT} = -10 \text{ dBm}, PN = -82 \text{ dBc/Hz at } 1 \text{ MHz offset}$$

148-170 GHz LO Tree and TX Amplifiers

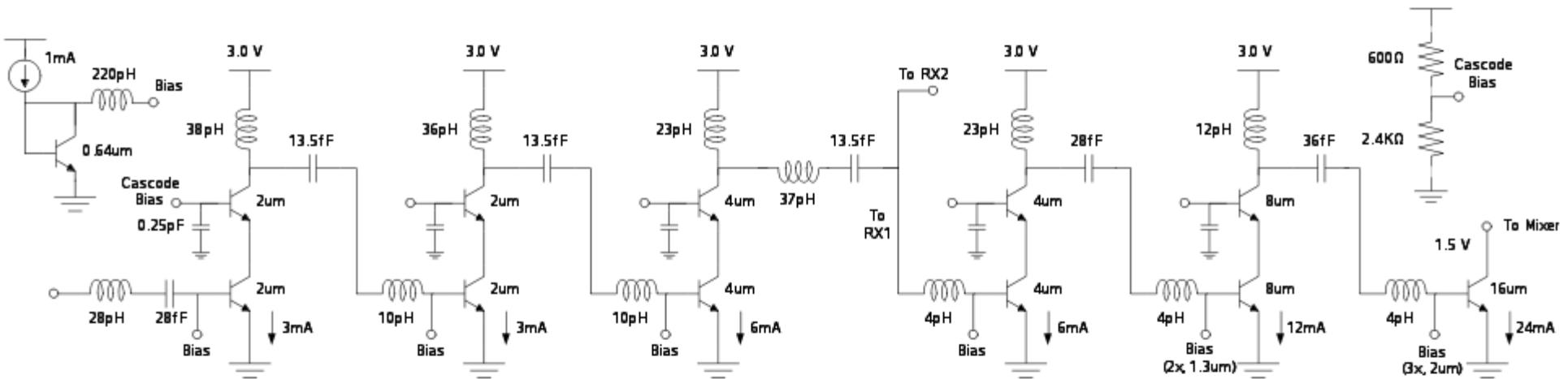

$$P_D = 126 \text{ mW}$$

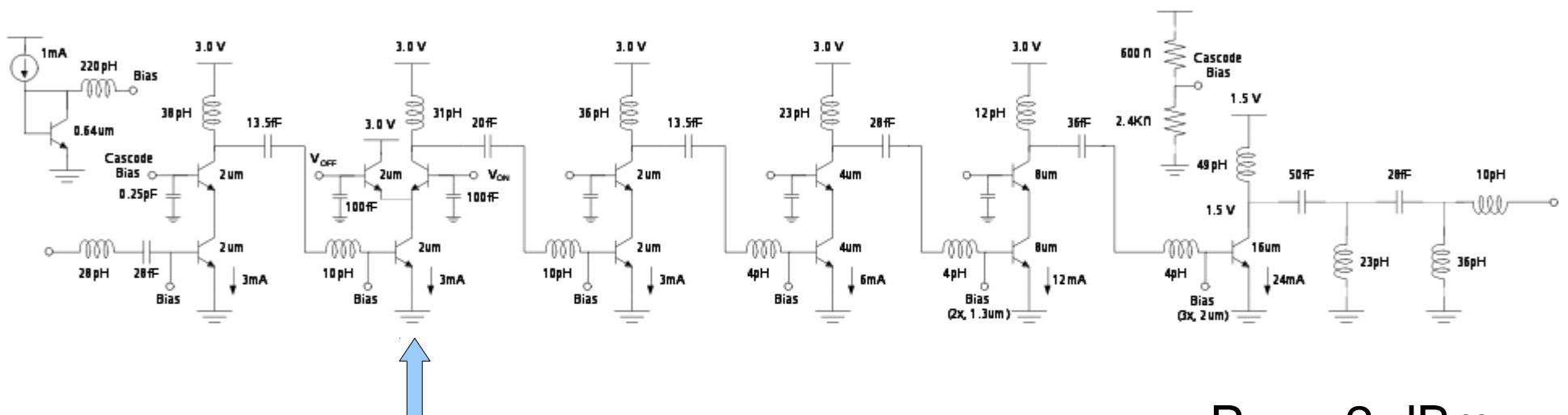


Amplitude Modulator

$$P_{\text{out}} > 2 \text{ dBm}$$


$$P_D = 117 \text{ mW}$$

148-170 GHz Low Noise Amplifier

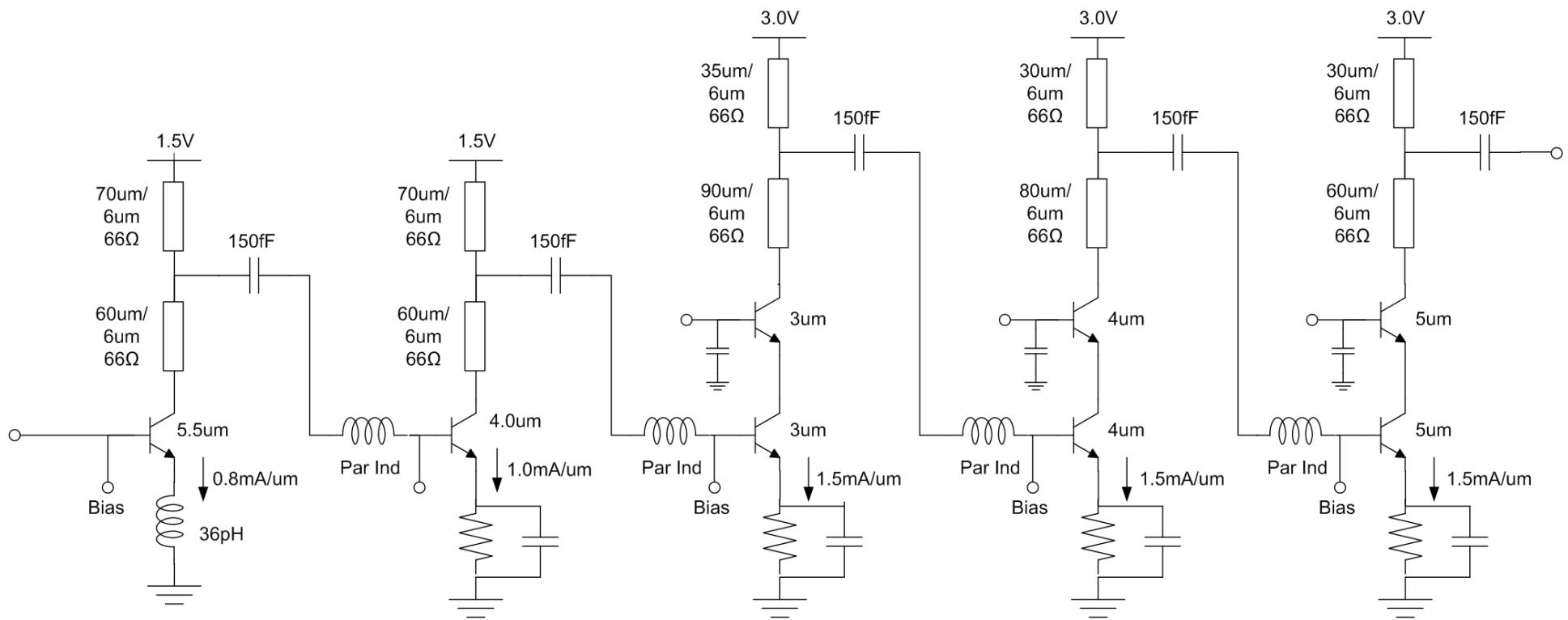

$P_D = 67 \text{ mW}$, Gain= 20 dB, NF < 12 dB.


Die photograph

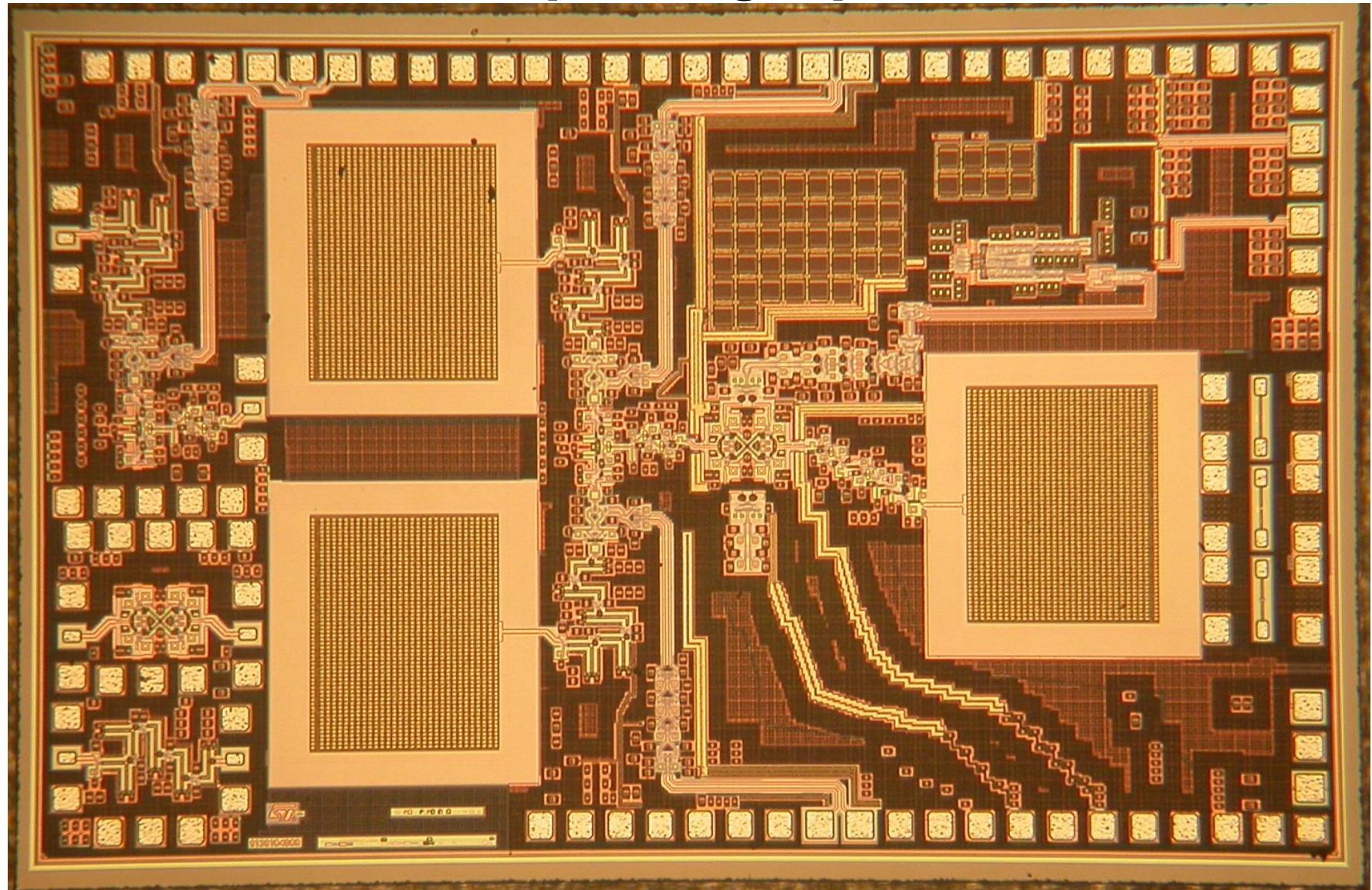


Chip: 2.1mm×2.9mm

130-nm BiCMOS9MW: SiGe HBT $f_T = 230$ GHz, $f_{MAX} = 280$ GHz


RX Breakout Gain and Noise Figure

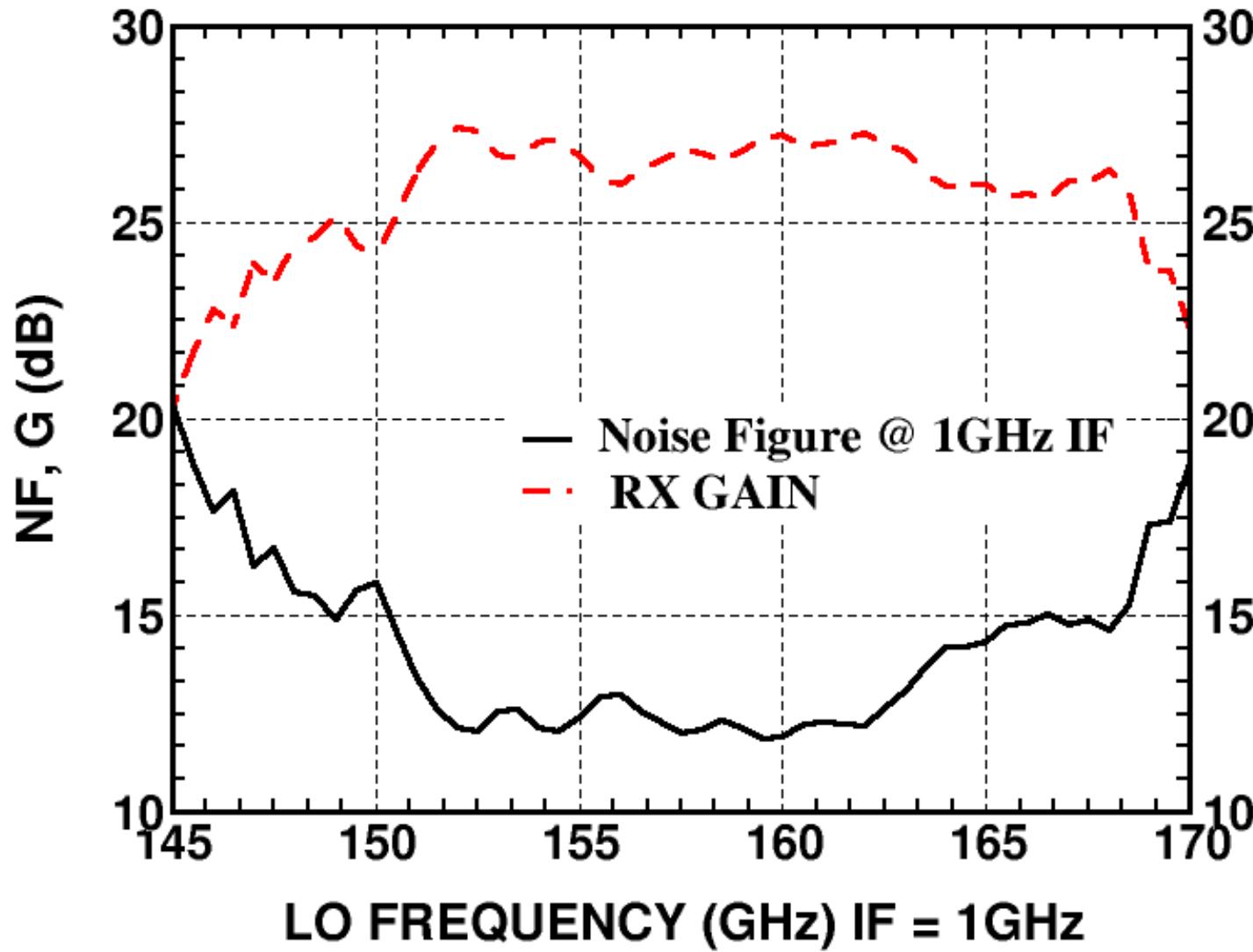

Transceiver PLL Phase Noise

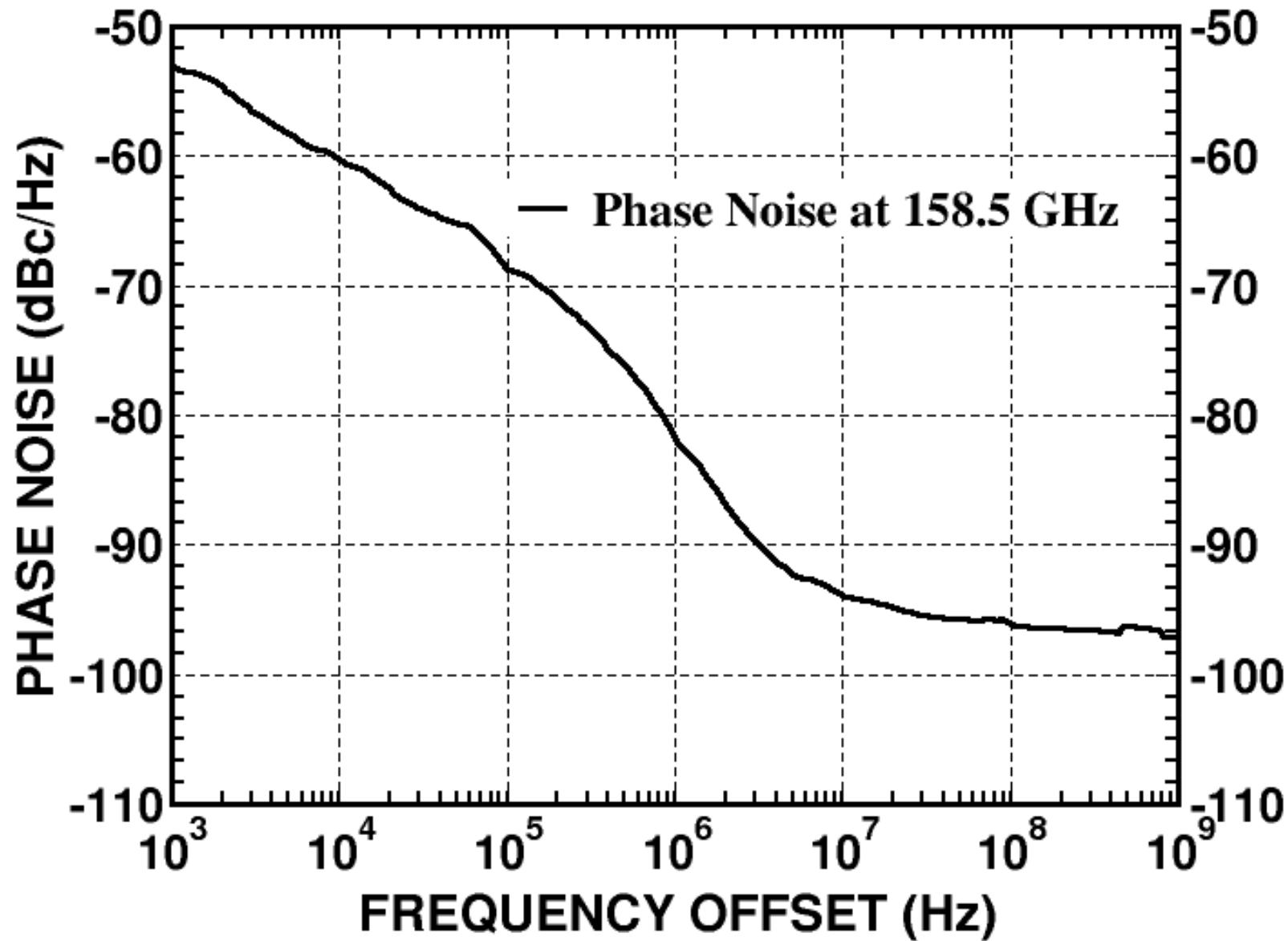


On-die Doppler Test

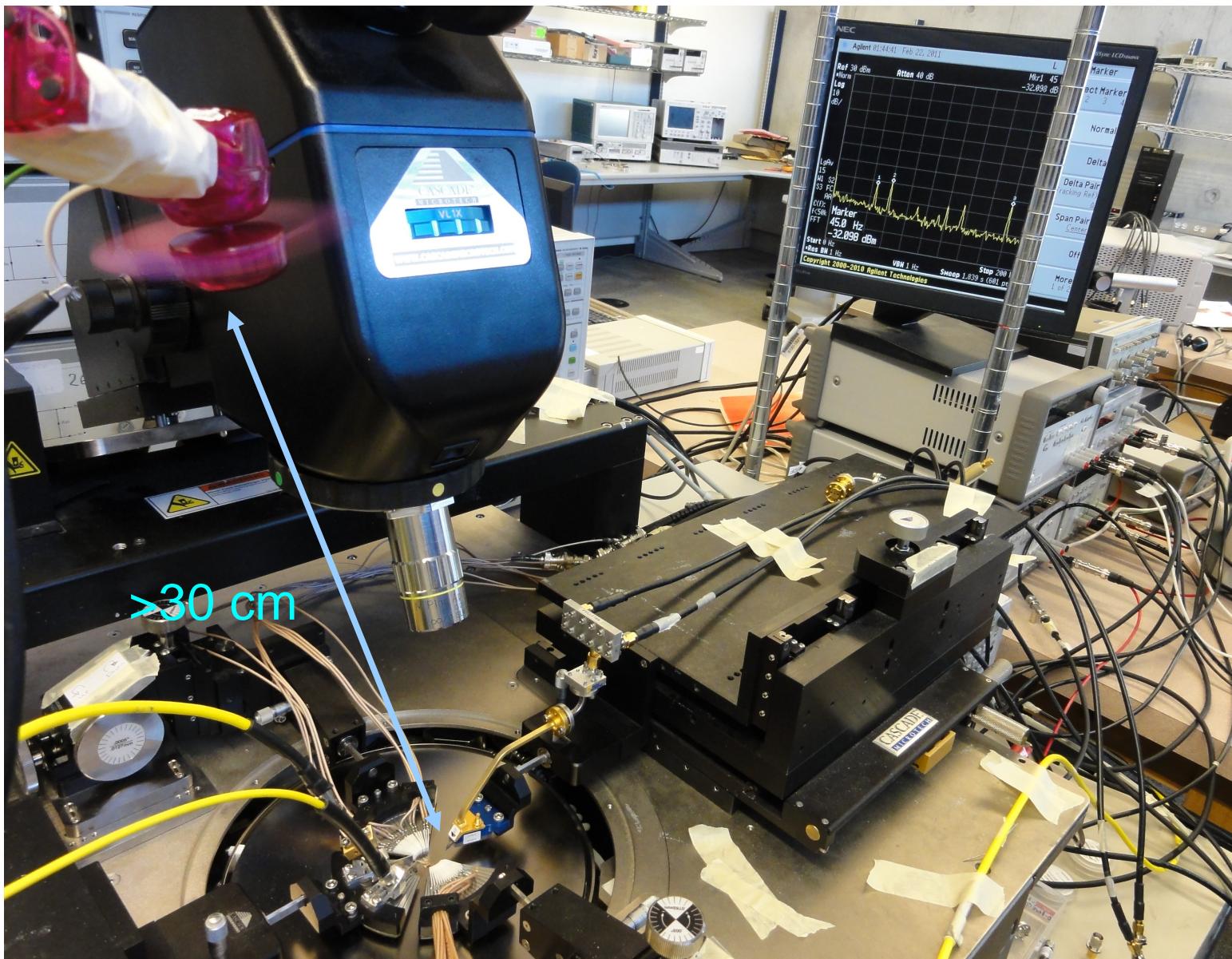


Outline

- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors

Monostatic single-chip sensor

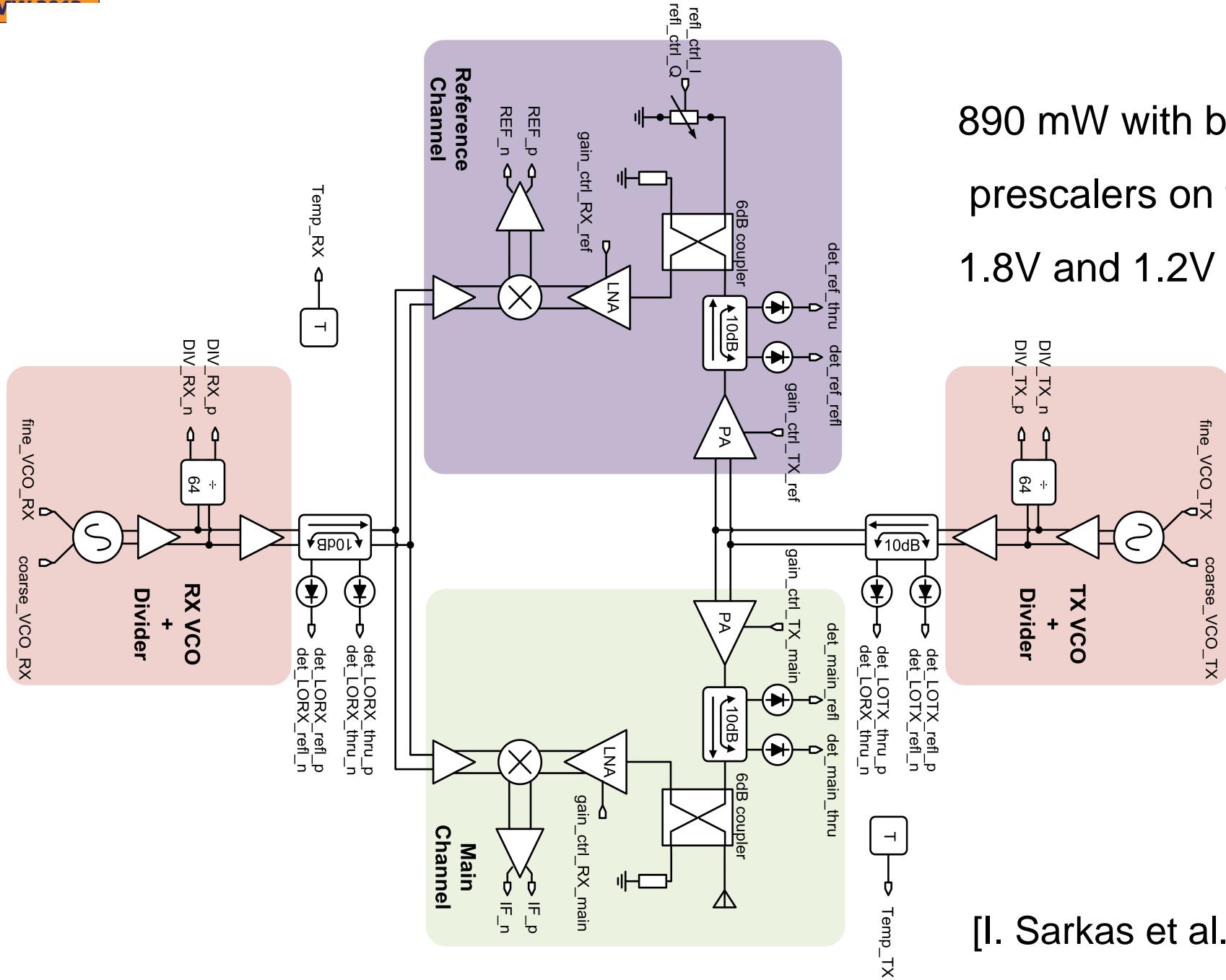

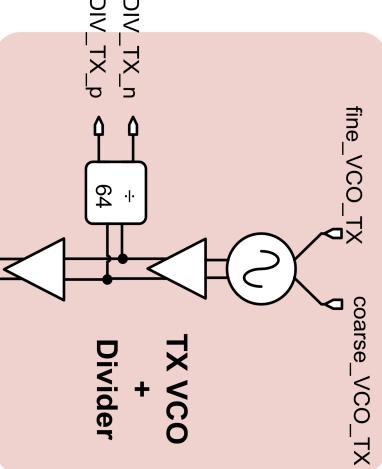890 mW with both
prescalers on from
1.8V and 1.2V supplies




[I. Sarkas et al. CSICS 2012]



Layout and performance summary

- BiCMOS9MW, $f_T/f_{MAX} = 230/280$ GHz
- Tuning range 143-152 GHz
- NF<10 dB, Pout >-6 dBm
- PN < -83 dBc/Hz at 1MHz
- $P_{DC} = 800$ mW
- Highest fundamental frequency transceiver

2.6mmx2.3mm


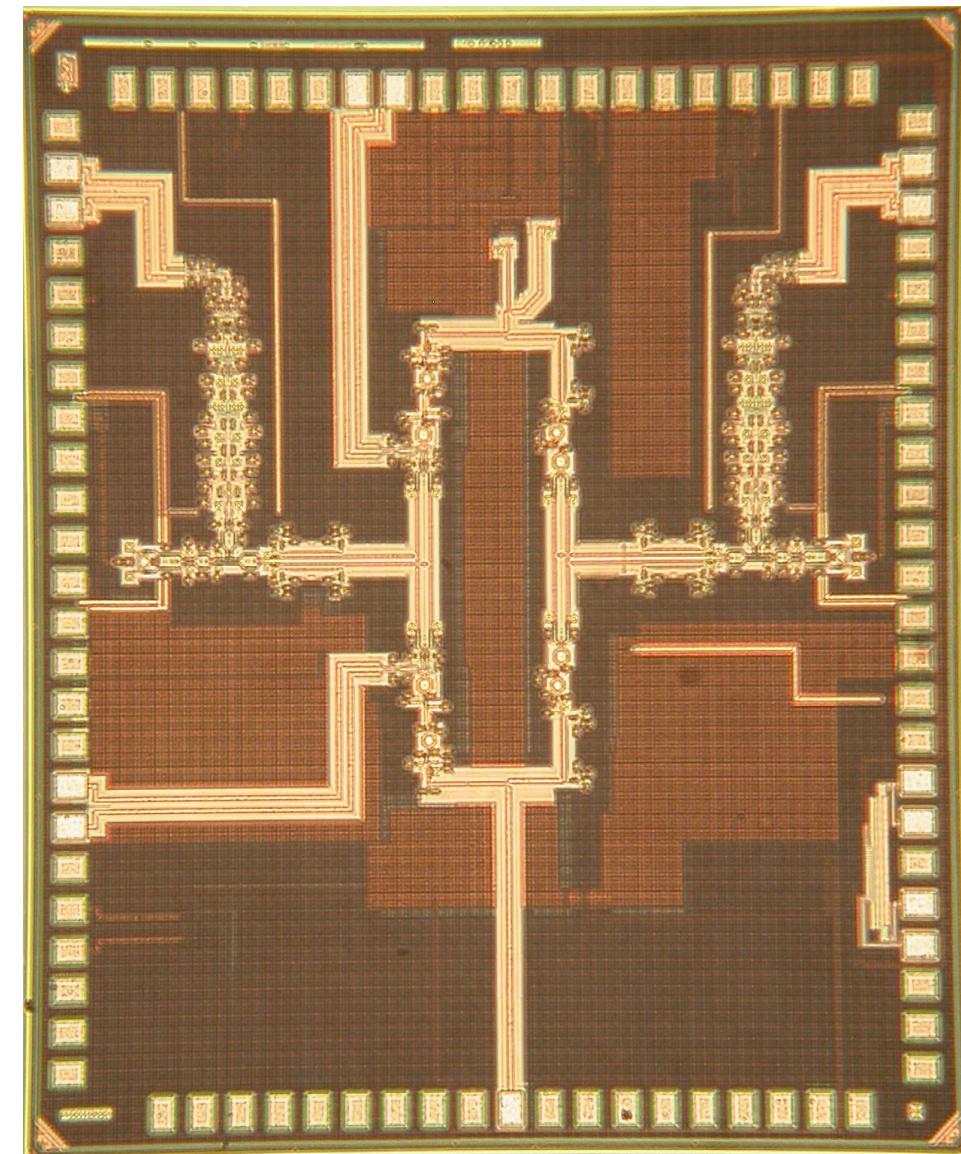


150-GHz Dynamic Divide-by-64

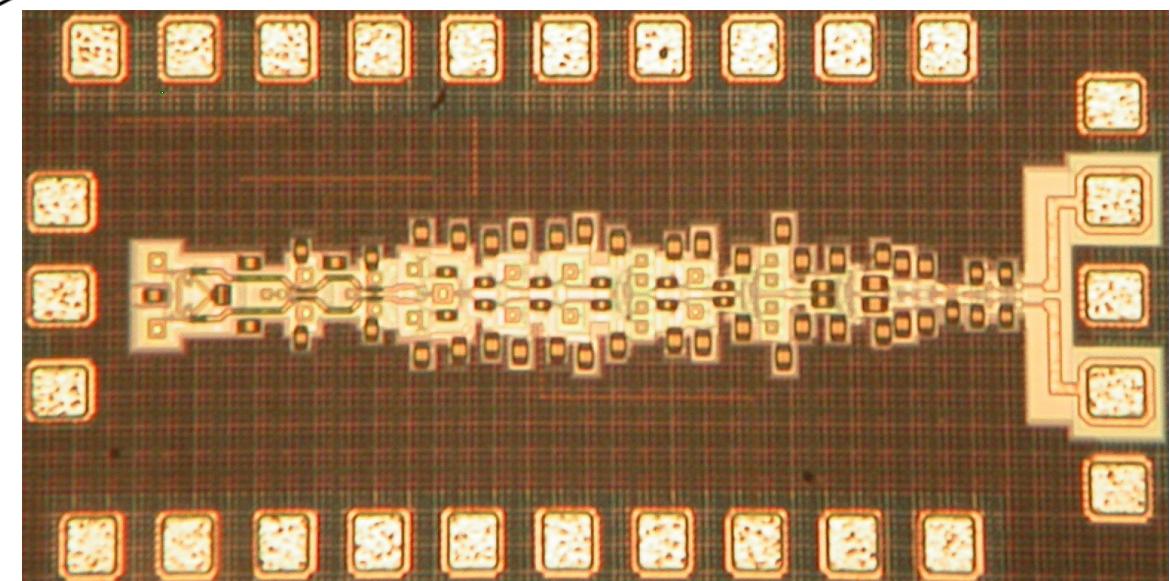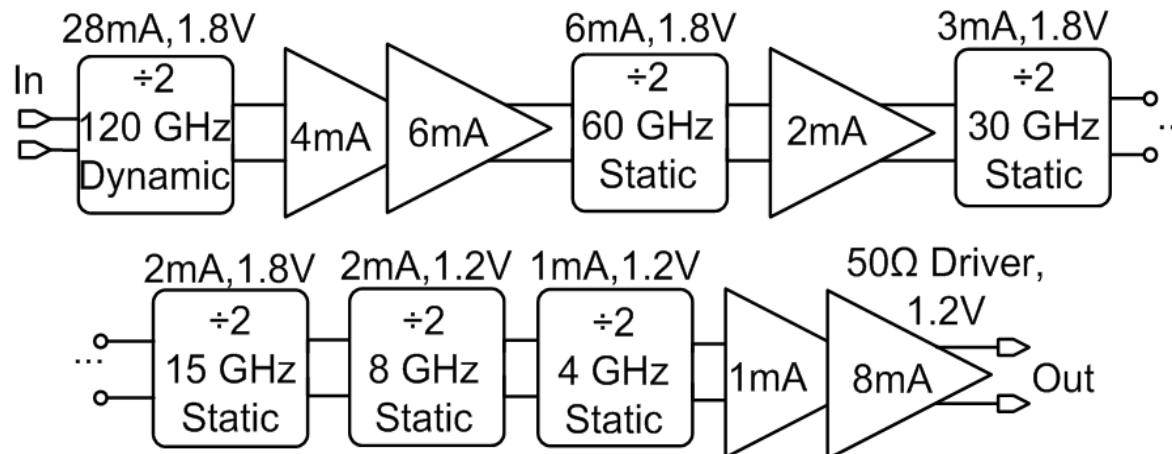


- Measured in test structure with 150-GHz VCO
- $1.8V/52mA + 1.2V/3mA = 97.2 \text{ mW} + 25.2 \text{ mW}$ in 50Ω buffer





Coupler with detectors

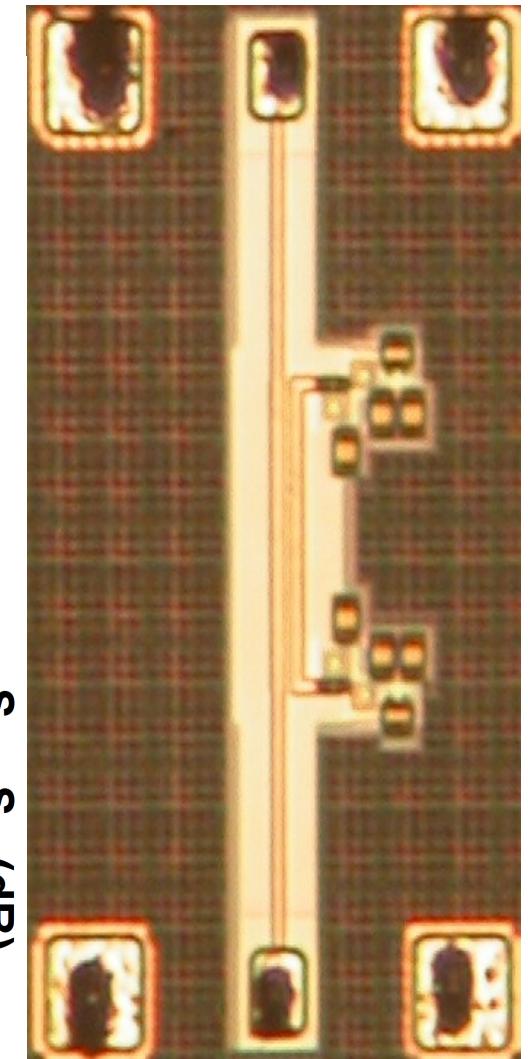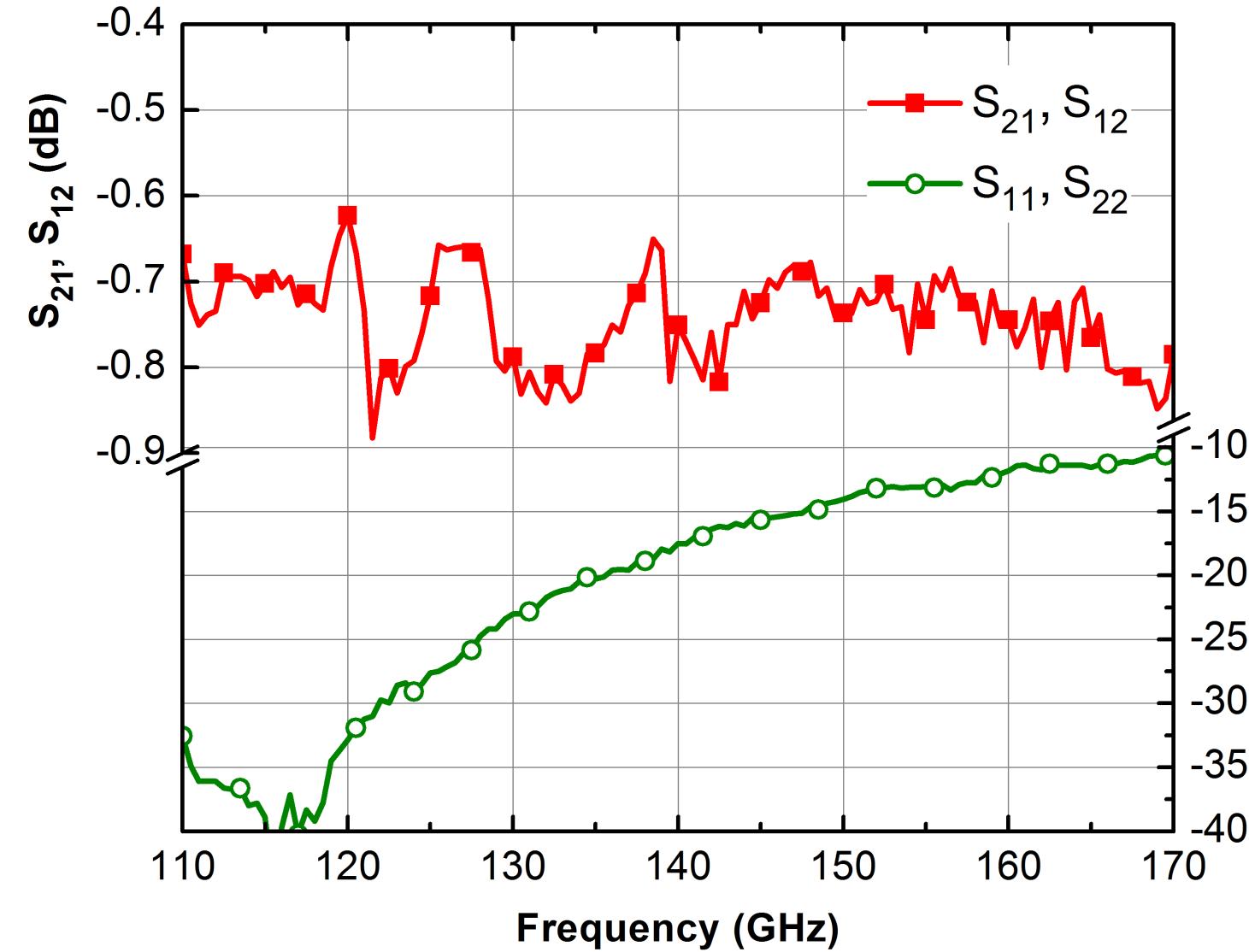



Coupler with detectors: Linearity

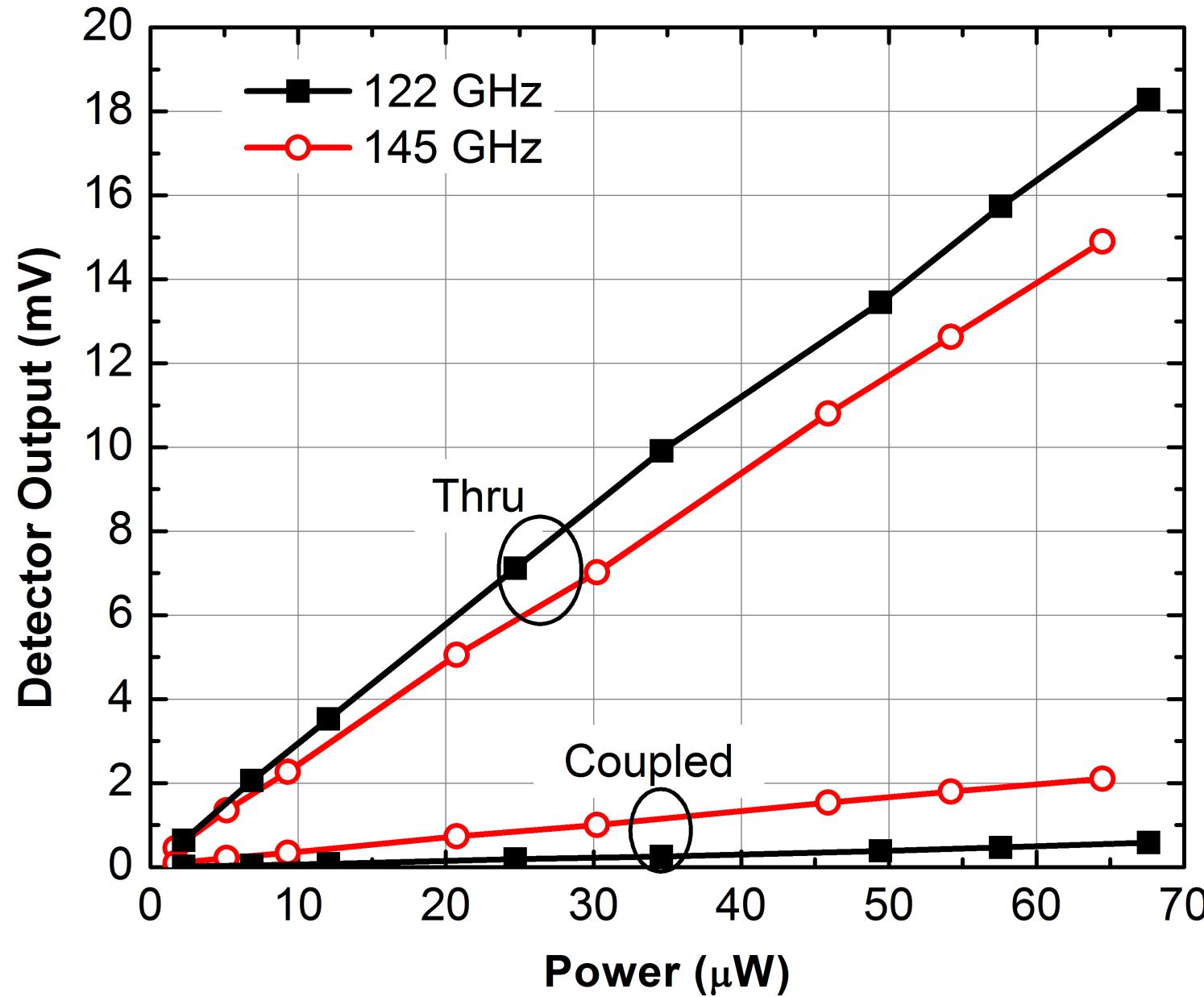

Digital Tuner States

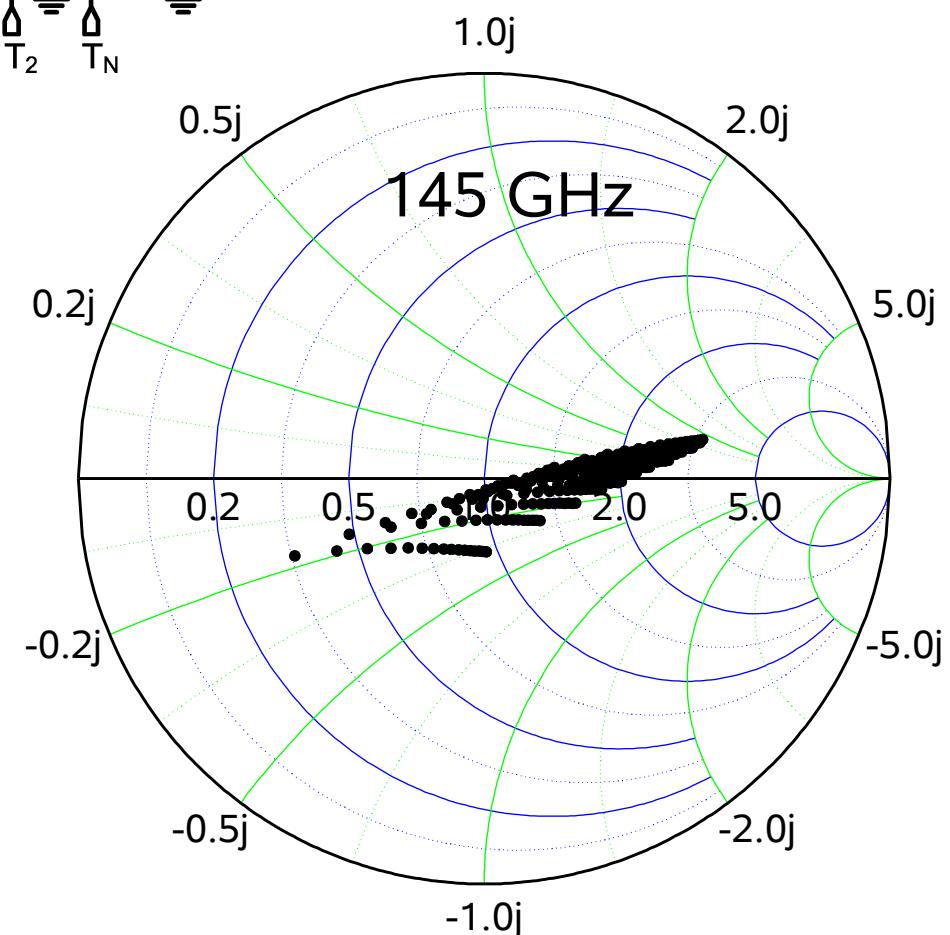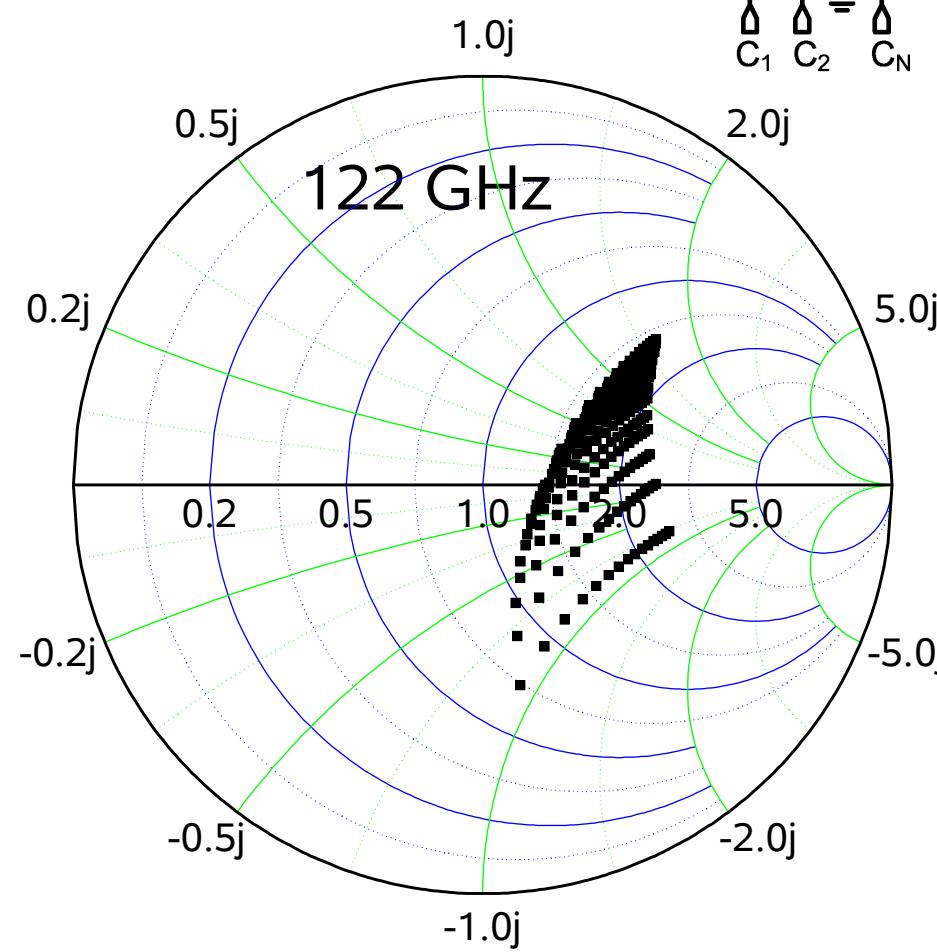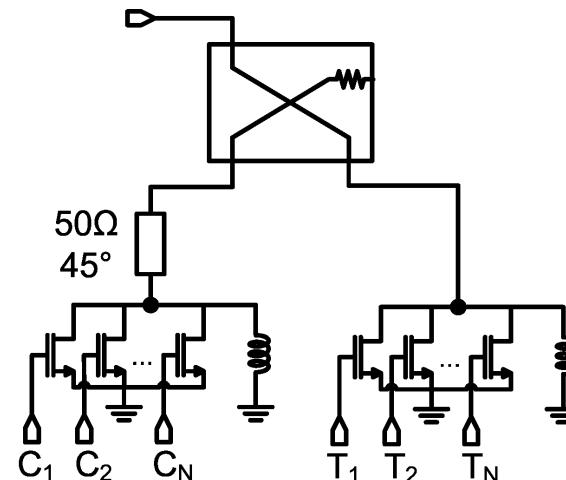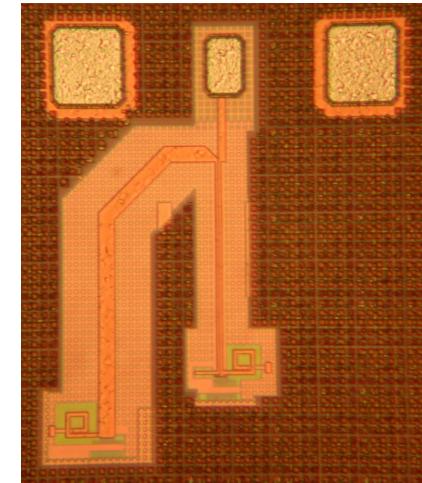


145 GHz Fundamental Frequency VCO

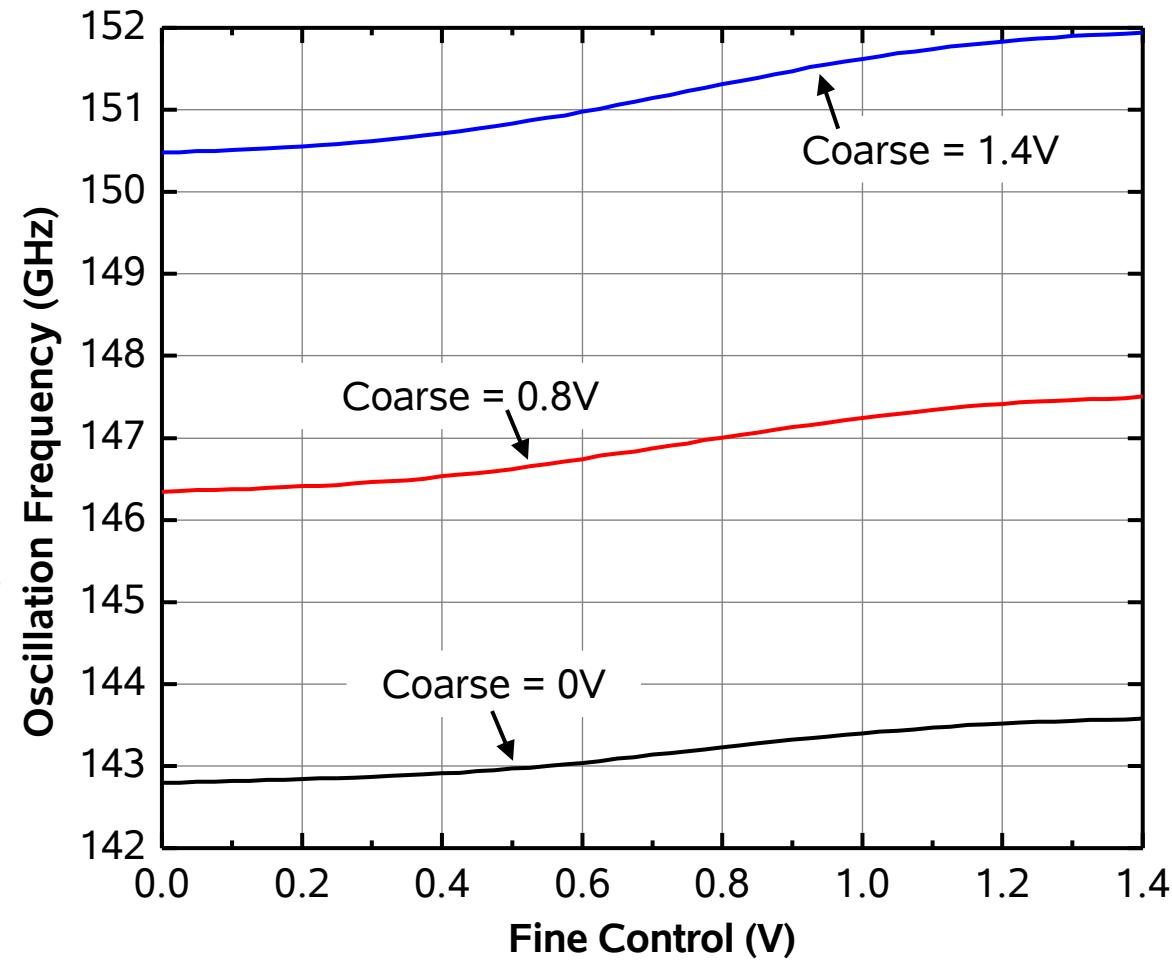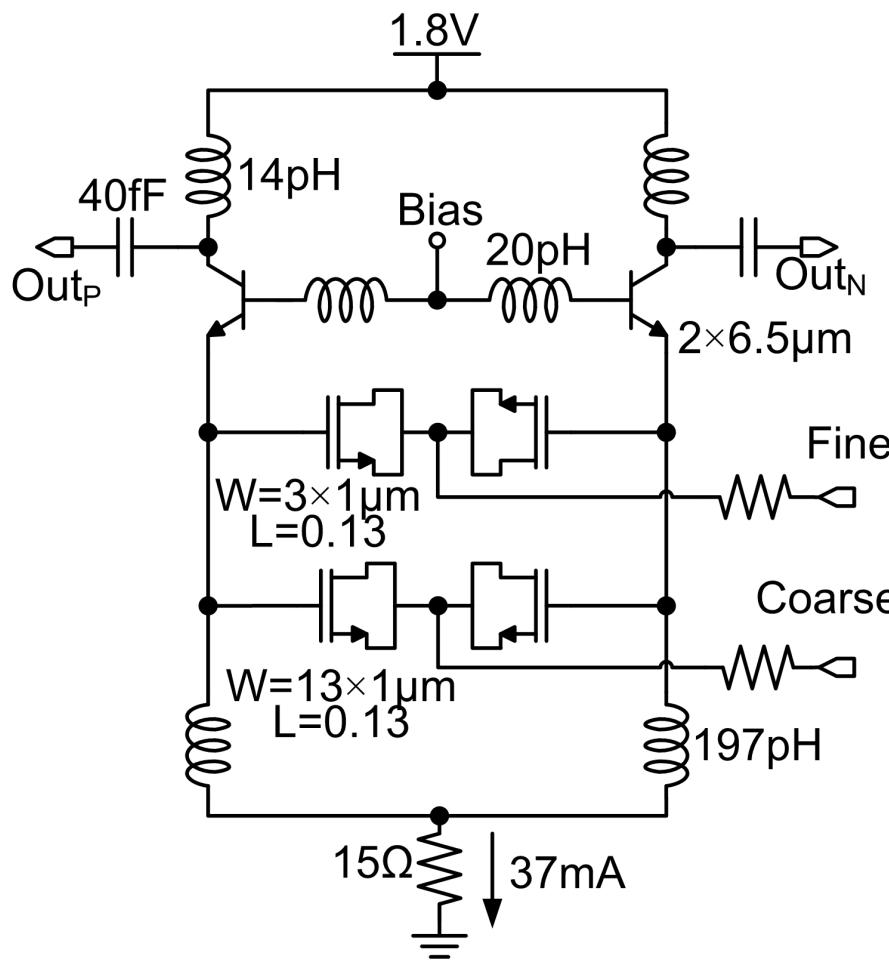


- 143-152 GHz tuning range
- PN=-103dBc/Hz @ 10MHz
- P_{DC} = 72 mW

Measured output power


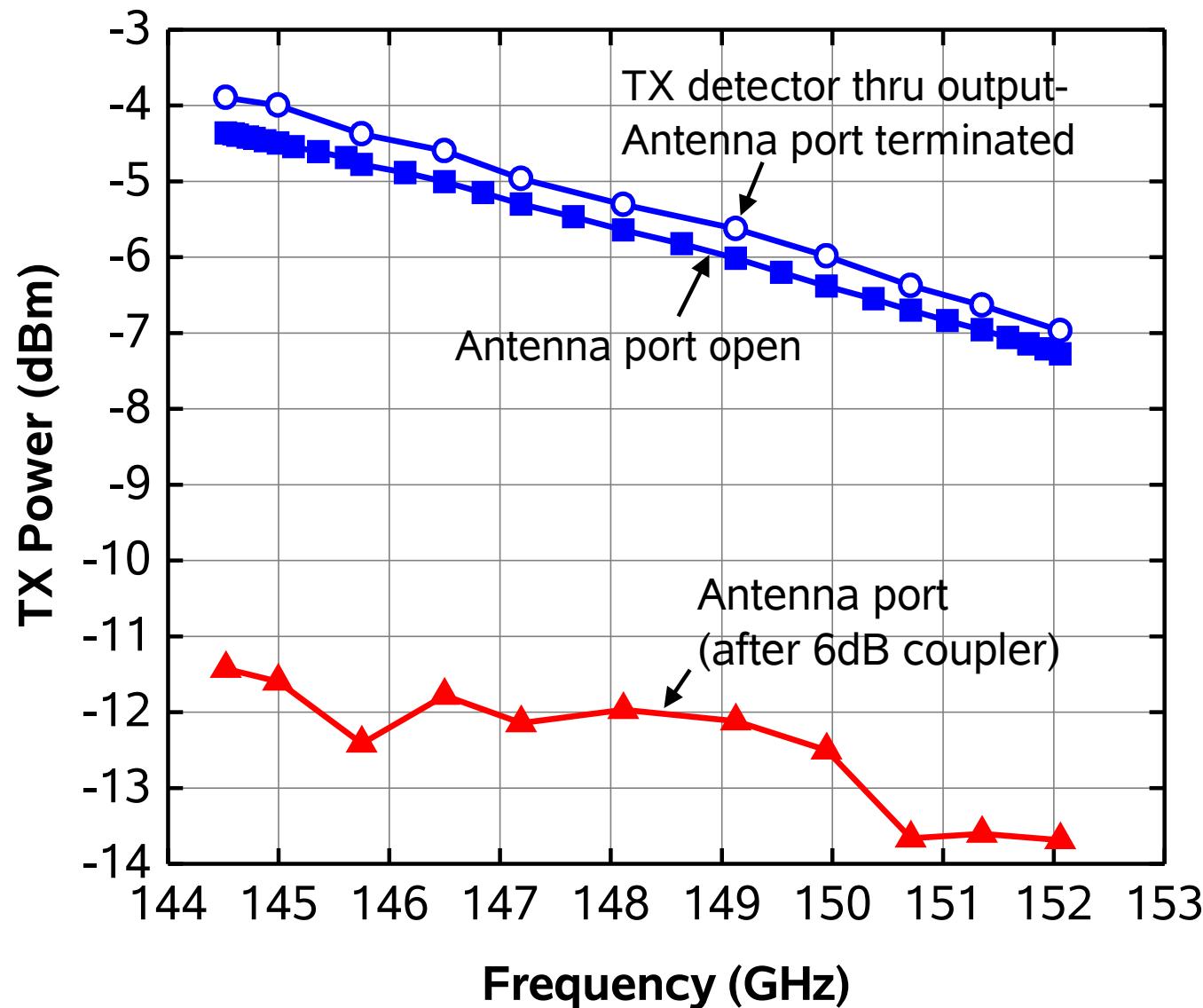


- Power at antenna port measured with ELVA power sensor
- On-chip and external measurements track very well

Receiver schematics

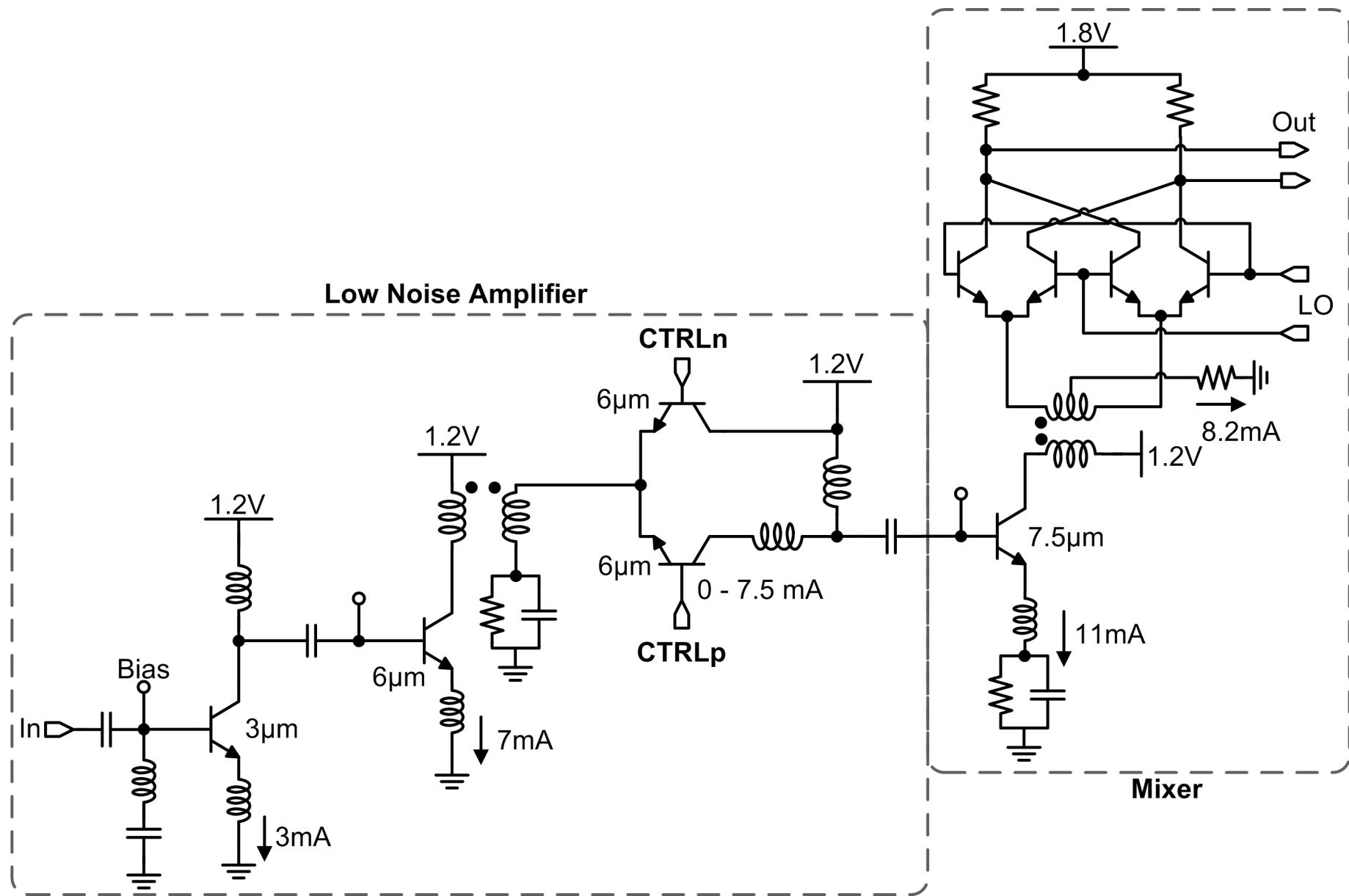


Receiver Gain and Noise Figure

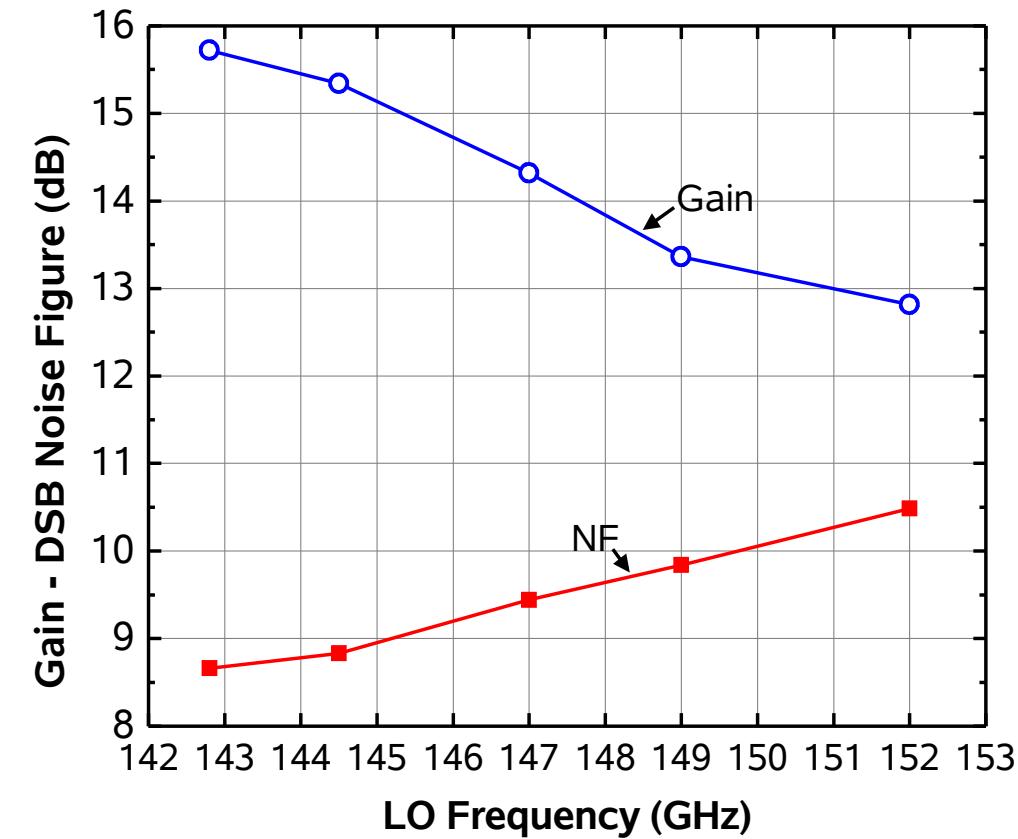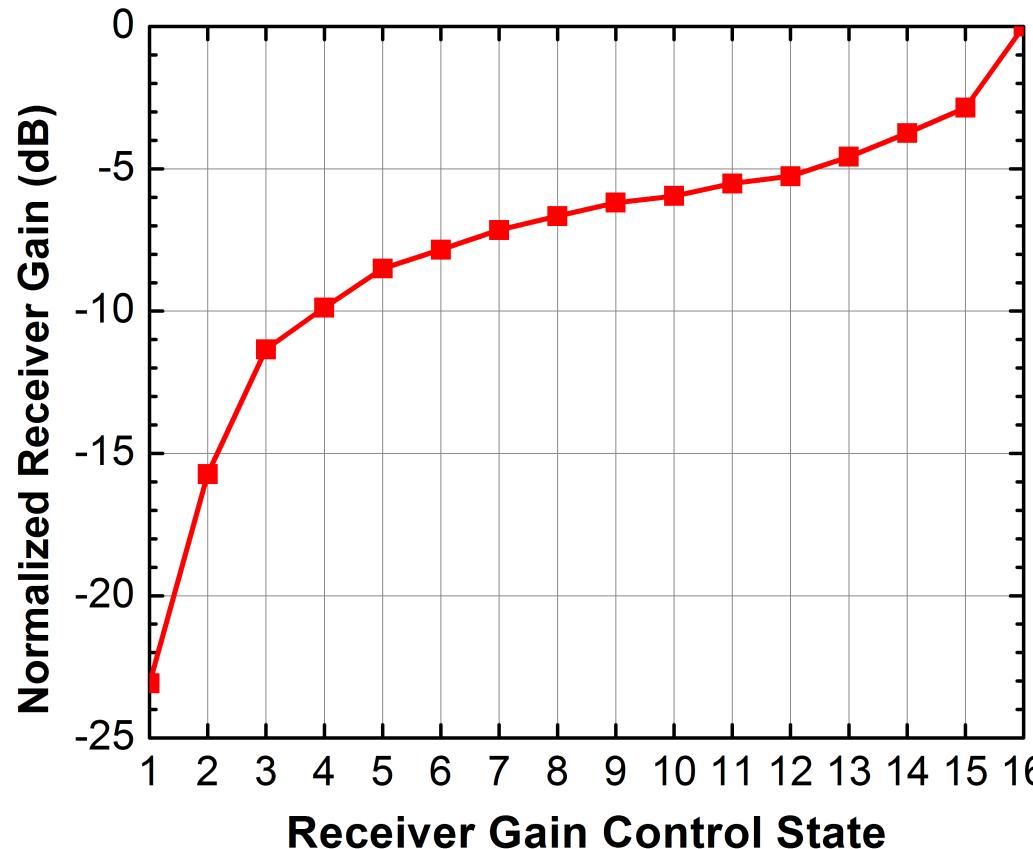

13-15 dB gain, 23 dB of gain control in LNA
Low noise figure: 8.5-10.5dB

Antenna and die in package

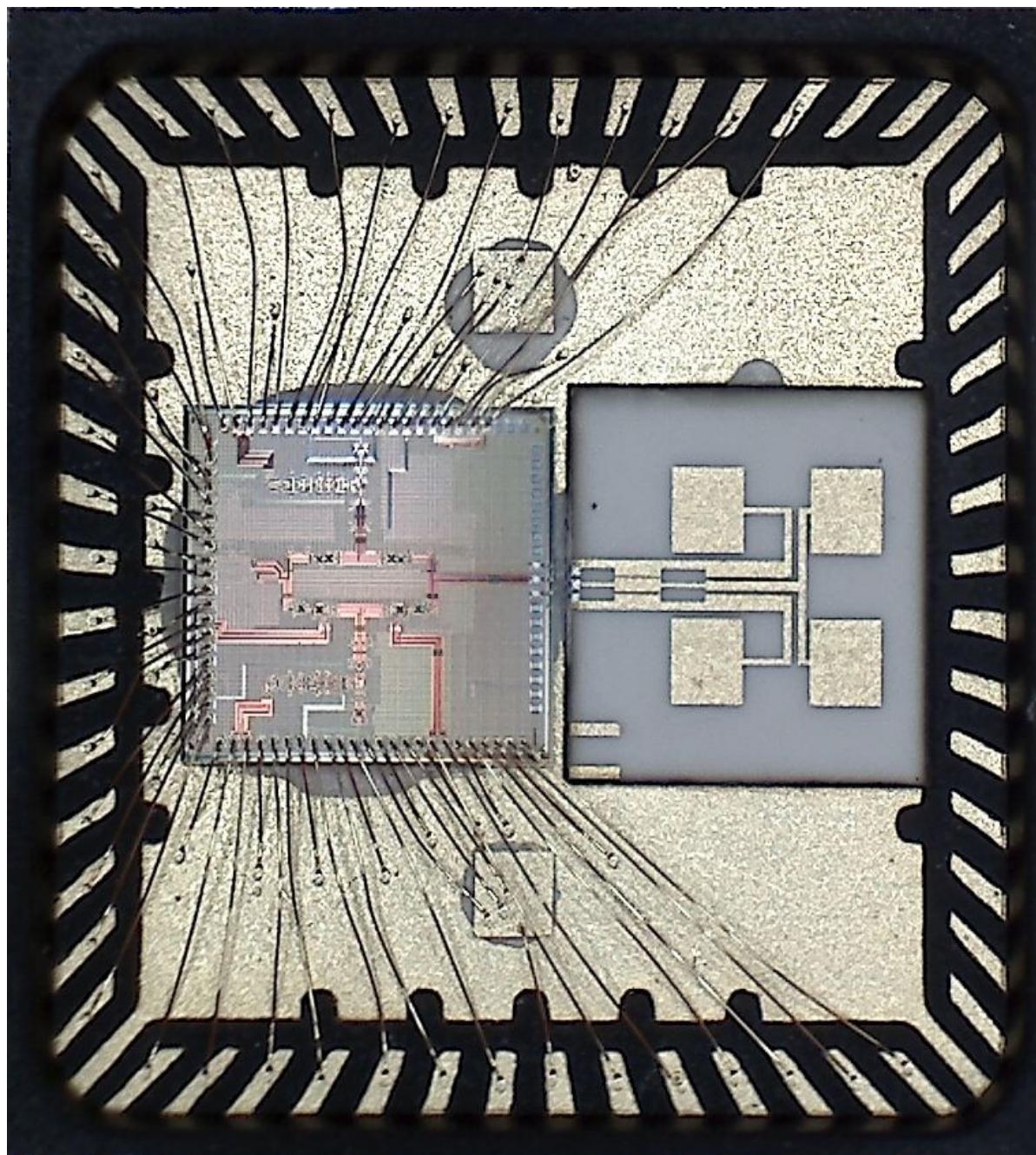


- QFN package with bondwire transition to antenna on alumina

Courtesy of Robert Bosch GmbH,
Karlsruhe Institute of Technology
and EU SUCCESS project
partners


Outline

- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors


240-GHz Transceiver Blocks

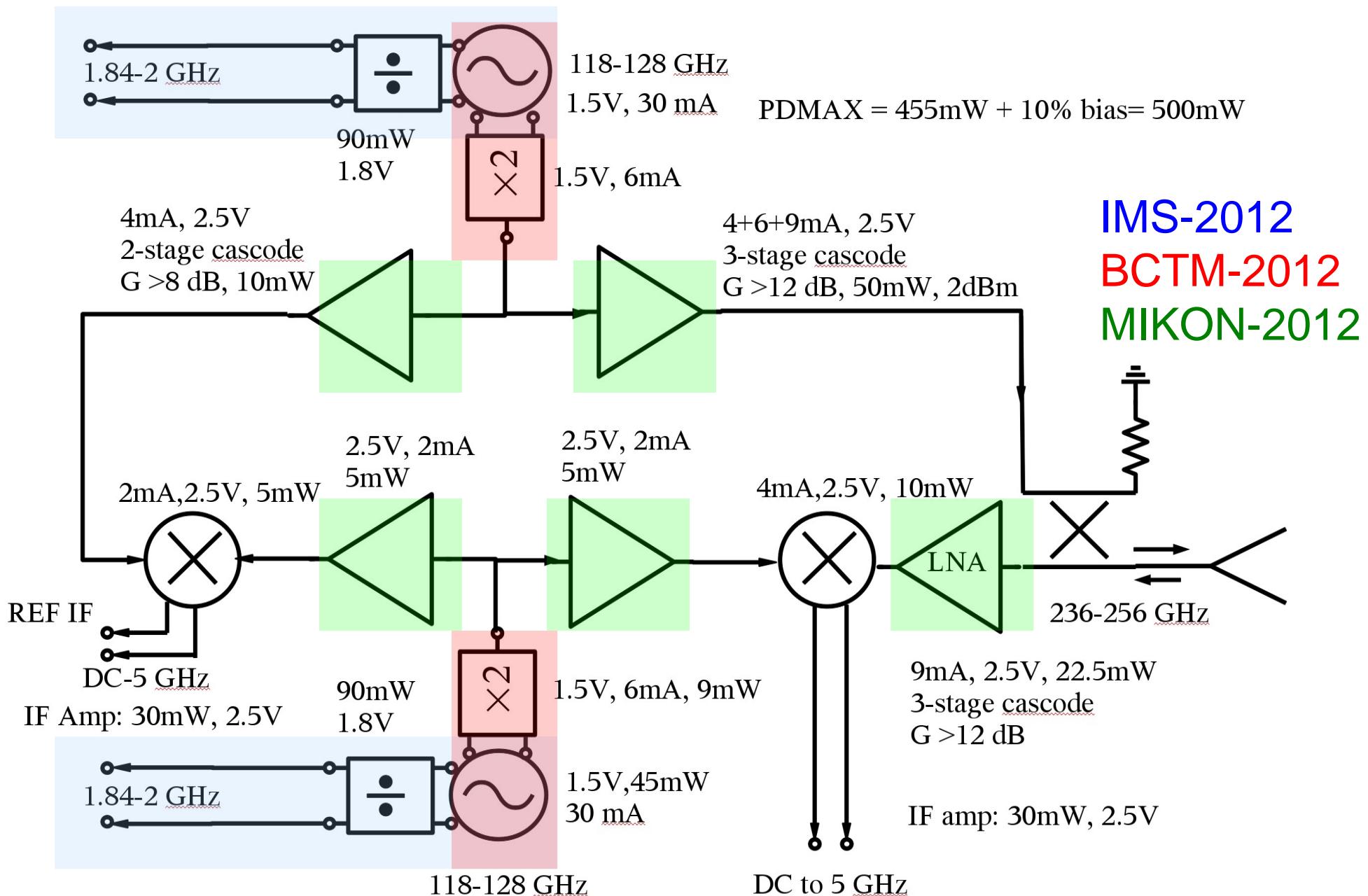

240-GHz Amplifier

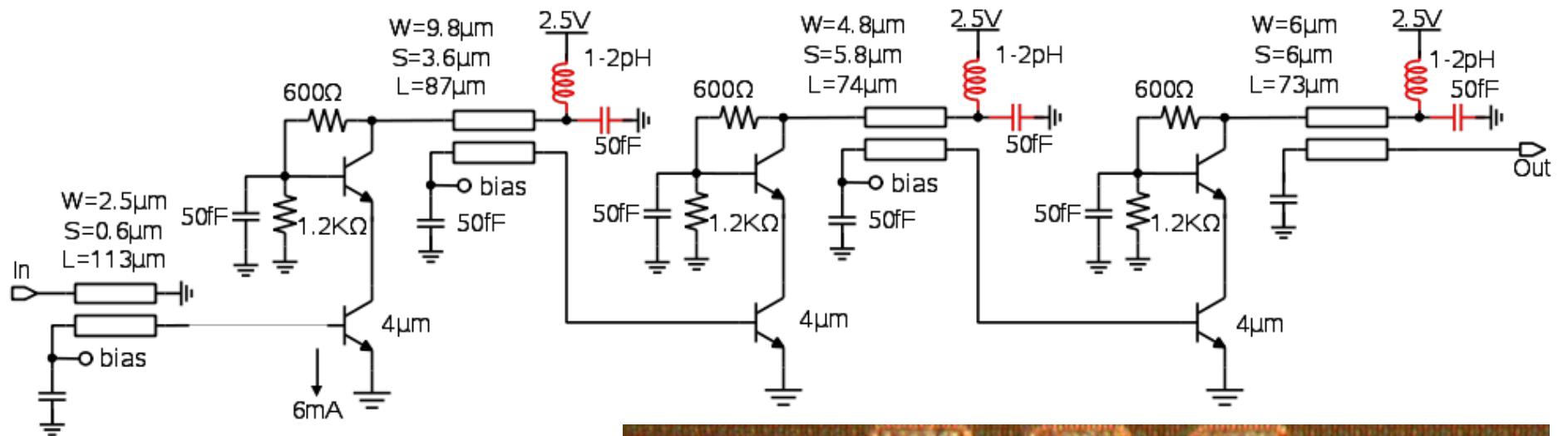


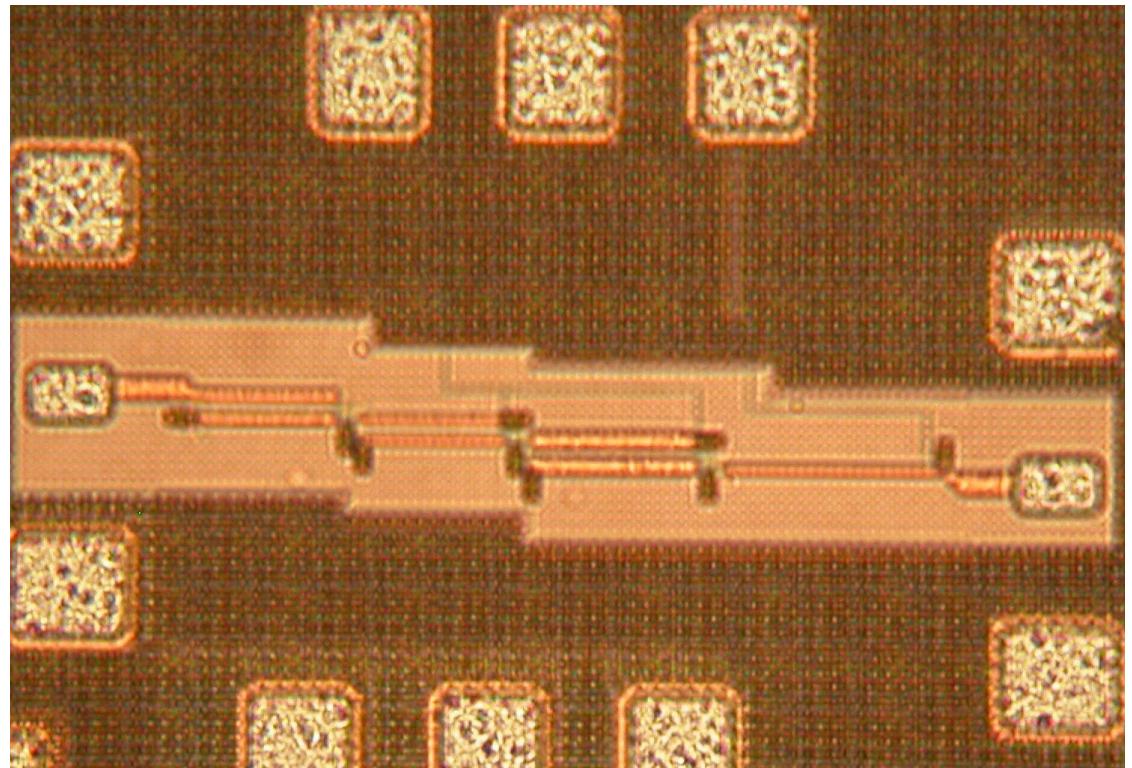SiGe HBT 300/400 GHz
 $P_D = 37.5 \text{ mW}$
 $G = 4.5 \text{ dB} @ 240 \text{ GHz}$




[I. Sarkas et al, MIKON 2012]

Measurements vs. sims

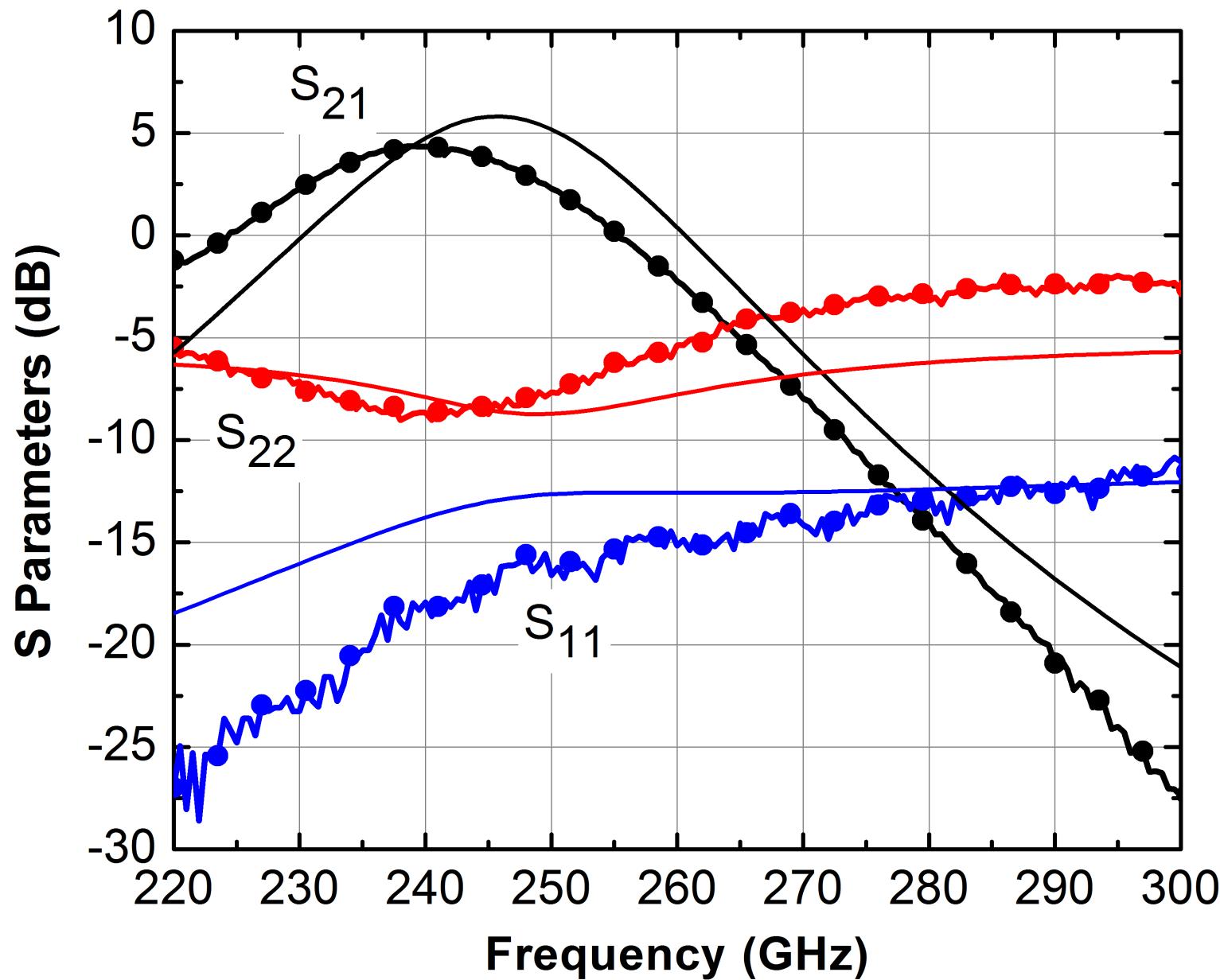

VCO Topology & Design

Topology

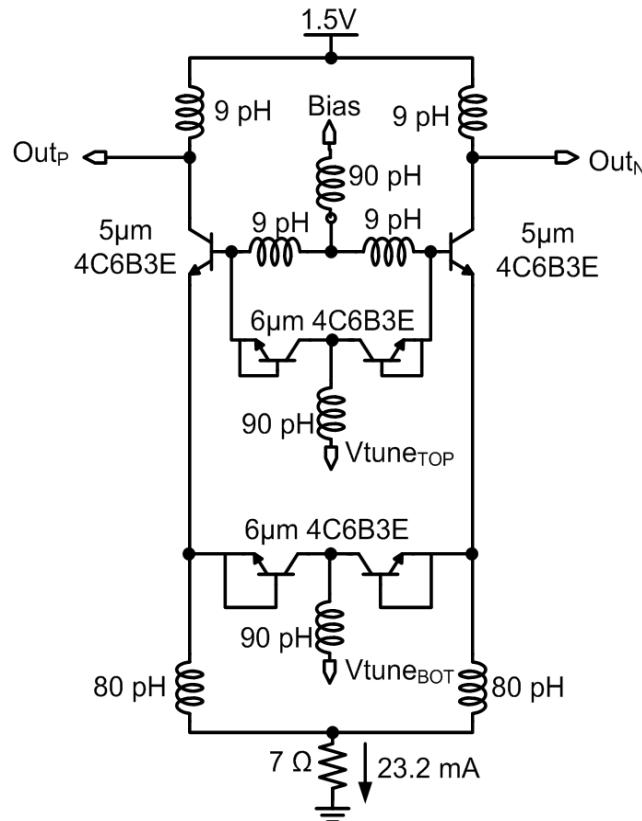


- Colpitts-Clapp for tuning [Pohl et al., CSICS 2008]
- $L_C \approx L_B$ for best performance
- L for bias noise filtering
- Colpitts above 200 GHz
- No MiM cap across BE junction
- HBT varactors (no AMOS)

Design (at 125 °C)

150-GHz VCO
[Balteanu et al.
IMS2012]

- Textbook: Based on small-signal sims of $Z(f)$
- Large signal verification

Multiplier Design Methodology

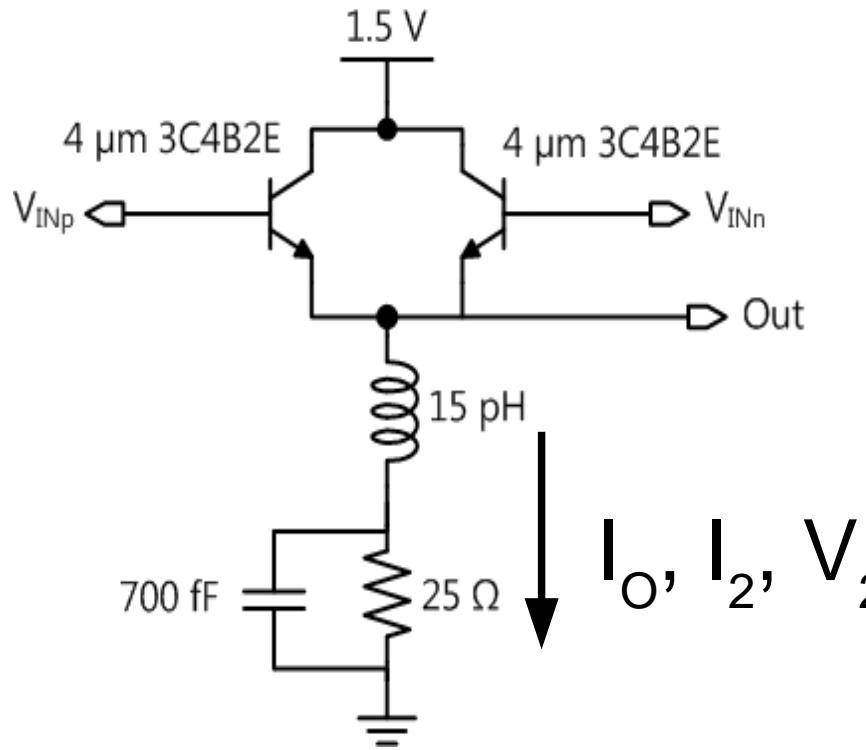

- Textbook Class-B PA-like design [S. Maas]
- EF output for VCO buffering
- $t_0/T = 118^\circ$
- $J_{MAX} = 24 \text{ mA}/\mu\text{m}^2$,

$$\eta_{DC} = \left| \frac{\cos\left(n\pi \frac{t_0}{T}\right)}{1 - \left(2n \frac{t_0}{T}\right)^2} \right| = 0.6488$$


$$I_0 = 2 \cdot I_{MAX} \frac{2t_0}{\pi T} = 9.7 \text{ mA.}$$

$$I_2 = 2 \cdot I_{MAX} \frac{4t_0}{\pi T} \left| \frac{\cos\left(2\pi \frac{t_0}{T}\right)}{1 - \left(4 \frac{t_0}{T}\right)^2} \right| = 12.5 \text{ mA}$$


$$P_L = \frac{V_2 \cdot I_2}{2} = 1.89 \text{ mW}$$

$$R_{LOPT} = \frac{V_2}{I_2} = \frac{0.3}{12.5 \text{ m}} = 23.88 \text{ Ohm.}$$

240-GHz VCO


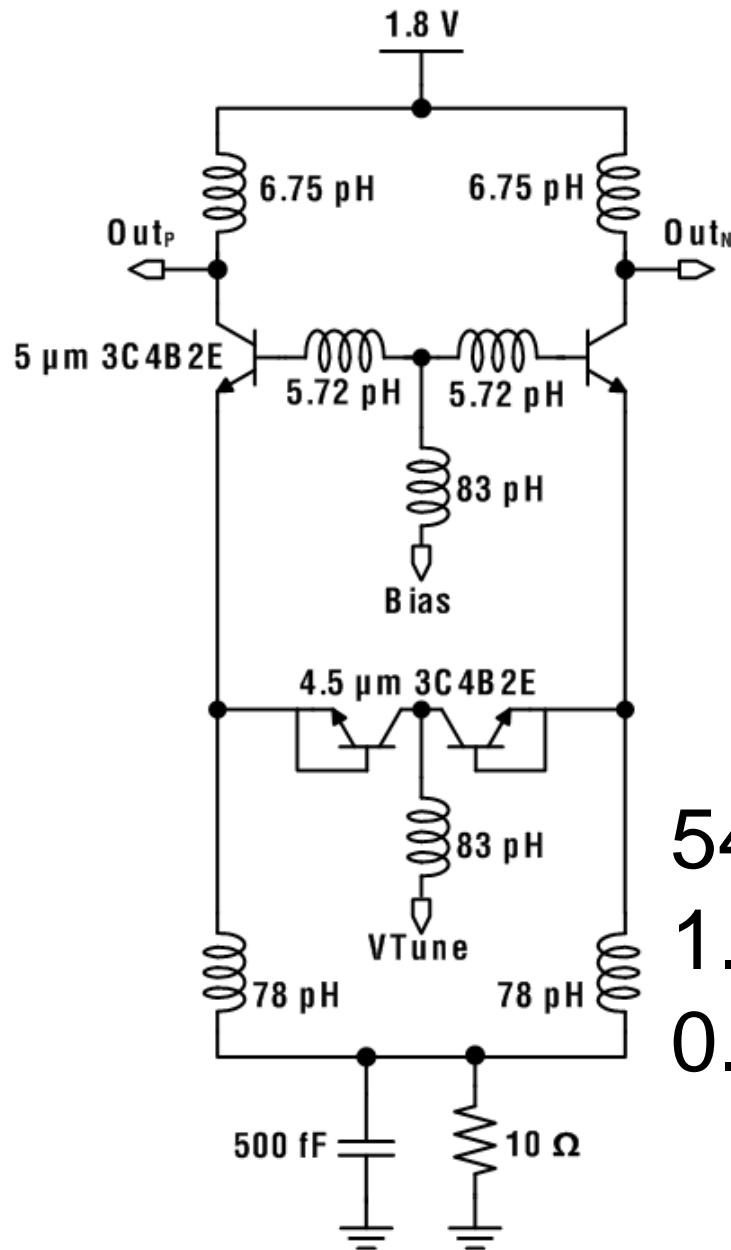


54 mW
1.5-1.8V
0.8%

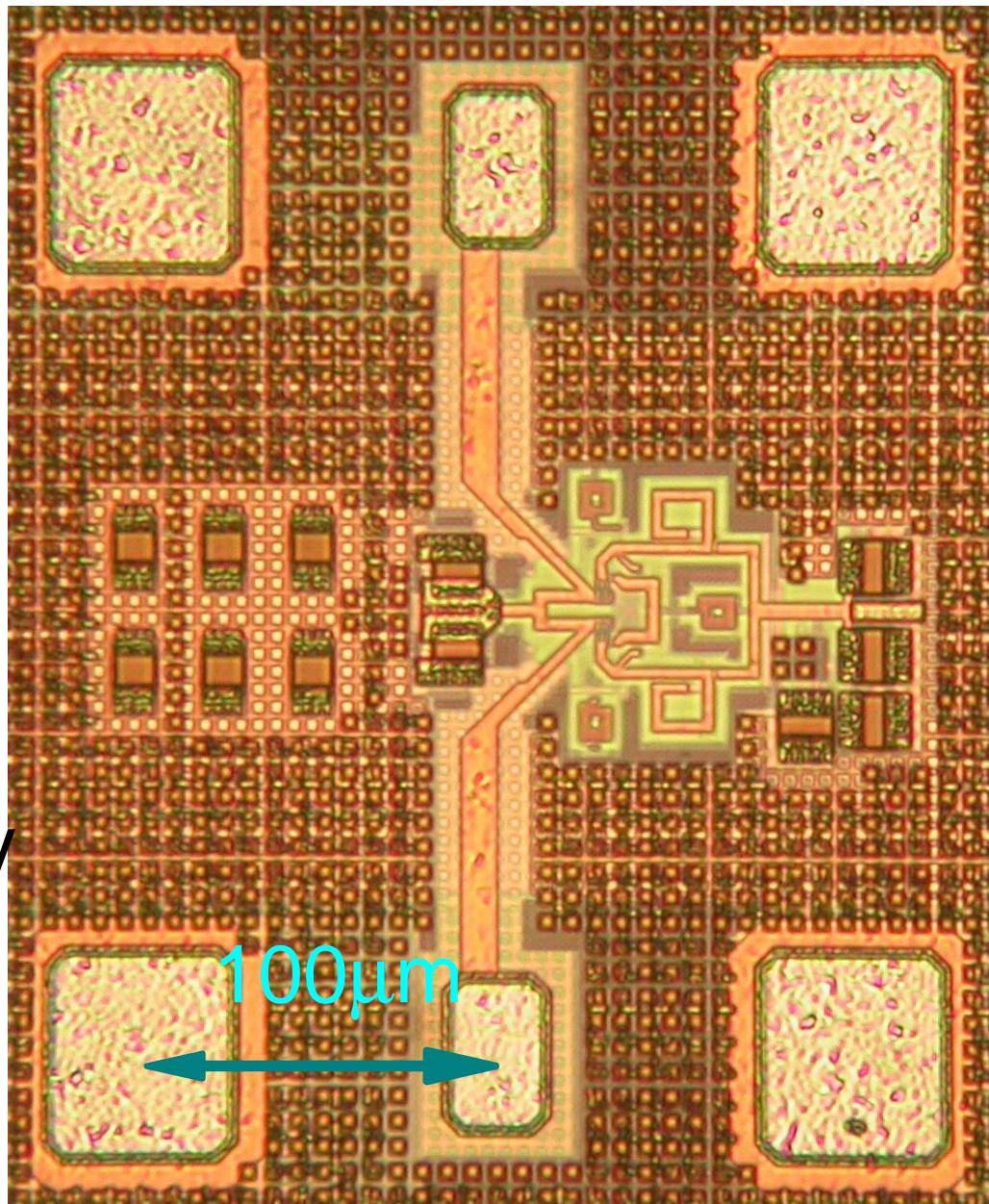



[A. Tomkins et al, BCTM 2012]

320-GHz Push-Push VCO

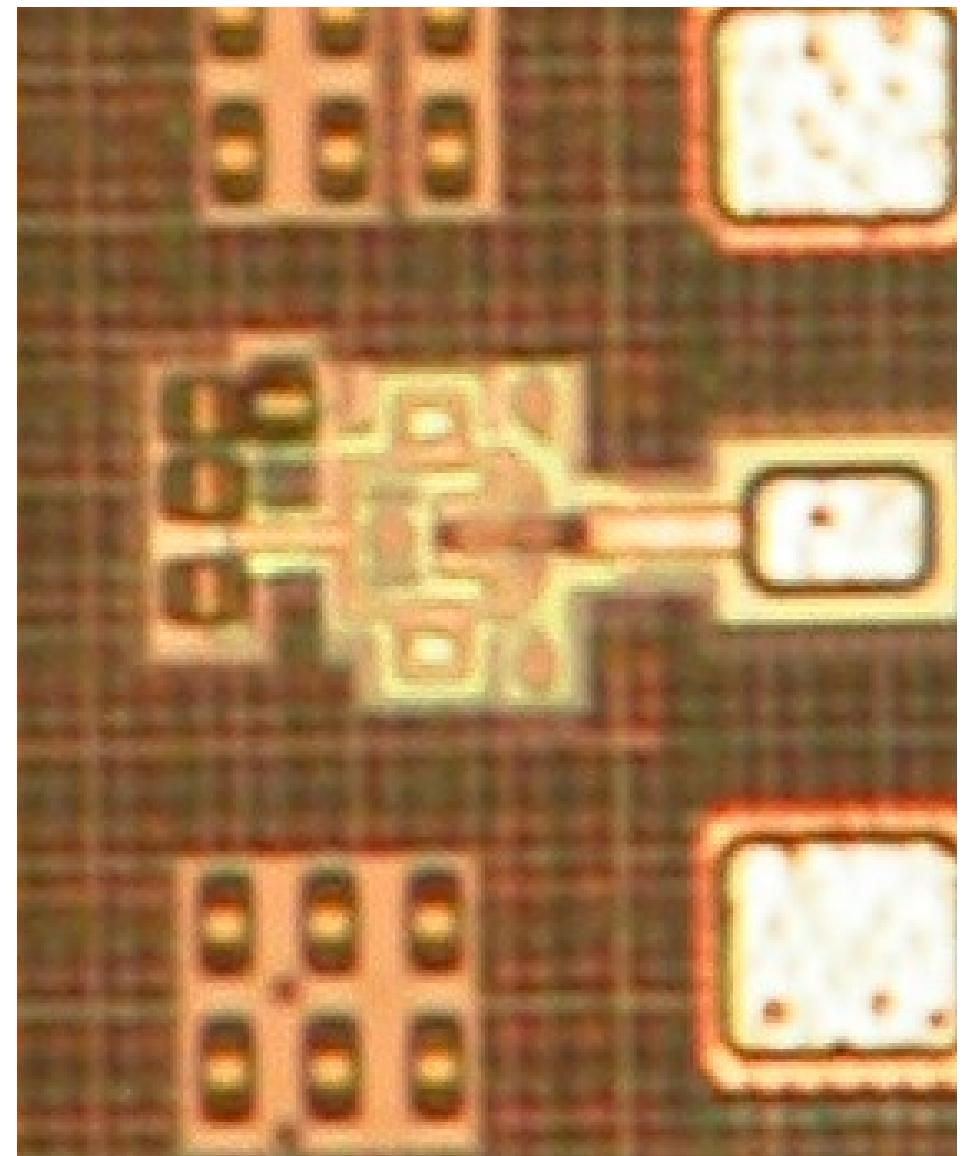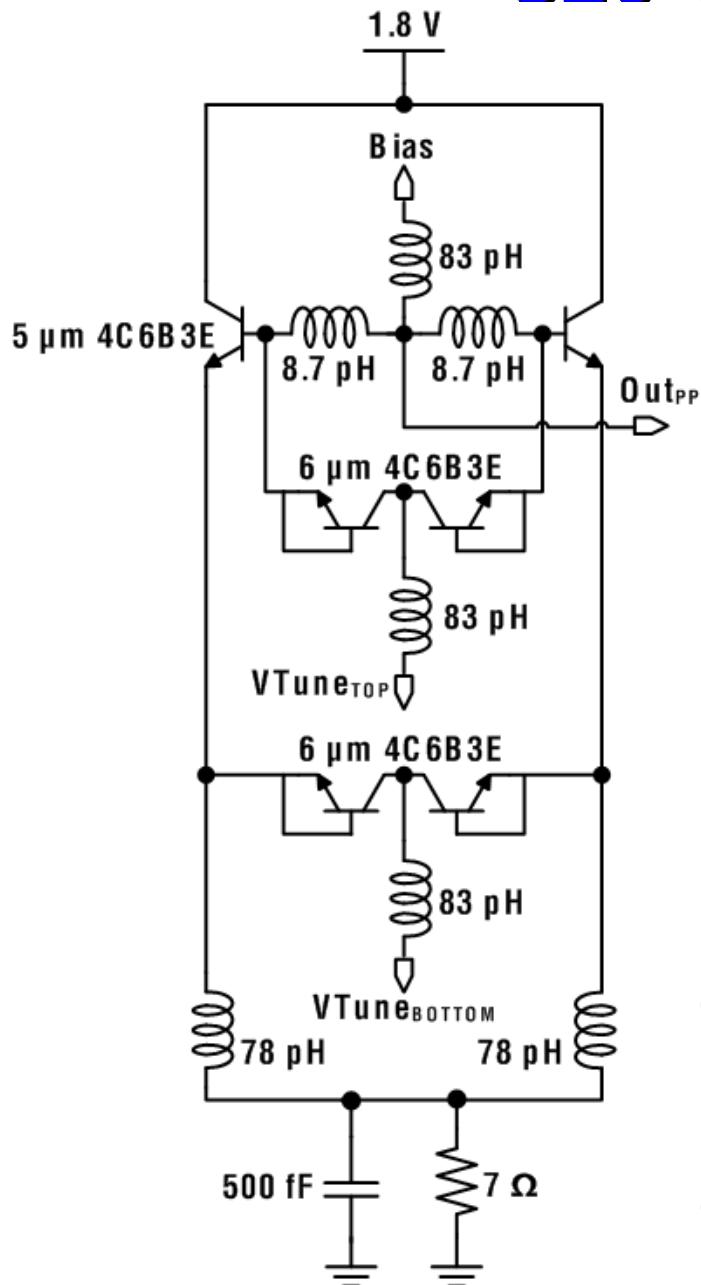

[A. Tomkins et al, BCTM 2012]


300-GHz VCO+Buffer+Doubler

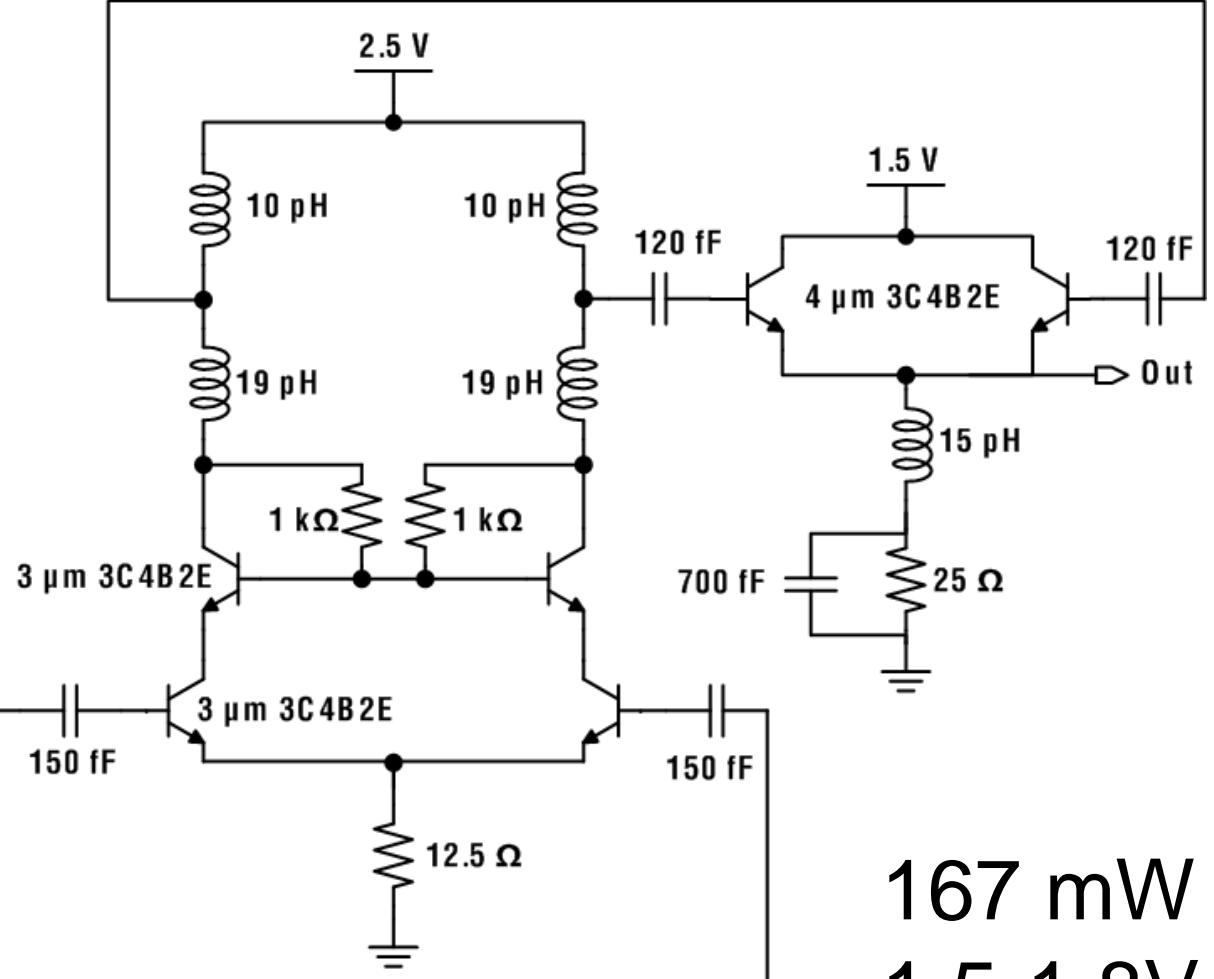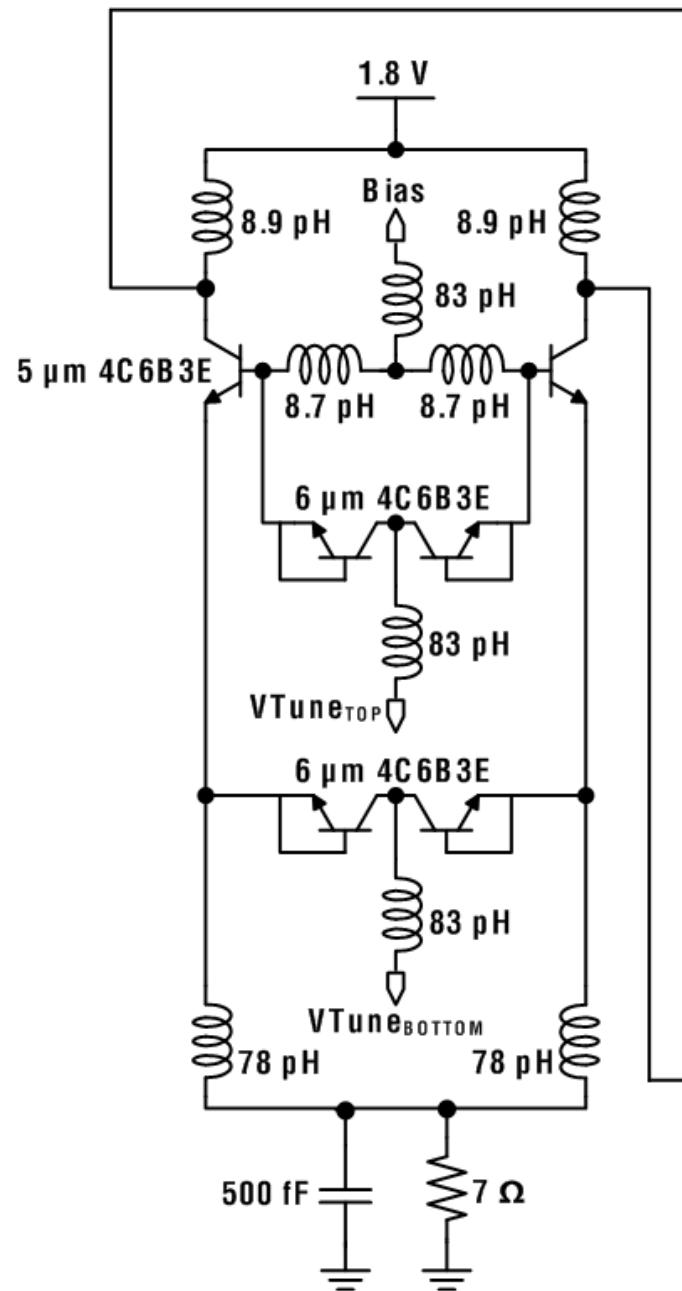

[A. Tomkins et al, BCTM 2012]

167 mW
1.5-1.8V
0.4%


Layout

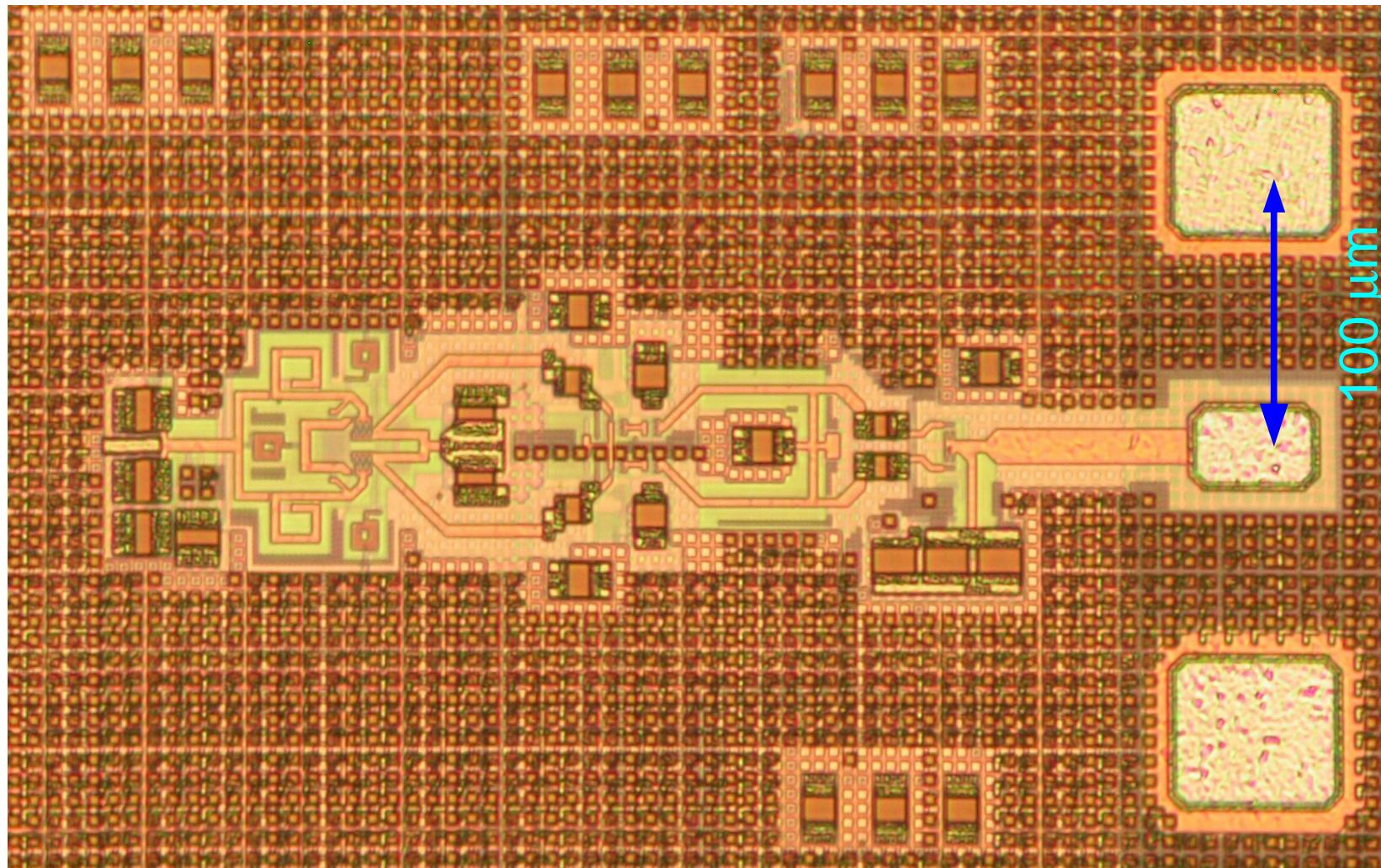


200+ GHz Signal Source Test Methodology

- S-parameters for $f_{osc}(V)$ from regions where $S_{11} > 0$ dB
[K. Yau et al., IEEE Micro, Feb. 2012]
- VNA downconverter to 300 MHz IF and PSA for tuning range and phase noise
- Erikson calorimeter for P_{out} vs. control voltage


Tuning Range: S-Params/Spectrum

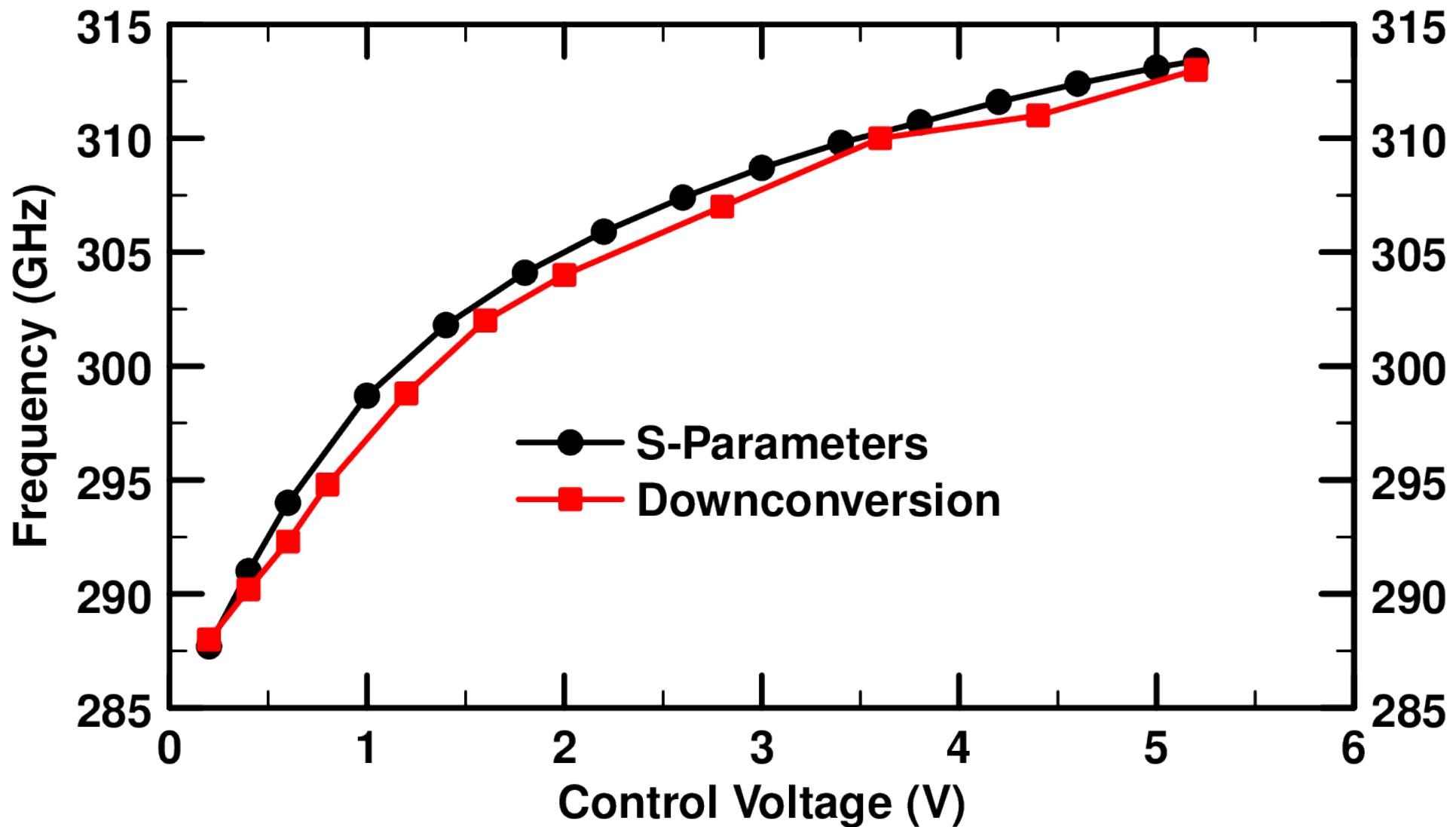


240-GHz VCO Phase Noise and P_{OUT}

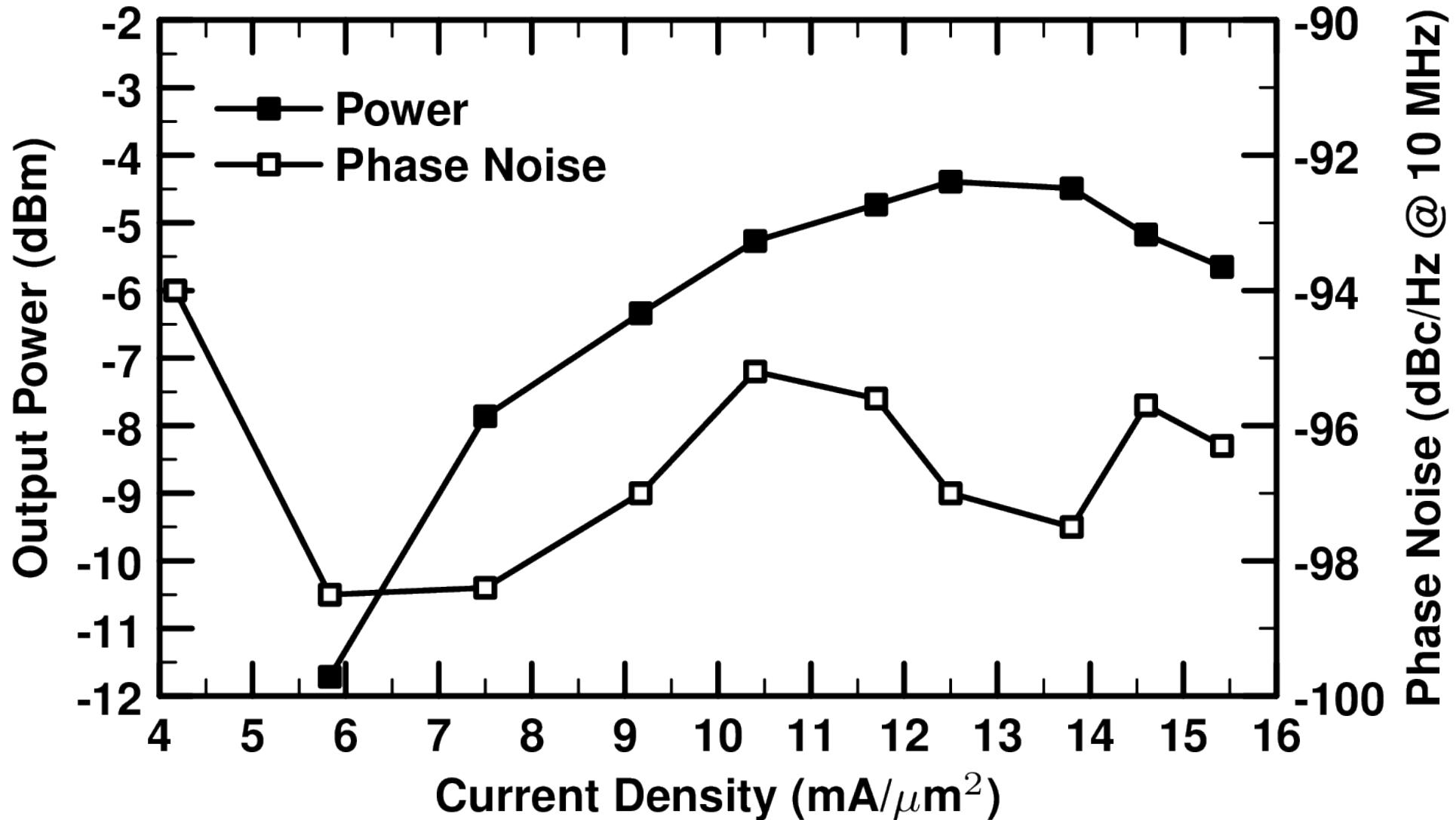


150/240 GHz VCO Comparison

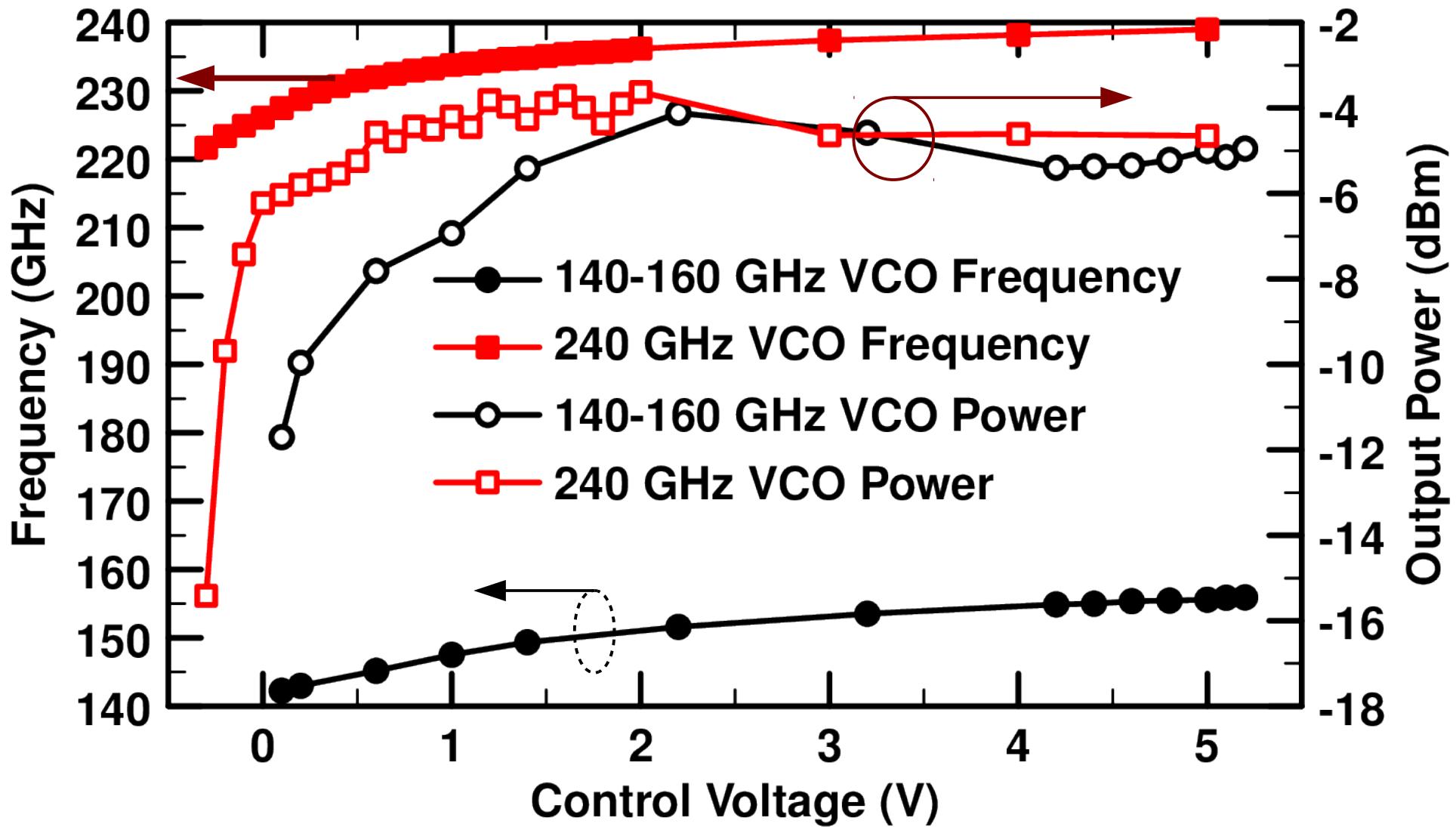

300-GHz Signal Source Comparison

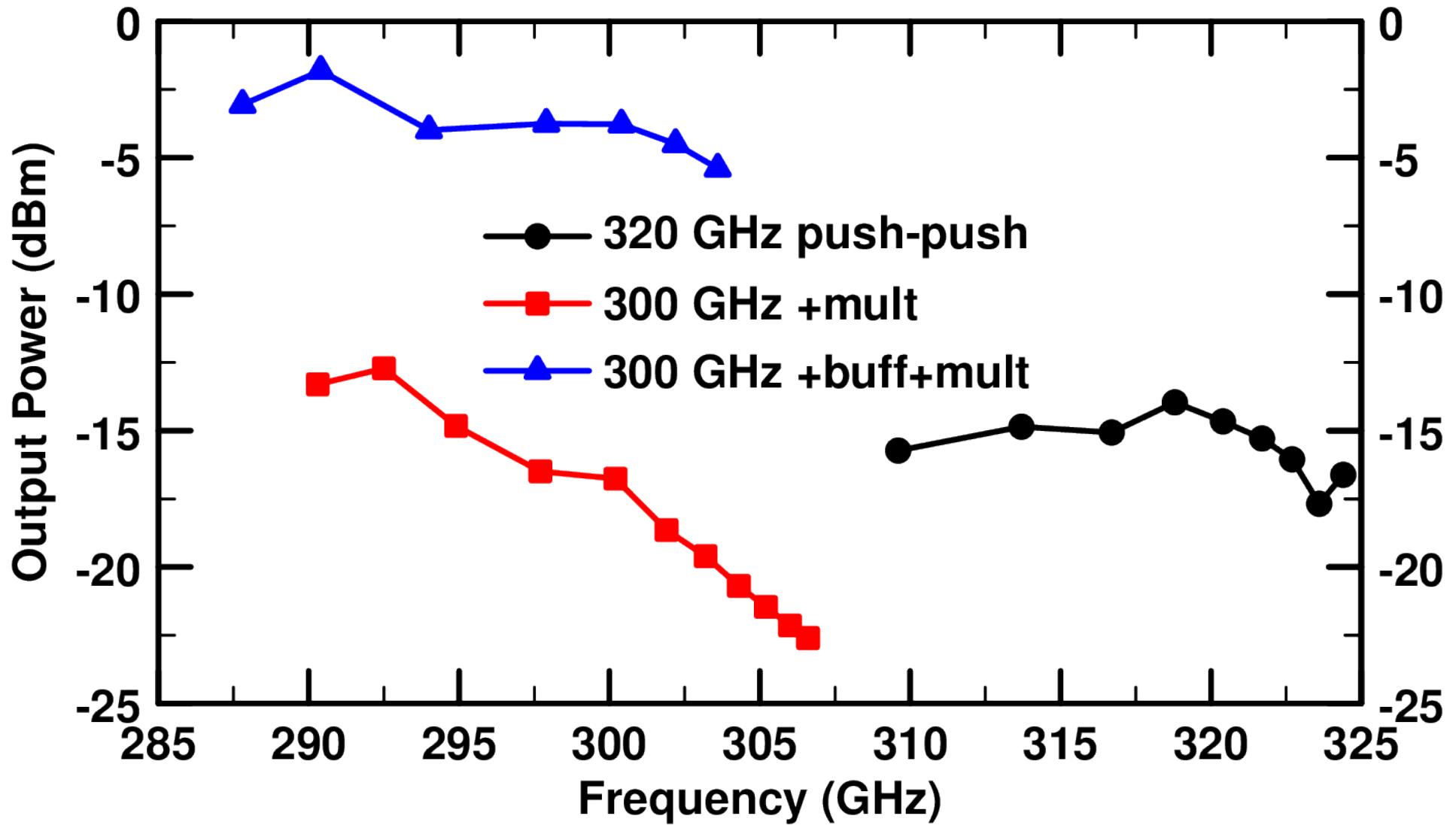


300-GHz Signal Source Comparison (ii)

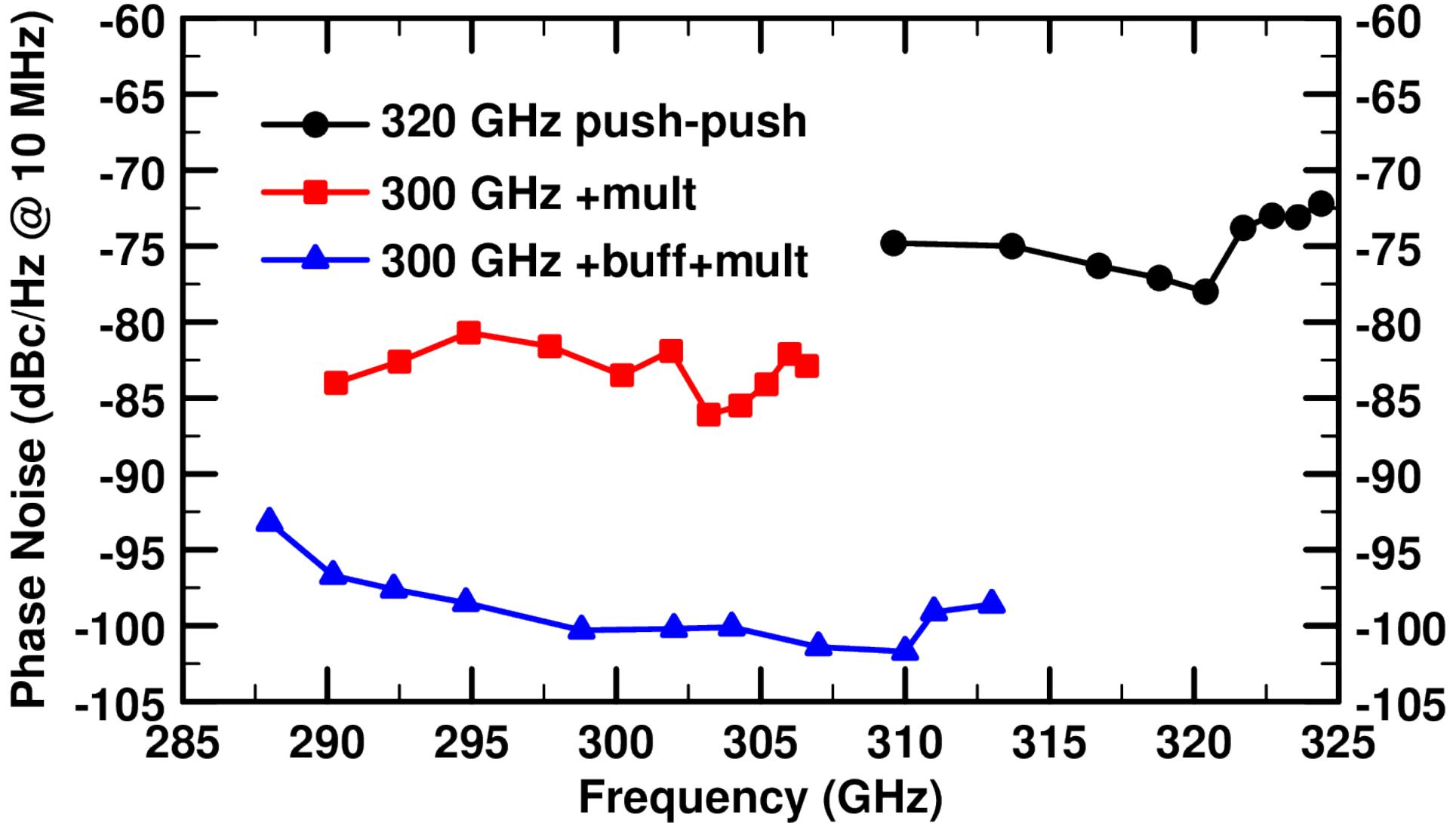


Phase Noise of VCO-doubler at 309 GHz

* Agilent 09:50:55 Feb 2, 2012

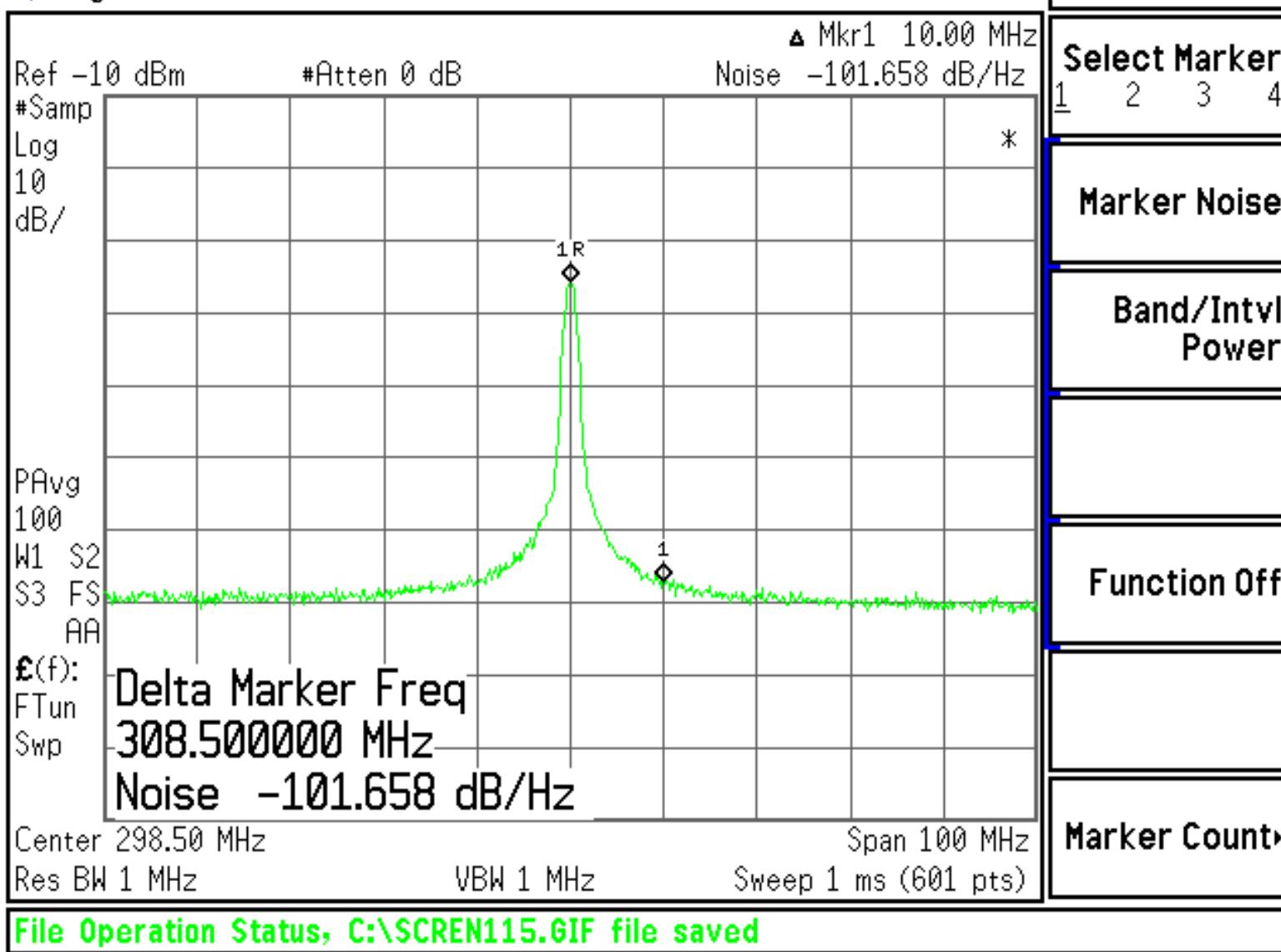


300-GHz vs. 150-GHz Phase Noise

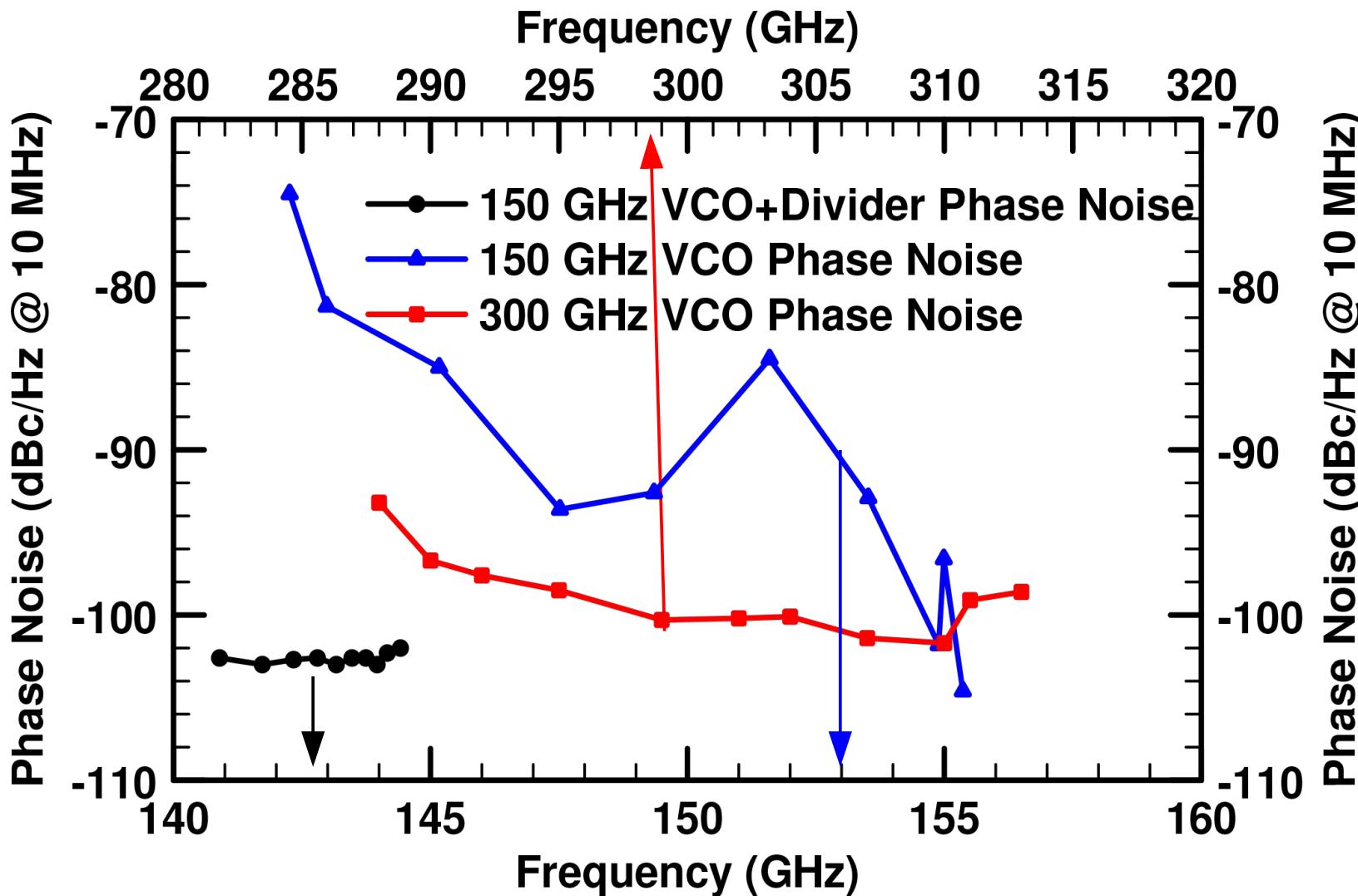

SAME VCO in BOTH!

480-GHz source: VCO+doubler

Did not detect signal yet!


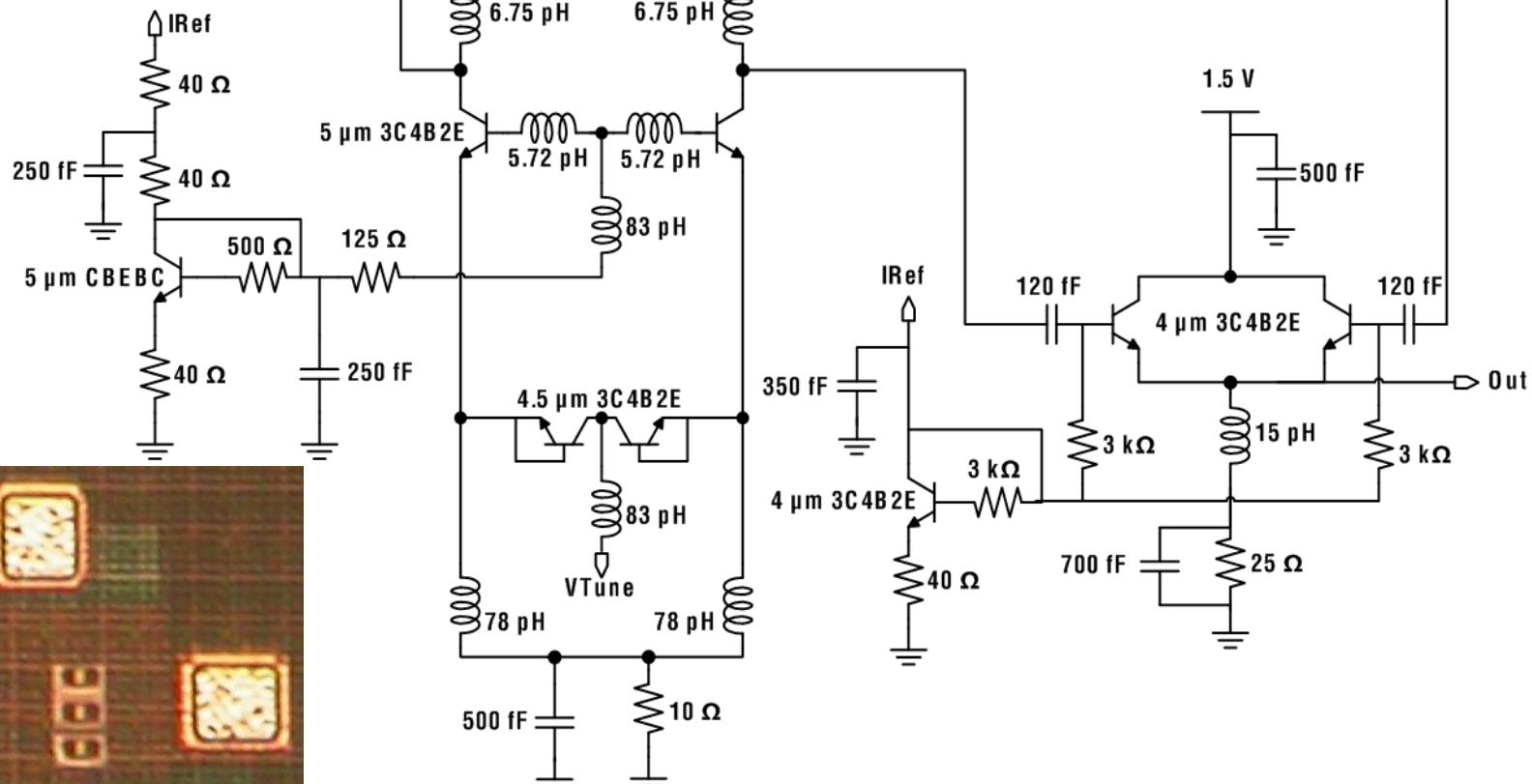


Conclusions

- D-Band Push-push & fundamental frequency transceivers
- On-die and in-package antennas
- 240-GHz fundamental VCO in SiGe
- Lowest phase noise 300-GHz signal source
- Buffer between VCO and doubler is critical
- 240-300 GHz transceiver feasible in 55-nm SiGe BiCMOS

Why 100-300 GHz?

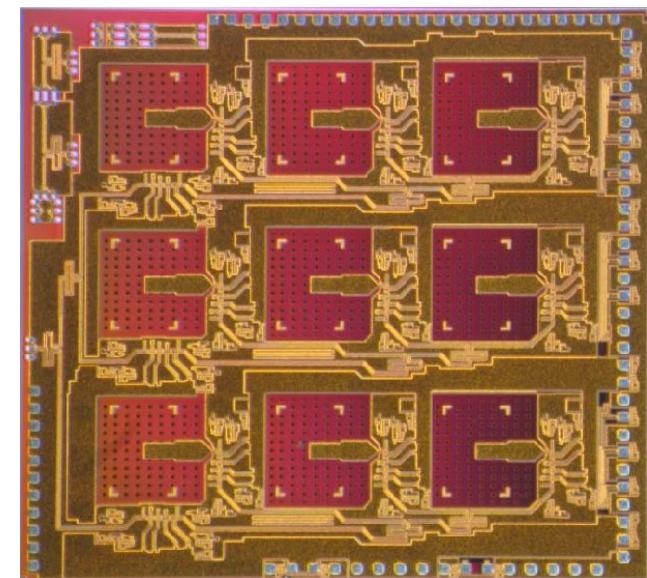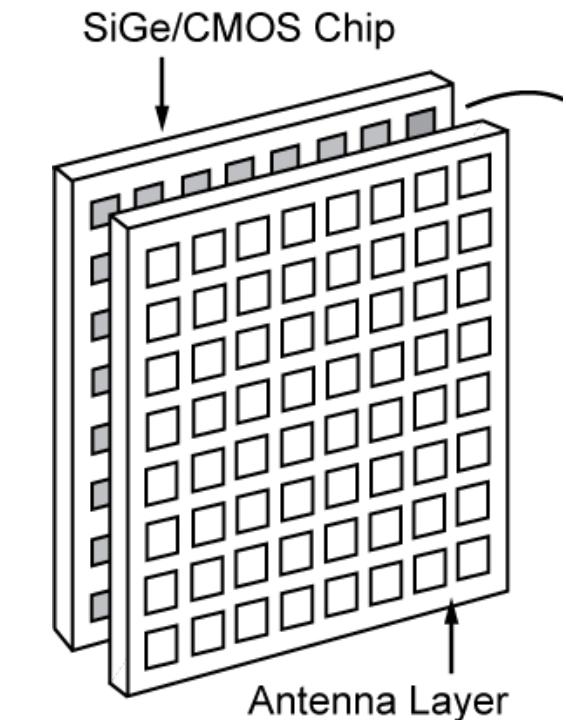
- Silicon transistors with $f_{MAX} > 400$ GHz
- Smaller wavelengths: high res, high BW
- Small antenna size with good gain
- Lower power LNA, mixer, receiver
- But...
 - ◆ higher power PLL,
 - ◆ reduced P_{out} ,
 - ◆ shorter range $\sim 1/f^2$ or $\sim 1/f^4$




Source: G. Rebeiz UCSD

Technology: 280/400 GHz SiGe HBT

Mm-wave 6-metal Cu BEOL + Alucap

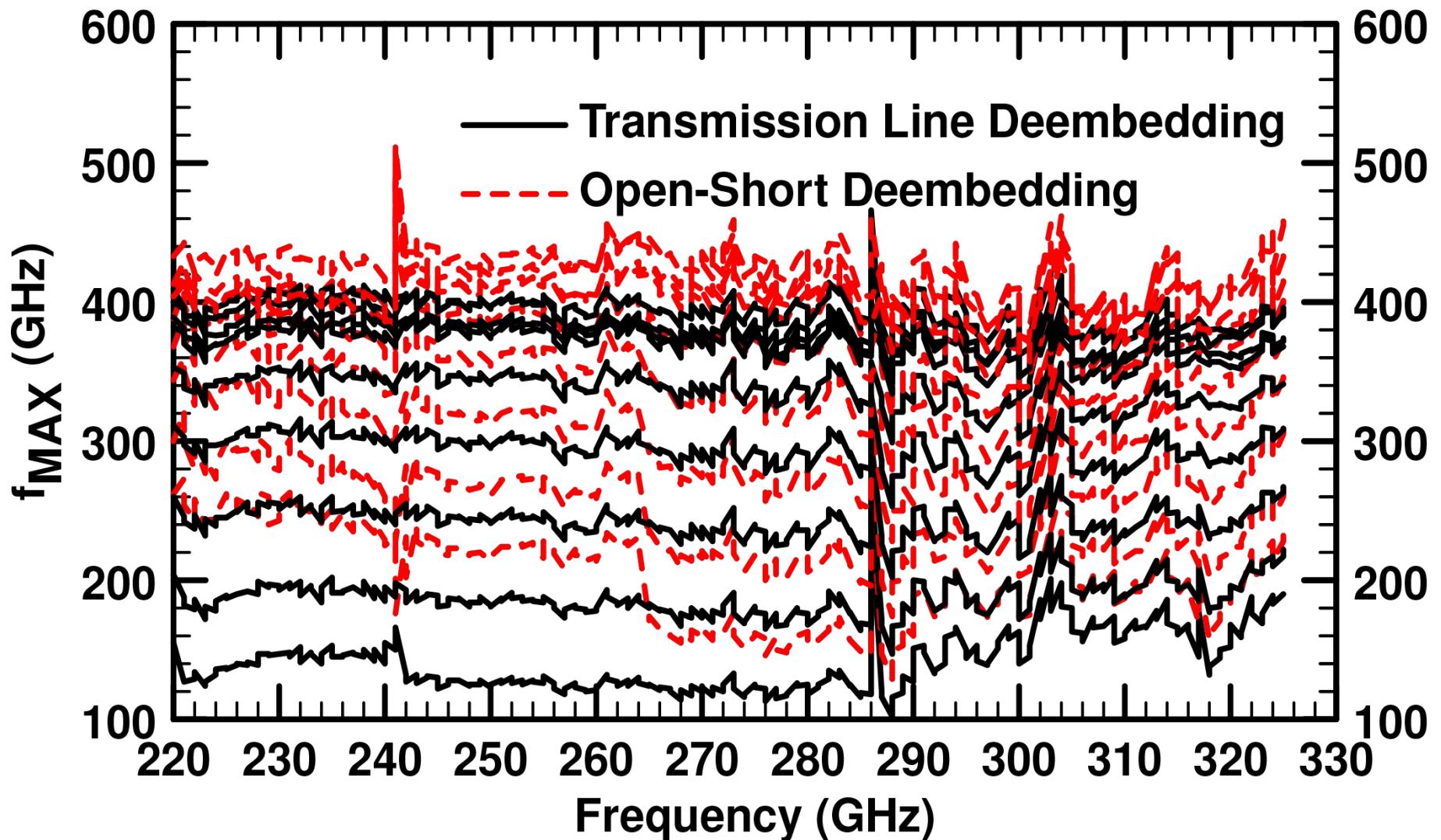


SiGe HBT Model Verification to 325 GHz

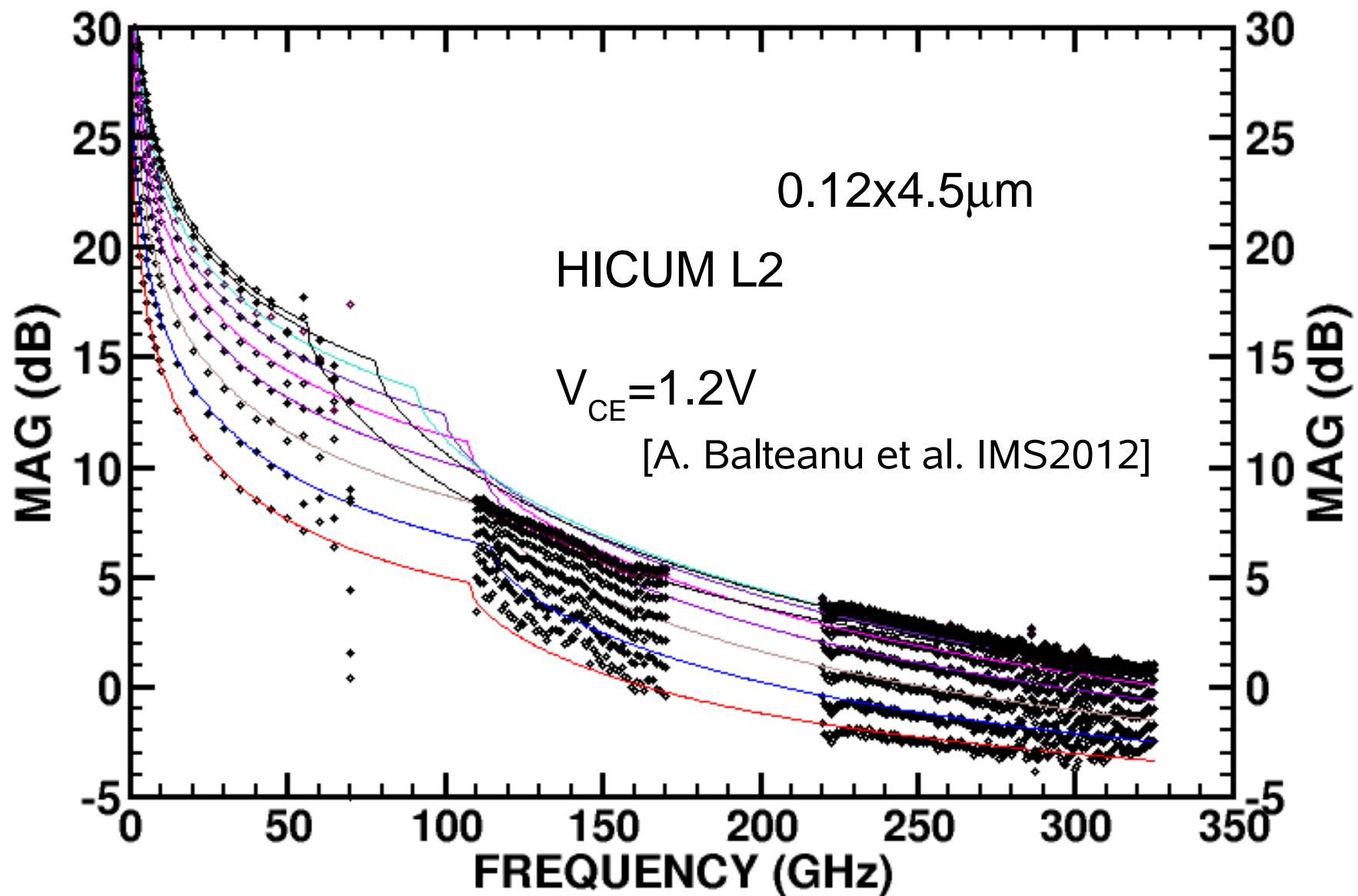

Outline



- Motivation
- Technologies
- 120-123 GHz Distance Sensor with above IC Antenna
- 150-170 GHz Transceiver with 3 on Die Antennas
- 143-150 GHz SUCCESS Sensor with BIST
- Potential Solutions for G-Band Sensors

120-GHz Distance Sensor

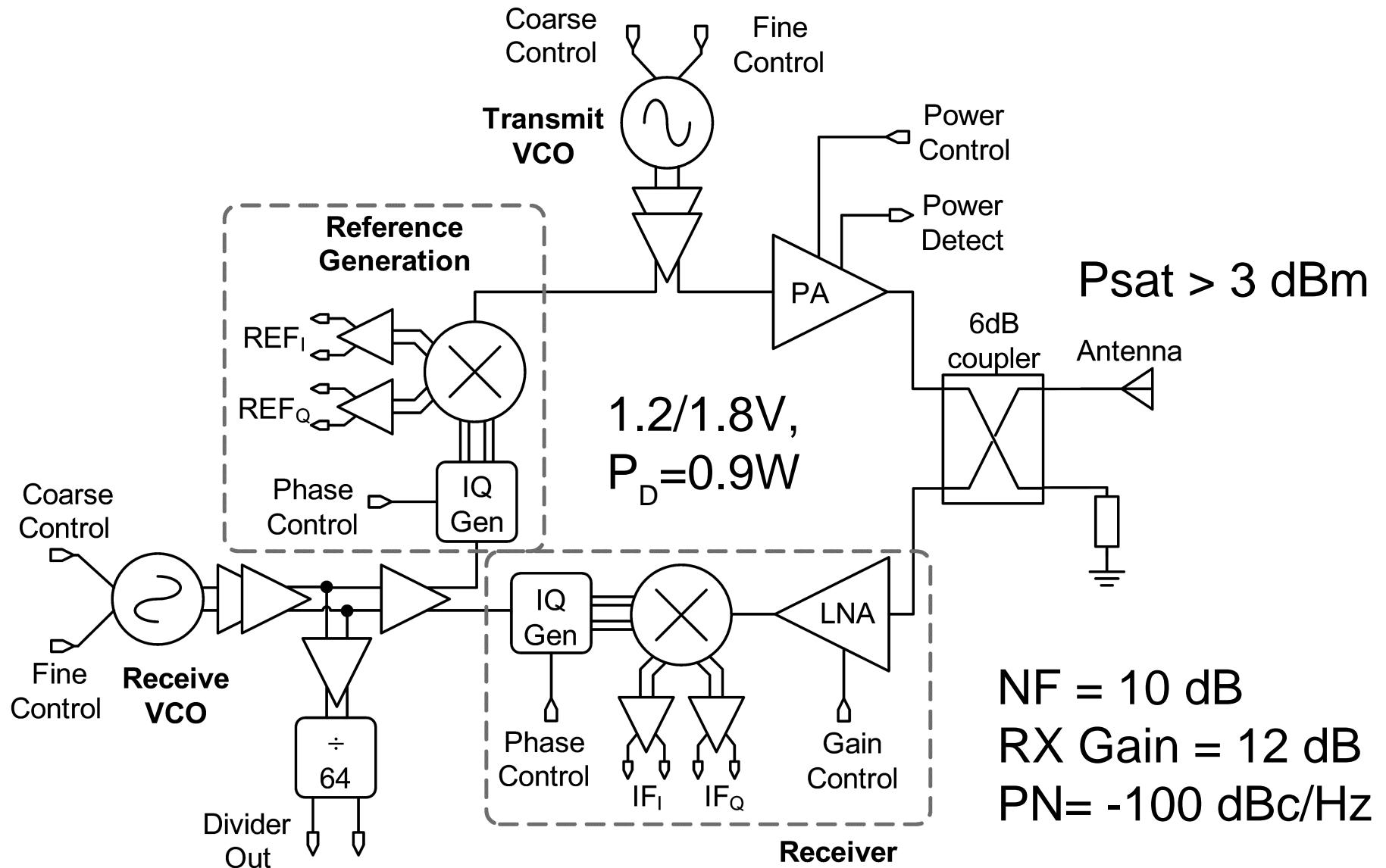

[I. Sarkas et al. Trans. MTT, March 2012]

Layout and Packaging

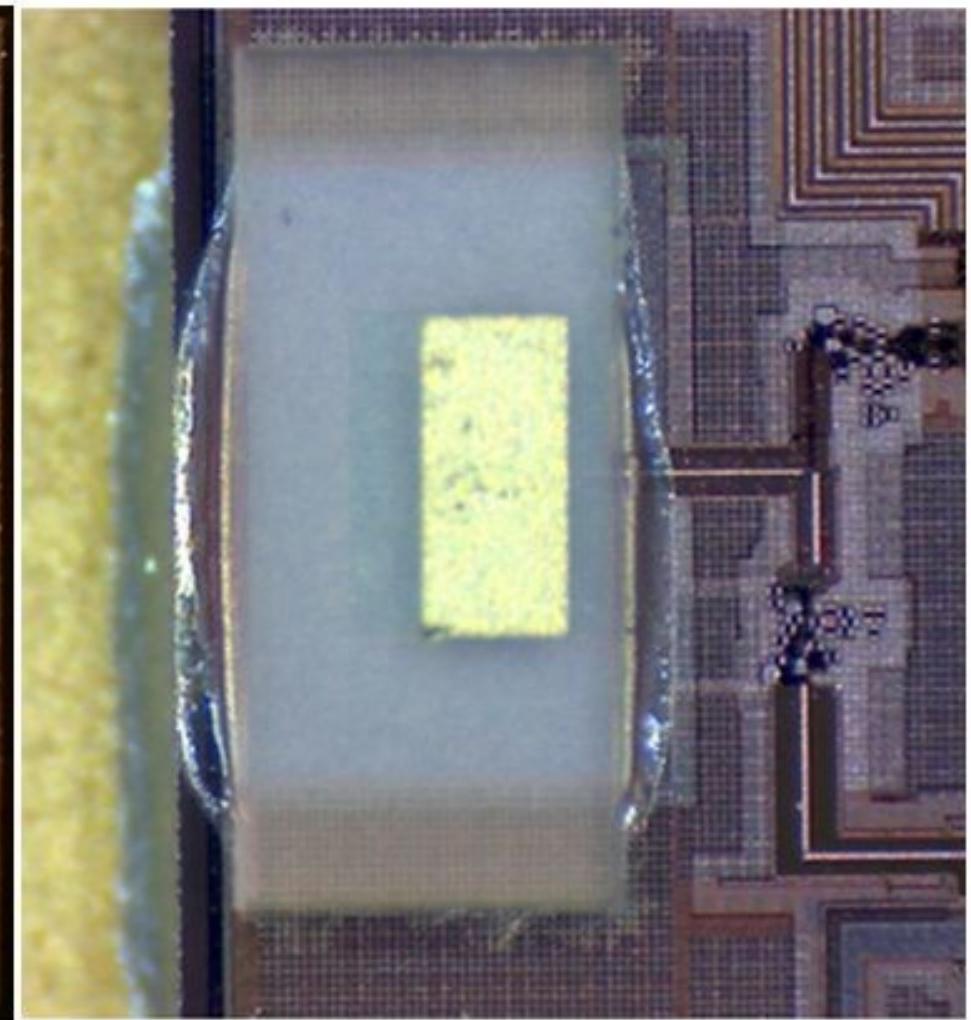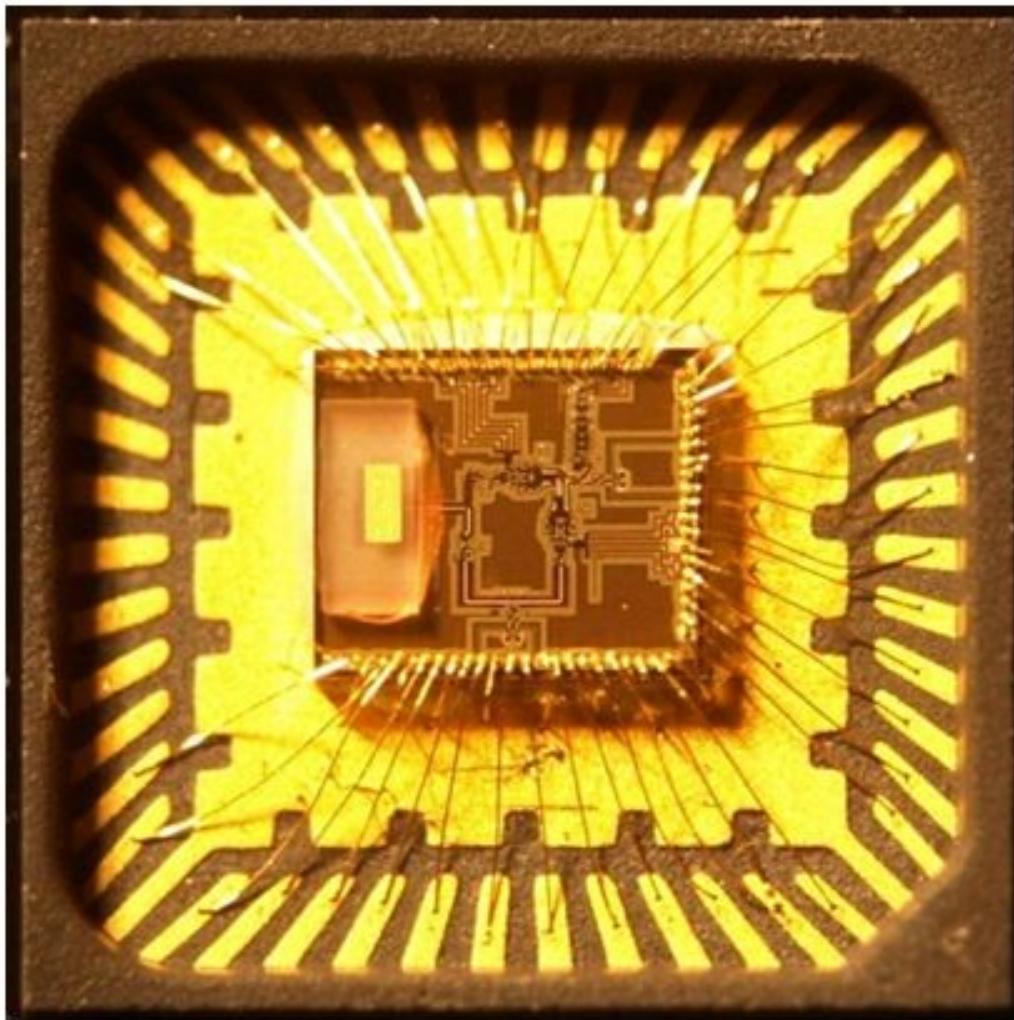


Chip: 2.2mm×2.6mm

Package: 7mm×7mm

Dr. J. Hasch


130-nm BiCMOS9MW: SiGe HBT $f_T = 230$ GHz, $f_{MAX} = 280$ GHz

Measured Output Power above Antenna

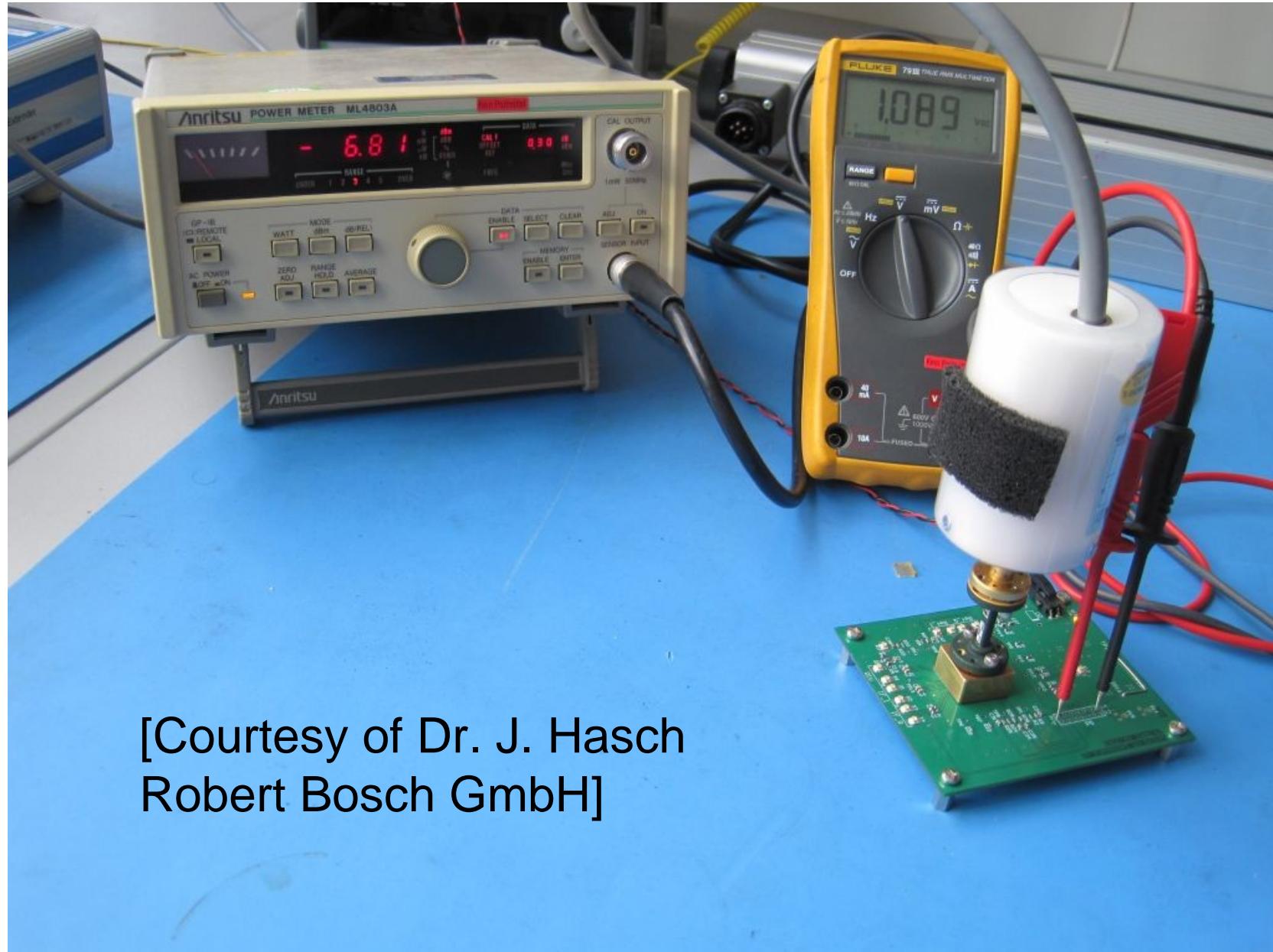



[Courtesy of Dr. J. Hasch
Robert Bosch GmbH]

150-GHz VCO-prescaler


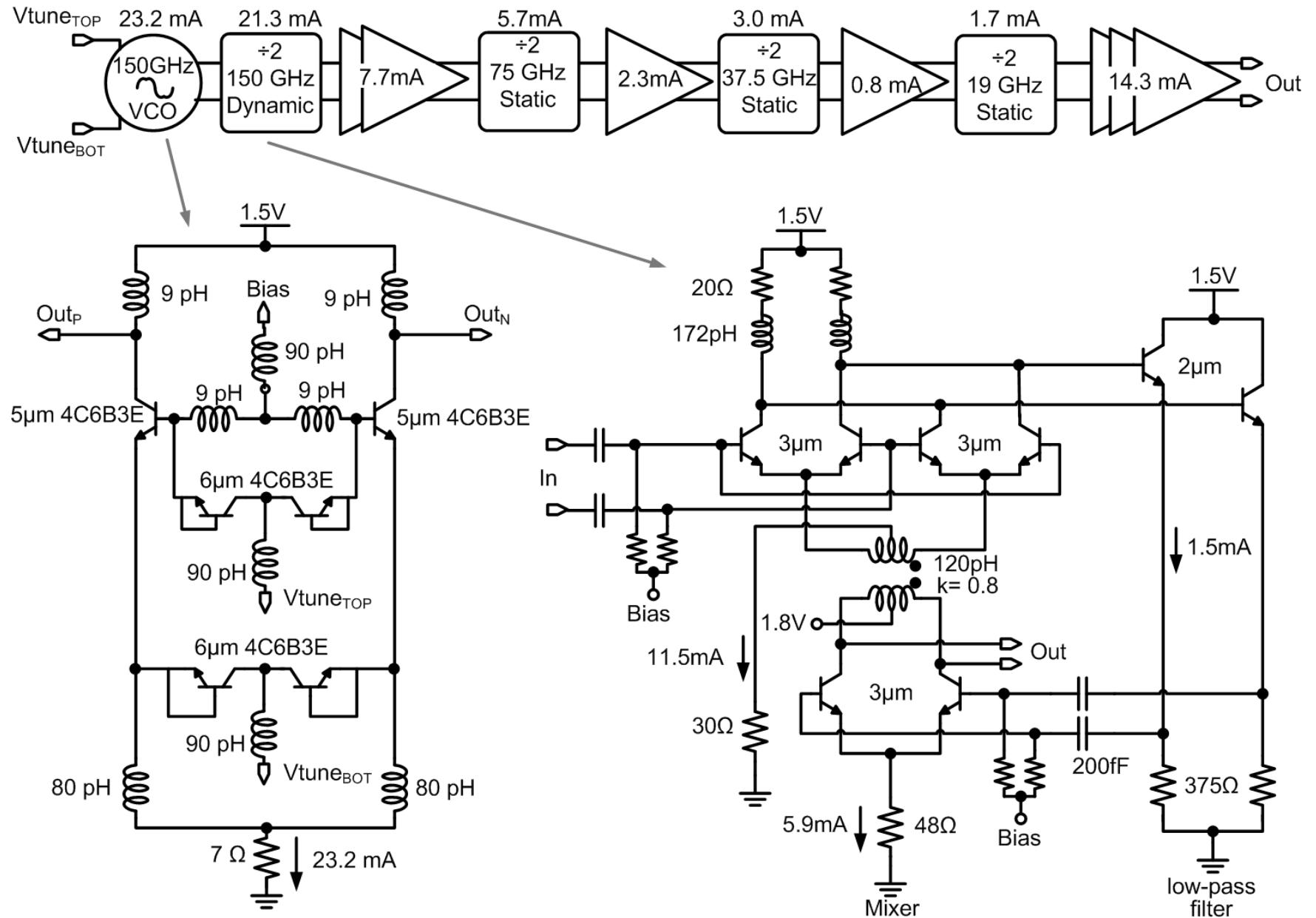


[A. Balteanu et al IMS 2012]

150-GHz VCO Synthesizer Measurements

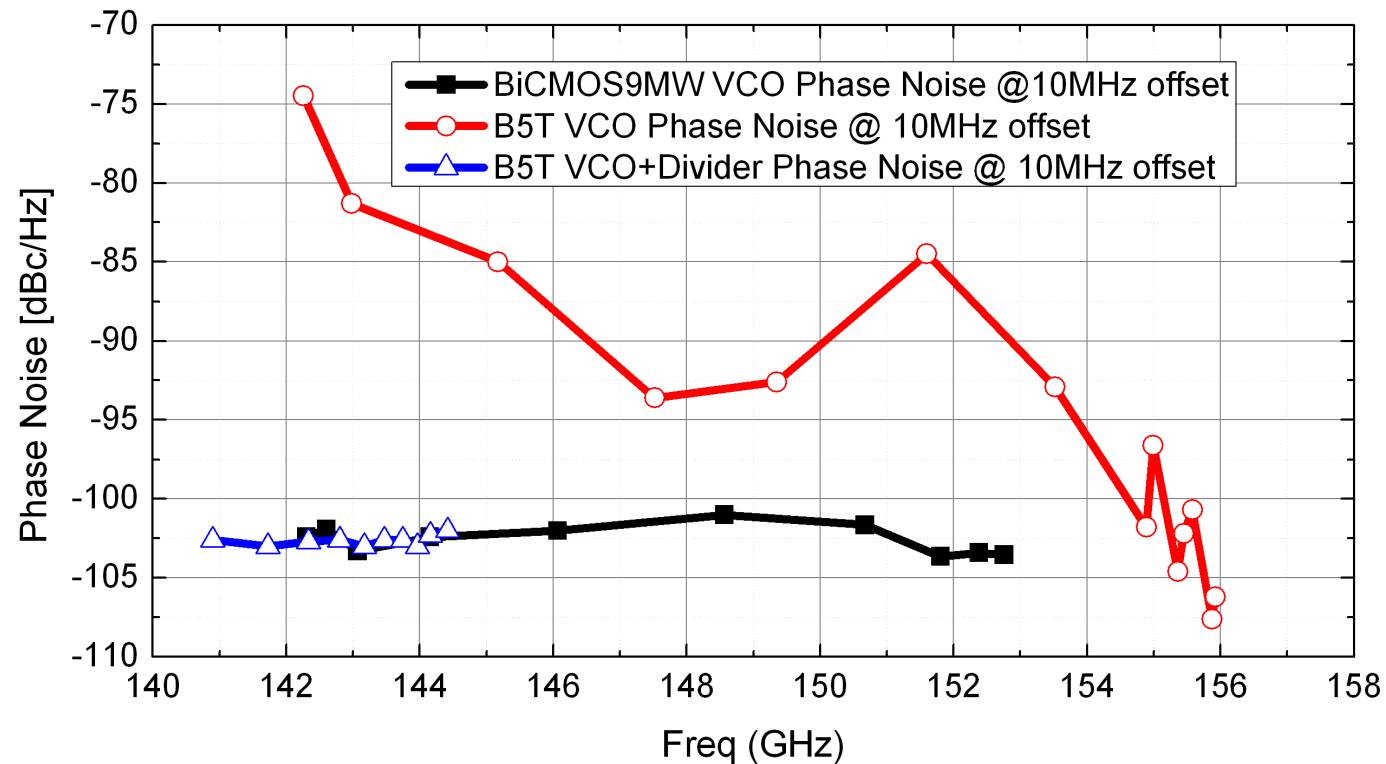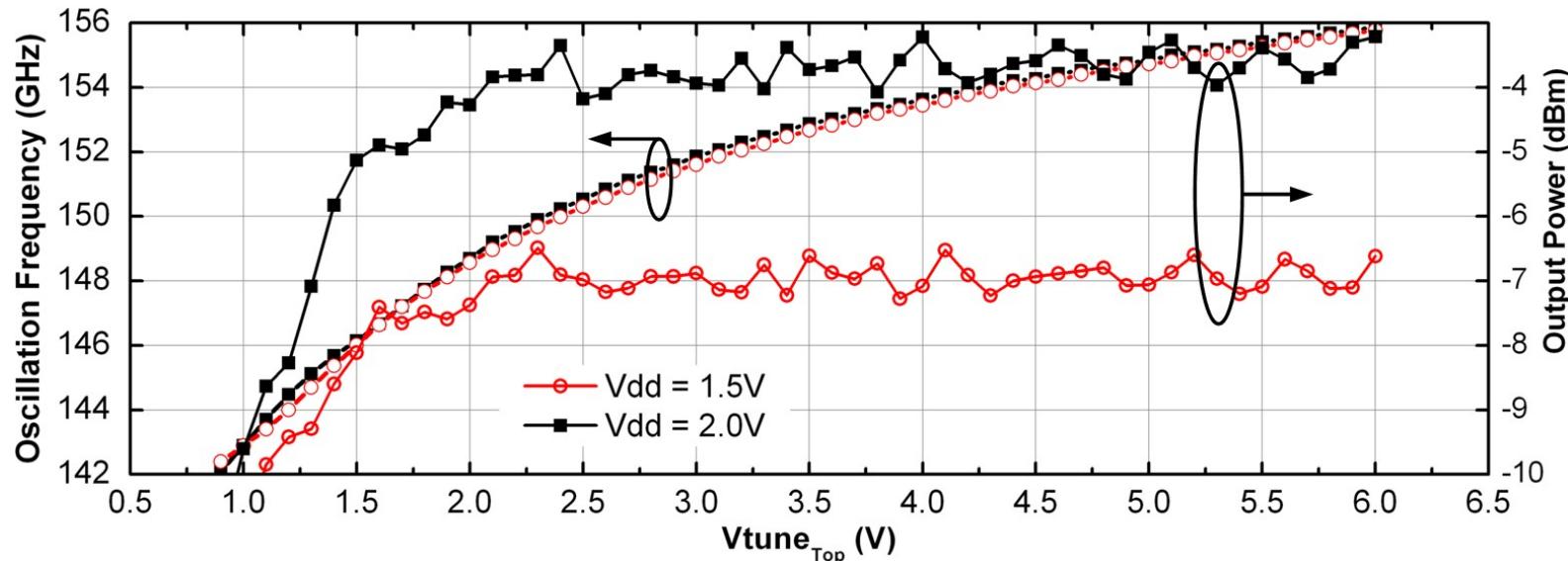


Packaging: QFN & wirebonding

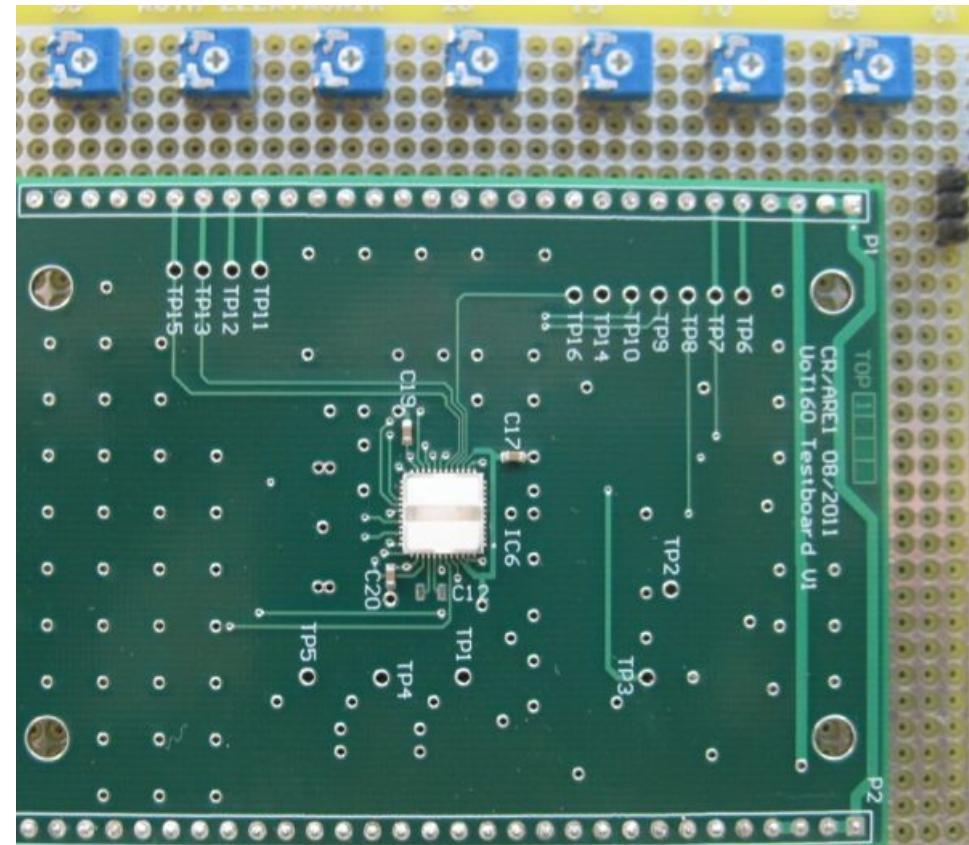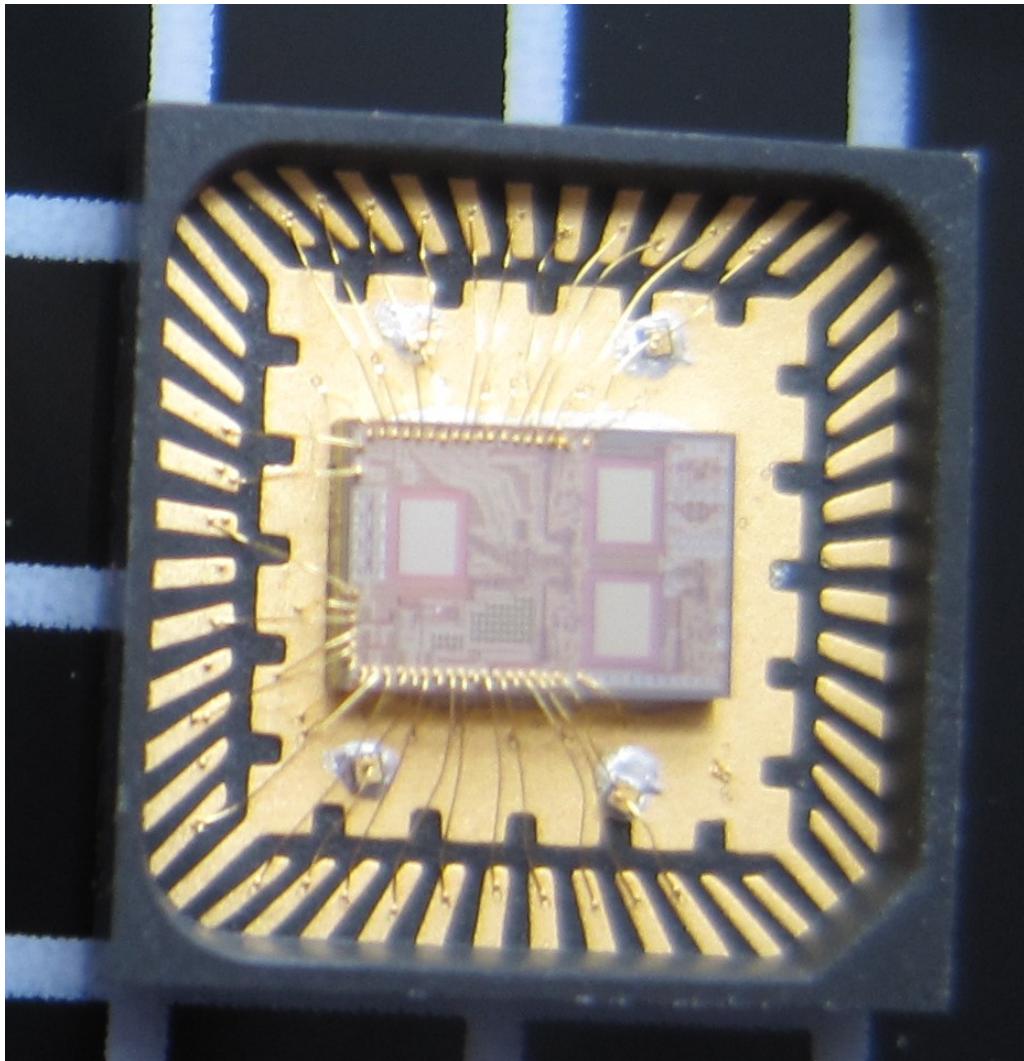

[Courtesy of Dr. J. Hasch
Robert Bosch GmbH]

In-package antennas simulation

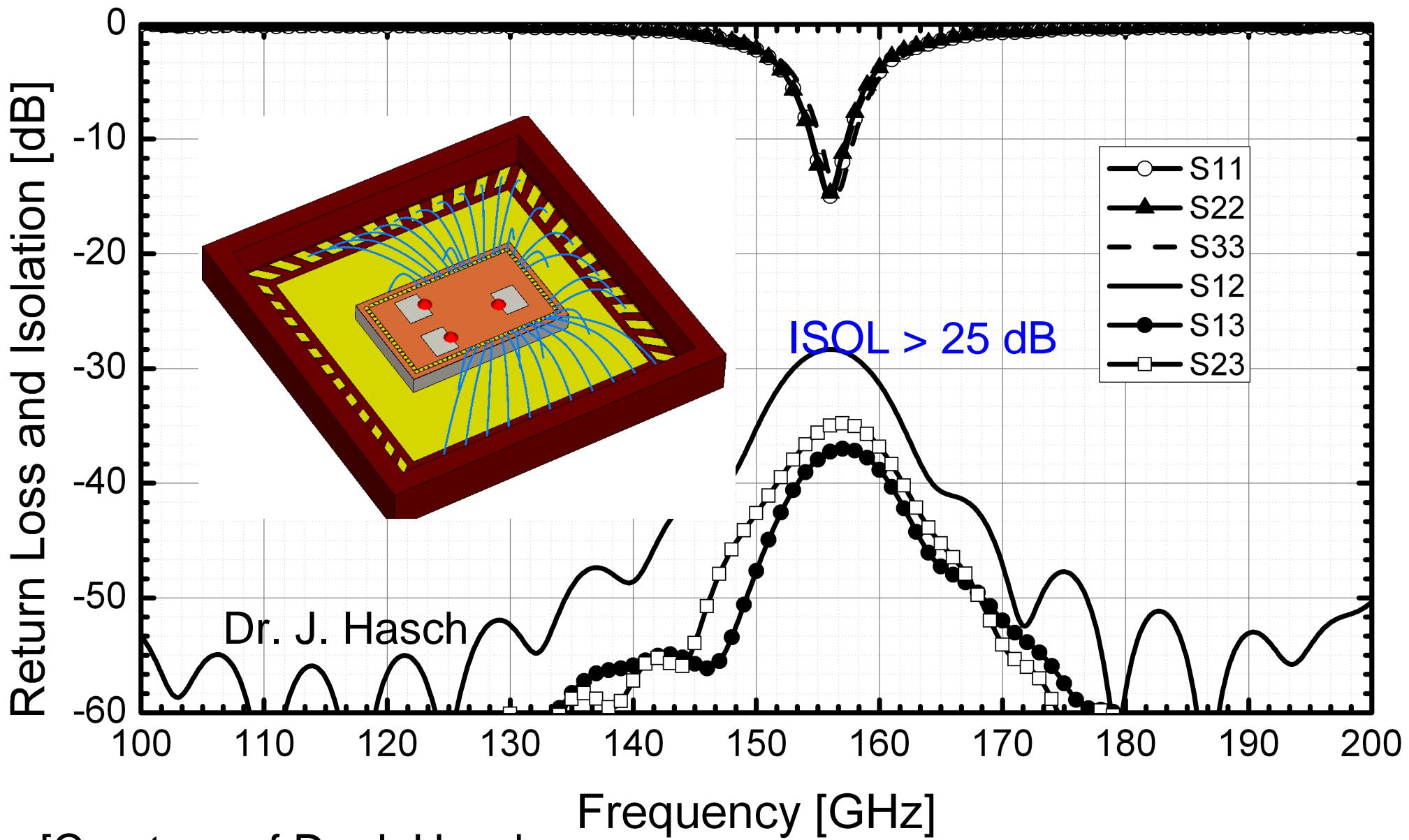

[Courtesy of Dr. J. Hasch
Robert Bosch GmbH]

Measured Pout and Phase Noise 300-GHz source: VCO+buffer+doubler

