

Practical Challenges for Electronic Dispersion Compensation in CMOS

Tony Chan Carusone
University of Toronto
tcc@eecg.utoronto.ca

July 23, 2007




Outline

- Architectures for CMOS EDC
- Linear equalizer implementations
- Feedback equalizer implementations
- Towards 40-Gb/s DSP-based EDC
- Conclusions



Electronic Dispersion Compensation

 - Perform CD compensation optically
- PMD compensation must be adaptive to track changes over milliseconds
- Fewer taps than EDC for both CD & PMD




Practical Challenges for Electronic Dispersion Compensation in CMOS



3

Electronic Dispersion Compensation

 - Possibilities
 - Linear equalization
 - Decision feedback equalization
 - MLSE



Practical Challenges for Electronic Dispersion Compensation in CMOS



4

DFE Design Parameters

$IN \rightarrow [b_0] \oplus [b_1] \oplus [b_2] \rightarrow [] \xrightarrow{CLK} [] \rightarrow OUT$

τ_F (for b_1, b_2), τ_B (for a_1, a_2)

5

DFE Design Parameters

$IN \rightarrow [b_0] \oplus [b_1] \oplus [b_2] \rightarrow [] \xrightarrow{CLK} [] \rightarrow OUT$

τ_F (for b_1, b_2), τ_B (for a_1, a_2)

Linear Equalizer
Feedback Equalizer

6

DFE Design Parameters

Challenges:

- Inherent delay-bandwidth-gain tradeoffs
- Timing critical path in the feedback equalizer
- Extensibility of analog/mixed-signal approaches to long impulse responses


Practical Challenges for Electronic Dispersion Compensation in CMOS 7

DFE Design Parameters

• N_F and N_B are chosen just large enough to cover the worst-case (i.e. longest) fiber pulse response


Practical Challenges for Electronic Dispersion Compensation in CMOS 8

DFE Design Parameters

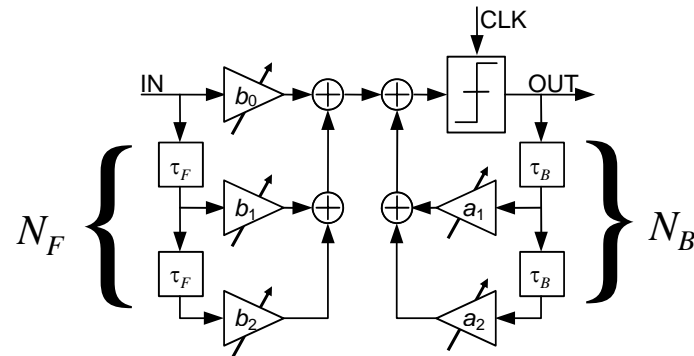

- τ_B is generally equal to one bit period since OUT is updated by the clock



DFE Design Parameters

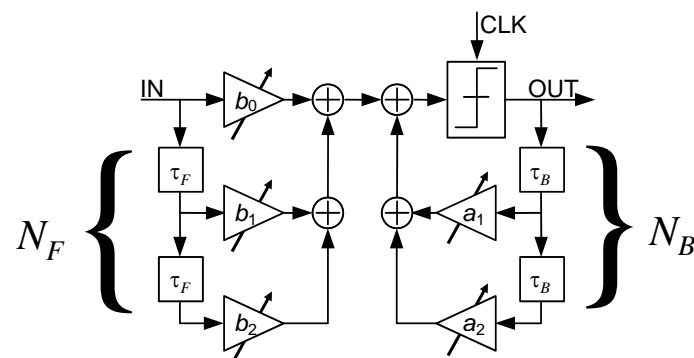


- τ_F can either be one bit period or a fraction thereof

Fractional vs. Baud-Rate Tap-Spacing

  - Fractional tap-spacing introduces correlation between neighboring tap signals
- This can cause the adaptation engine to become “confused” and to converge slowly, or diverge
- Example:
 - 7-tap linear equalizer
 - Ideal LMS adaptation




Fractional vs. Baud-Rate Tap-Spacing

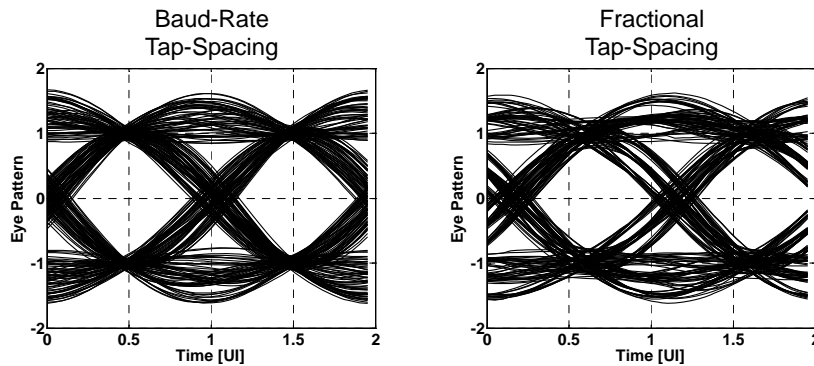

- Negligible difference in performance



Implementation of Linear Equalizer

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



13

3-Tap Traveling Wave Filter

 


Passive delay lines consume no power

Practical Challenges for Electronic Dispersion Compensation in CMOS




14


3-Tap Traveling Wave Filter

 

3-Tap Traveling Wave Filter

 

3-Tap Traveling Wave Filter

 

$$\text{Tap spacing : } \tau = 2\sqrt{LC}$$

$$\text{Delay Line Bandwidth : } f_{3\text{dB}} = \frac{1}{\pi\sqrt{LC}} = \frac{2}{\pi\tau}$$

$$\text{Maximum gain per tap } \propto C$$



Practical Challenges for Electronic Dispersion Compensation in CMOS



17

3-Tap Traveling Wave Filter

  - Example: Simulated 3-section lumped-LC delay line designed for 25-ps tap spacing (baud-rate tap spacing at 40 Gb/s)




Practical Challenges for Electronic Dispersion Compensation in CMOS



18

6-Tap Traveling Wave Filter

 

Tap spacing : $\tau = \sqrt{LC}$



Delay Line Bandwidth : $f_{3dB} = \frac{2}{\pi\sqrt{LC}} = \frac{2}{\pi\tau}$

Maximum gain per tap $\propto C/2$




6-Tap Traveling Wave Filter

  - Example: Simulated 6-section lumped-LC delay line designed for the same total delay



3-Tap Crossover TWF

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



21



3-Tap Crossover TWF

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



22

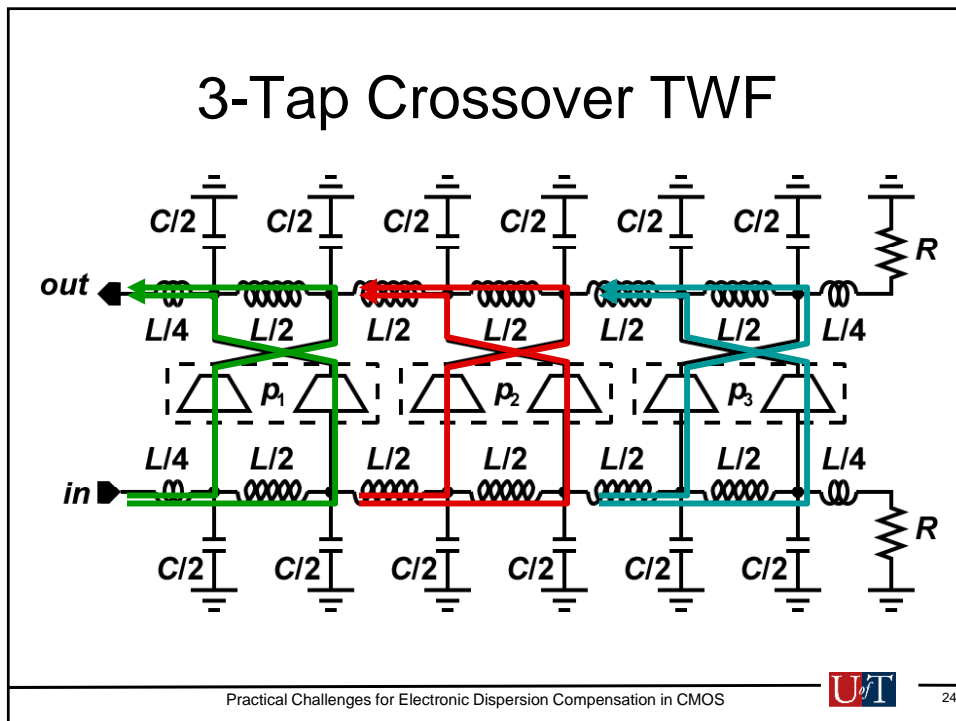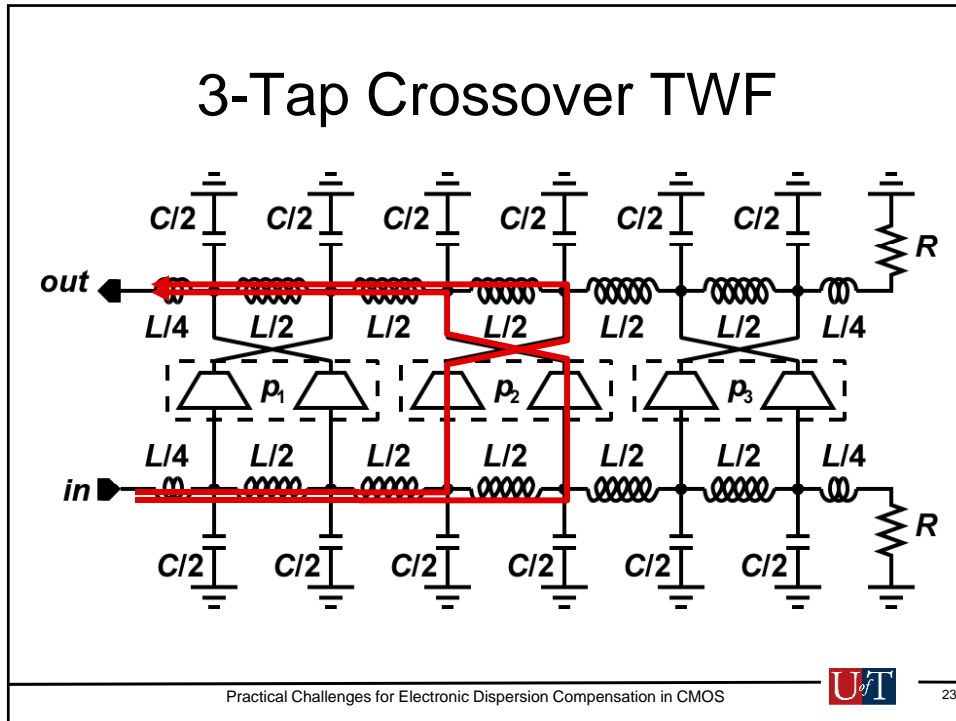

3-Tap Crossover TWF

 

$$\text{Tap spacing : } \tau = 2\sqrt{LC}$$


$$\text{Delay Line Bandwidth : } f_{3\text{dB}} = \frac{2}{\pi\sqrt{LC}} = \frac{4}{\pi\tau}$$

$$\text{Maximum gain per tap } \propto C$$

Summary

	Tap spacing	Delay line bandwidth	Max. gain per tap
3-tap TWF	$2\sqrt{LC}$	$\frac{1}{\pi\sqrt{LC}}$	$\propto C$
6-tap TWF	\sqrt{LC}	$\frac{2}{\pi\sqrt{LC}}$	$\propto C/2$
3-tap CTWF	$2\sqrt{LC}$	$\frac{2}{\pi\sqrt{LC}}$	$\propto C$

Prototype Implementation

 

- 90-nm CMOS process
- 24 mW from 1-V supply


Practical Challenges for Electronic Dispersion Compensation in CMOS



27

30-Gb/s Equalizer in 90-nm CMOS

Jonathan Sewter, M.A.Sc.

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



28

30-Gb/s Equalizer in 90-nm CMOS

Jonathan Sewter, M.A.Sc.

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



29

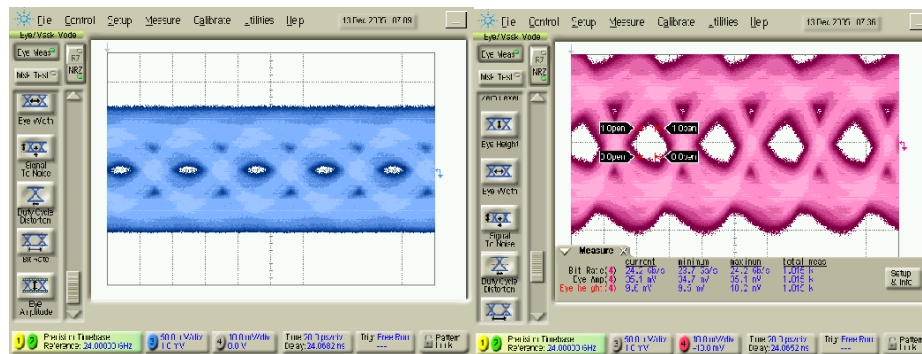Input and output eye diagrams at 20 Gb/s over 12-dB loss channel




Practical Challenges for Electronic Dispersion Compensation in CMOS




30

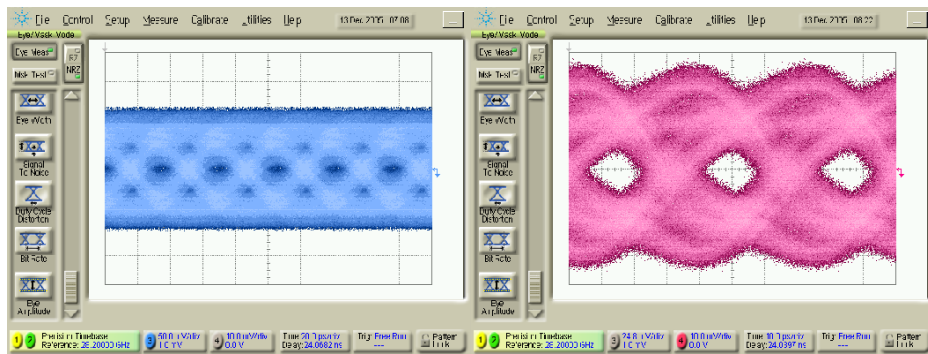
Input and output eye diagrams at 25 Gb/s over 13-dB loss channel



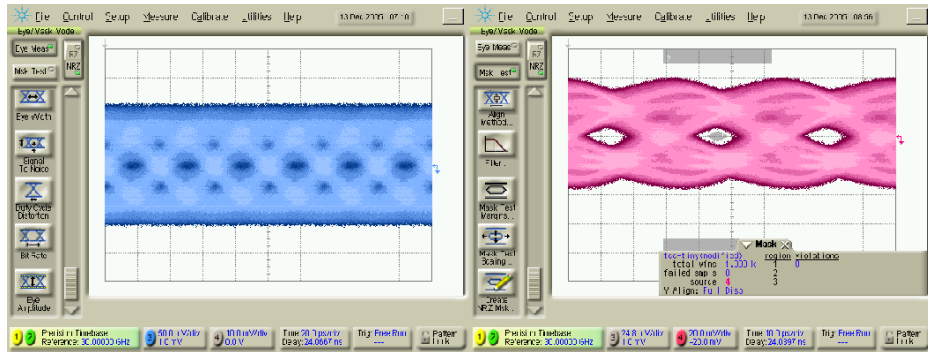Input and output eye diagrams at 30 Gb/s over 14-dB loss channel



3-Tap Crossover TWF

 


Tap spacing : $\tau = 2\sqrt{LC}$

Delay Line Bandwidth : $f_{3dB} = \frac{2}{\pi\sqrt{LC}} = \frac{4}{\pi\tau}$

Maximum gain per tap $\propto C$

3-Tap Crossover TWF

 


Tap spacing : $\tau = 2\sqrt{LC}$

Delay Line Bandwidth : $f_{3dB} = \frac{3}{\pi\sqrt{LC}} = \frac{6}{\pi\tau} ???$

Maximum gain per tap $\propto C$

3-Tap Crossover TWF

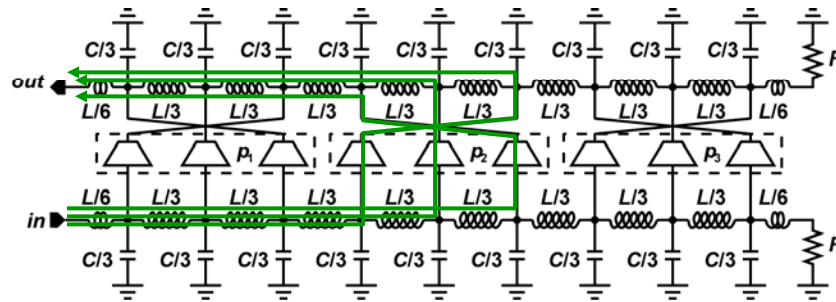


Practical Challenges for Electronic Dispersion Compensation in CMOS



35

3-Tap Crossover TWF

 


- **Problem:** The crossover routing could introduce skew and crosstalk between paths that must be matched

Practical Challenges for Electronic Dispersion Compensation in CMOS



36


Folded-Cascade TWF

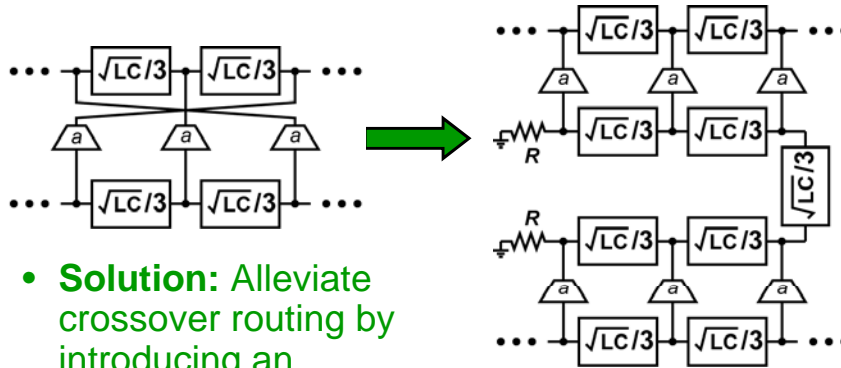

- **Solution:** Alleviate crossover routing by introducing an intermediate “folded” transmission line


Folded-Cascade TWF

 - Each path through this network goes through 5 delay sections and 2 amplifiers




Folded-Cascade TWF

 - Each path through this network goes through 5 delay sections and 2 amplifiers
- Each path has a gain of a^2 (assuming lossless delay elements)




Folded-Cascade TWF

 - Each path through this network goes through 5 delay sections and 2 amplifiers
- Each path has a gain of a^2 (assuming lossless delay elements)
- There are 9 such paths
 - Total gain through this tap is $9a^2$




Folded-Cascade TWF

 - **Alternate interpretation:**
This is a cascade of 2 distributed amplifiers
- Each has a gain of $3a$ (assuming lossless delay elements)
- Total gain is $9a^2$



3-Tap Folded-Cascade TWF

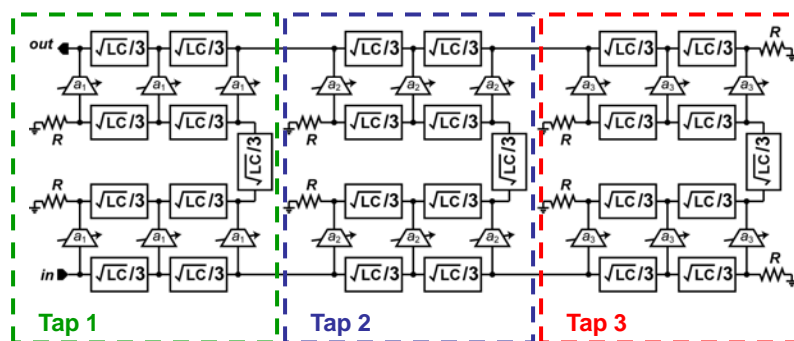


- Example: 3-tap FIR filter

40-Gb/s Equalizer in 0.18- μm CMOS

Jonathan Sewter, M.A.Sc.

 - 0.18 μm CMOS ($f_T = 45 \text{ GHz}$)
- 3-tap filter
- Fully differential
- Analog control of tap weights
- 70 mW from a 1.8 V supply




Practical Challenges for Electronic Dispersion Compensation in CMOS



43

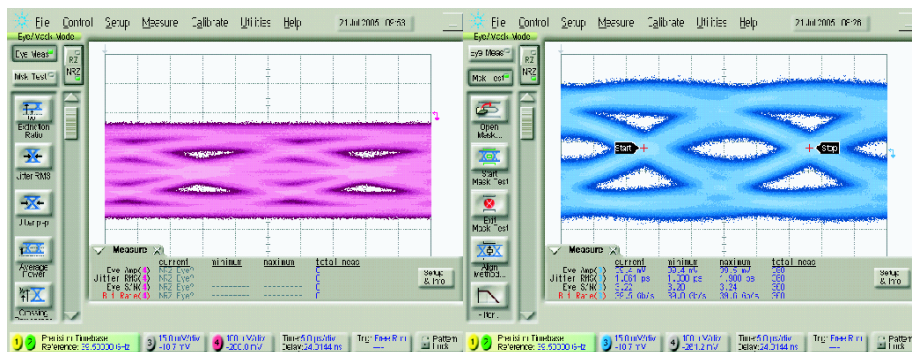Input and output eye diagrams at 40 Gb/s over 15-dB loss channel




Practical Challenges for Electronic Dispersion Compensation in CMOS




44

Implementation of Feedback Equalizer

 


DFE Critical Path

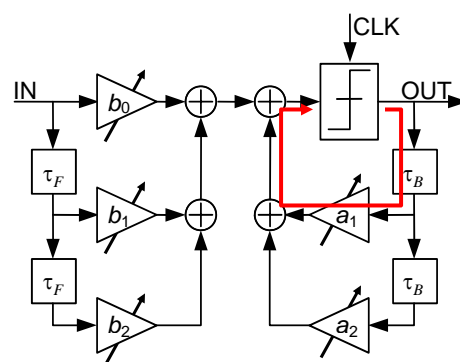

Infinite Impulse Response Filter


George Ng, M.A.Sc. candidate

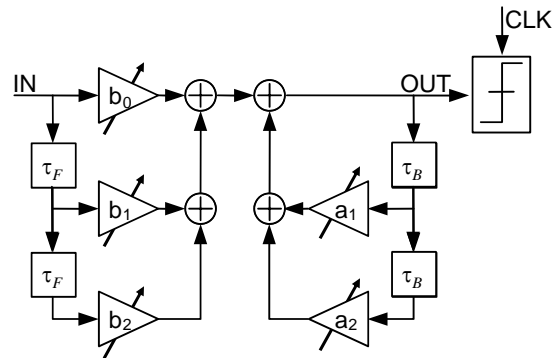


✓ Eliminates timing critical path
 ⇒ Broadband operation possible in CMOS

✗ Possible instability of the filter
 ✗ Complicates the adaptation algorithm

Lookahead DFE

 


Lookahead DFE

 


- Make a decision assuming the last bit was +1

Lookahead DFE

 


- Make a decision assuming the last bit was -1

Lookahead DFE

 


- Choose between the two digitally

Lookahead DFE

 

- ✓ Shortened critical path
- ✗ Parallelism demands more power consumption
- ✗ Clock distribution is a challenge

Lookahead DFE Implementation

 


Practical Challenges for Electronic Dispersion Compensation in CMOS



53

40-Gb/s 1-tap DFE Implementation

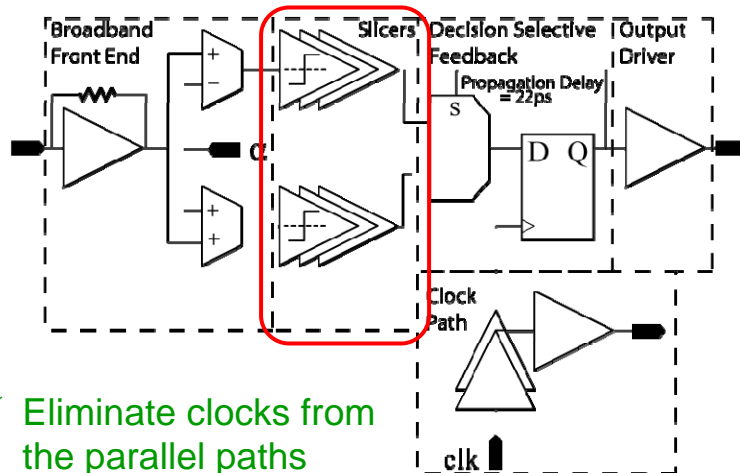

✓ Eliminate clocks from the parallel paths


Practical Challenges for Electronic Dispersion Compensation in CMOS



54

40-Gb/s Decision-Feedback Eq.

 Adesh Garg, M.A.Sc. (with Prof. S. Voinigescu)




Practical Challenges for Electronic Dispersion Compensation in CMOS




40-Gb/s Eye Diagrams

Input Eye – 9-ft Electrical Cable

 

Equalized Output Eye

 

Jitter_{pp} = 5.11ps; SNR = 9.1


Rise time = 13.67ps; V_{pp} = 320mV

Practical Challenges for Electronic Dispersion Compensation in CMOS




Towards 40-Gb/s DSP-based Receivers

Traditional receiver:

 


DSP-based receiver:

 

- **Requires 40-Gsample/sec A/D converter**


Ultra High Speed A/D Conversion

 

CMOS 30-GS/s Track & Hold


Shahriar Shahramian, Ph.D. Candidate (with Prof. S. Voinigescu)

 - 0.13- μm CMOS process
- 270-mW from 1.8-V supply
- 6.5 ENOB over 7-GHz bandwidth




30-GSample/sec Operation

5-GHz input

 

7-GHz input

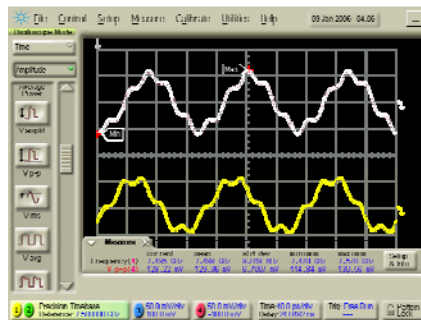

Summary

- Baud-rate tap-spacing in equalizers are amenable to robust adaptation
- Techniques to alleviate the inherent delay-bandwidth-gain tradeoffs in linear equalizers
- Techniques to alleviate the timing bottleneck in the feedback equalizer
- Progress towards 40-GSample/sec DSP-based equalizer